

# The Bits In-Between

## An EE's Guide to Survival Between Microphone and Voice Coil

Bruno Putzeys

Hypex Electronics, Grimm Audio, The Netherlands

On the occasion of the 123rd AES Convention, October 6, 2007


# Copyright Notice

- This presentation ©2007 Bruno Putzeys, Hypex Electronics, Grimm Audio.
- Do not distribute this file, instead link to this file on the Hypex or Grimm Audio web site.
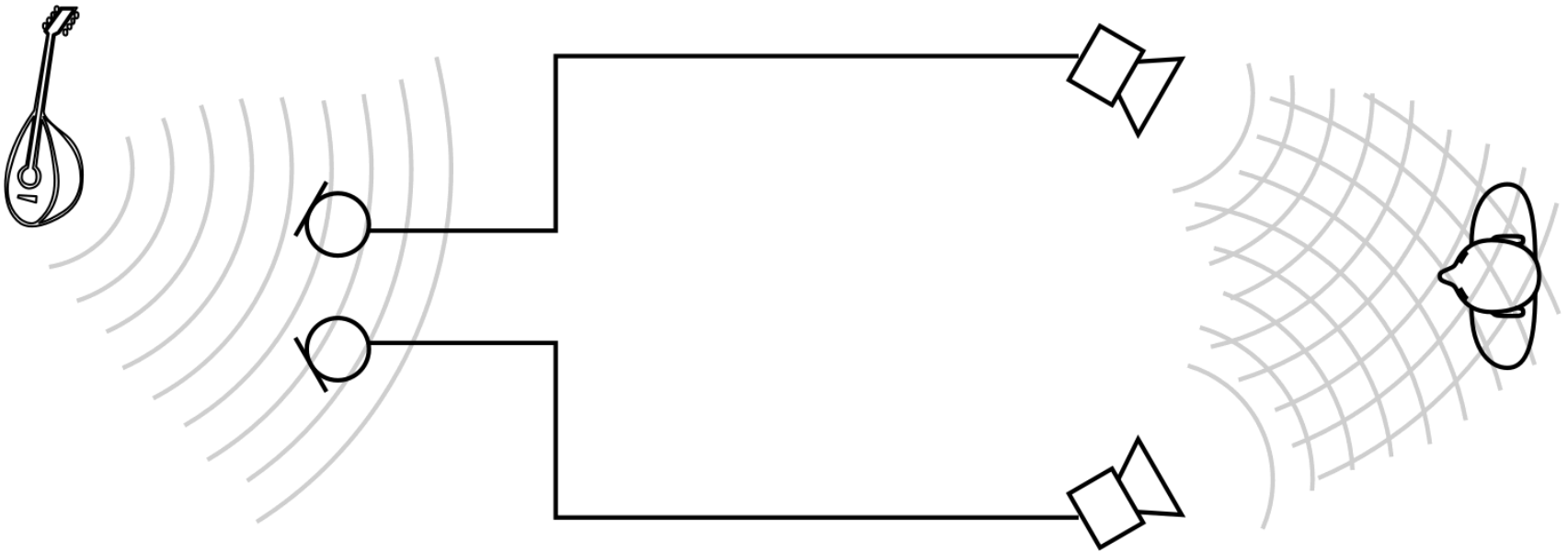
# A bit of Perspective

It's all in the head


Transducer theory without psychoacoustics=rubbish


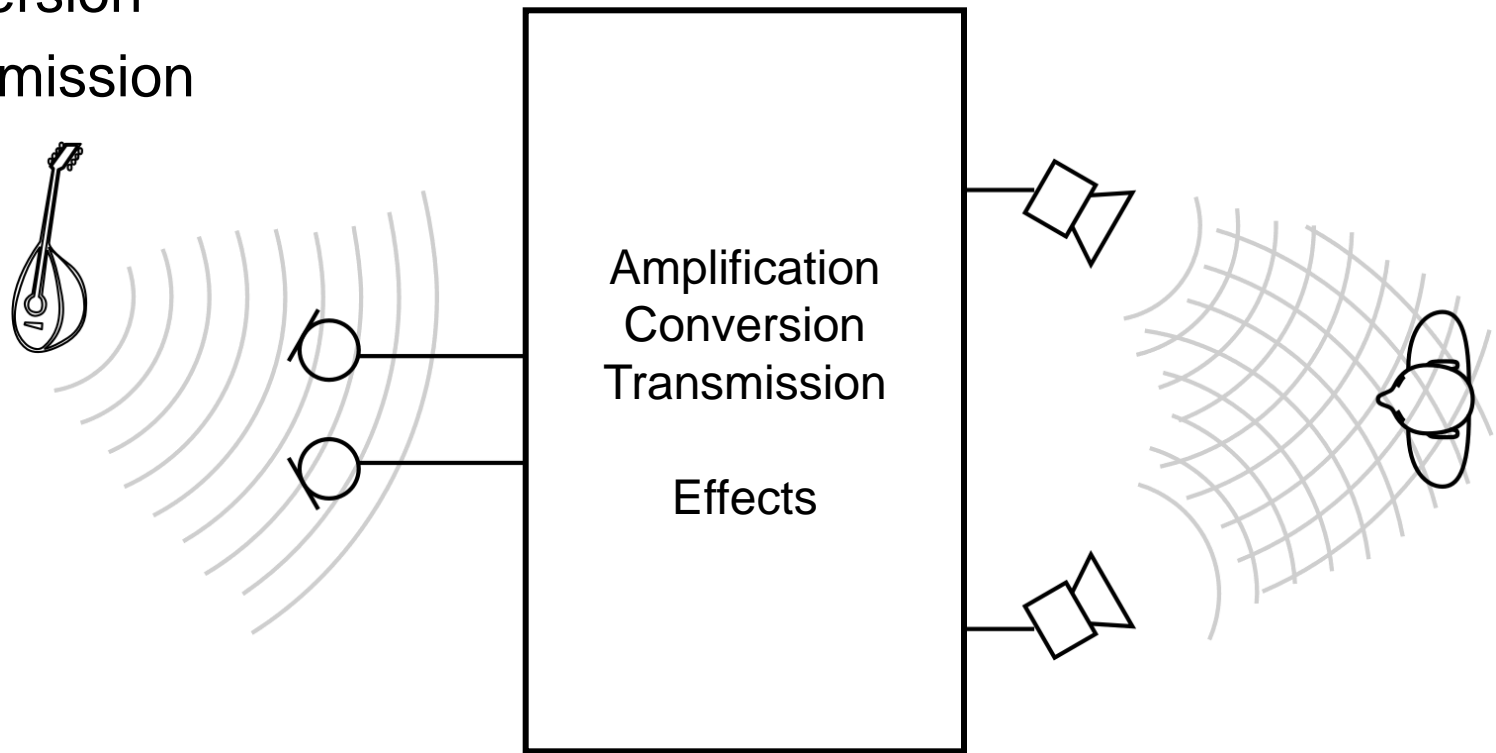
# A bit of Perspective

The parts most covered in mystique are in fact the utilitarian ones:

- Amplification
- Conversion
- Transmission



- Only effects gear should modify the signal audibly

# Contents

- Revealed Preference. Running after your ears.
- Unhappy about Negative Feedback?
- Hands-On Op Amp Theory. How they work. Or sometimes don't.
- Minimalist design, or not? Handle Lightly Those Electrons.
- That Digital Sound: Sampling theory is the solution, not the problem.
- Asynchronous SRC: The fine print: it's only 99% digital.
- Digital loudspeaker EQ and cross-over: Just another tool in the box.
- EMI behavior of class D amplifiers. Listen To The Radio.
- Requirements for SMPS in power amps. Mo' power.
- Intelligent Design in Audio: Subcontracting Audio Design

# Revealed Preference: Euphonic or Transparent?

## How Do You Listen?

1. “Preference Test”: compare to reference product
  - Design cycle converges on “best sounding”.
2. “Bypass Test”: compare output to input
  - Design cycle converges on “maximally transparent”.

## Note different meanings of “transparent”

- Audiophile: Barrage of fine detail
- Pro: no audible difference between in and out.

# Revealed Preference: Euphonic or Transparent?


## Reference Listening Fallacies: Yeah but...

- “I’m listening for the most neutral sound, not for the sound I like best”
  - Result will be what you *think* is most neutral...
    - ...Not what you *really* like best
    - ...Not what is *truly* transparent
- “I go to live concerts regularly to recalibrate my ears”
  - No actual reproduction takes place (audio=illusion).
  - Your design will be specialised to make your favourite recordings sound realistic

} *Worst of both worlds!!!*

# (When) Does Negative Feedback Sound Bad?

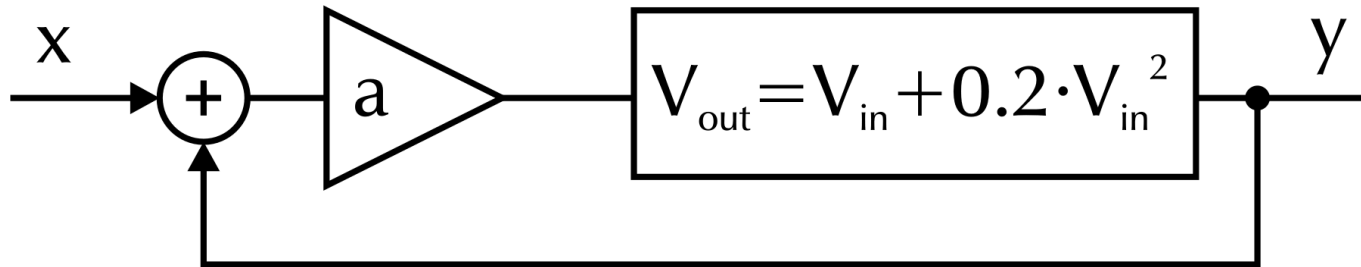
Example non-linearity: pure second order function





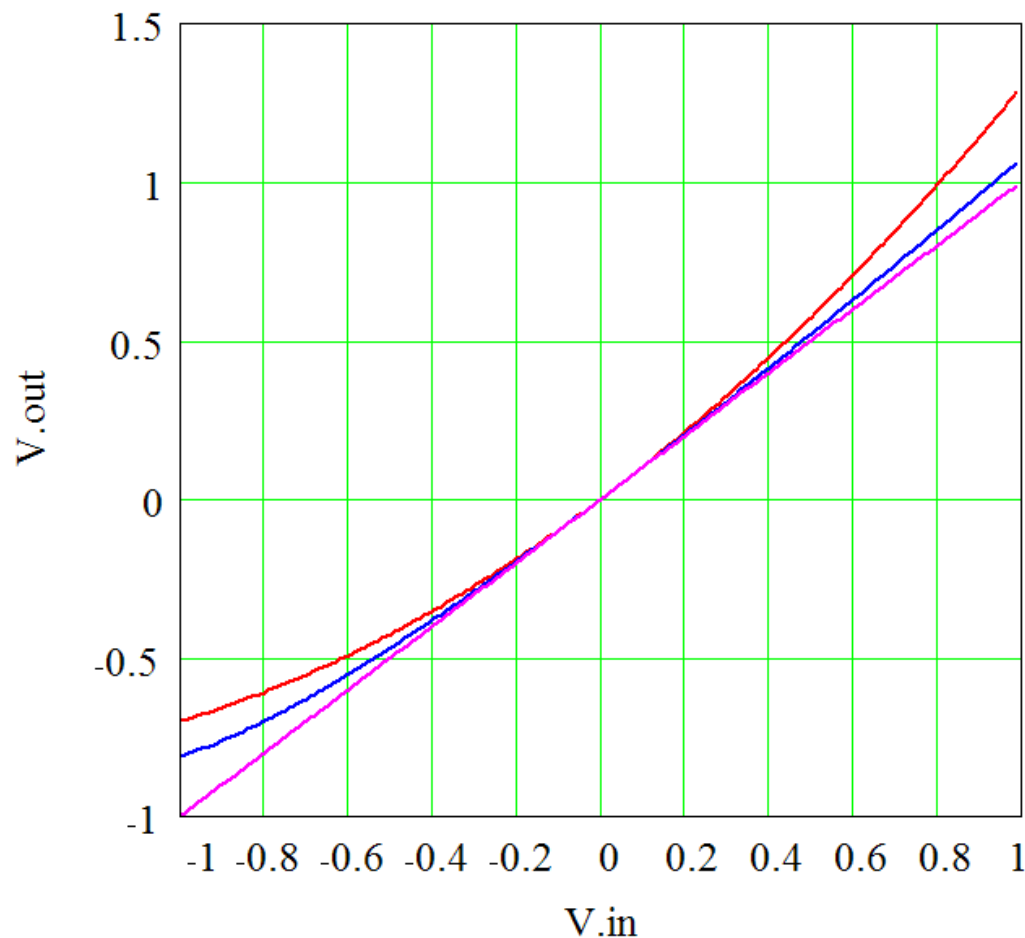
# (When) Does Negative Feedback Sound Bad?

- Feedback results in “intermediate” shaped transfer (function has a square root in it)



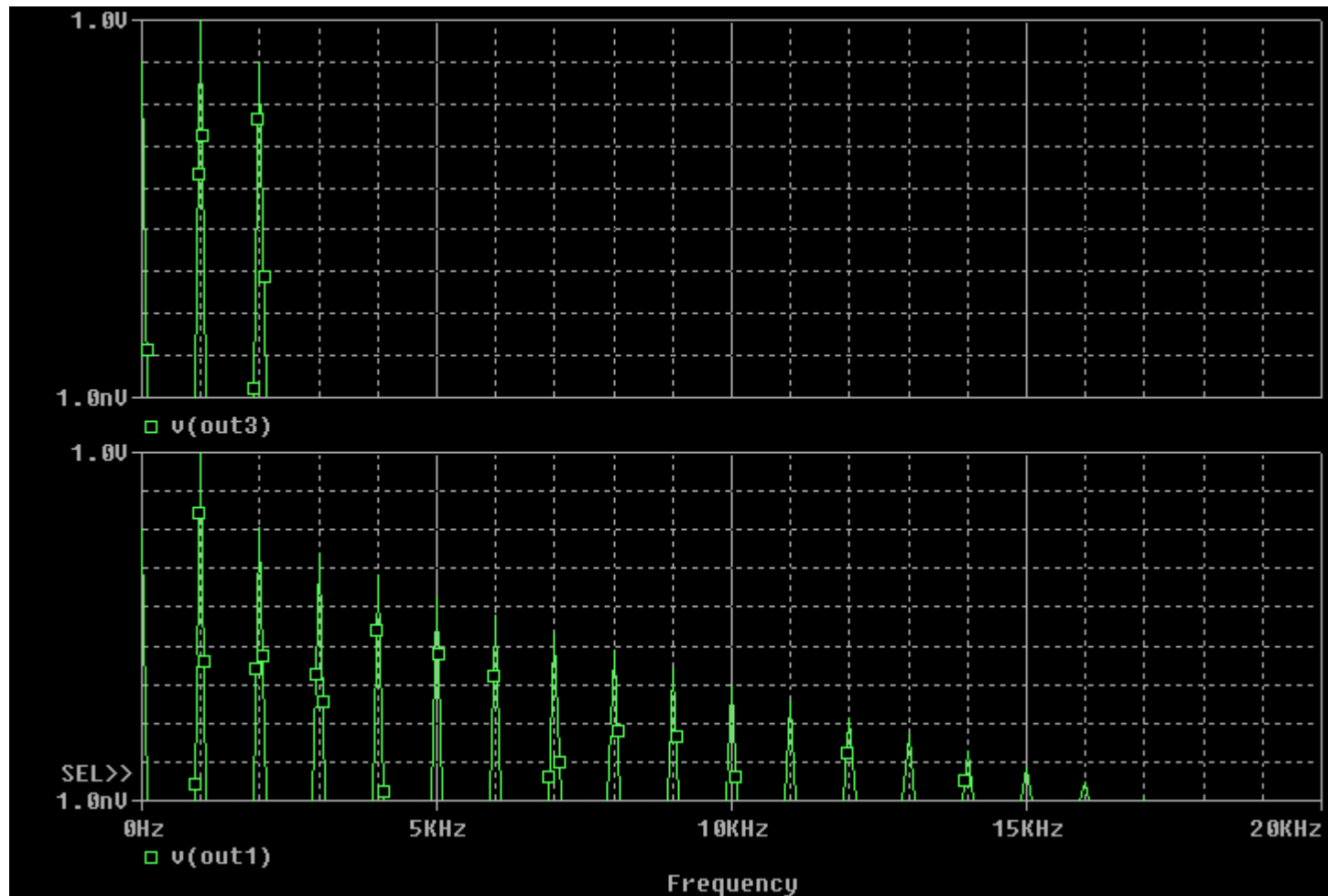
# (When) Does Negative Feedback Sound Bad?


- 2nd harmonic drops.
- New harmonics appear, including odd ones!


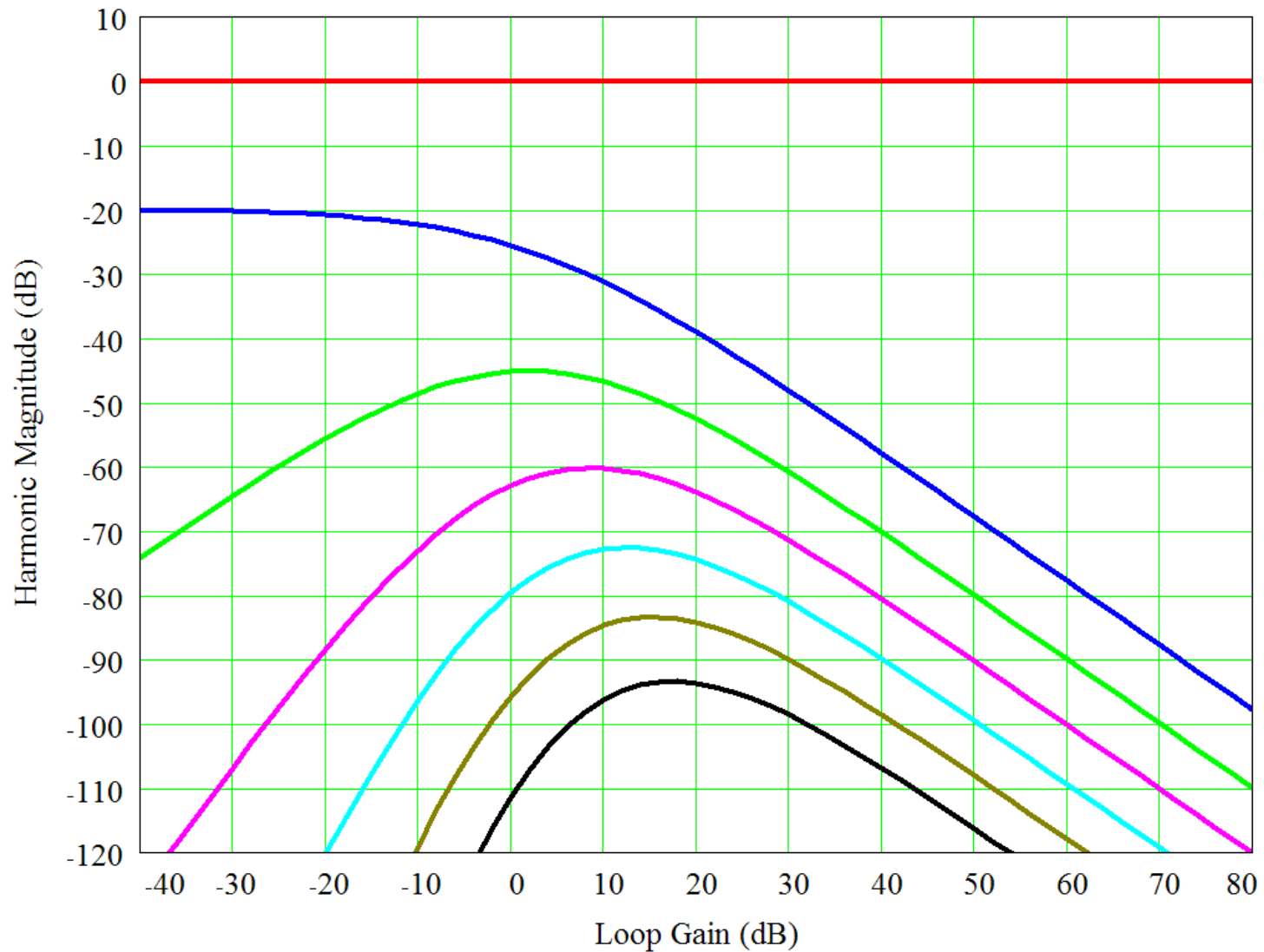
# (When) Does Negative Feedback Sound Bad?


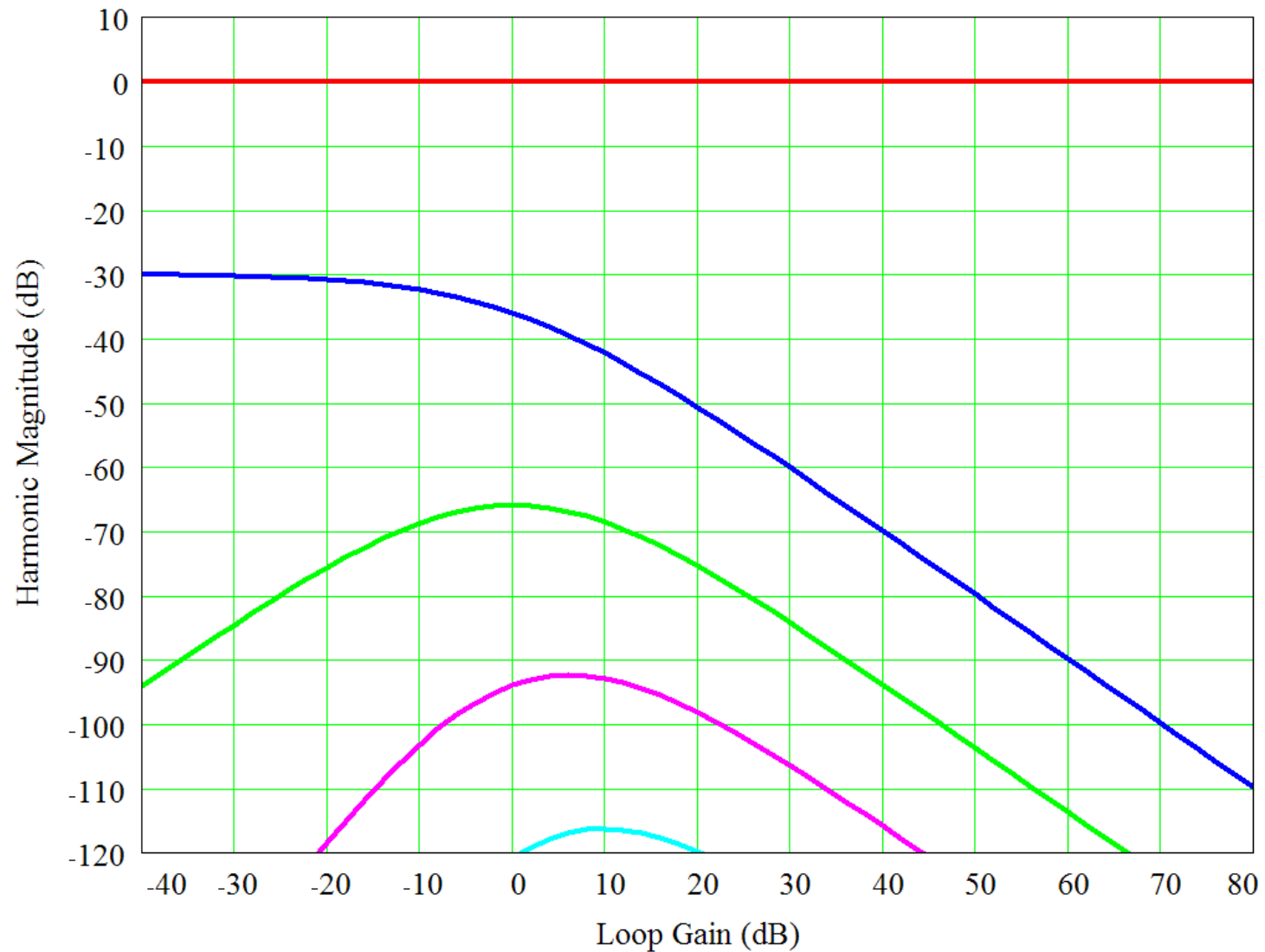
# (When) Does Negative Feedback Sound Bad?




# Negative Feedback Guidelines (1)

- Practical open-loop errors are too large for guaranteed transparency.
- Feedback is the most effective tool for reducing errors
- Moderate loop gain does more harm than good in realistic circuits.
- Improved open-loop linearity reduces NFB-related products by a greater extent.

Don't Be a Wimp. Use NFB and use tons of it.


# Hands-On Op Amp Theory

This is a voltage amplifier...

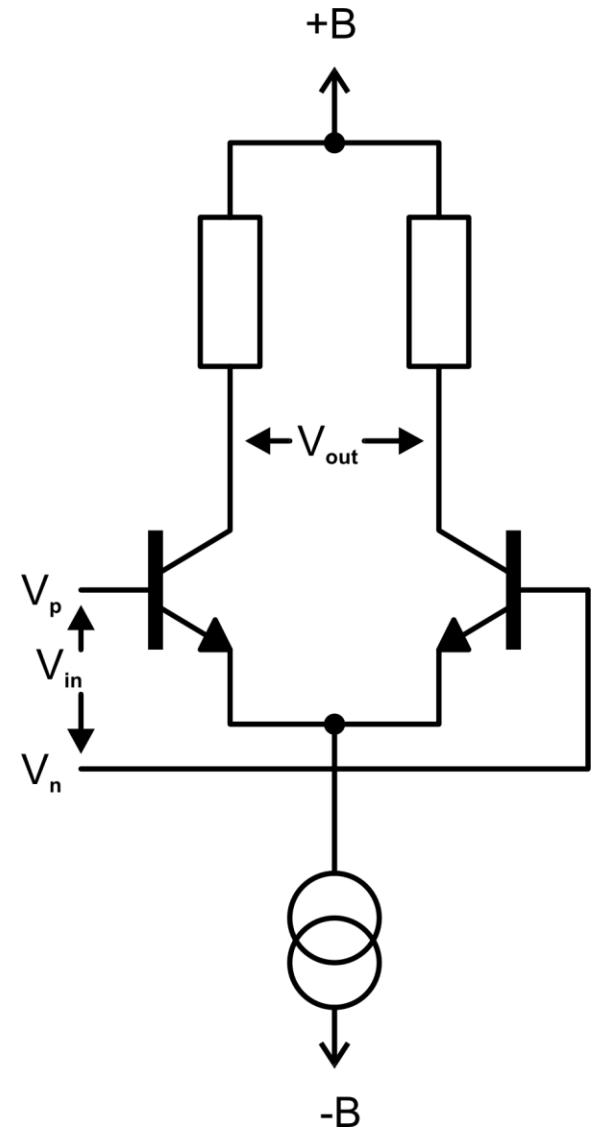


# Hands-On Op Amp Theory

...This is not!

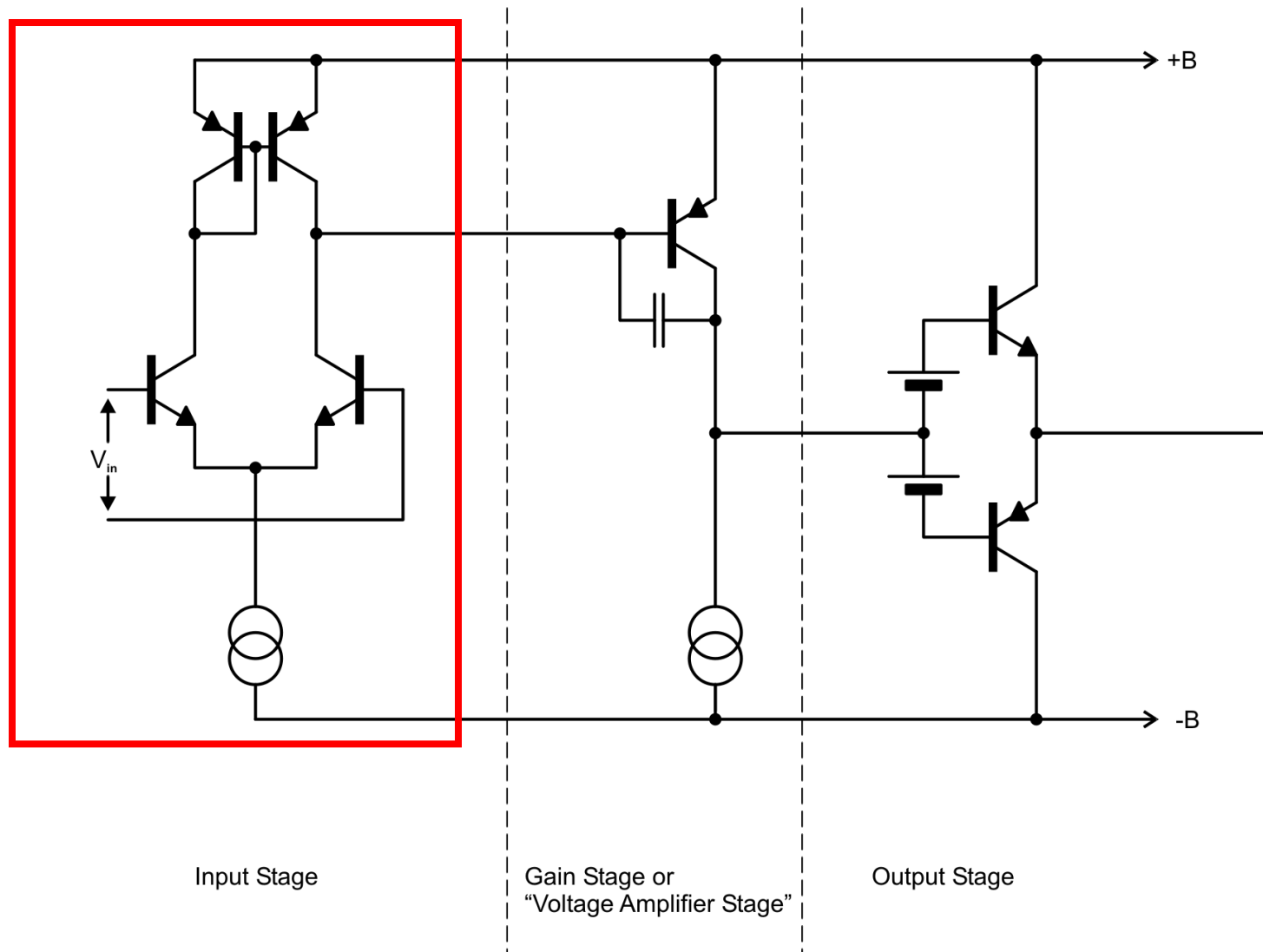

# Hands-On Op Amp Theory

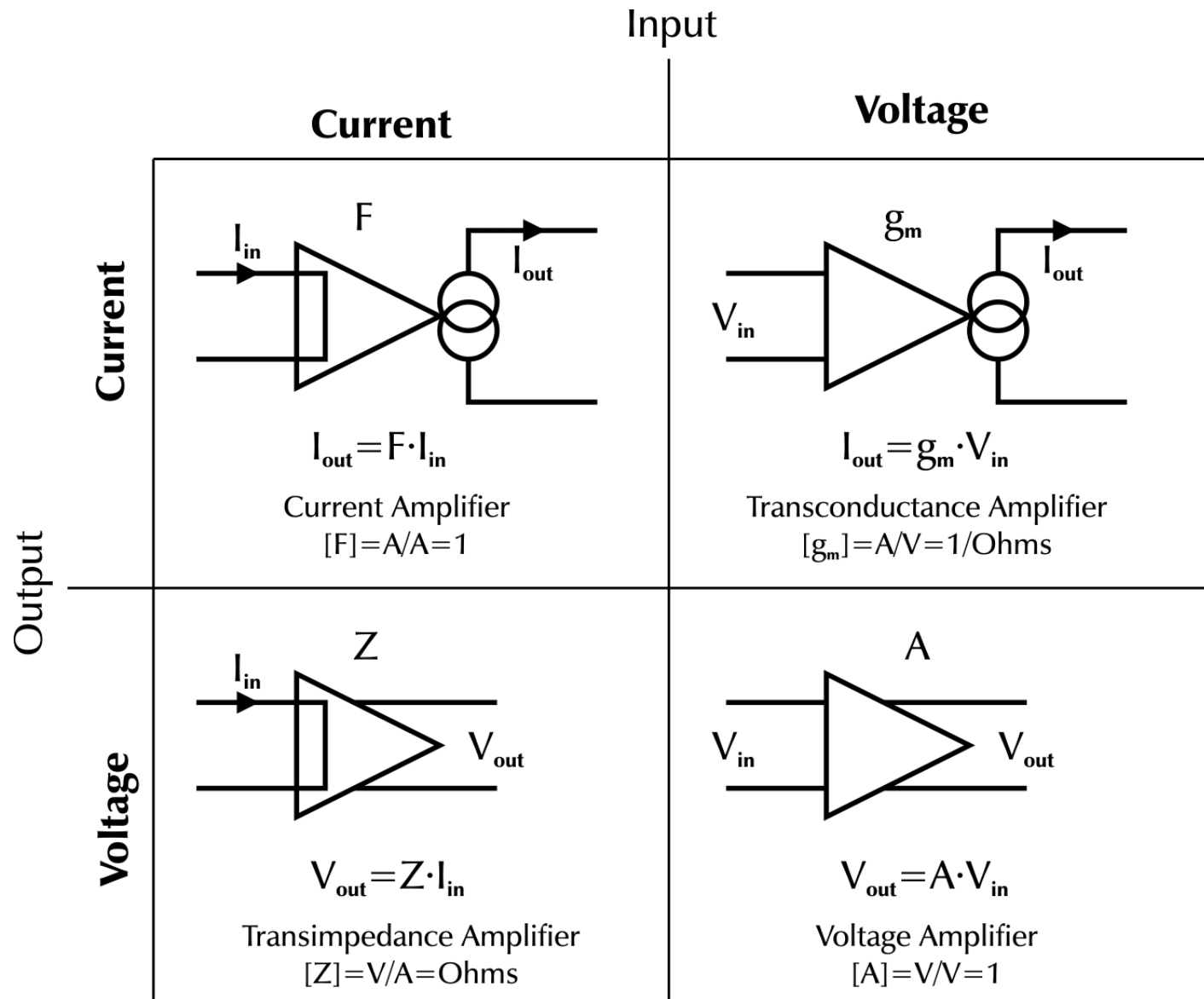





# Hands-On Op Amp Theory
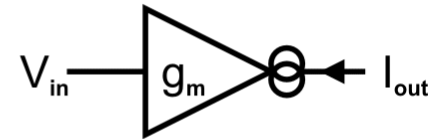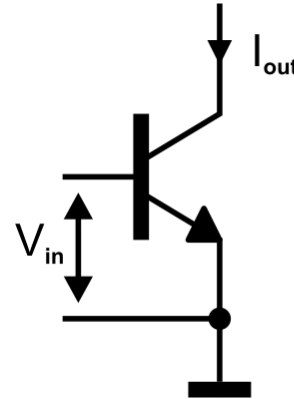
## Transconductance Amplifiers



- Common Emitter Circuit

- $g_m = I_E / 26\text{mV}$
- Moderate  $Z_{in}$
- High  $Z_{out}$



- Common Source Circuit

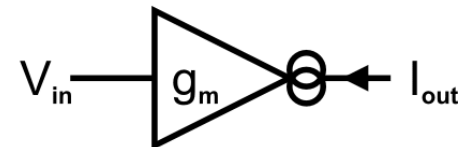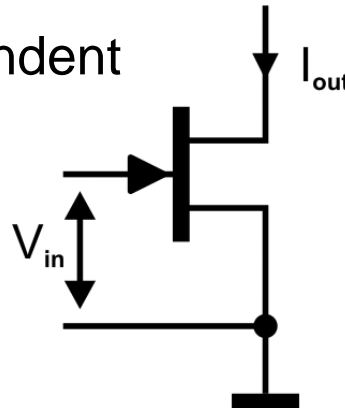- $g_m$  = device and current dependent
- Very high  $Z_{in}$
- High  $Z_{out}$





# Hands-On Op Amp Theory
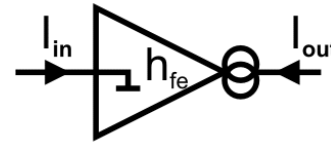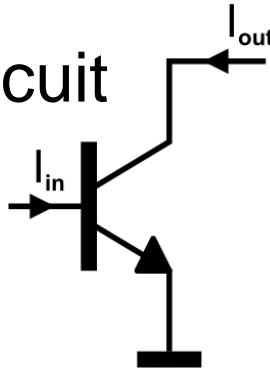
## Current Amplifiers



- Common Emitter Circuit

- $A_I = h_{fe}$
- moderate  $Z_{in}$
- high  $Z_{out}$





- Common Base Circuit (=cascode)

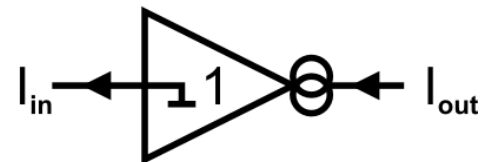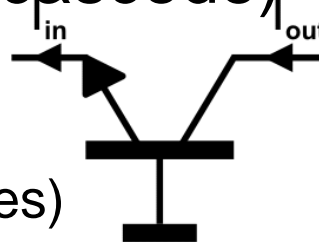- $A_I \approx 1$
- low  $Z_{in}$
- Very high  $Z_{out}$  ( $C_{cb}$  dominates)



- Current Mirror

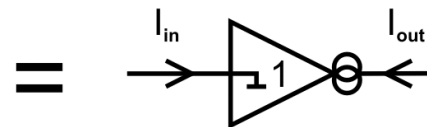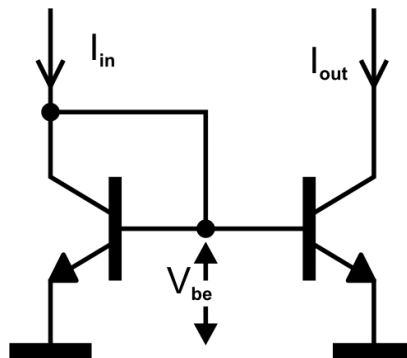- $A_I \approx 1$
- low  $Z_{in}$
- High  $Z_{out}$





# Hands-On Op Amp Theory
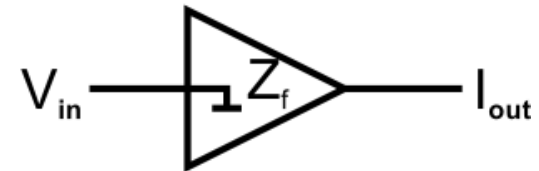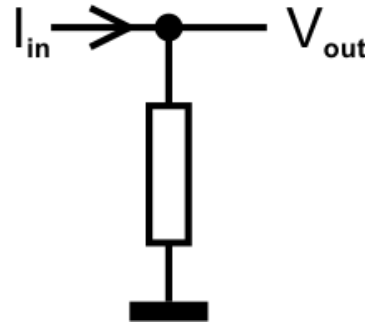
## Transimpedance Amplifiers (I/V converters)



- No fundamental circuit, except perhaps:

- $Z_{in}=Z_{out}$ =“Low” only  
if source and load are  
high-Z



- Feedback type I/V

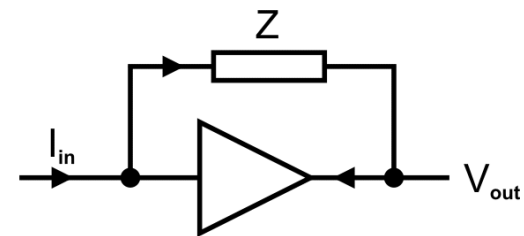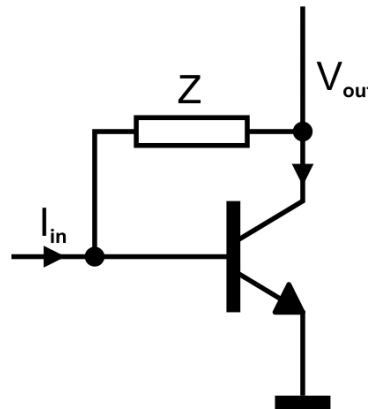- $Z_{in} \approx 1/g_m$
- $Z_{out} \approx 1/g_m$




# Hands-On Op Amp Theory

## Voltage Amplifiers



- Only one truly fundamental voltage amplifier:

- Very High  $Z_{in}$
- Low  $Z_{out}$

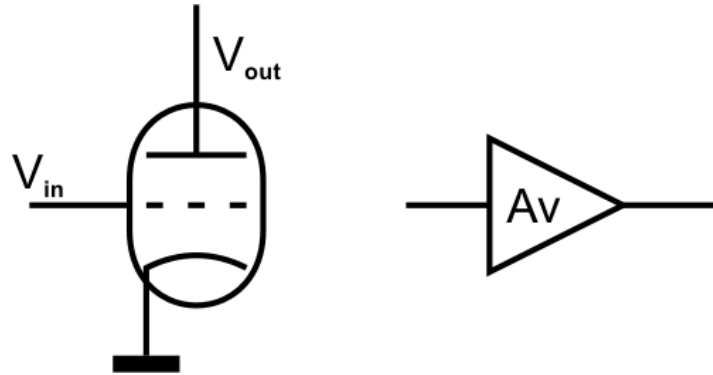


- Follower = transcond. amp with voltage feedback.

- High  $Z_{in}$
- $Z_{out} = 1/g_m$

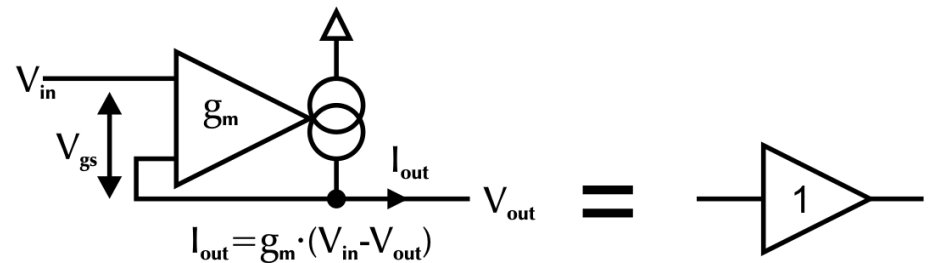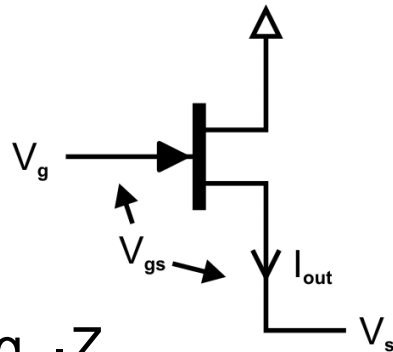


- Loop Gain =  $g_m \cdot Z_L$


# Hands-On Op Amp Theory

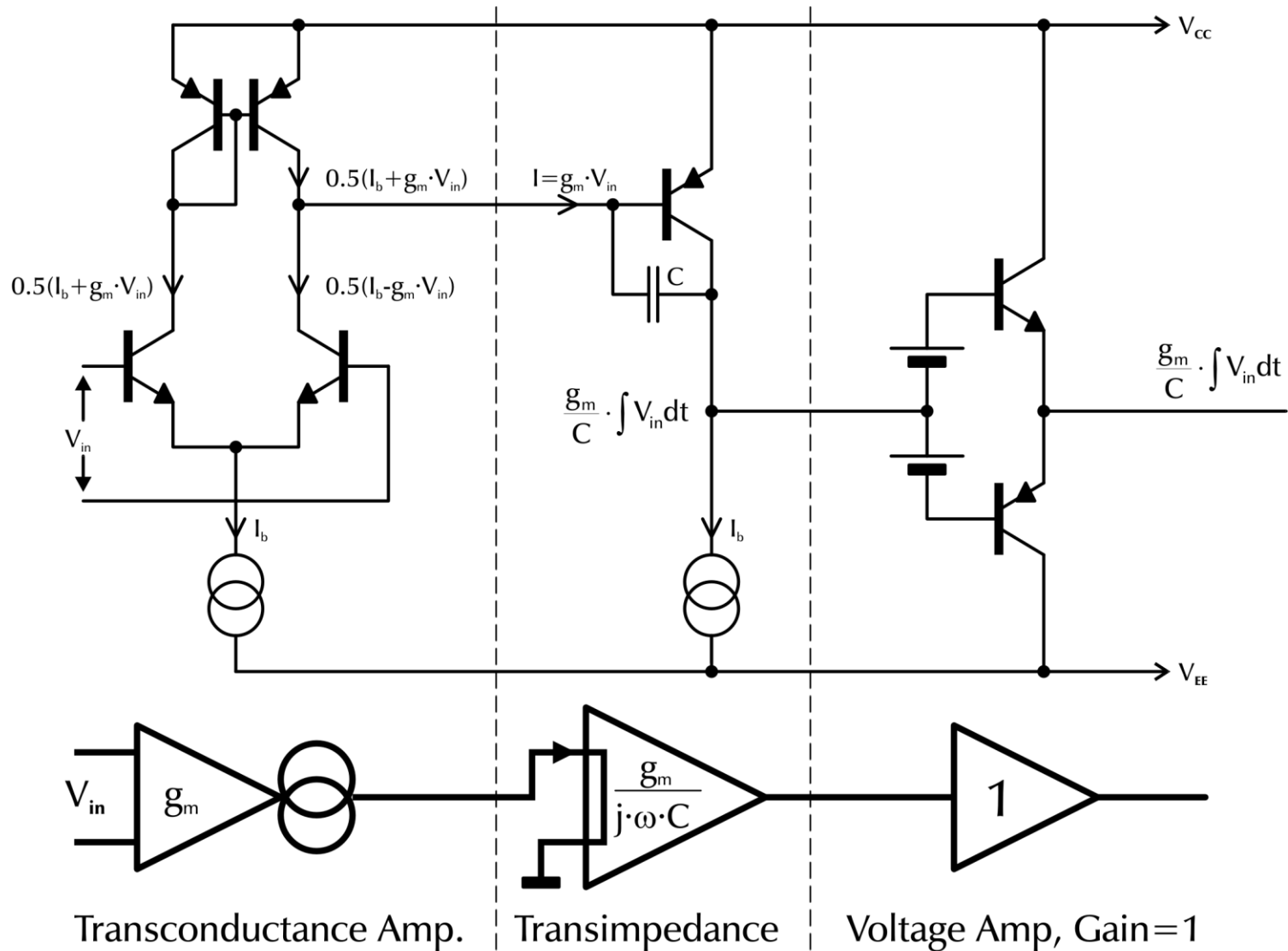

# Hands-On Op Amp Theory

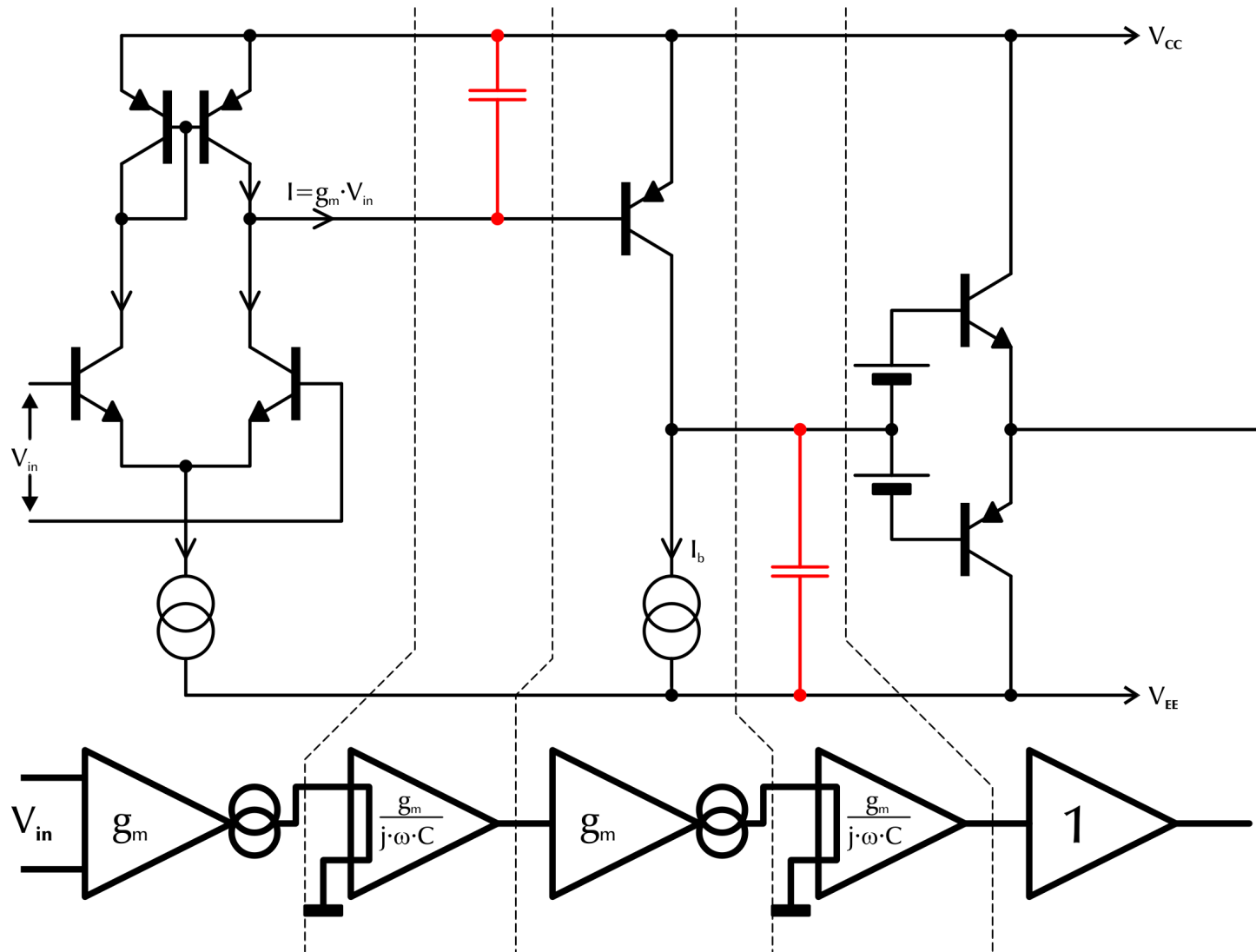

# Hands-On Op Amp Theory

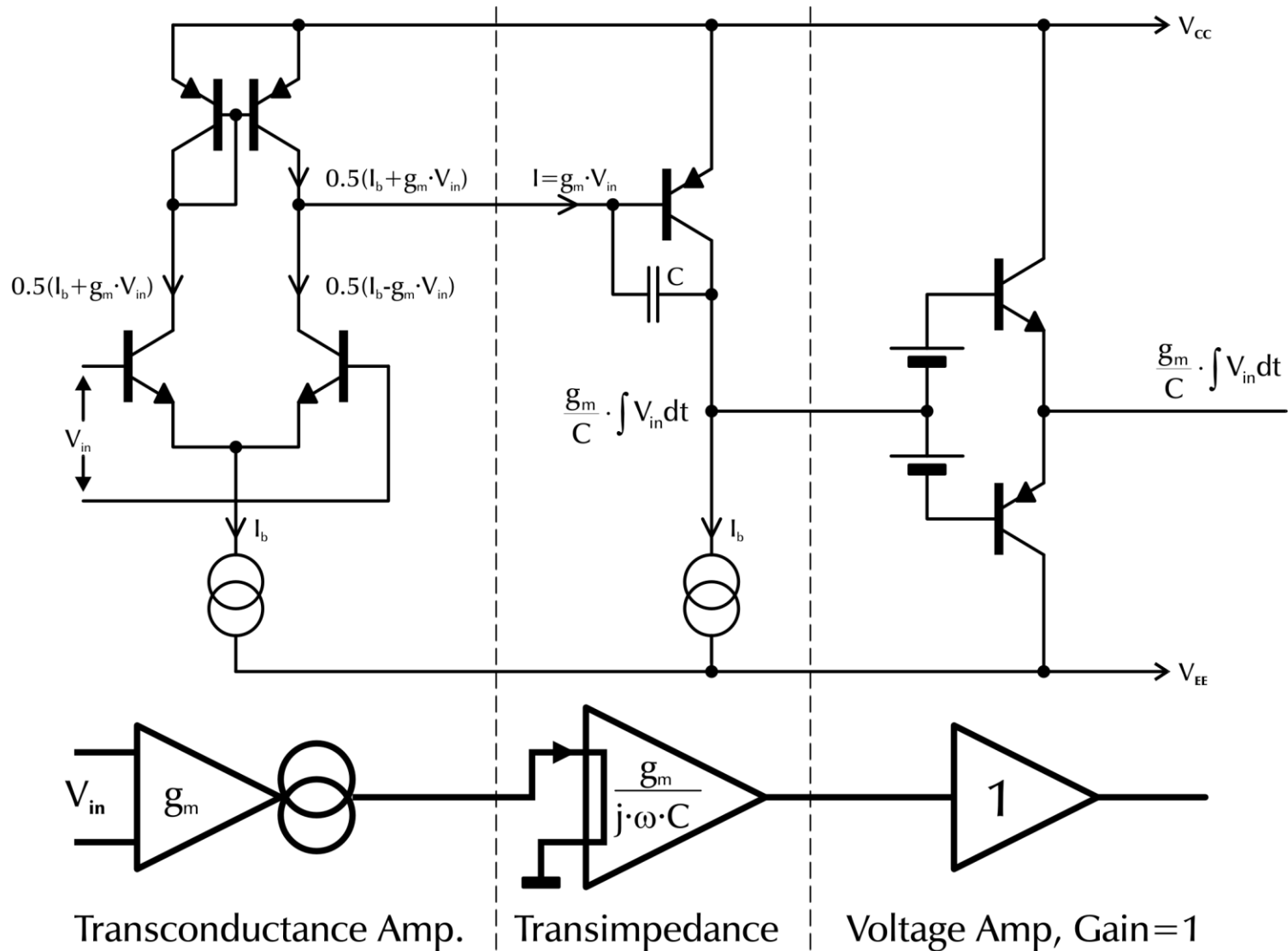

# Hands-On Op Amp Theory

An op amp is an integrator


$$|A_v(f)| = \frac{g_m}{C} \cdot \frac{1}{2 \cdot \pi \cdot f} = \frac{g_m}{2 \cdot \pi \cdot C} \cdot \frac{1}{f}$$

$$GBW = \frac{g_m}{2 \cdot \pi \cdot C}$$



# Hands-On Op Amp Theory

An op amp is an integrator

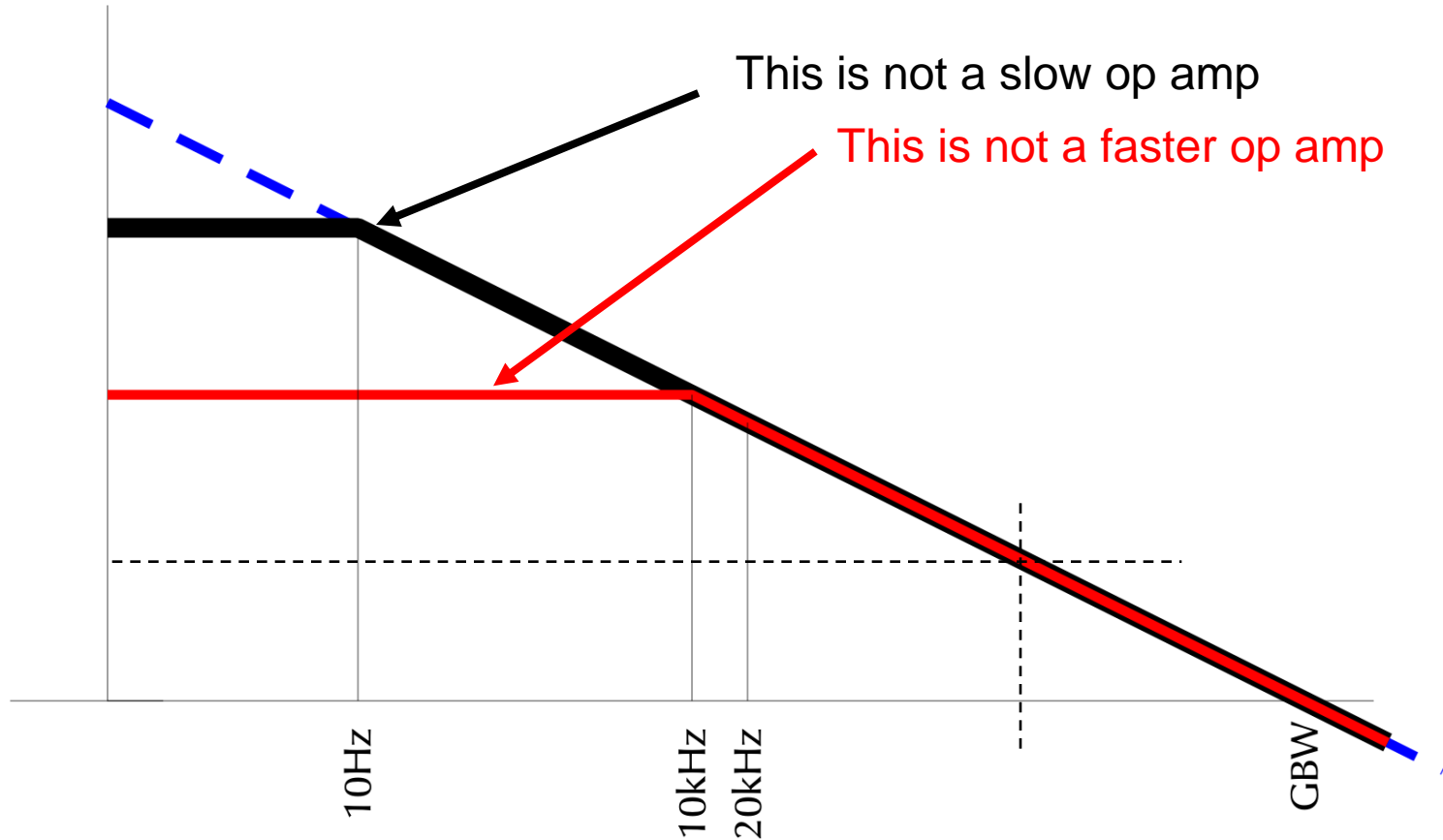

# Negative Feedback Guidelines (2)

## Impact of integrating character on sound

- Loop gain drops 20dB/decade
  - ⇒ Closed-loop THD increases with frequency
  - ⇒ Spectral distribution shifts towards higher frequencies
- Euphony In Action! Rising THD vs frequency profile has a recognisable sonic signature.
  - HF is only mildly affected except in very bad cases.
  - Bottom end becomes extremely “tight”, “powerful” and “controlled”.
  - Often attributed to “huge current reserve” of behemoth power stage. Really caused by HF THD of sluggish amp.
  - Propagates “Damping Factor” myth.


# Negative Feedback Guidelines (2)

Not scientifically established but useful nonetheless:

- When you're strapped for loop gain at 20kHz, limit low-frequency loop gain to the same value.
- THD becomes higher but constant throughout the audio band.
- Colouration becomes less obvious and less annoying.

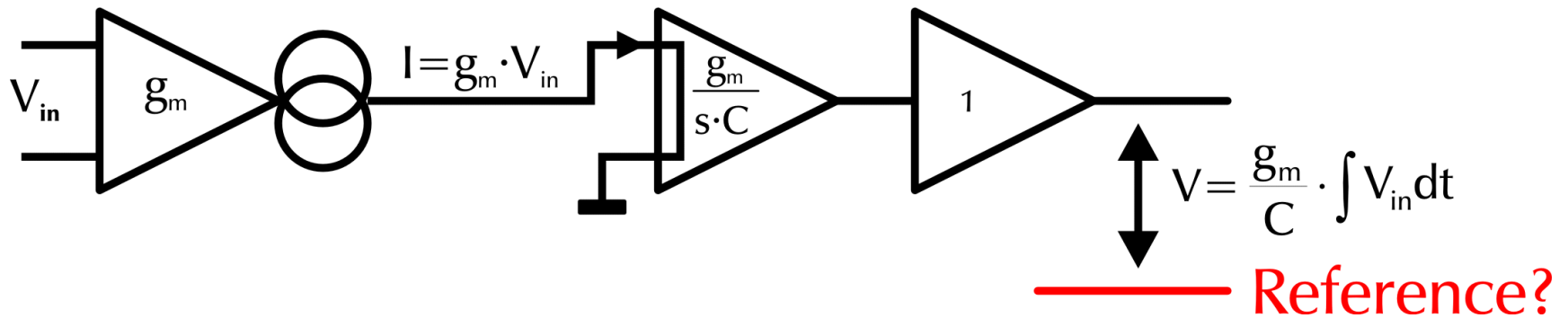
# Hands-On Op Amp Theory: The PSRR Gotcha

Hang on... What's the output voltage referring to?



# Hands-On Op Amp Theory: The PSRR Gotcha


Here!!!

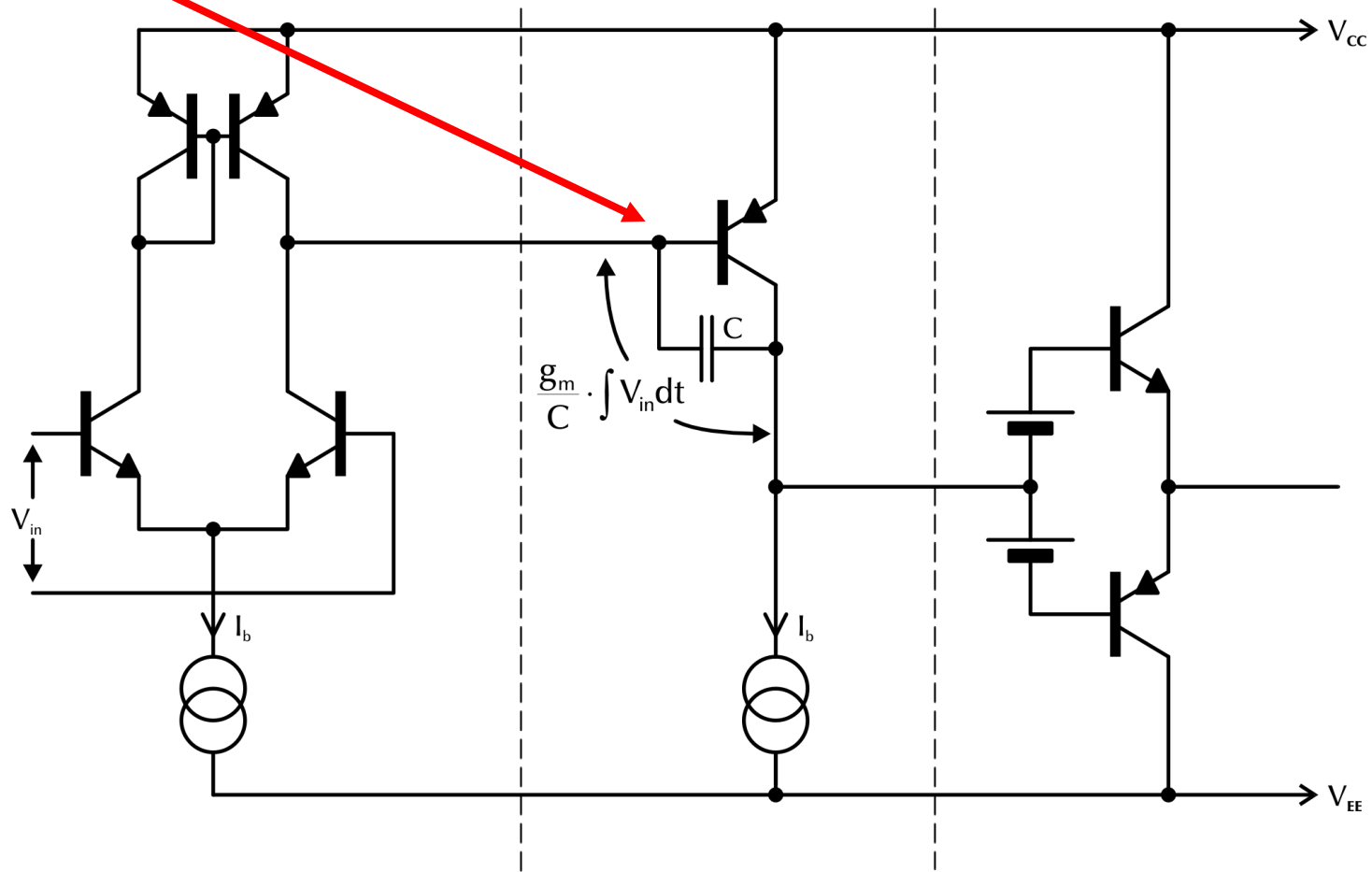
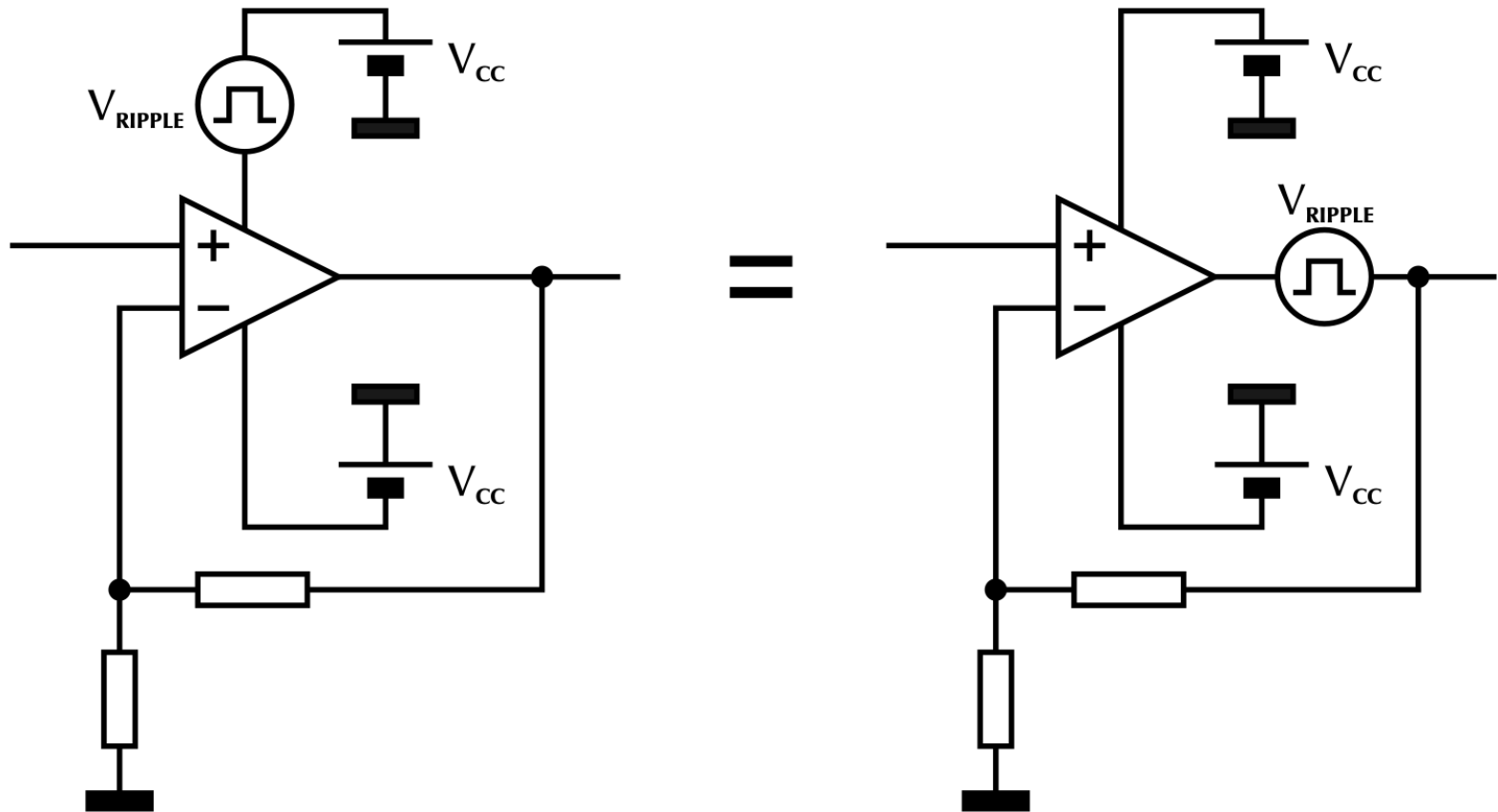
# Hands-On Op Amp Theory: The PSRR Gotcha

So really...



$$V_{\text{out}} = 2 \cdot \pi \cdot \text{GBW} \cdot \int V_{\text{in}} dt + \underline{\underline{V_{\text{CC}}}}$$



# Hands-On Op Amp Theory: The PSRR Gotcha

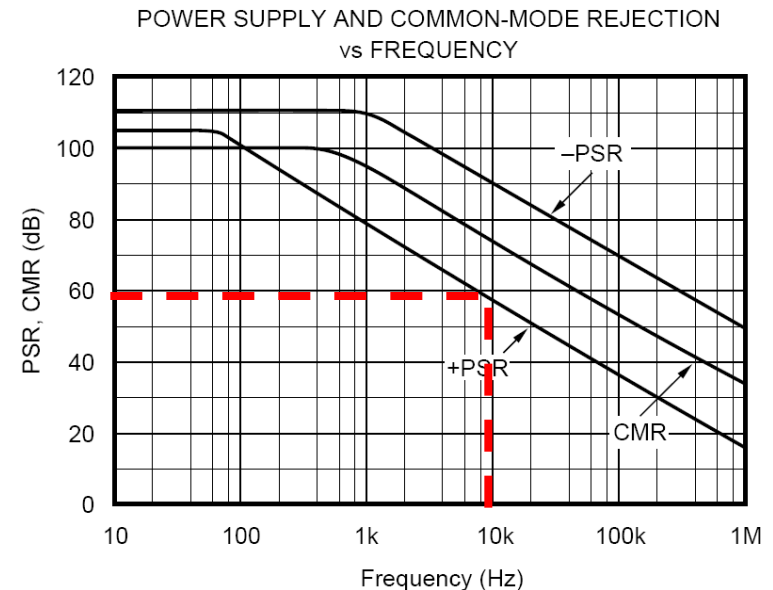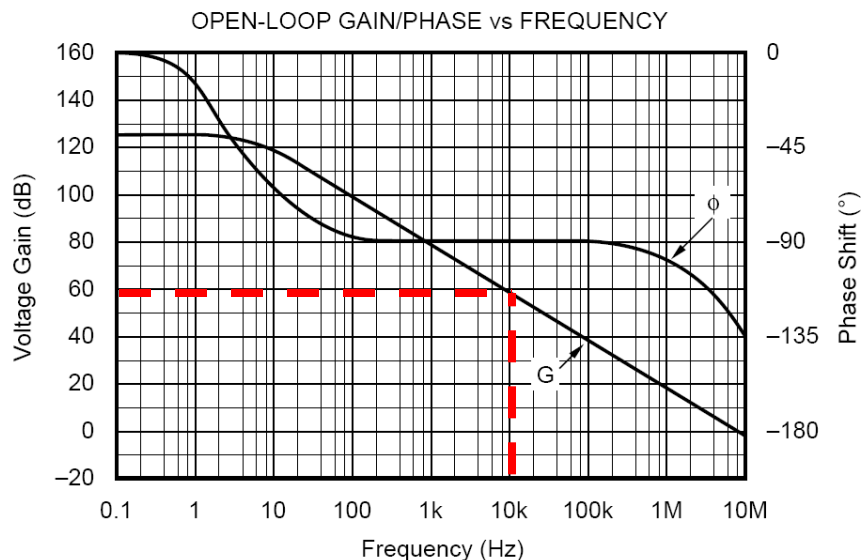
## The PSRR Gotcha:

- One rail is output reference
- PSRR is essentially ZERO
- Measured PSRR =  $A_L \approx A_{V,OL} - A_{V,CL}$
- PSRR in typical audio app is not astronomical



# Hands-On Op Amp Theory: PSRR fixes

## “Folded Cascode” Amp

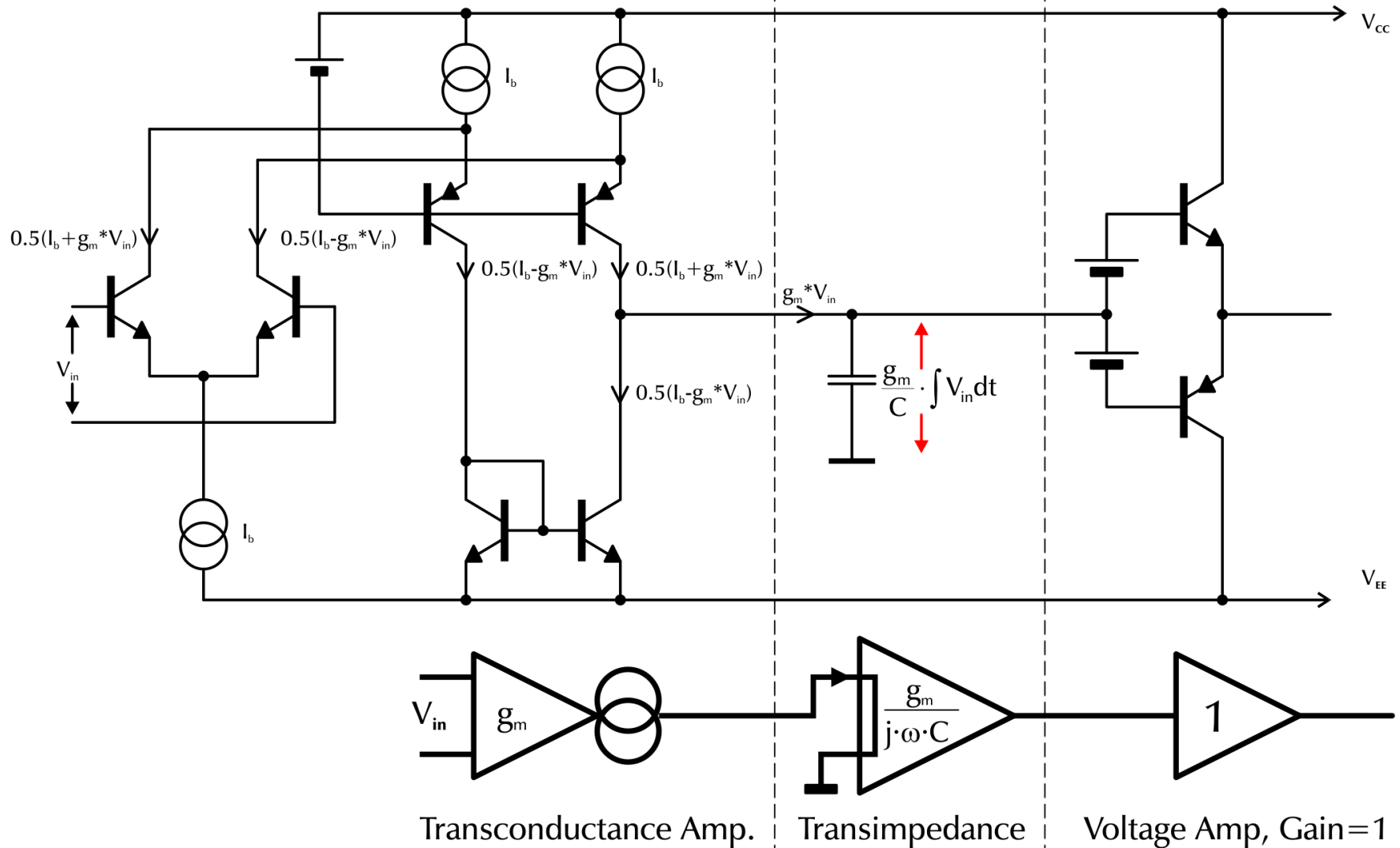




# Hands-On Op Amp Theory: PSRR fixes

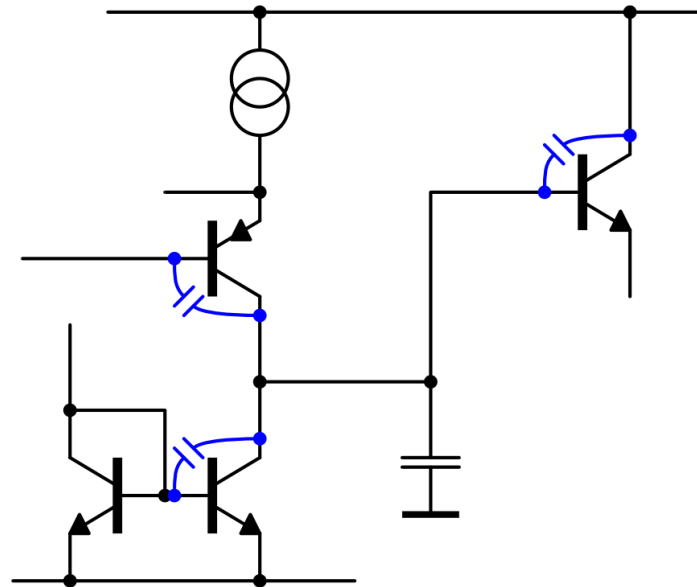
# “Folded Cascode” Amp

- Pro:
  - Output Reference is Ground
- Con
  - Buffer impedance is critical
  - Bias sources add noise
  - Non-linear circuit capacitance adds to integration cap



# Hands-On Op Amp Theory: PSRR fixes

## Cascoding the current junction

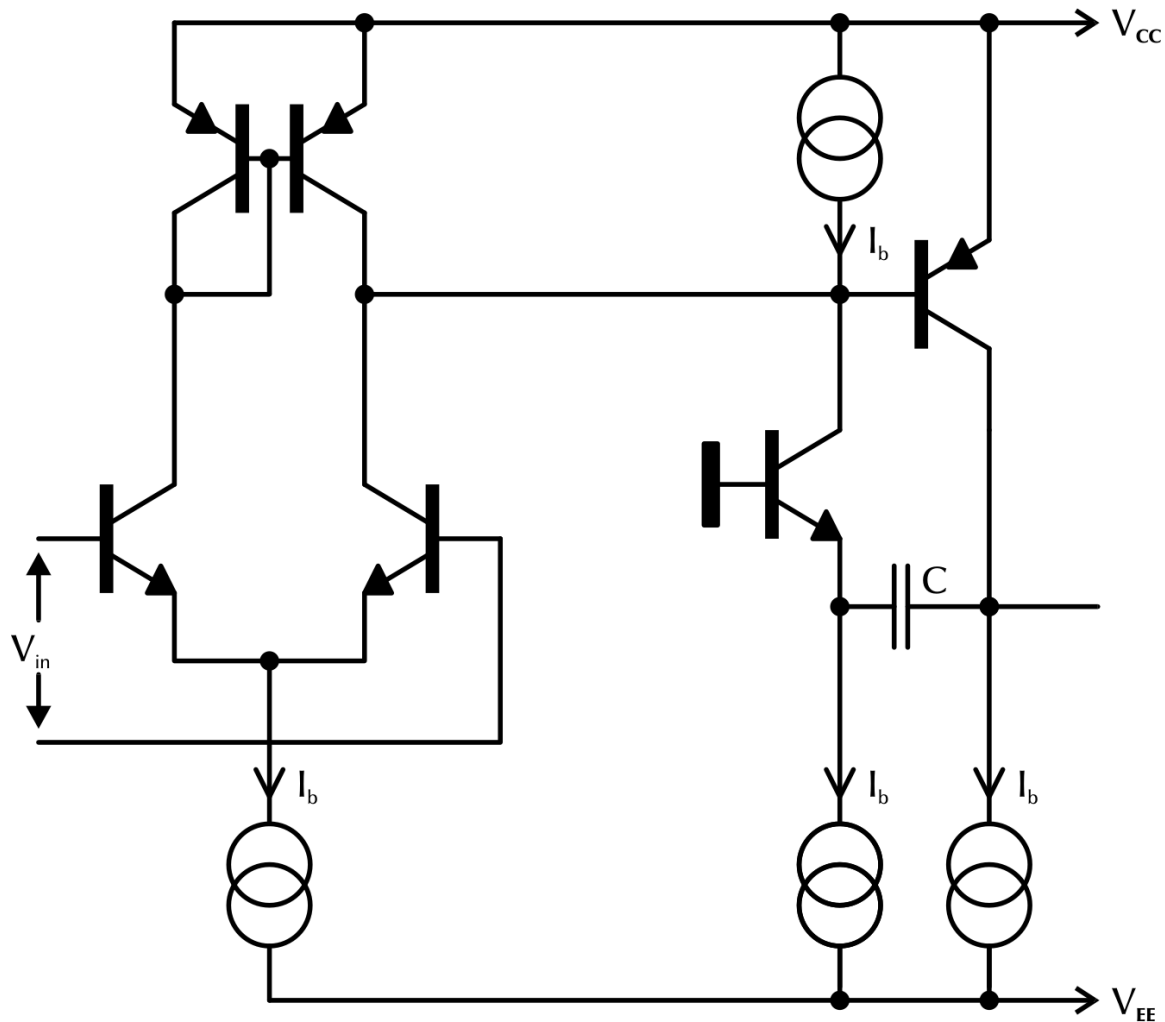

# Hands-On Op Amp Theory: PSRR fixes

## Cascoding the current junction

- Pro:
  - Reference is made explicit
  - Other advantages of feedback transimp stage remain
- Con:
  - Bias sources add noise to Transcond stage output current


# Hands-On Op Amp Theory: CM distortion

## Manifestation

- 20dB/dec THD increase
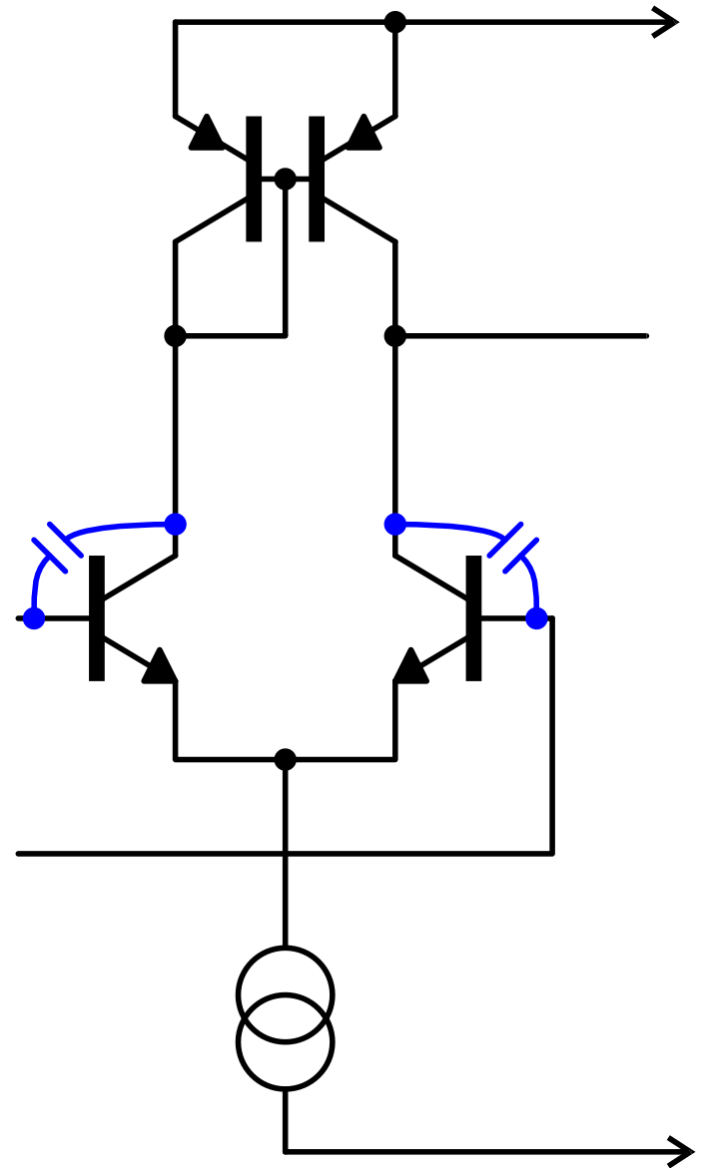
## Causes

- Non-linear input capacitance
  - Dominant problem
- Transistor mismatch
  - Also limits DC PSRR
- Load mismatch
  - All but negligible effect



# Hands-On Op Amp Theory: CM distortion

## Circuit sensitivity

- All 3 effects happen in noninverting mode
- None happen in inverting mode



# Hands-On Op Amp Theory: CM distortion

## Always Invert?

- Guaranteed fix
- Useless in low-noise circuits.
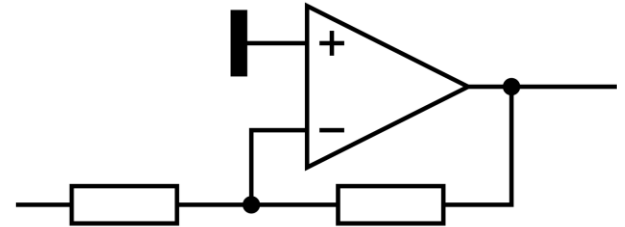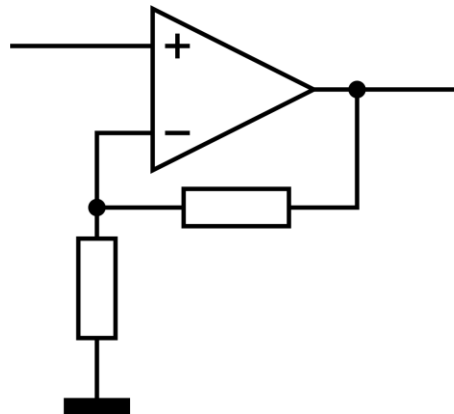
## Impedance Matching


- Eliminates dominant cause
- Source impedance not always known
- Noise penalty



# Hands-On Op Amp Theory: CM distortion

## Input Stage Improvements


- Boot strapped cascode

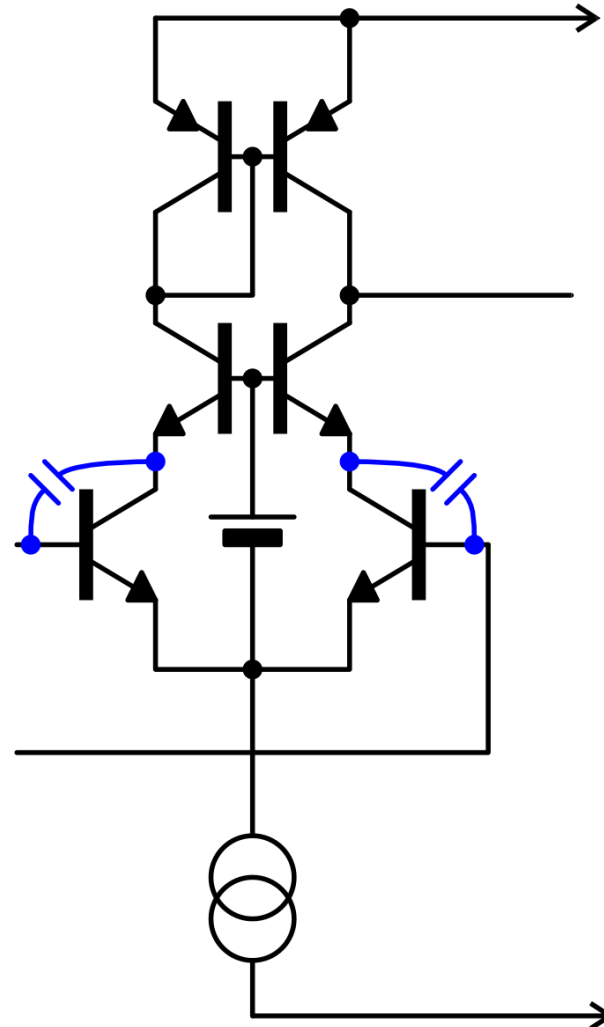

# Hands-On Op Amp Theory: CM distortion

## Input Stage Improvements

- Boot strapped folded cascode

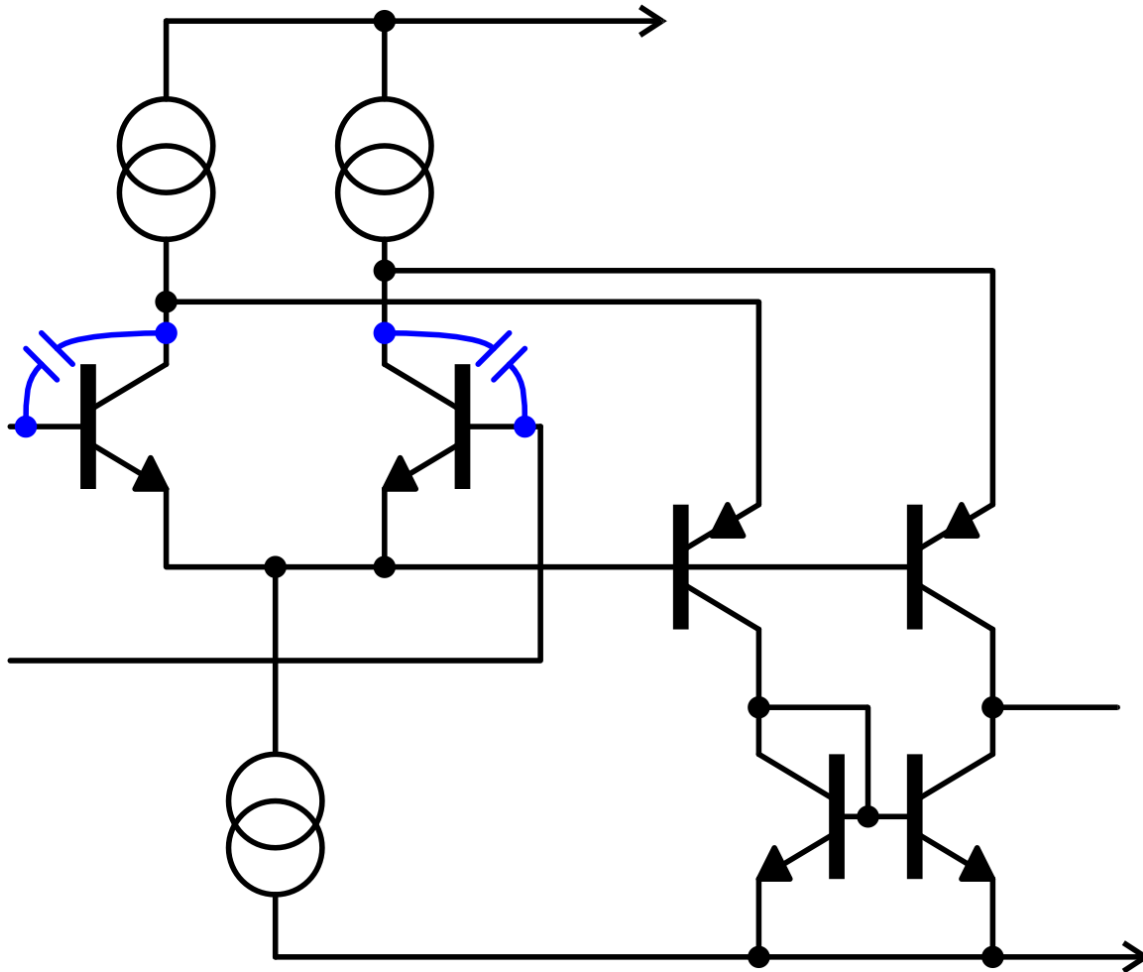



# Hands-On Op Amp Theory: Going discrete?

## Reasons for going Discrete

- Need more headroom
- Trade typical IC compromises for better performance
  - Input Common Mode range
  - Low-supply operation
  - Lack of 6th connection

## Not reasons for going Discrete

- “Discrete is better”
  - Come off it, IC technology is mature
  - Discrete copy of IC op amp has the same drawbacks

# Minimalist Design, or maybe not?

## Basic premise of minimalism

- “Any component a signal passes through, degrades it”
  - Underlying assumption: the whole is always the sum of the parts
- Associated philosophy: “zero feedback”

...do I sense a self-fulfilling prophecy coming?



# Minimalist Design, or maybe not?

Source of the confusion: inaccurate wording.

- Let's correct this:  
“Any *process* a signal goes through, degrades it”
- A bunch of parts enclosed in a feedback loop = ONE process.
  - Result is not “sum of parts”.
  - Neither mathematically, nor sonically.
- Can a process be improved by adding parts? Yes it can!

# Minimalist Design, or maybe not?

## Example 1: Cascode

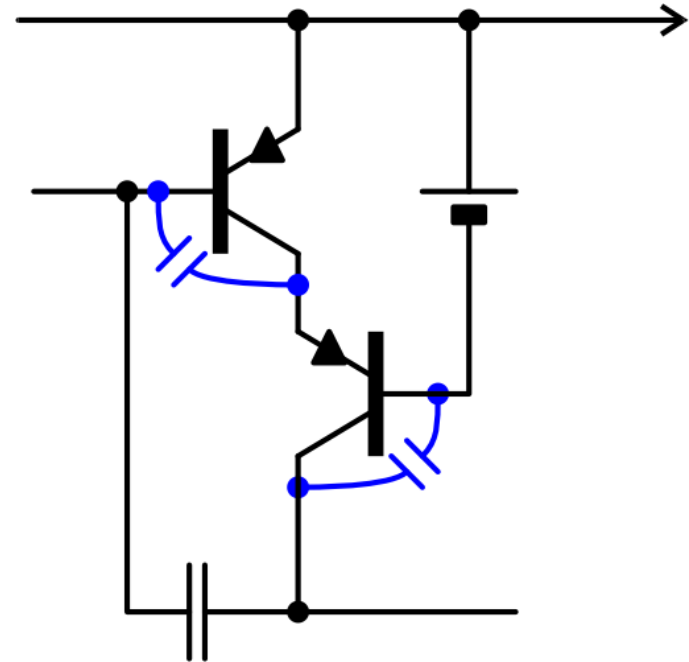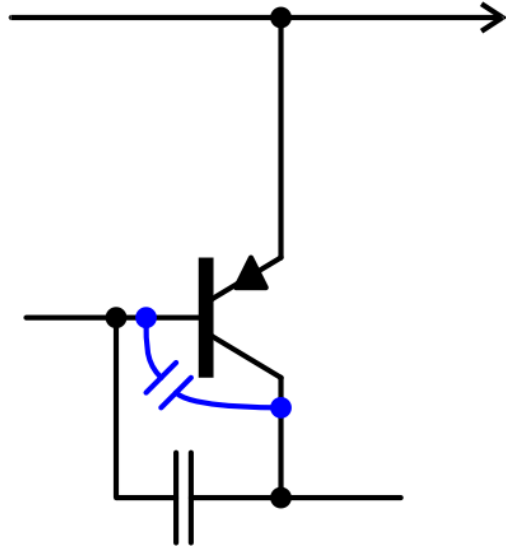


- Cascoding is also accepted by minimalists
  - Undercuts the “sum of parts” premise

# Minimalist Design, or maybe not?

Example 2: 4th order low-pass filter.

- First try: Minimalist, only one op amp

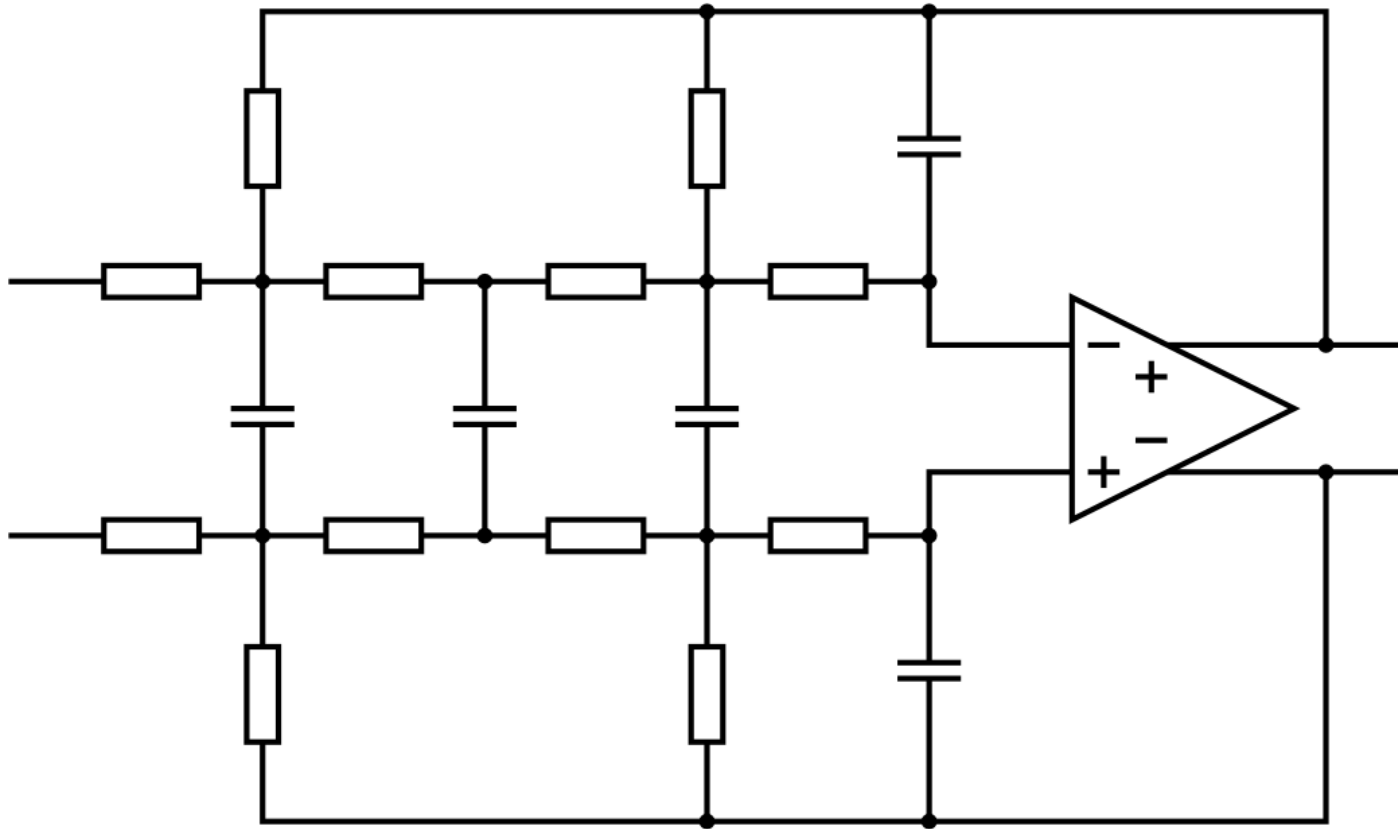


# Minimalist Design, or maybe not?

Problem: Noise gain is high

- Noise outstrips DAC's
- Op amp is starved of loop gain
- Frequency response deviates noticeably from ideal
- THD comes out of noise floor
  - Worse than 2 separate 2nd order sections
  - Sounds worse too...
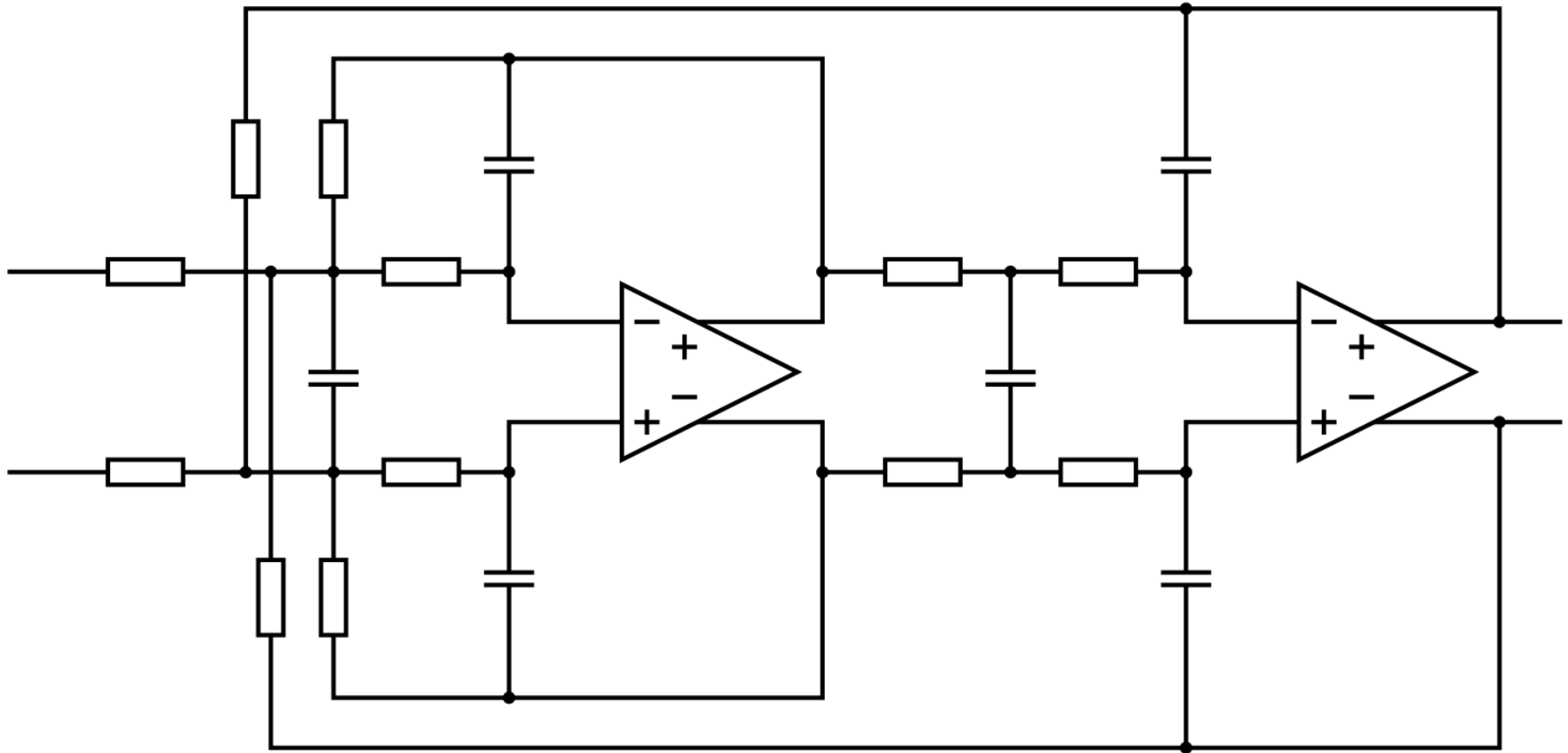
# Minimalist Design, or maybe not?

Second try: Two-op amp filter w/ global feedback



# Minimalist Design, or maybe not?


## Second try: Two-op amp single stage filter

- Complexity doubles
- Either stage adds loop gain to the other.
- THD is lower than a single stage (and unmeasurable)
- Converter chain is now audibly transparent



# Digital Filters in AD/DA Converters

## Sampling Theory's Basic Promise

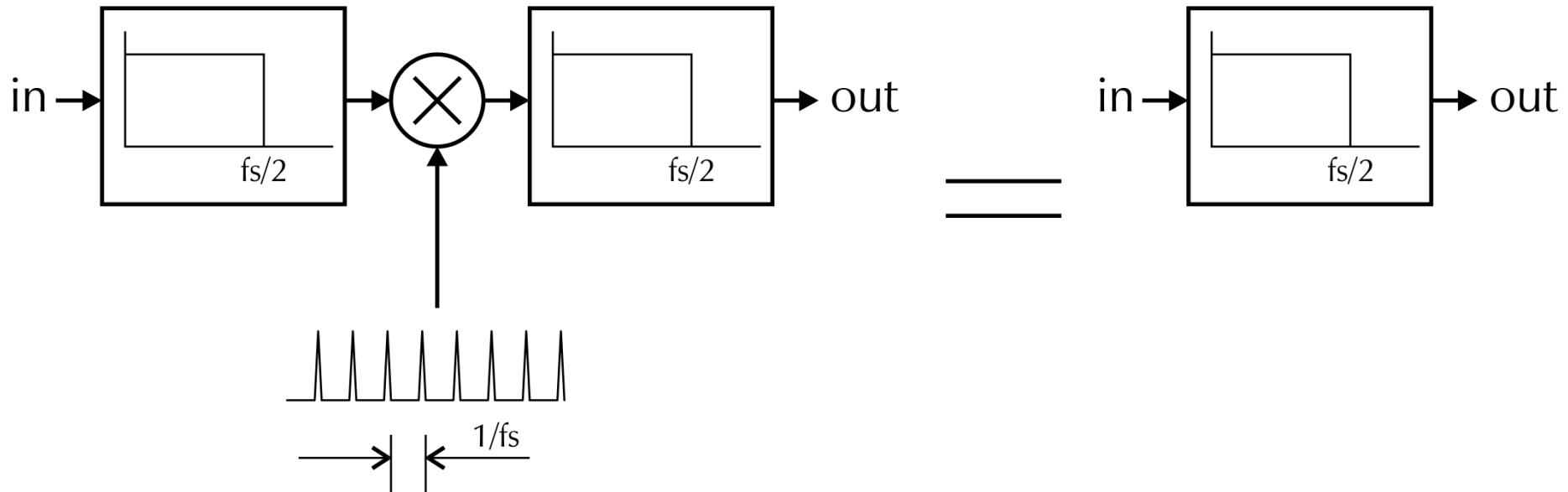

*A sampler flanked by low-pass filters with sufficient attenuation at  $f_s/2$  does exactly the same as the low-pass filters alone.*


# Digital Filters in AD/DA Converters

## The TOA Cue Fallacy

- “The ear can detect a 2 $\mu$ s Time-Of-Arrival difference”
  - Correct! (0.2° lateral shift in stereo image)
- “So we need 500kHz sampling”
  - Uhhh not quite...


# Digital Filters in AD/DA Converters

## The Promise in Practice

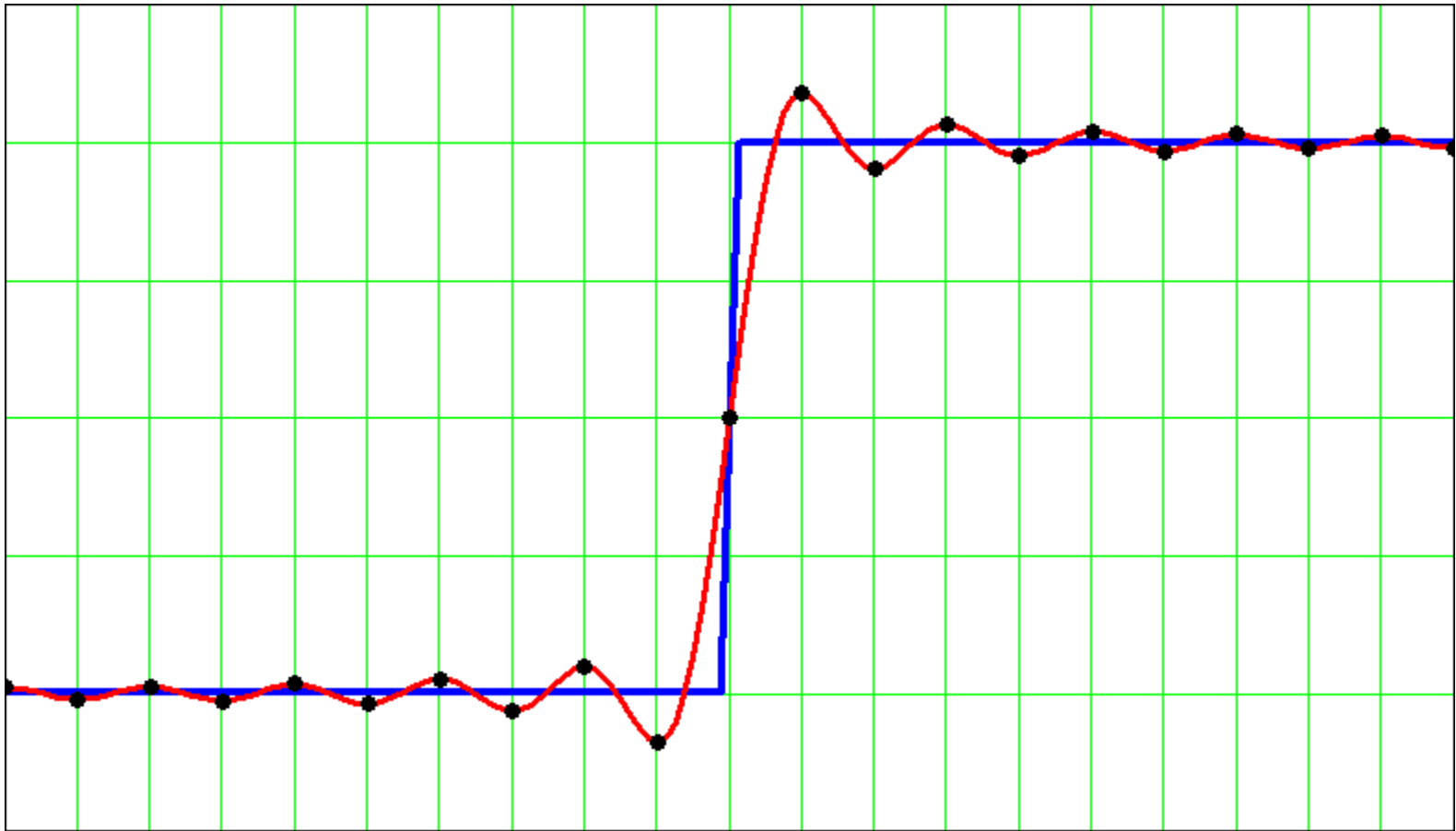


# Digital Filters in AD/DA Converters

## The Promise in Practice

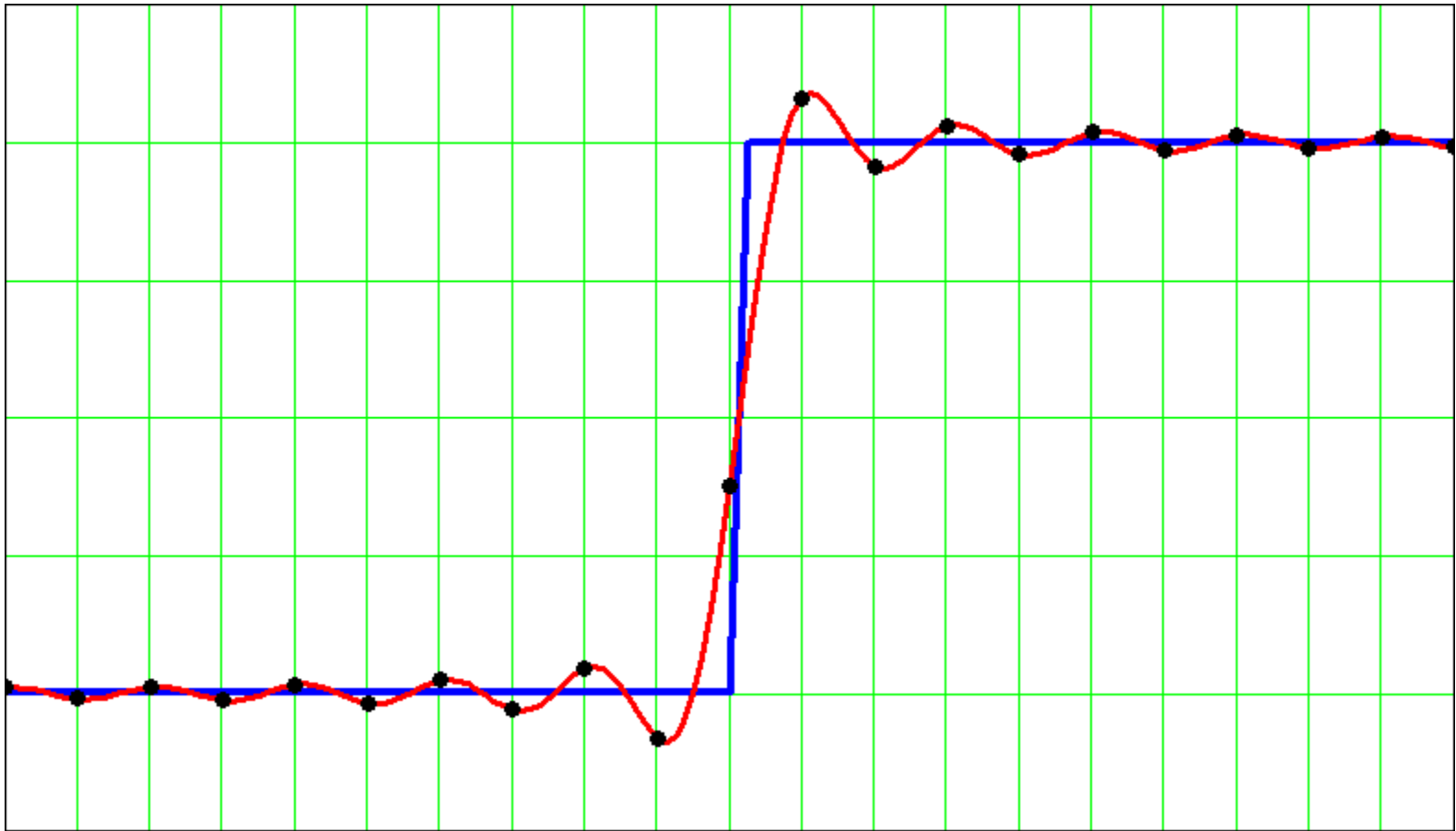


# Digital Filters in AD/DA Converters

## The Promise in Practice

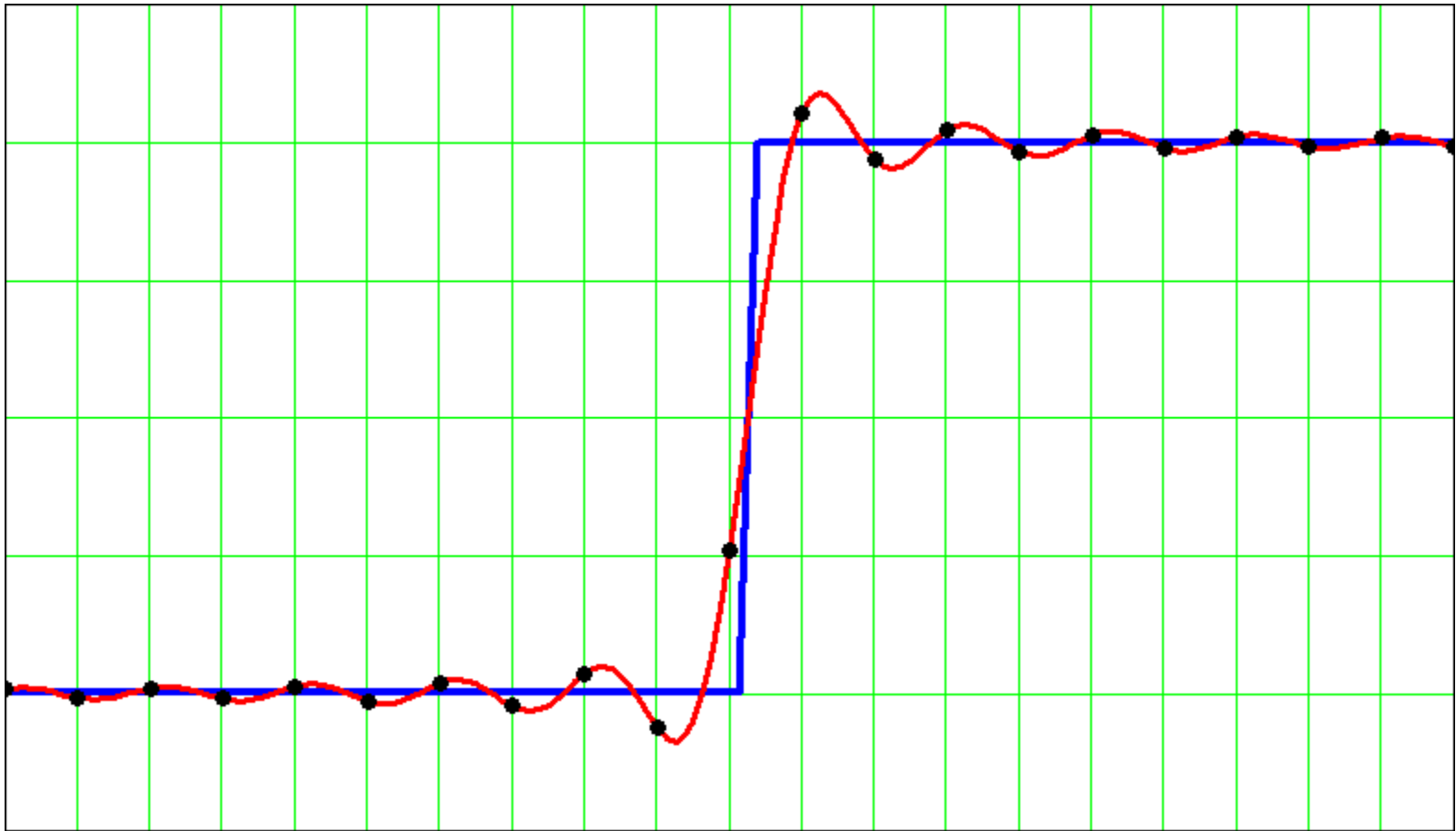


# Digital Filters in AD/DA Converters

## The Promise in Practice

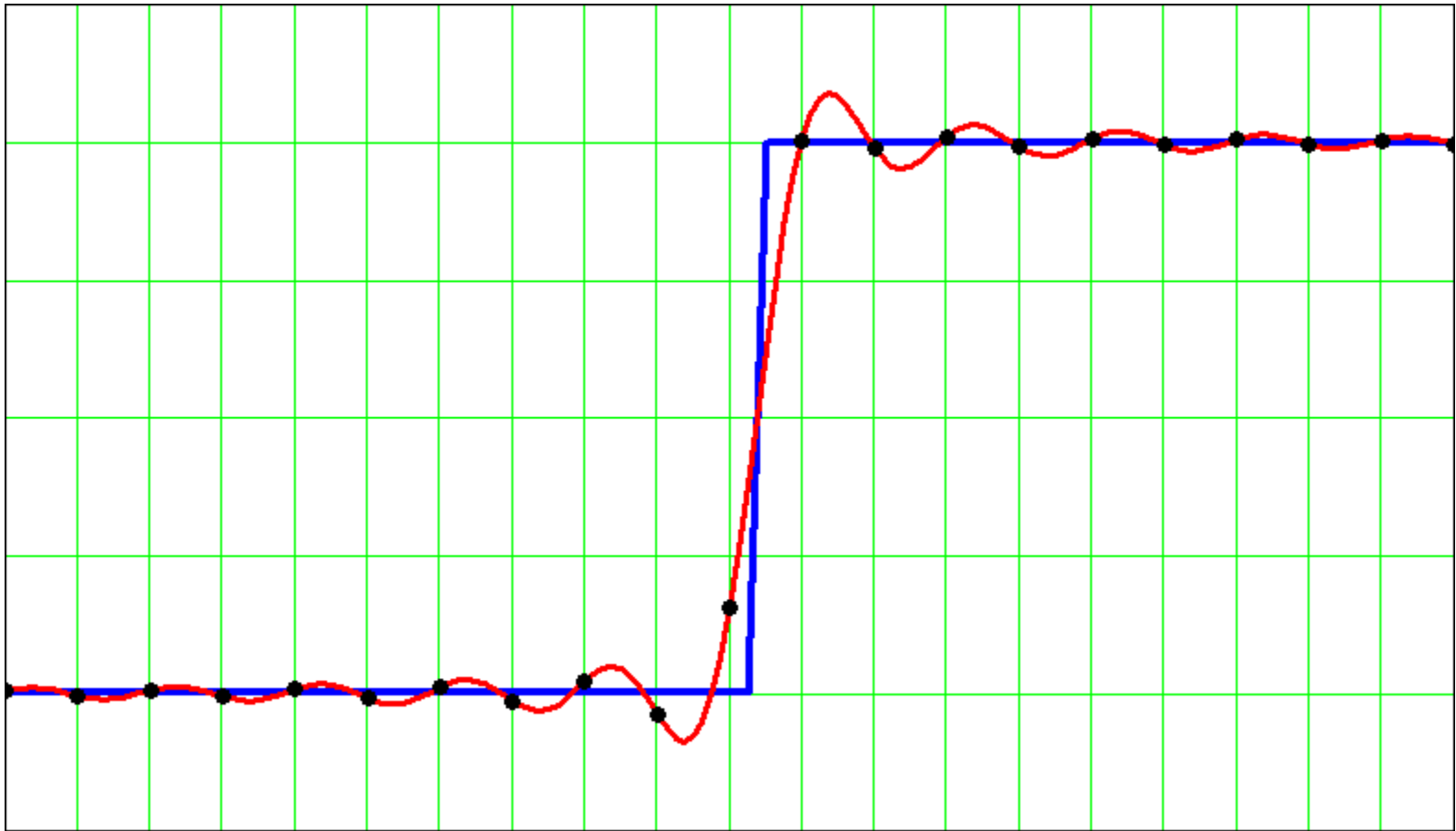

# Digital Filters in AD/DA Converters


## The Promise in Practice

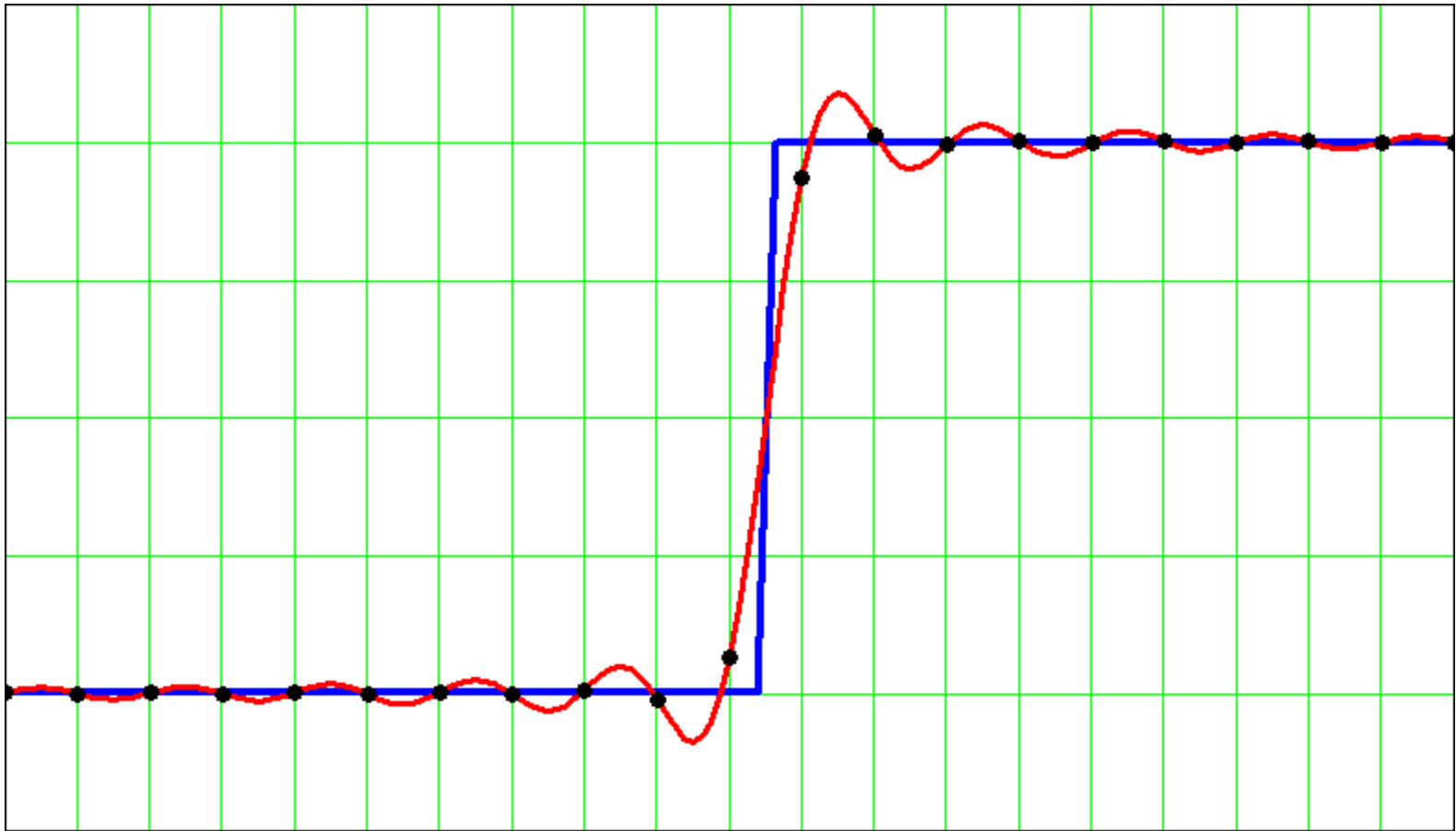

# Digital Filters in AD/DA Converters
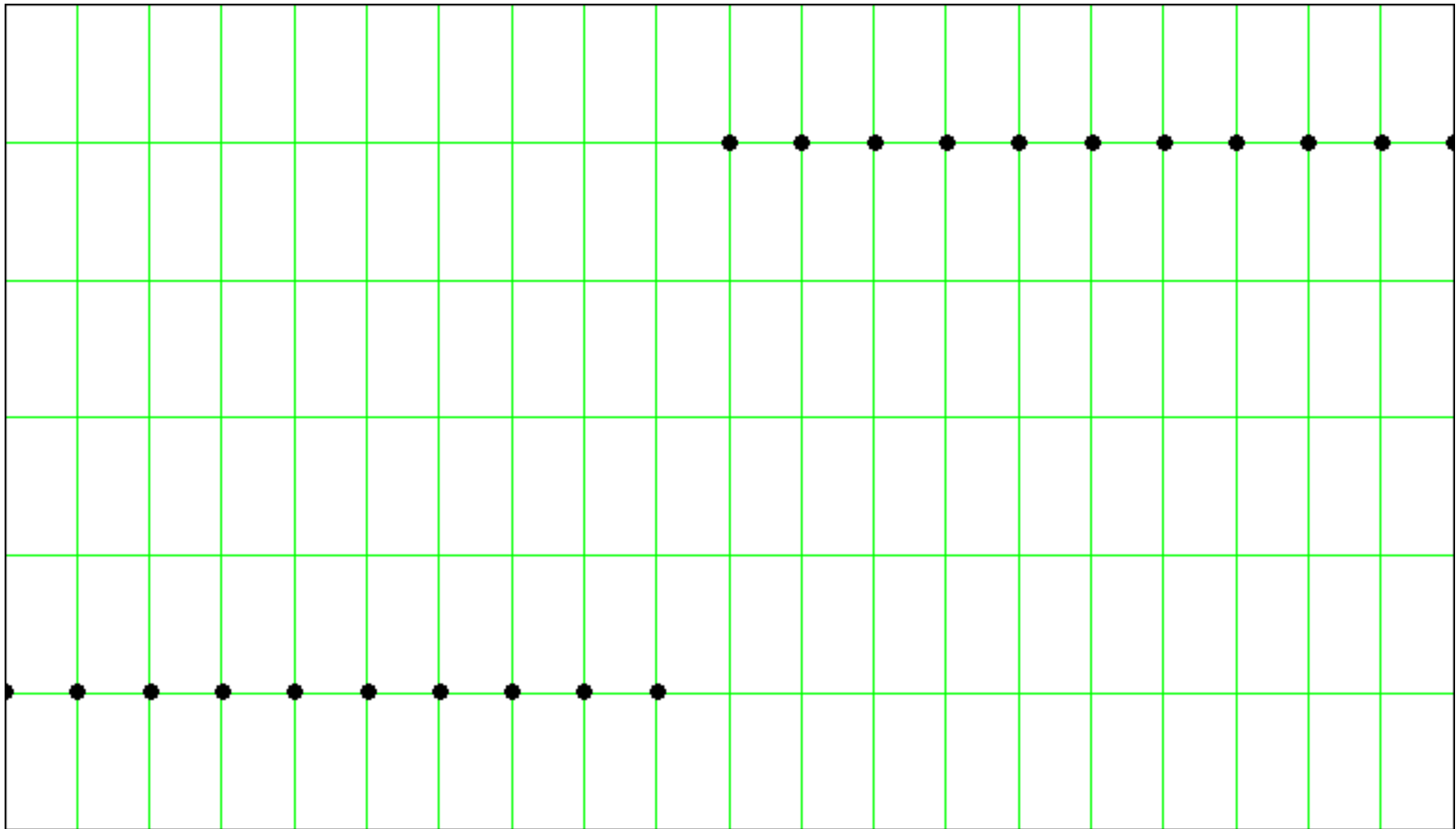
## The Nonoversampling Fallacy

- “Digital Square Wave” test signal looks like this:






# Digital Filters in AD/DA Converters
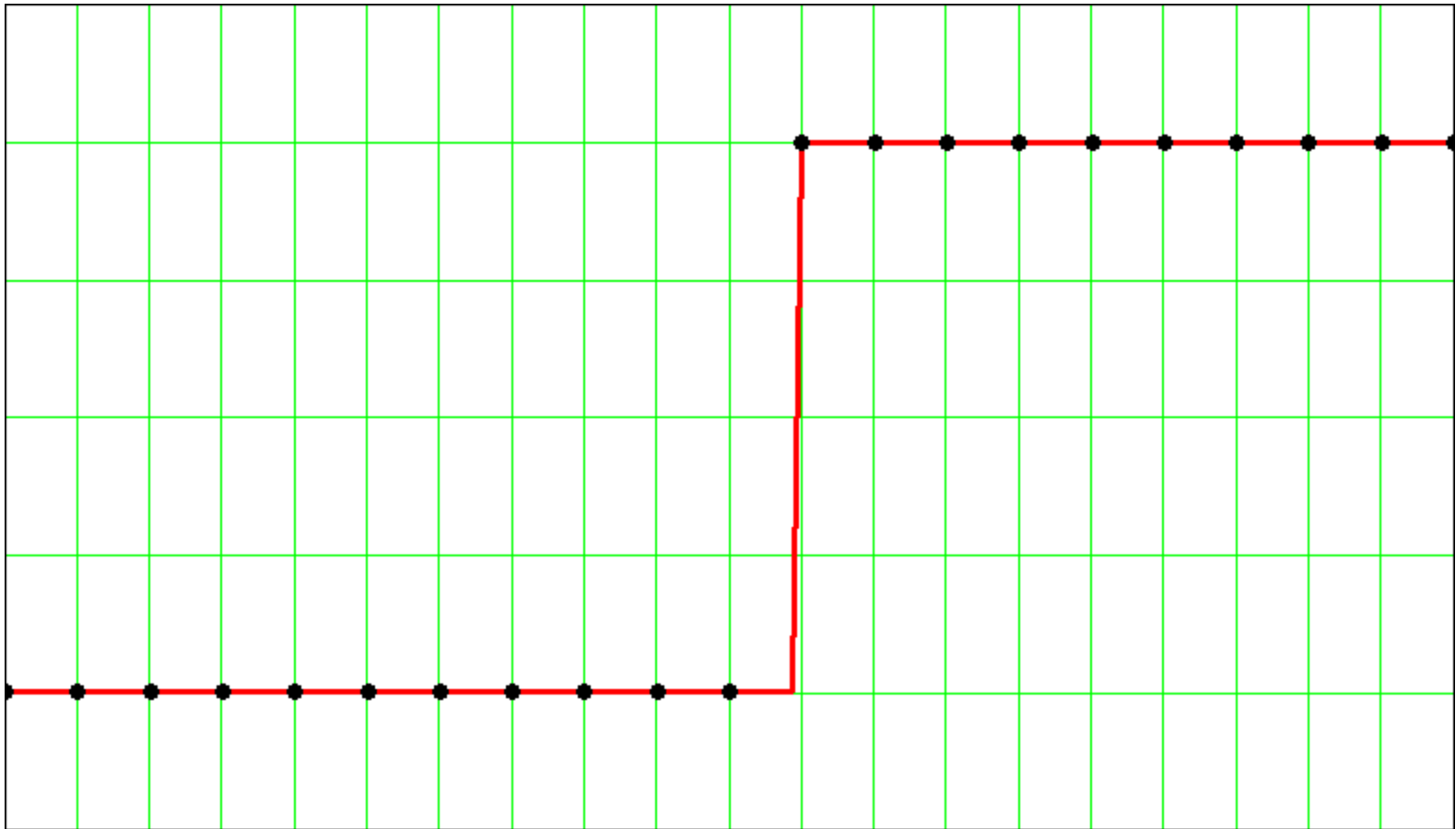
## The Nonoversampling Fallacy


- After “NOS conversion” (=zero order hold) we get:



# Digital Filters in AD/DA Converters

## The Nonoversampling Fallacy

- Now insert a half-sample delay:

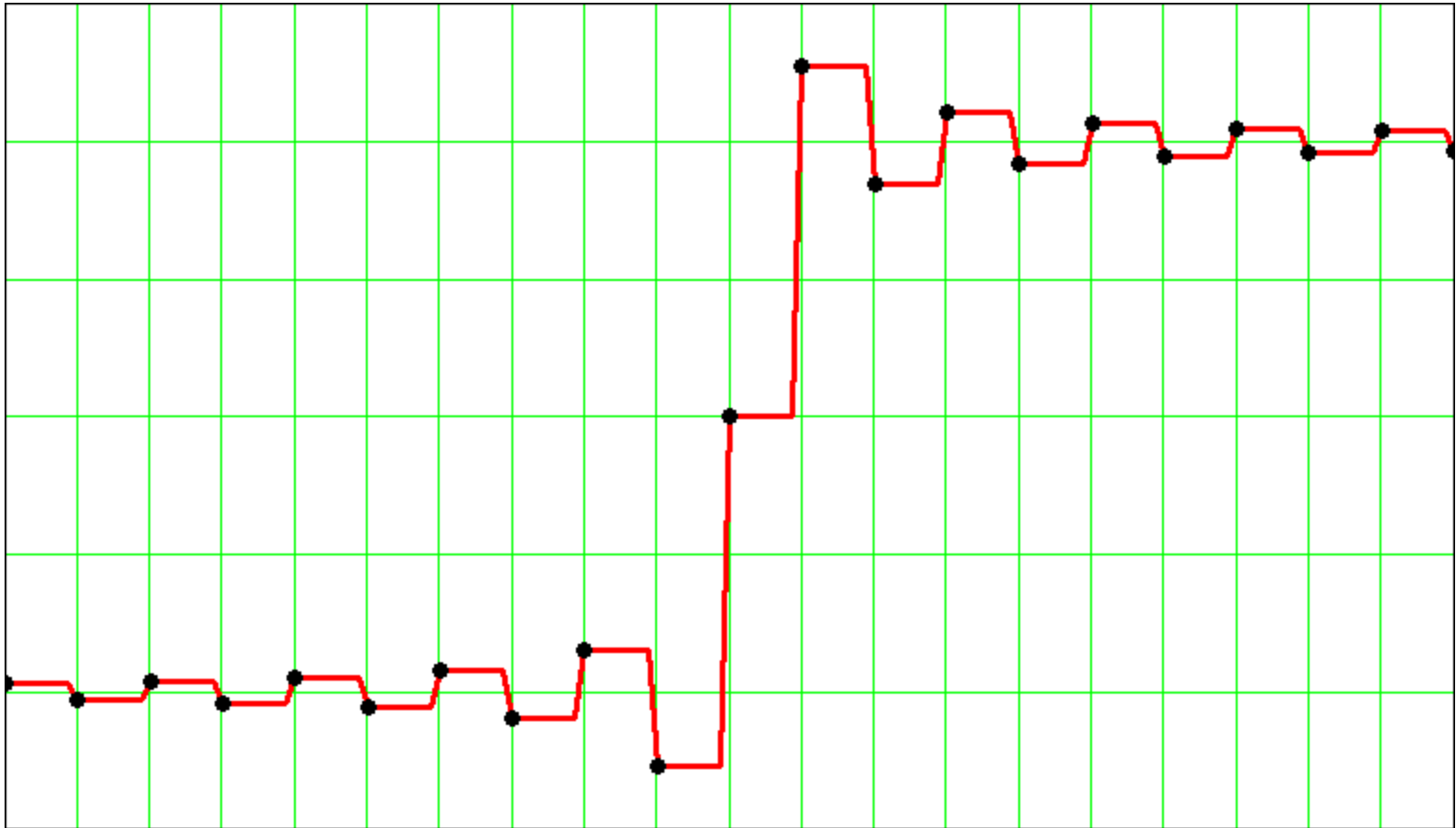


# Digital Filters in AD/DA Converters

## The Nonoversampling Fallacy

- Impulse Response becomes time-variant
- Fallacy was facilitated by the “Digital Squarewave” signals from test kit and test discs.

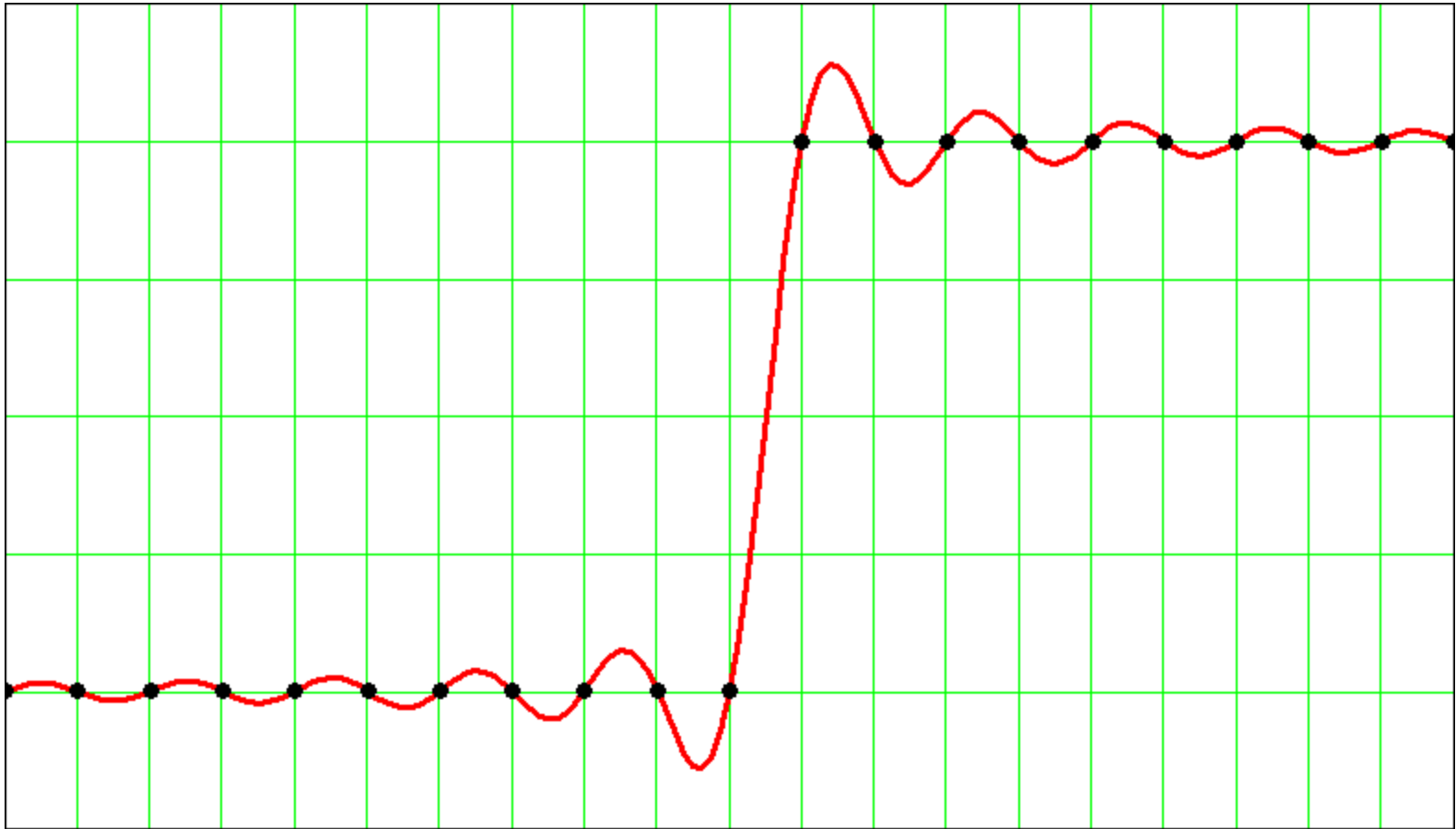
# Digital Filters in AD/DA Converters

- The “Digital Step Function” reconstructs like this:



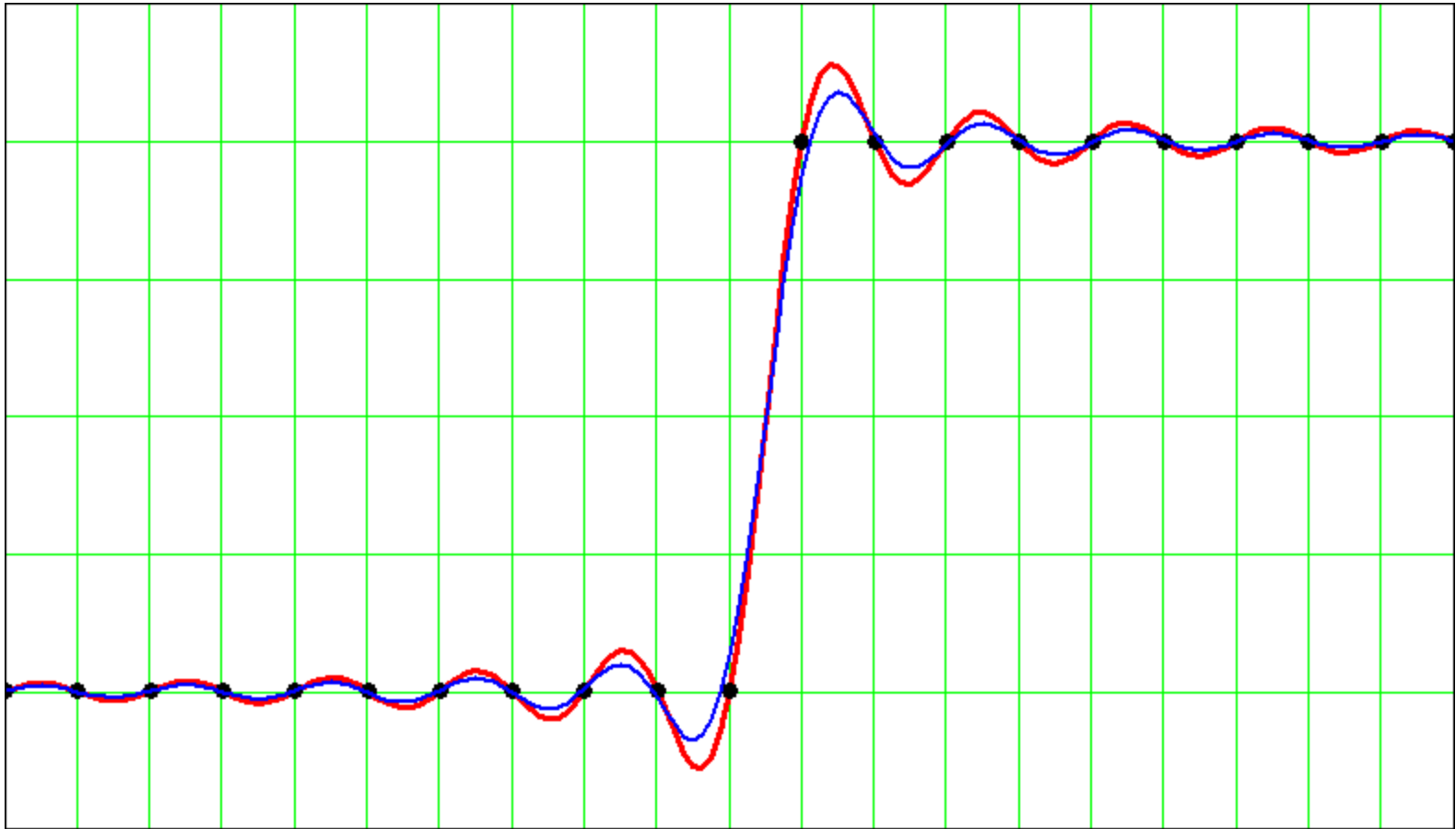
# Digital Filters in AD/DA Converters

- Contrast with an actual band-limited step function



# Digital Filters in AD/DA Converters

- Compare the spectra

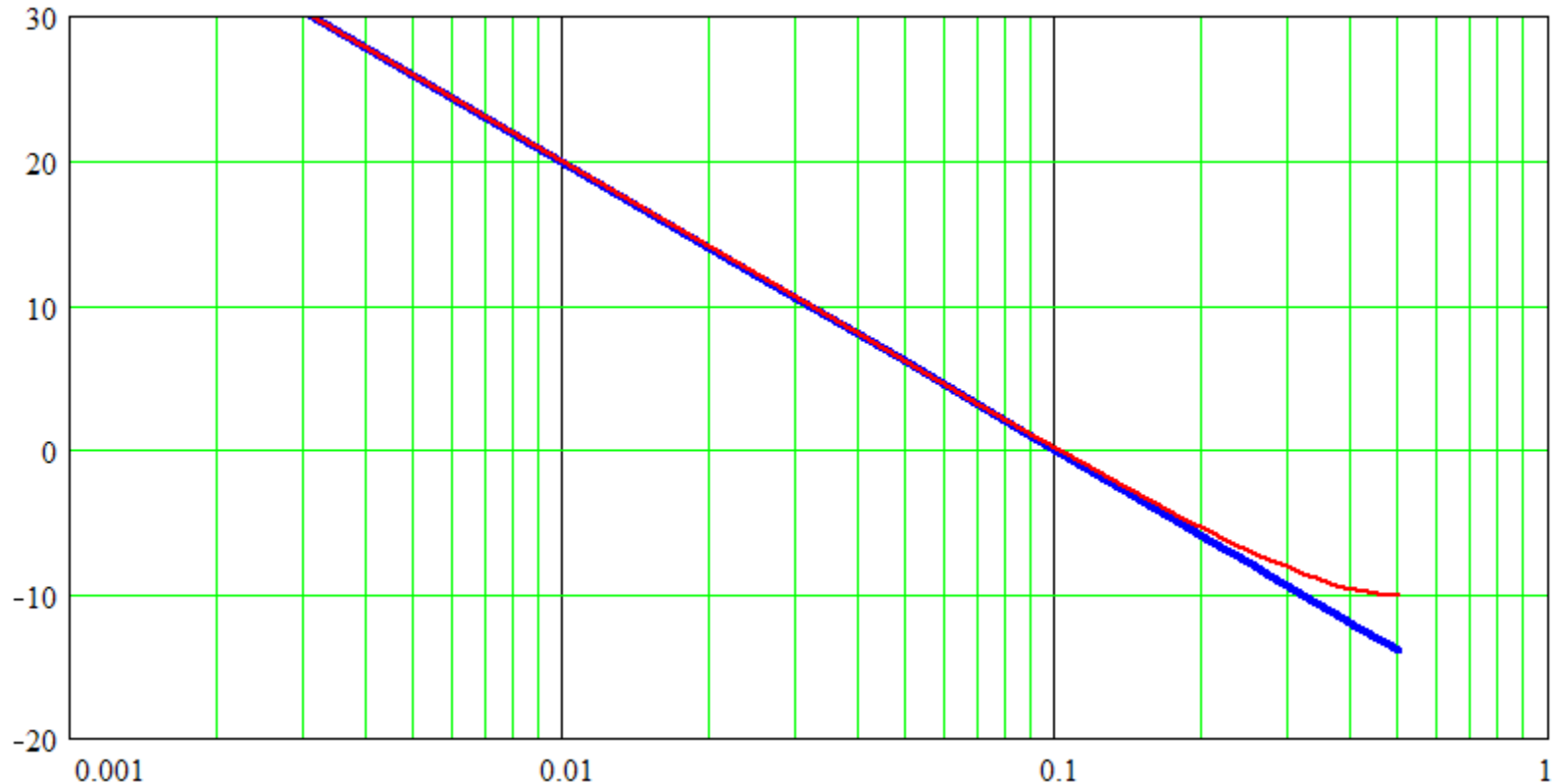


Dear test equipment designers: please provide a “true square wave” of arbitrary frequency

# NOS Rundown

- NOS DAC may sound OK
  - We really don't notice much beyond 20k...
- NOS DAC sometimes sounds better than *same* DAC with digital filter
  - DAC in these experiments is invariably ladder type
  - Glitch contribution goes up with sampling rate
  - Latch signal passes through filter chip (increased clock jitter)
- None relate to impulse response
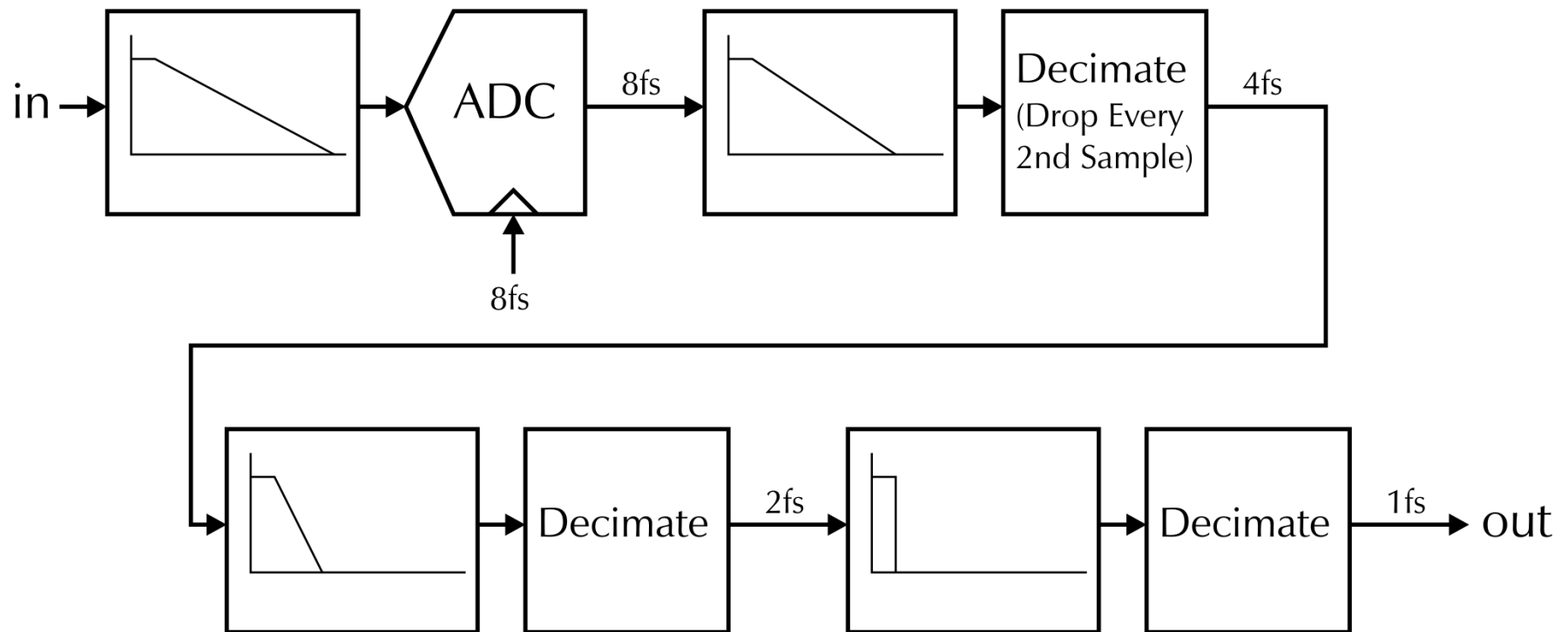
# Digital Filters in AD/DA Converters


- Antialias filtering in contemporary ADC's is mostly done digitally, in a "decimation chain"






# Digital Filters in AD/DA Converters

Gabarith for 8fs -> 4fs filter stage

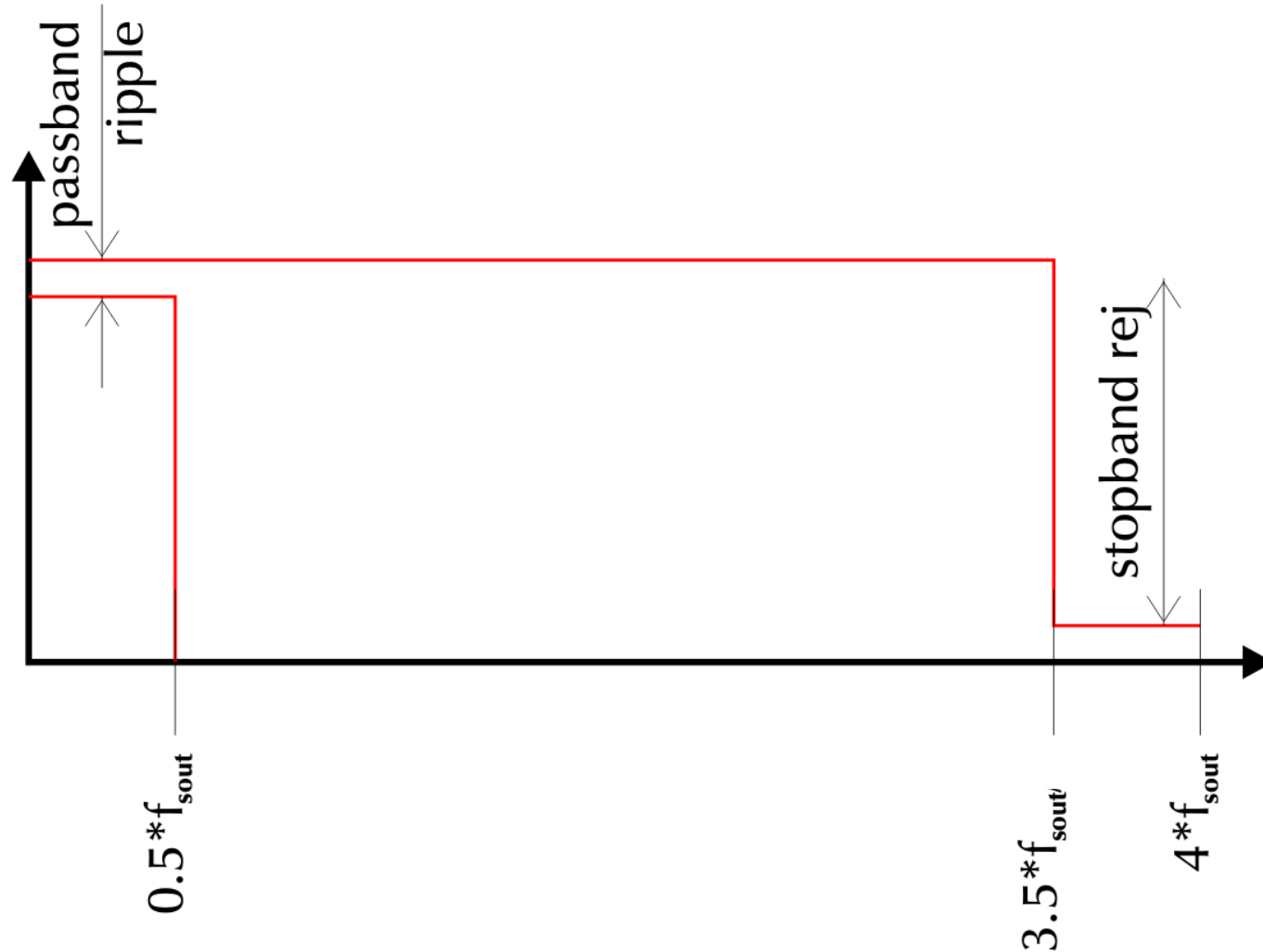

# Digital Filters in AD/DA Converters

Gabarith for 4fs -> 2fs filter stage

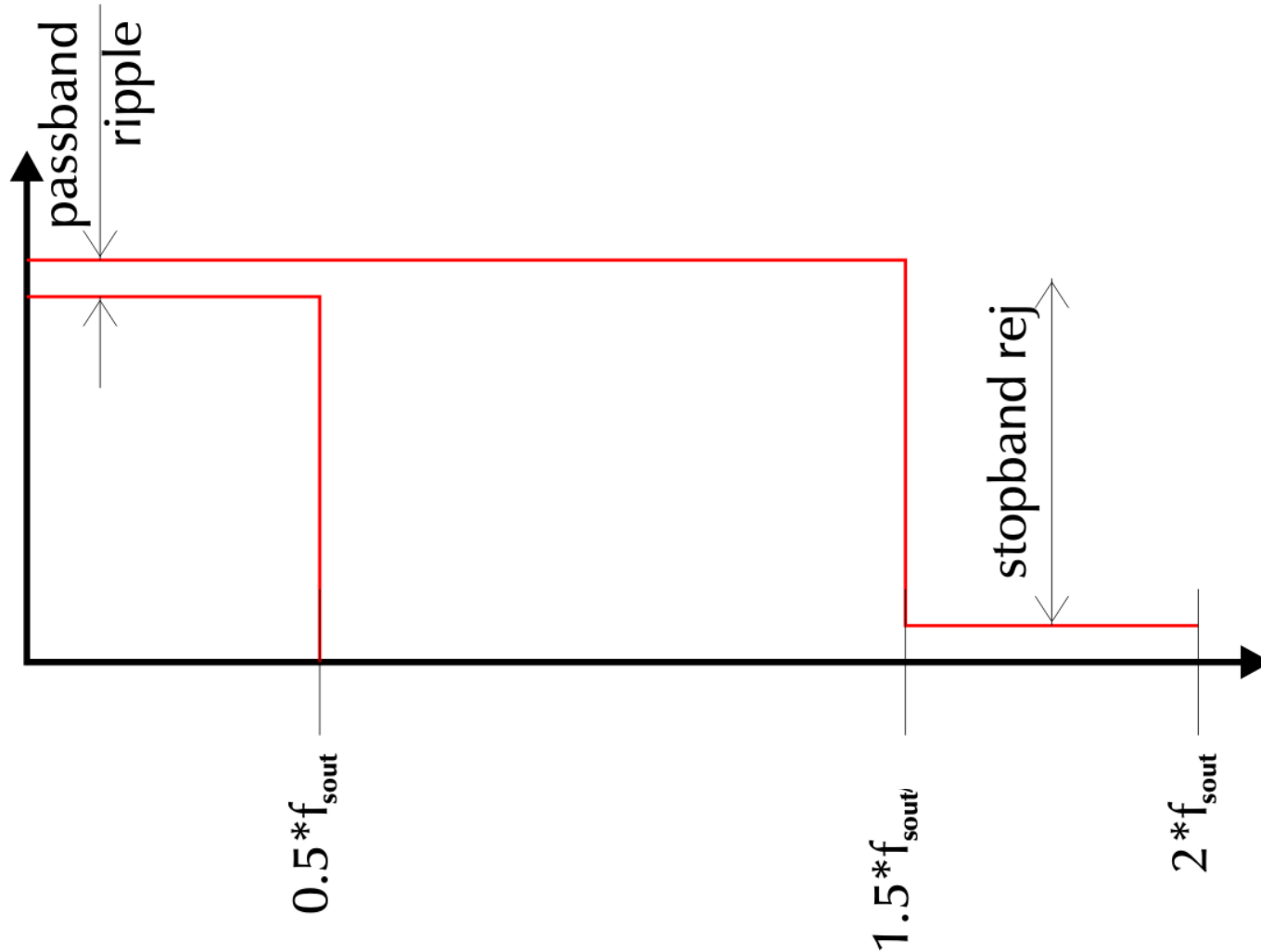


# Digital Filters in AD/DA Converters

A perfect candidate: The Half-Band filter

- Magnitude response is chosen symmetrical round 0.25fs and 0.5.
  - Stop band =  $0.5f_s$  - pass band
  - Stop band rejection = stop band ripple


# Digital Filters in AD/DA Converters

## Half-Band filter, Magnitude Response

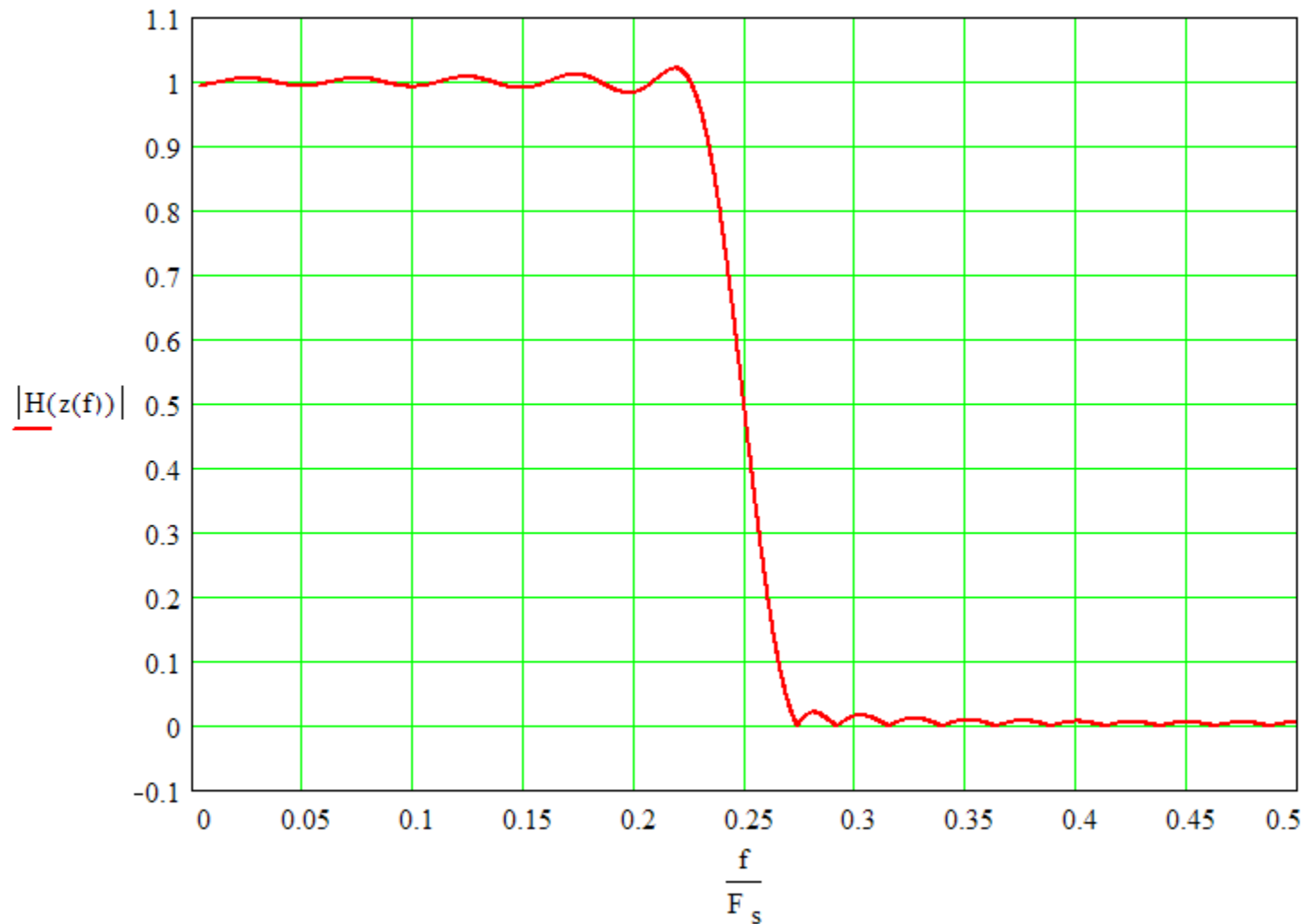


# Digital Filters in AD/DA Converters

## Half-Band filter, coefficients

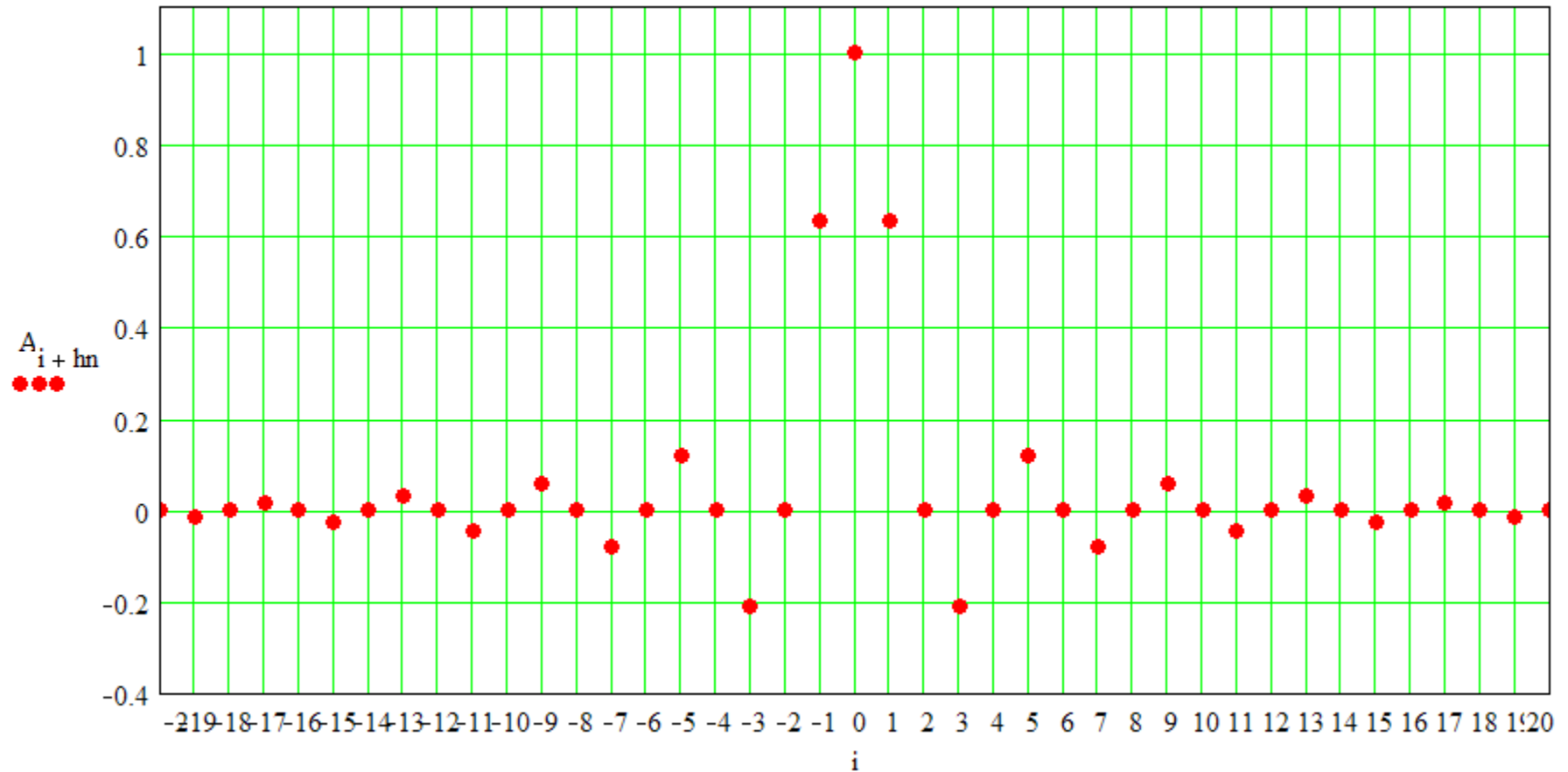
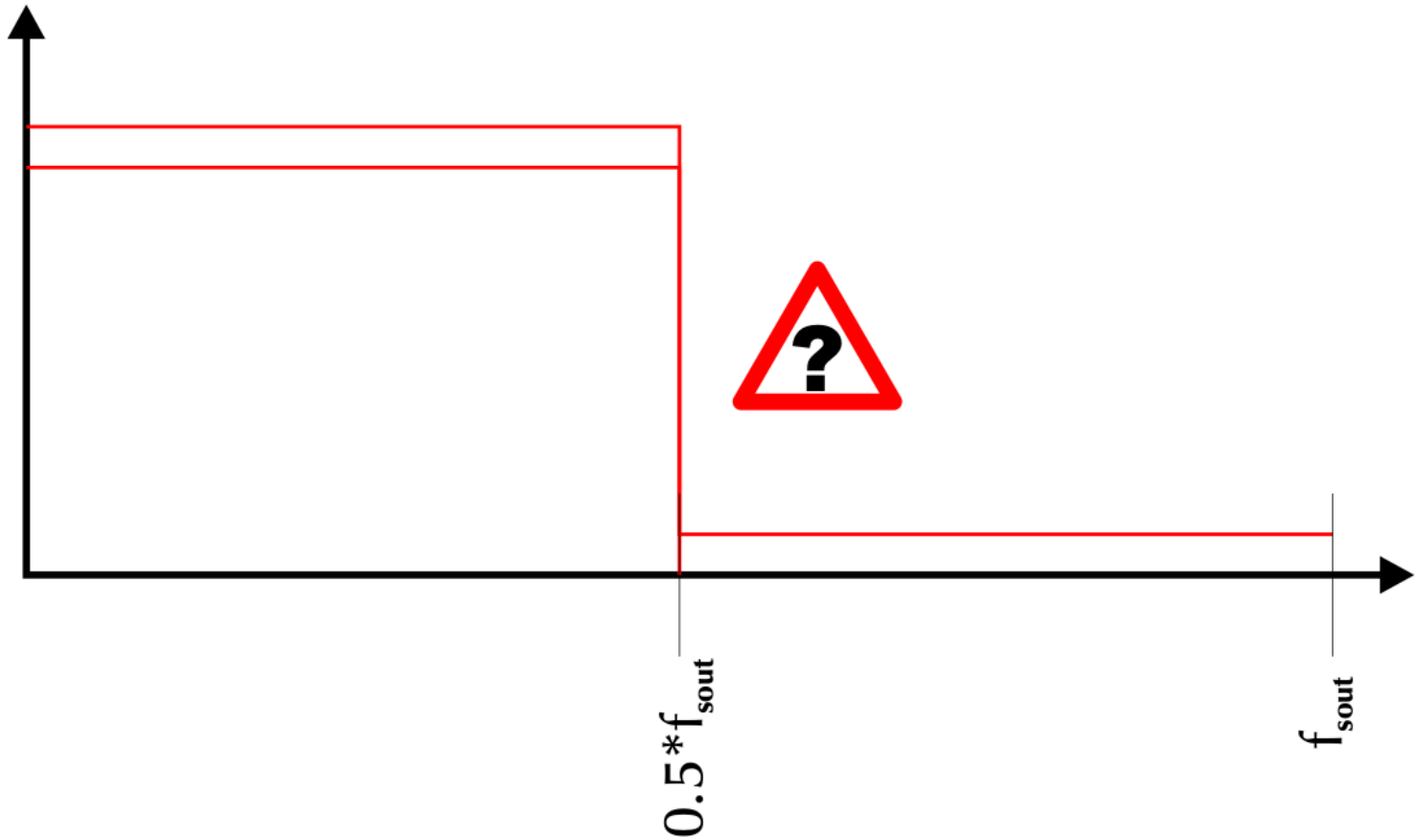
# Digital Filters: Design Compromises


Gabarith for  $2f_s \rightarrow 1f_s$  filter stage.



Oops.
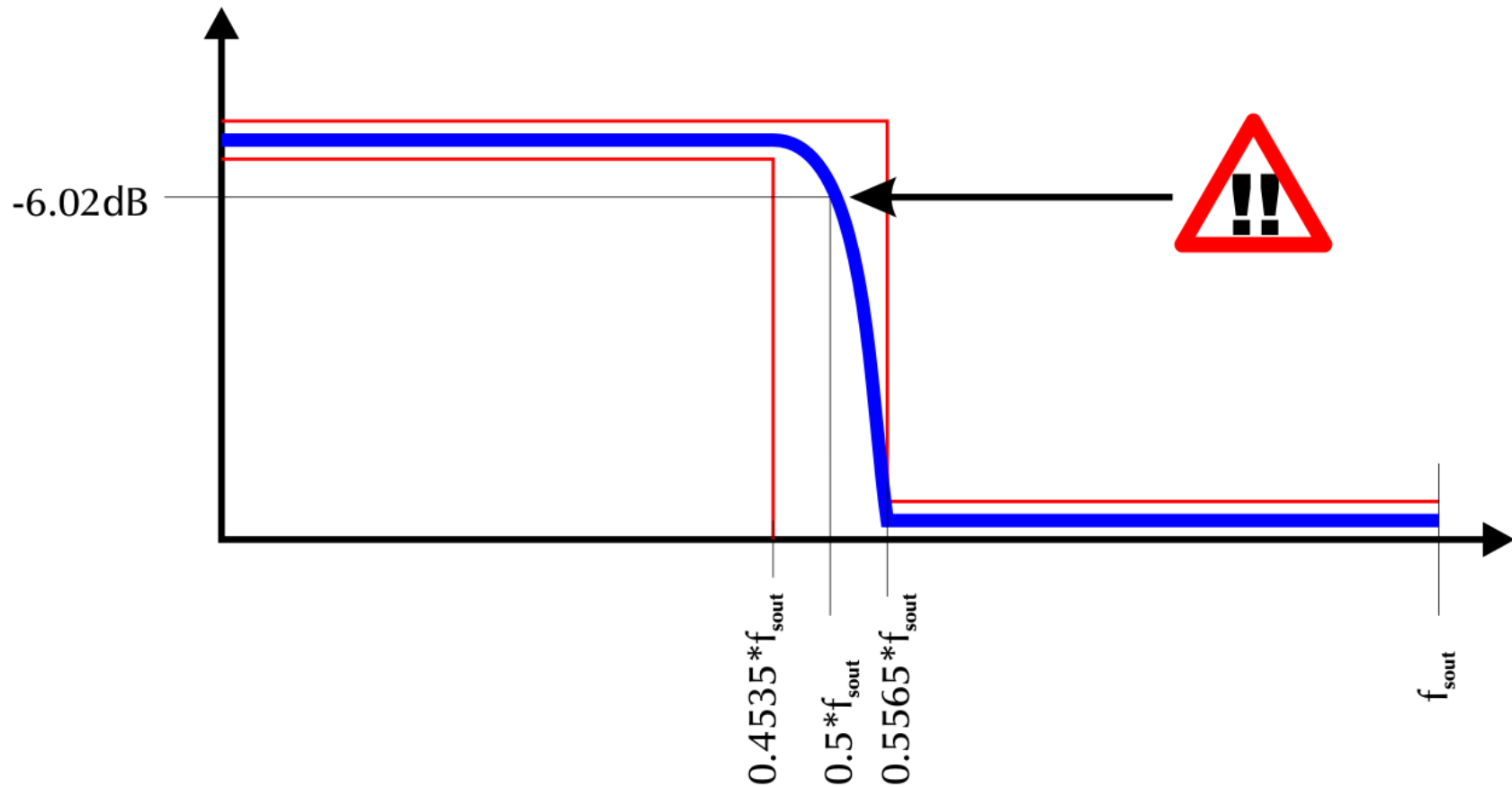
# Digital Filters: Design Compromises

Typical final stage in commercial converters



Cut & dried breach of Nyquist criterion!

# Digital Filters: Design Compromises

$$0.4535 * 44.100\text{kHz} = 20.000\text{kHz}$$




# Digital Filters: Design Compromises

# Result

- [illegible]

# Digital Filters: Design Compromises

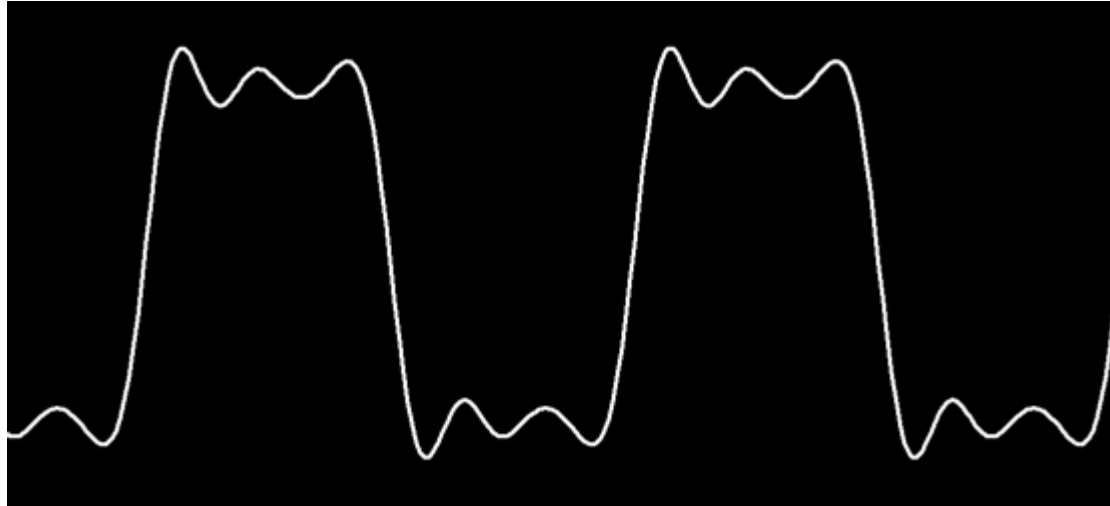


To human ears:

- TOA cues are affected for signals with significant HF.
  - Sibilants in choral music, wind and string instruments smear across the whole stereo image.
- Nearly no impact for panpot stereo.
  - Alias components are in phase across channels

# Digital Filters: Design Compromises

## How to Salvage a Burnt Steak

- Cut off the blackened bits.

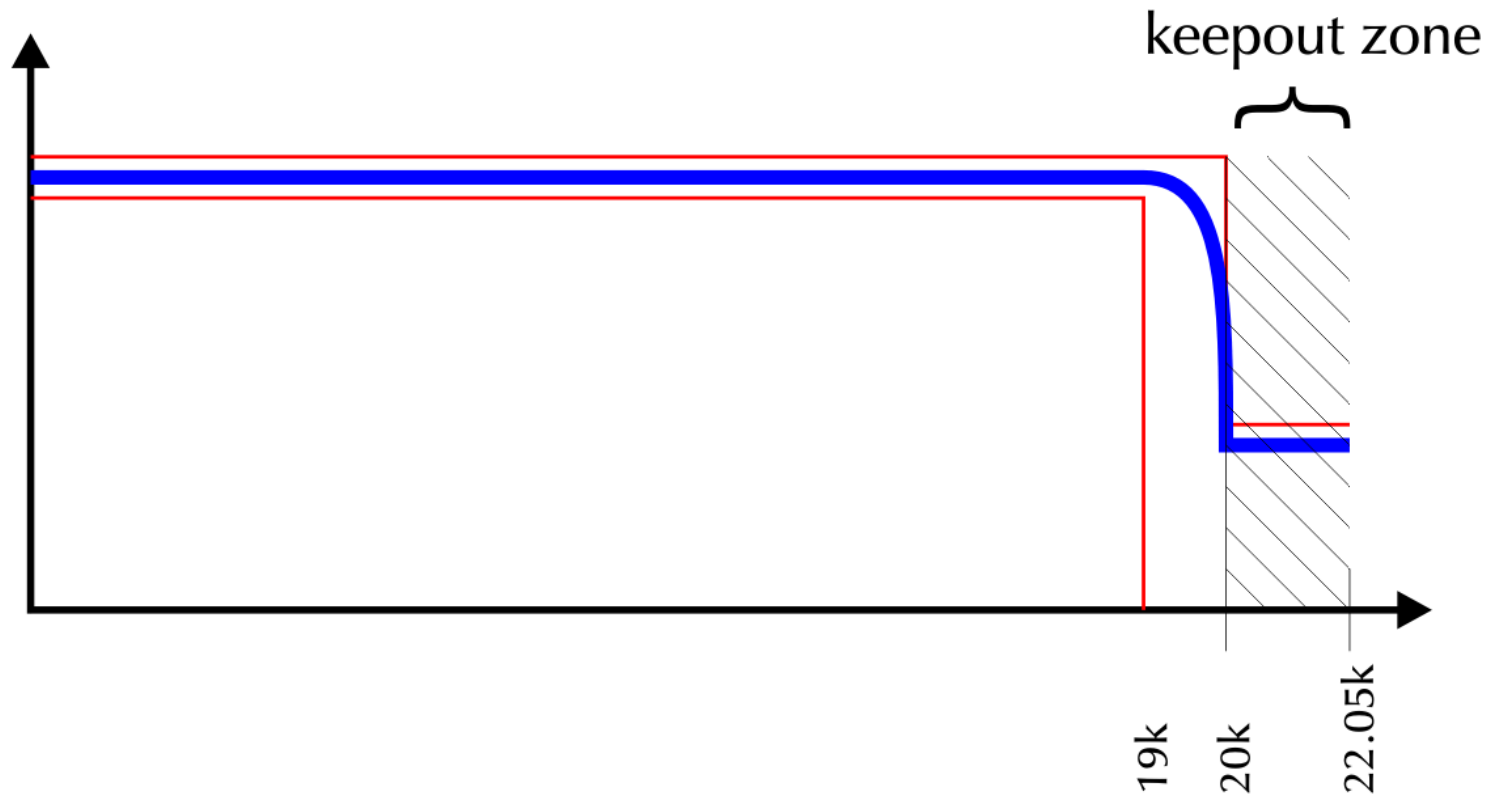

# Digital Filters: Design Compromises


## Applicability of Steak-Salvaging filter.

- Use once in the entire record-replay chain
  - The rest of the chain may keep using halfbands.
- Check by ear
  - The 44.1kHz version has a sonic signature.
  - Weigh against improved imaging.

# Digital Filters: Design Compromises

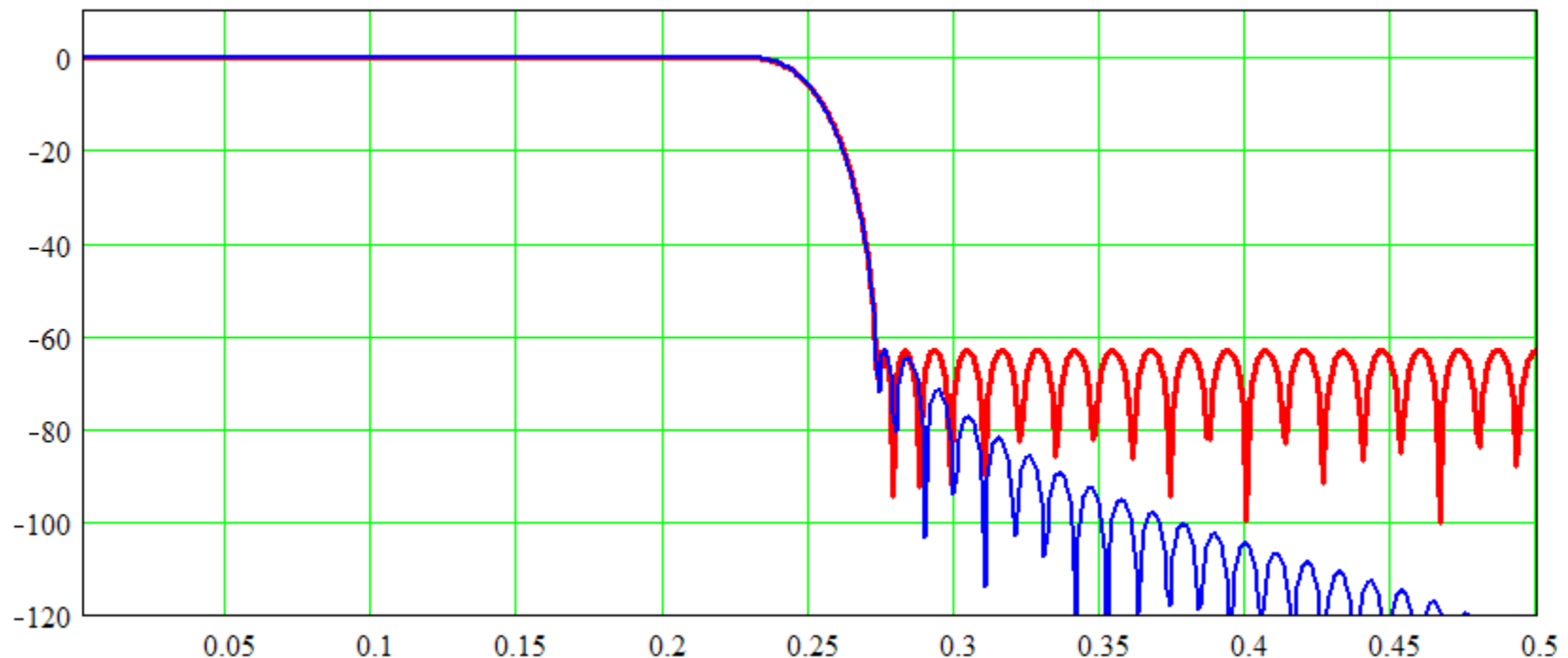
## The Equiripple Filter

- “Just Enough” attenuation = minimum number of coefficients.
- Windowed Sinc filters roll off further inside the stop band. Unnecessary attenuation increases length.
- Example: **Equiripple, 75 taps**. **Windowed, 95 taps**.



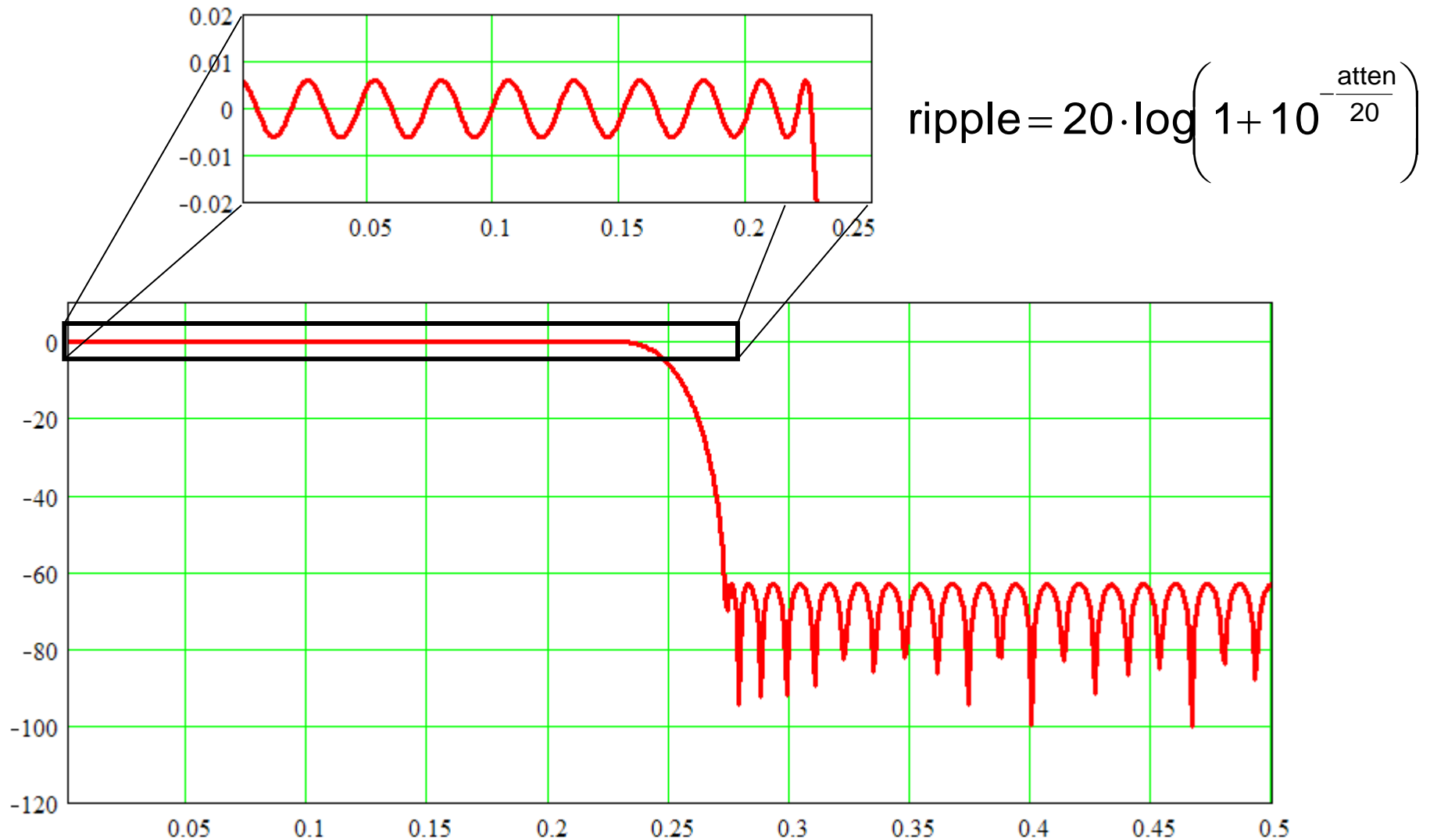
# Digital Filters: Design Compromises

In a halfband filter, ripple and attenuation are linked



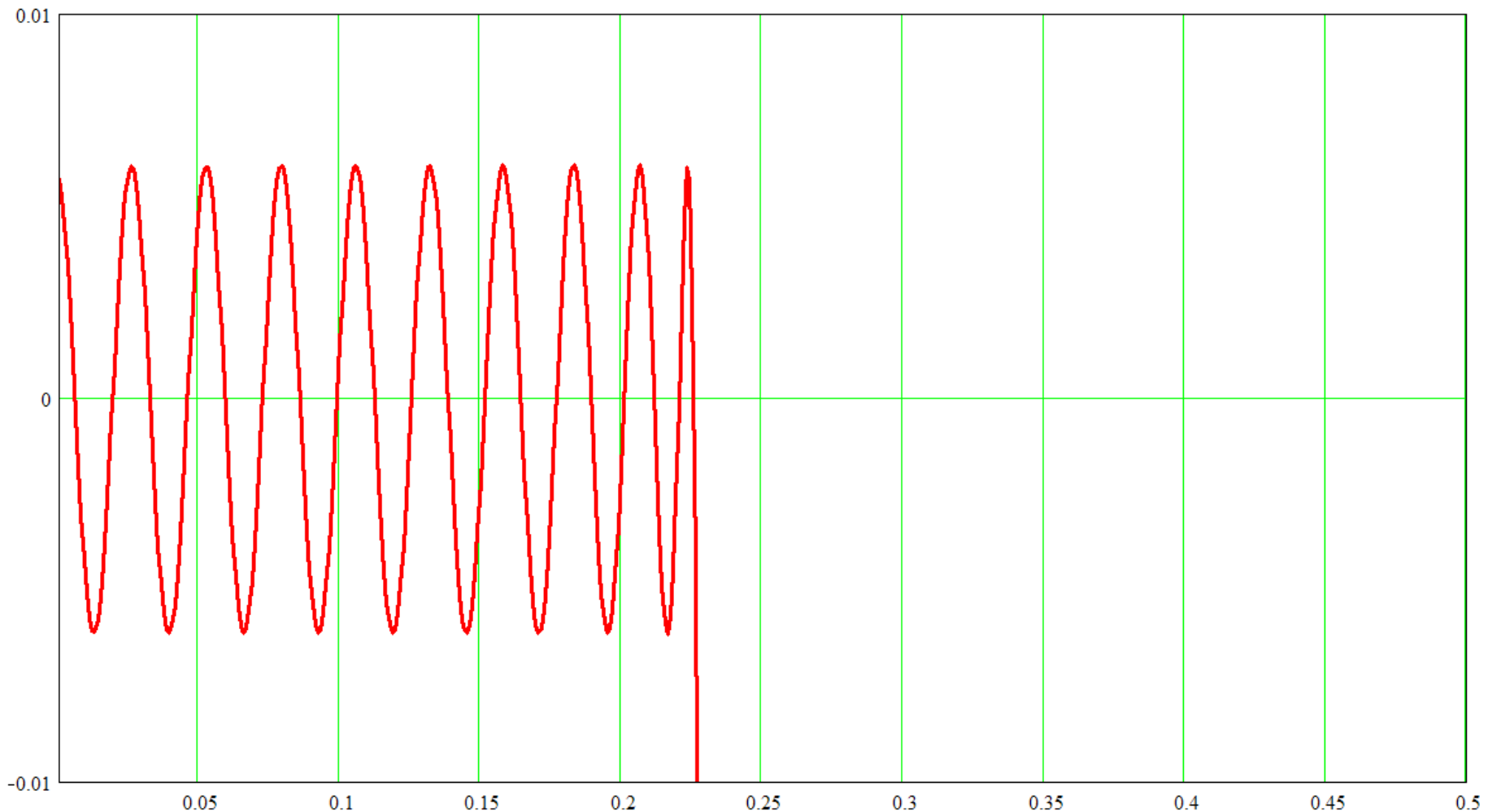
# Digital Filters: Design Compromises

Ripples are equal in amplitude and nearly equally spaced. Spacing  $\approx 2/(\text{\#taps}+1)$


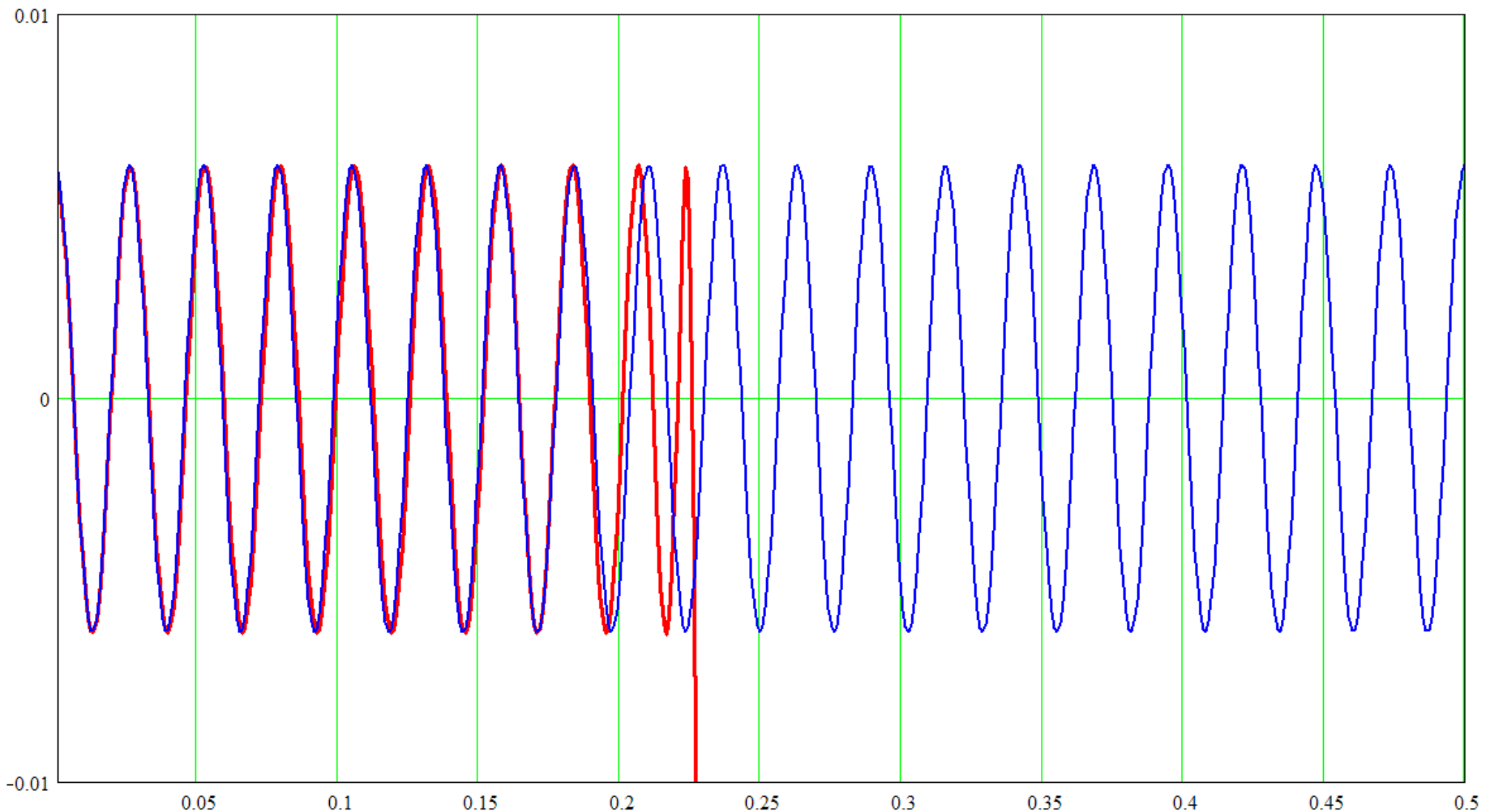
# Digital Filters: Design Compromises


Let's define another linear-phase filter with nearly the same in-band response




 
# Digital Filters: Design Compromises


Impulse response of that filter (exaggerated):



- Constant in-band ripple equates to echos at the ends of the filter.
- Amplitude of echos = stop band attenuation – 6dB
- Post-echo is certainly masked. Pre-echo possibly not.



# Digital Filters: Design Compromises
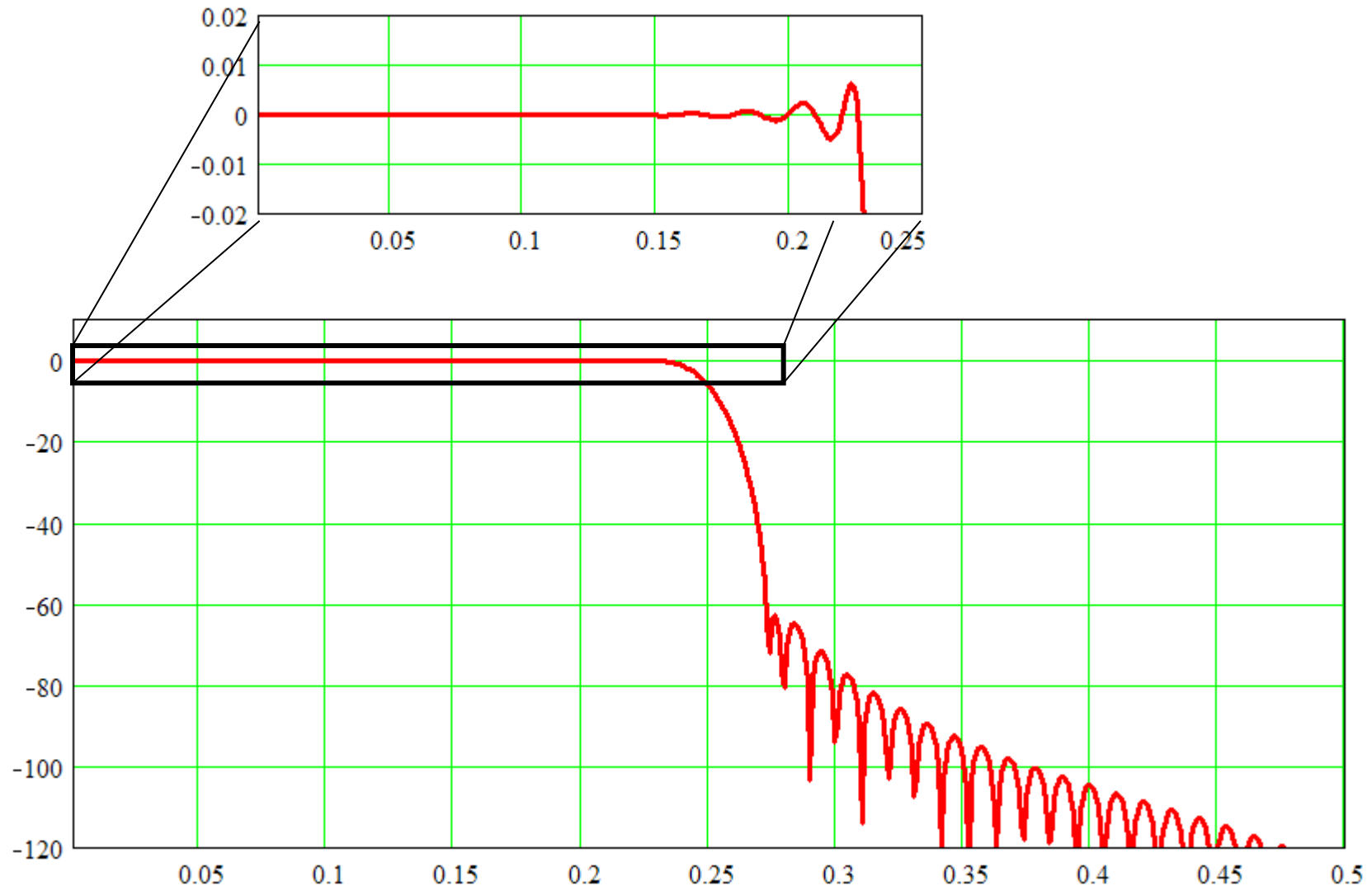
## Close-up of ripple of windowed sinc filter



# Digital Filters: Design Compromises

Compare 2 halfband filters at 95 taps

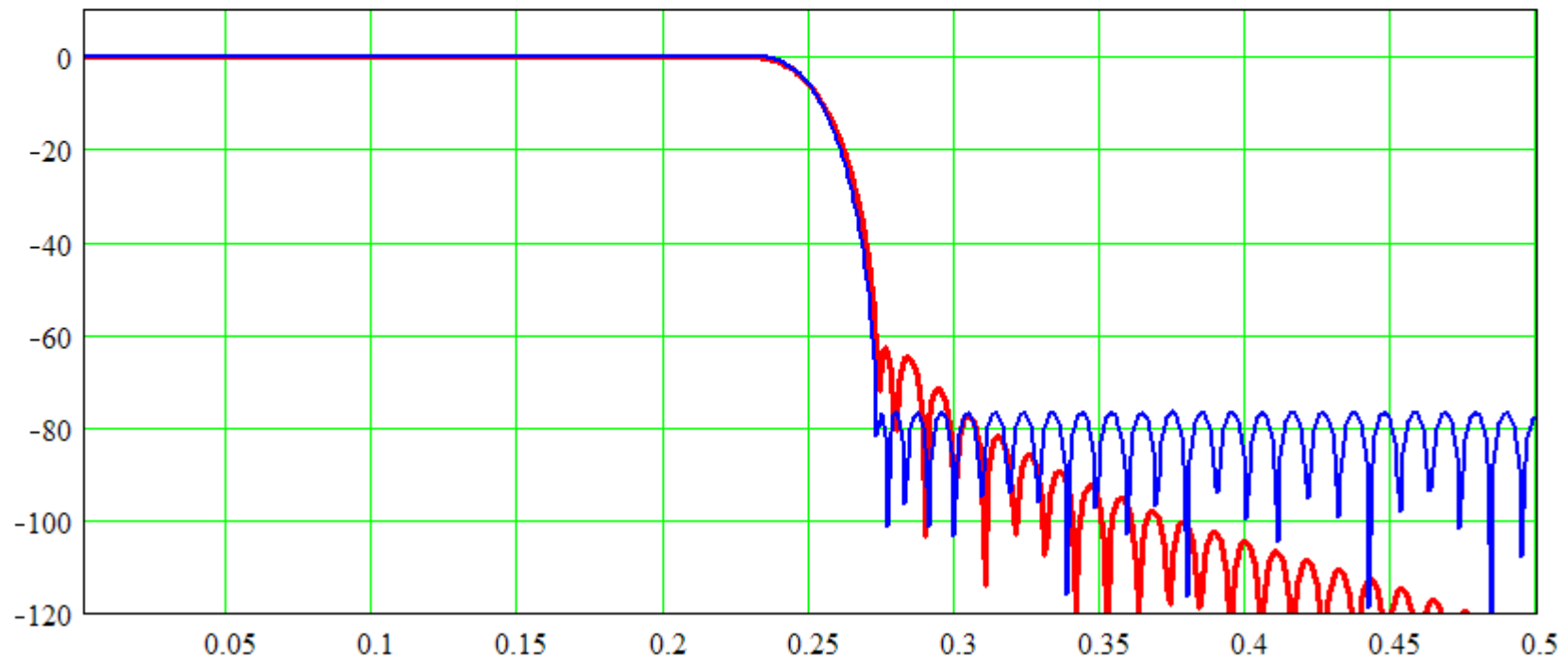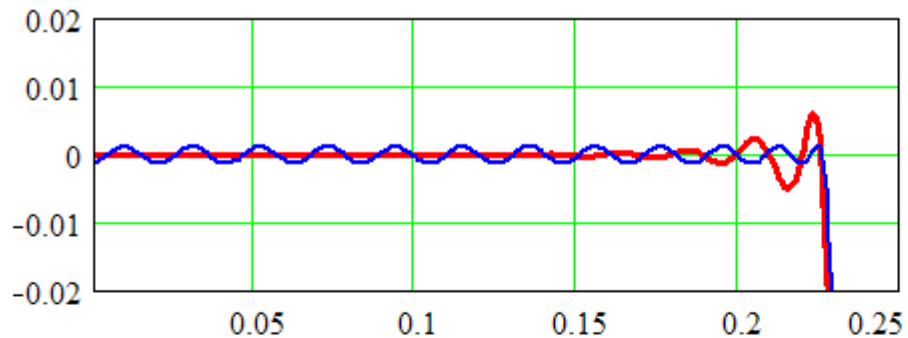

# Digital Filters: Design Compromises

## Import on “digiphobia”

- Classic argument against digital: “pre-ringing”
  - Little serious evidence of audibility of pre-ringing outside the audio band exists.
  - Looks like a red herring
- 2 common implementation problems were identified
  - Aliasing and Pre-Echo
  - Audible deficiencies are linked to compromising.
  - Solved by better adhering to theory, not deviating further.
- Pre-ringing hypothesis is not needed!
  - You Hear What You Hear but it's Not What You Think.


# Testing the Pre-Ringing Hypothesis

## Testing audibility of brick wall filtering

- Use a 96kHz or 192kHz recording.
- Slice off 0.4535-0.5fs area.
- Test the following filters (never decimate):
  - 20kHz sharp-rolloff
  - 20kHz slow-rolloff
  - 40kHz sharp-rolloff

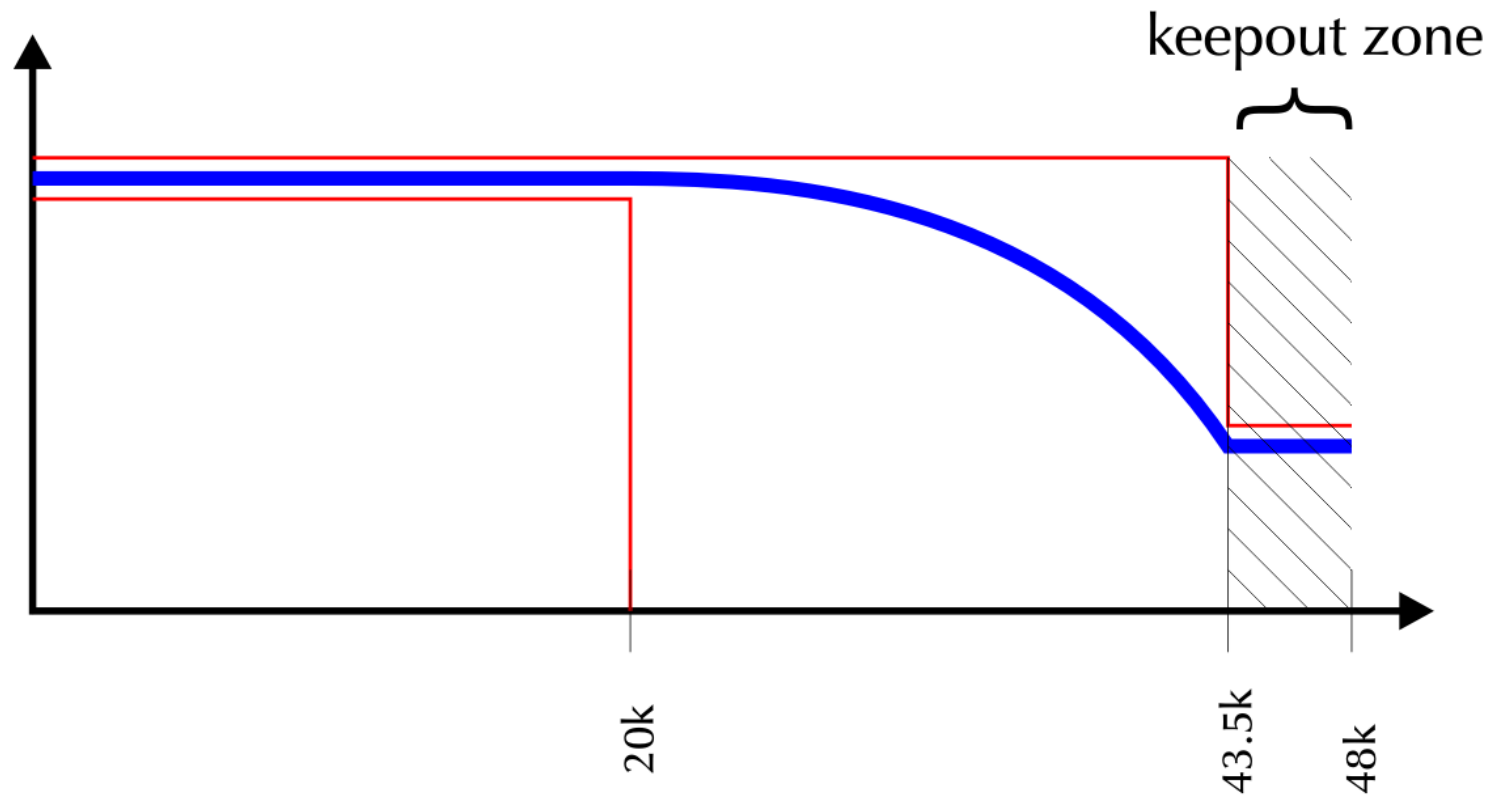
# Testing the Pre-Ringing Hypothesis

Effect of Slow-Roll Filter after the fact...


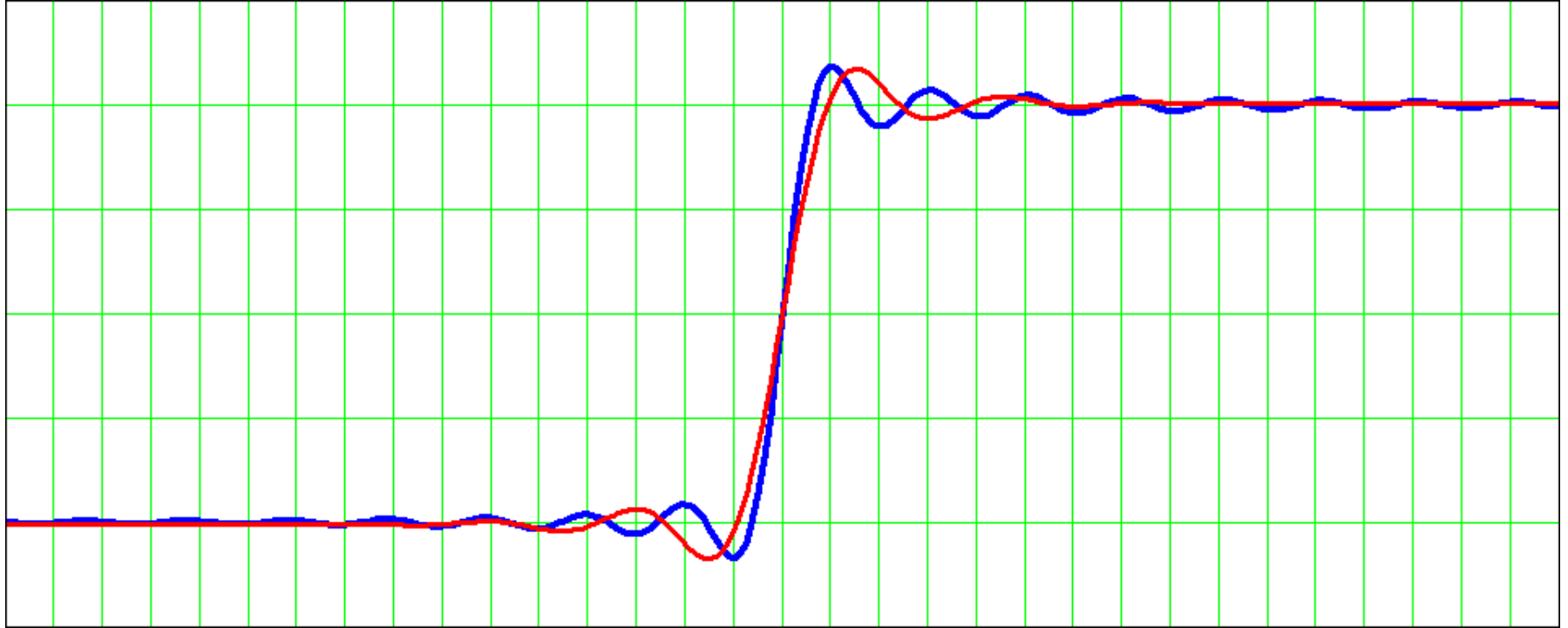
# Testing the Pre-Ringing Hypothesis

...reverses effect of sharp rolloff filters



(example: standard 96kHz AD/DA with slow LPF inserted)

# Testing the Pre-Ringing Hypothesis

Should we put Slow-Rolloff filters in IC's?



- NO! Compounded SR filters amount to a brick wall.
- Only brick-wall filters are “idempotent”.
- Use brick-wall filters throughout and shape response only once.



# Testing the Pre-Ringing Hypothesis
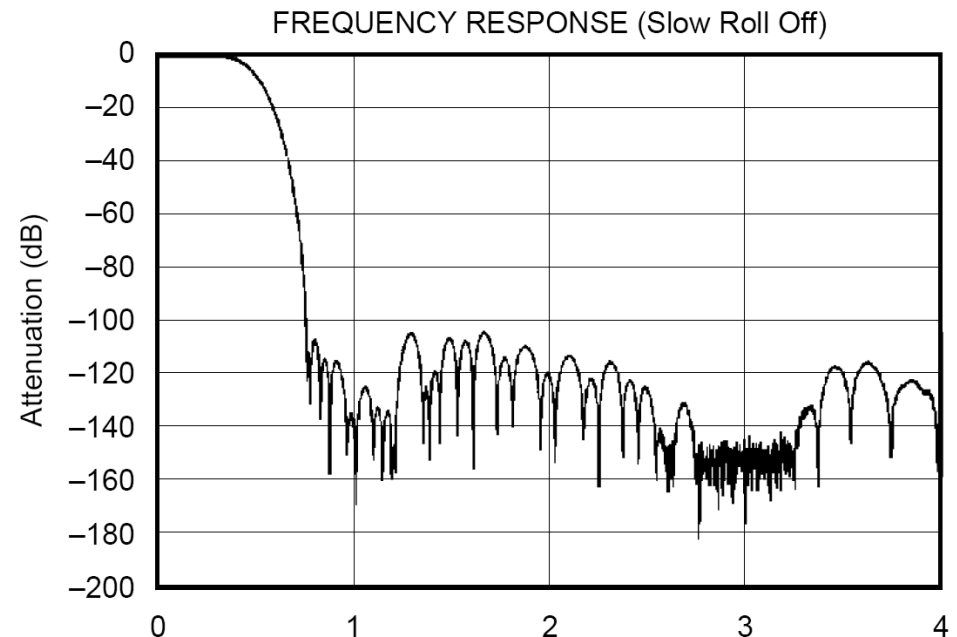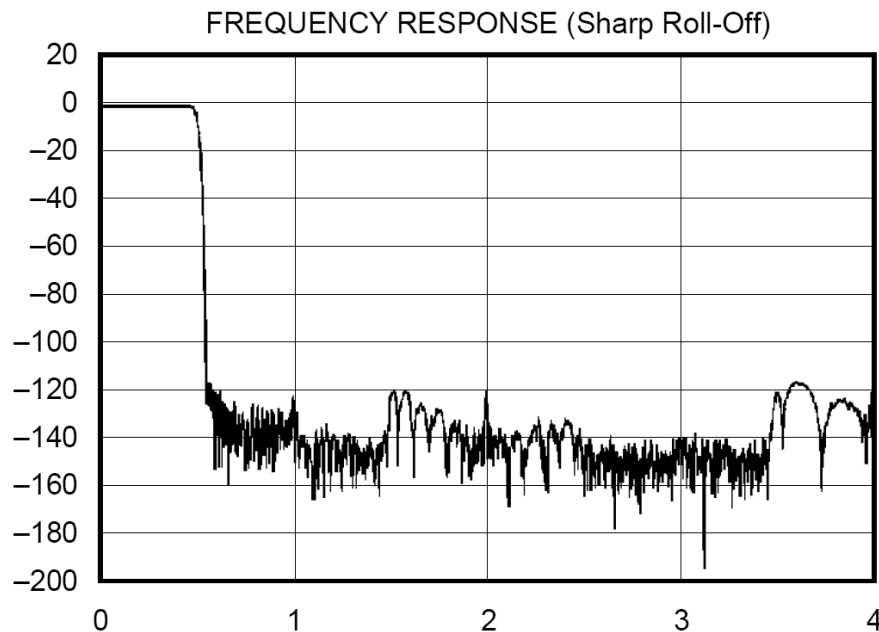
## How About The Slow-Rolloff Filters in Chip XYZ?

- Intended to reduce latency, NOT improve sound quality



# Testing the Pre-Ringing Hypothesis

## The Phase-Optimised Filter

- Reduces pre-ringing at the expense of post-ringing



- Magnitude response is maintained
- Cost-effective implementation (IIR+short FIR at  $f_{\text{sout}}$ )
- Reduces latency with minimal loss of sound quality

# Testing the Pre-Ringing Hypothesis

Are phase-optimised filters a good thing?

- YES. Much better tradeoff between audio performance and latency.


Should phase-optimised filters be standard?

- NO. One pass may be inaudible but 2 passes? 10?
- “Improved sound quality” claim is based on pre-ringing hypothesis.

# Asynchronous SRC: The Fine Print

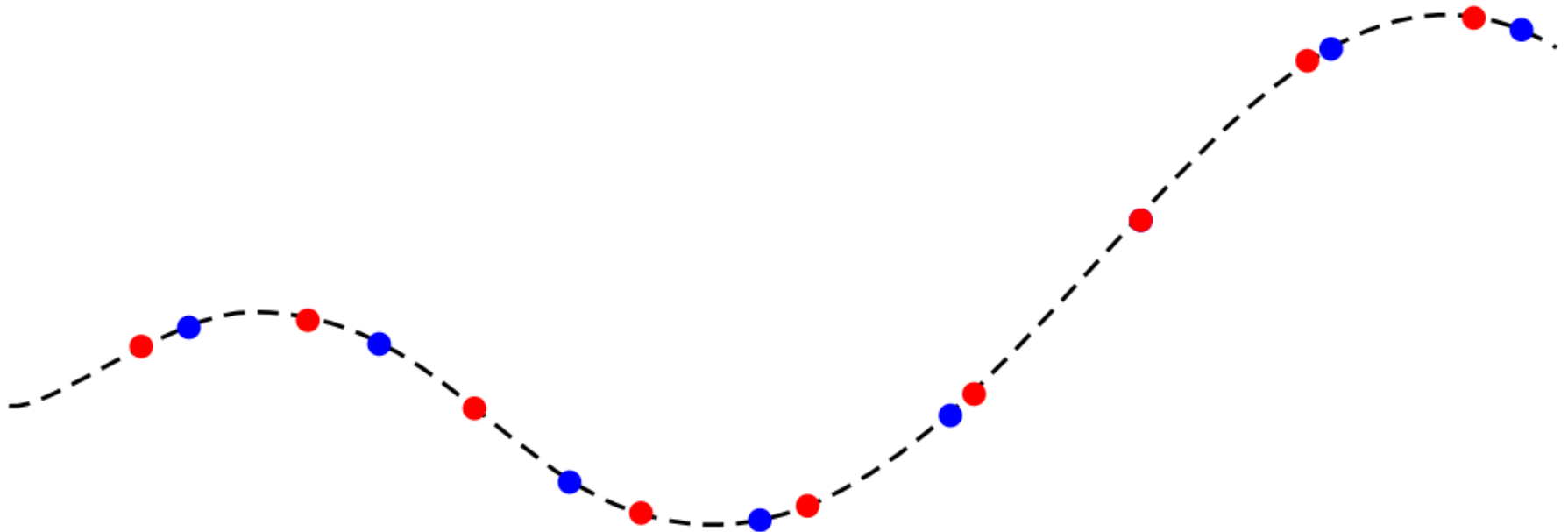
## What SRC does

- Reconstruct waveform, resample at new rate
- Done by interpolation



# Asynchronous SRC: The Fine Print
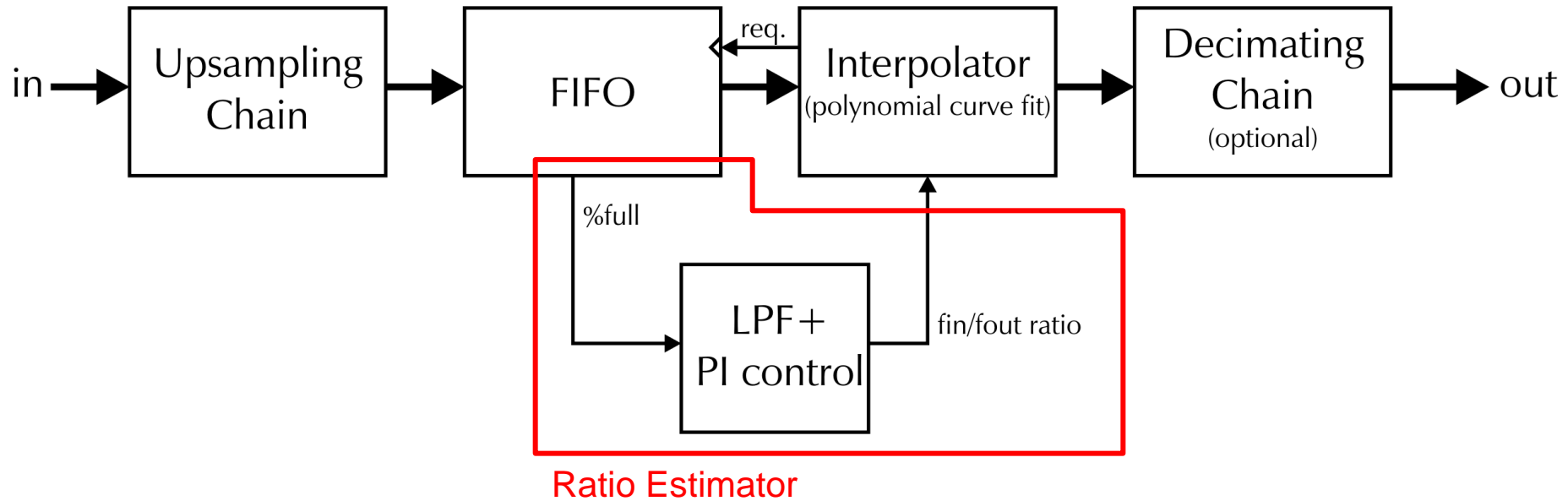
## Basic Concept of Asynchronous Sample Rate Conversion




- When  $f_{\text{sin}}/f_{\text{sout}}$  ratio indication is correct, interpolator will read FIFO exactly as often as it is written.
- $f_{\text{sin}}/f_{\text{sout}}$  ratio is updated to keep FIFO half full.
- Hardware implementations have separate Ratio Estimators
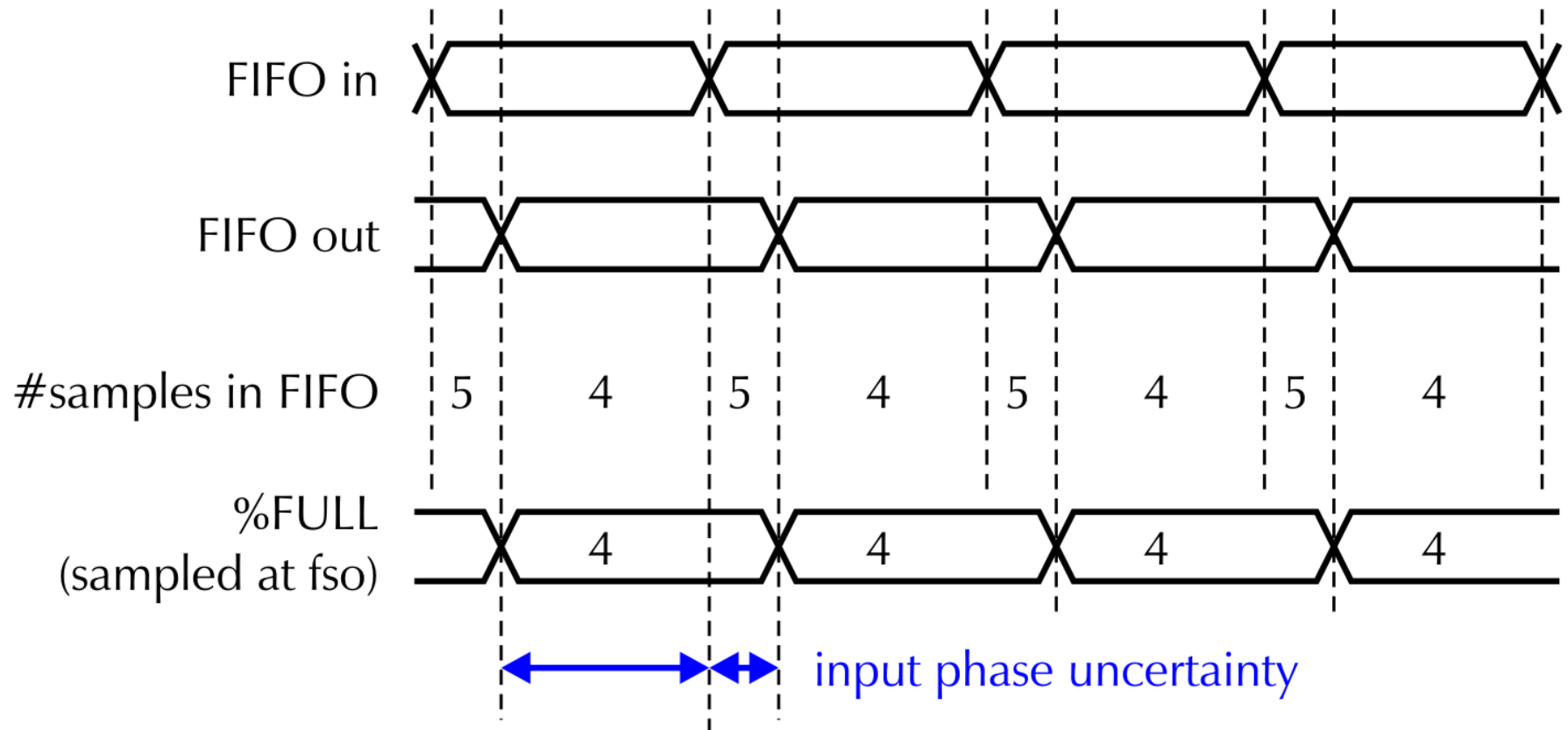
# Asynchronous SRC: The Fine Print

Basic problem of ASRC: measurement accuracy


- Accuracy = sampling rate of Ratio Estimator


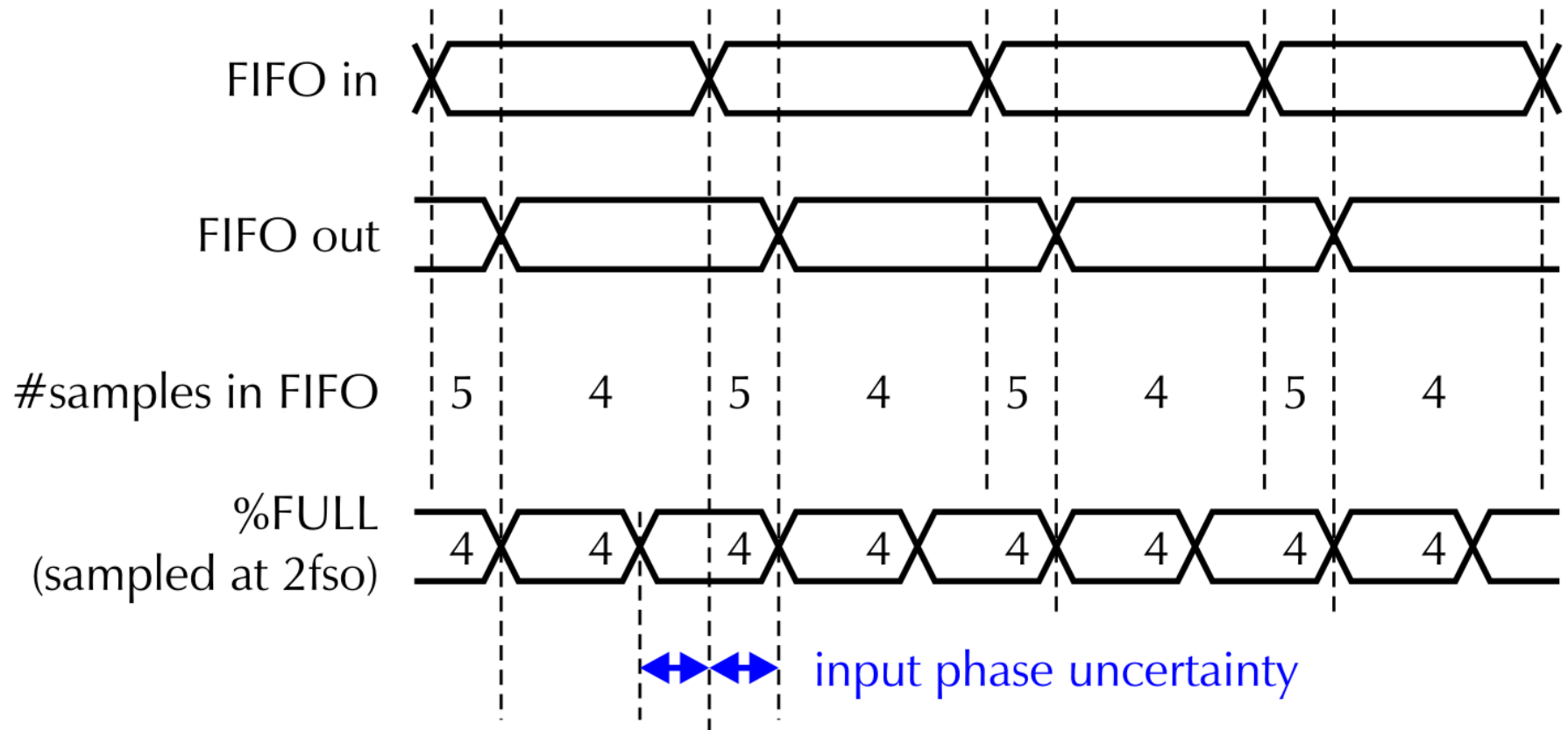
# Asynchronous SRC: The Fine Print


Basic problem of ASRC: measurement accuracy

- Accuracy = sampling rate of Ratio Estimator



# Asynchronous SRC: The Fine Print

Spectral makeup  
of “output jitter”

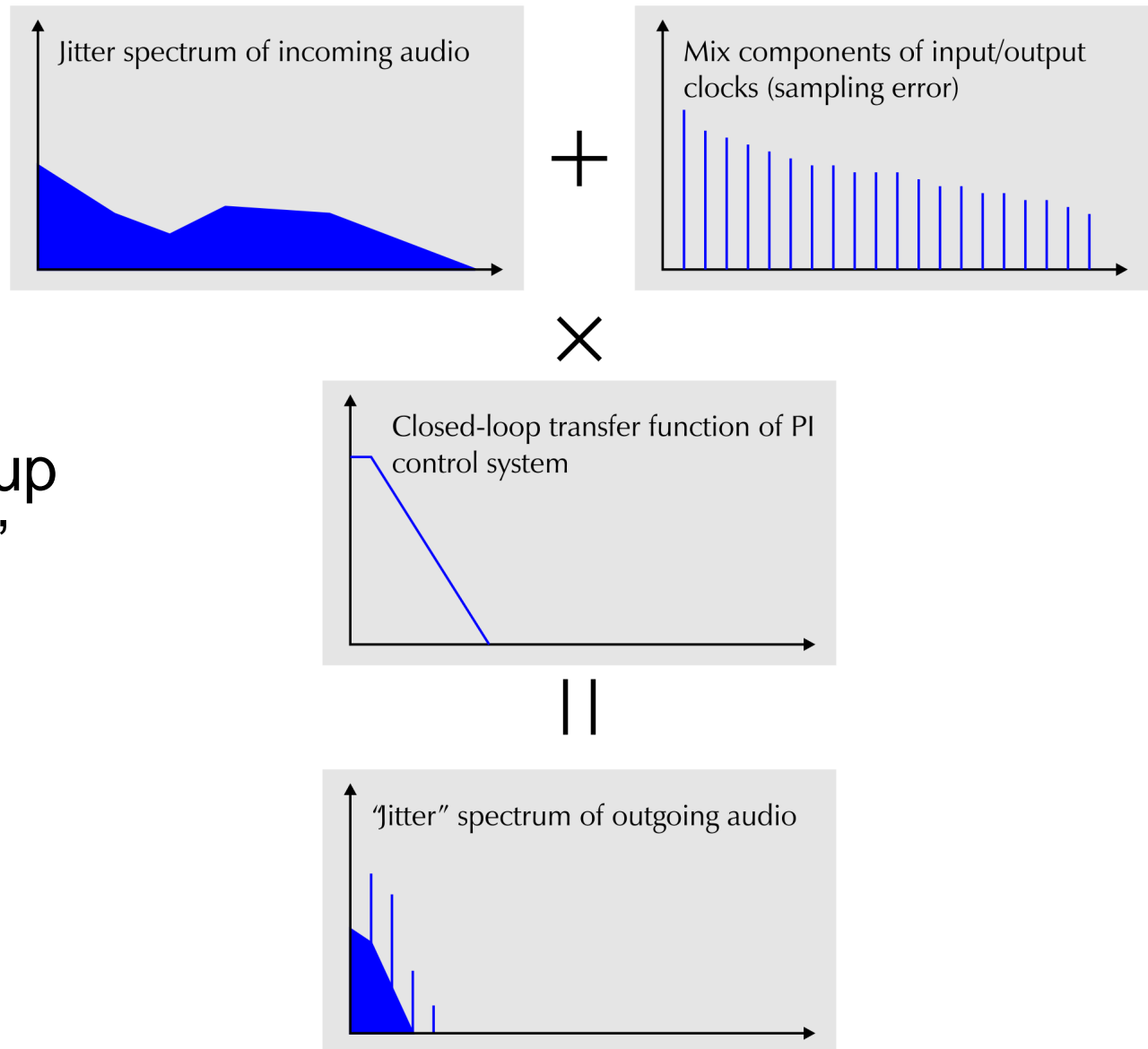




# Asynchronous SRC: The Fine Print
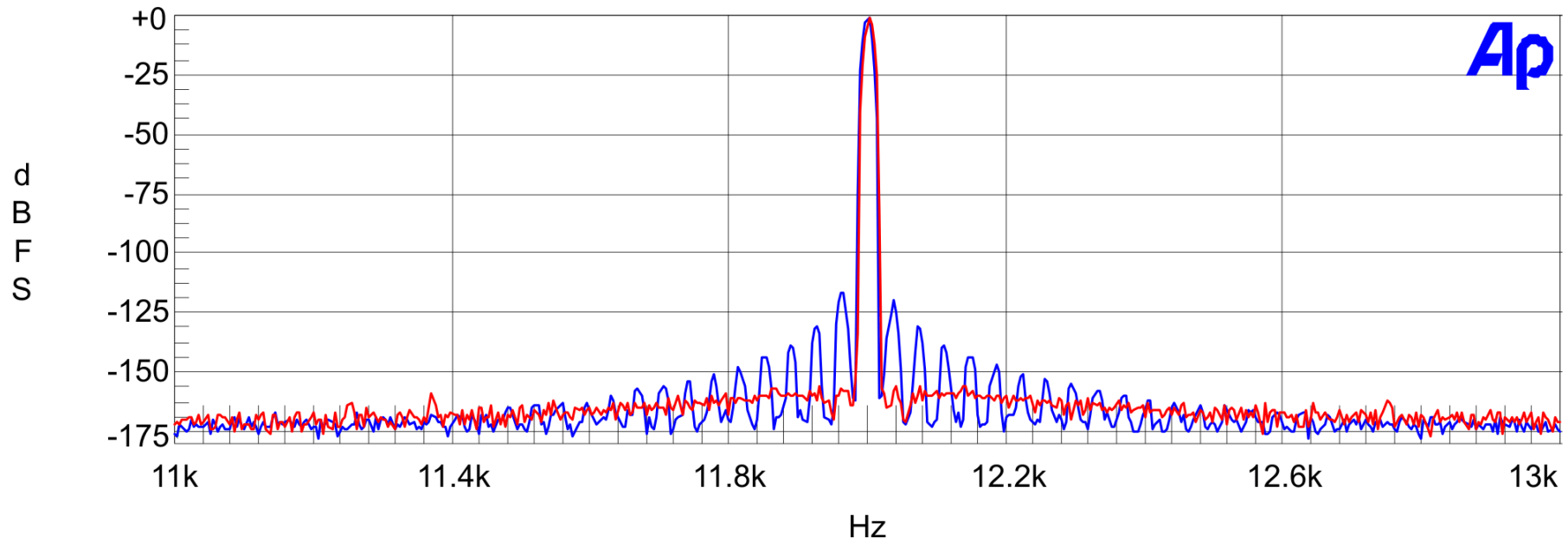
## Example IC ASRC


- Output rate = 47.999kHz
- Input rate = 48kHz (blue), 48.025kHz (red)
- Separate independent clock osc drives SRC process



# Asynchronous SRC: The Fine Print
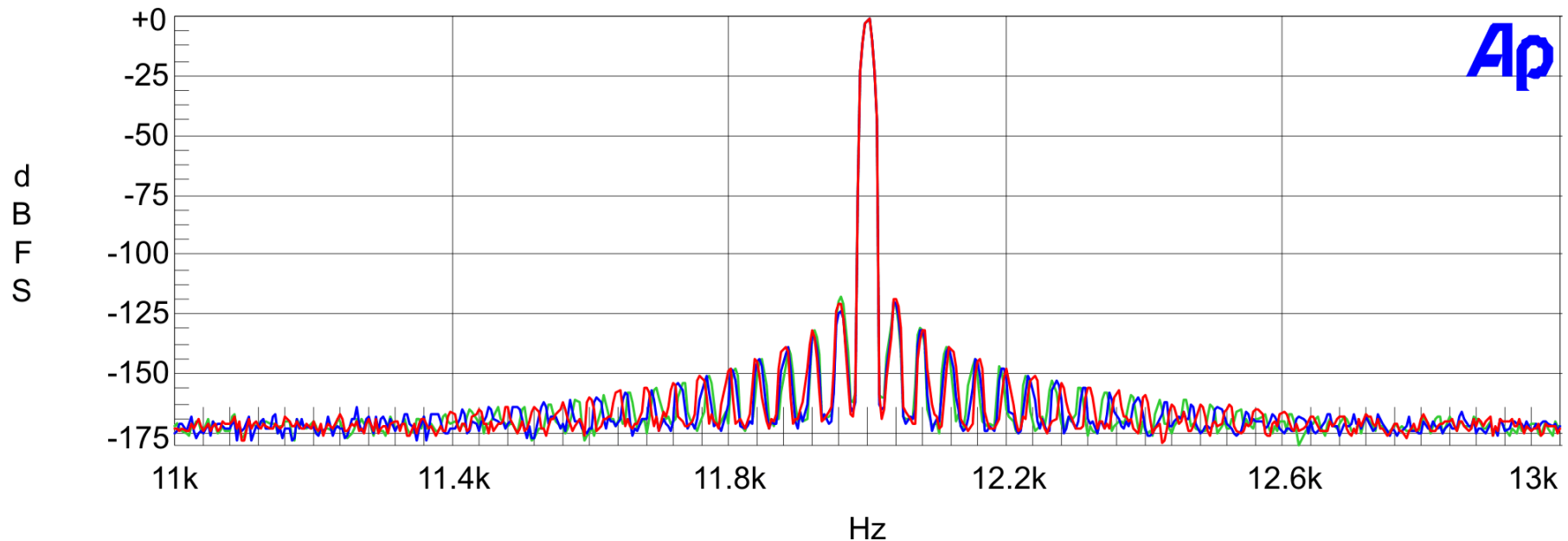
## Example IC ASRC

- Output rate = 47.999kHz. Input rate = 48kHz (blue)
- Separate independent clock osc drives SRC process.  
Oscillator can temperature = 25°C 40°C 55°C



# Asynchronous SRC: The Fine Print

## The Headline

- ASRC's greatly attenuate input jitter...

## The Fine Print

- ...but add a lot of their own before doing so!
- And encode the remainder in the data!
  - Signal degradation is irreversible
- ASRC is not a fully digital process!
  - Frequency is a physical quantity = analogue
  - Ratio between independent oscillators = analogue

# Asynchronous SRC: The Fine Print

## Good Uses for ASRC

- Synchronisation in a mixed-rate environment
- Jitter reduction in DAC. *Run the DAC at an odd rate!*

## Not Good uses for ASRC

- Blanket synchronisation issue solver
- Mastering (use synchronous or software based SRC e.g. Barbabatch)

## Utterly Repugnant uses for ASRC

- Jitter removal device in one-box players
- “Upsampler” in consumer devices

# DSP Filters For Loudspeakers

## The Siren Song

- Perfect amplitude/phase/impulse response
- From any speaker
  - Measure speaker response, invert, apply FIR, presto!
- Ultra-steep, linear-phase cross-over

## The standard approach

- Impulse inversion method.
- Corrects all linear distortions, including echo's.

# DSP Filters For Loudspeakers


OK, let's try this!

- Test Mule:
  - 2x5" woofer (Vifa OEM)
  - 1" tweeter (Morel)
  - Classic MTM arrangement




# DSP Filters For Loudspeakers

## On-Axis Response

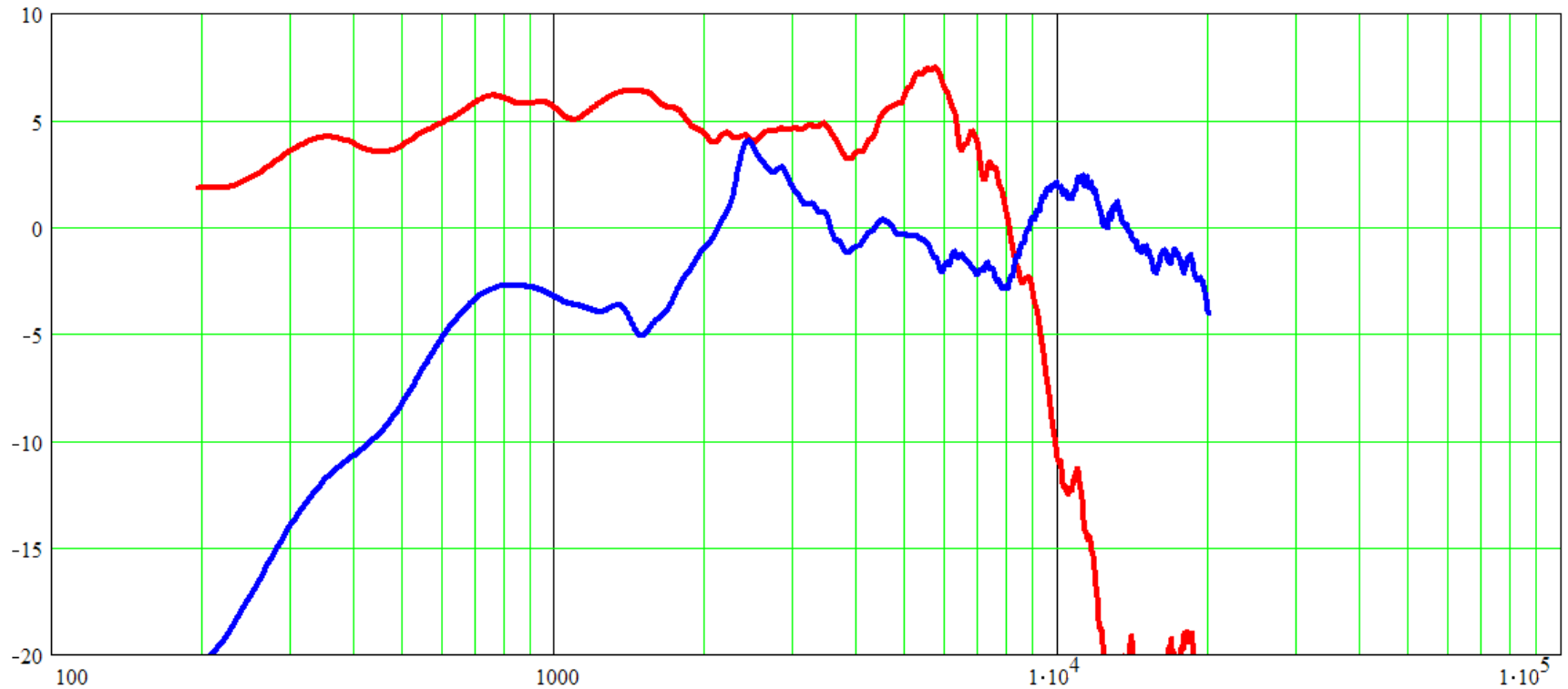

# DSP Filters For Loudspeakers

## 30° Horizontal Off-Axis Response

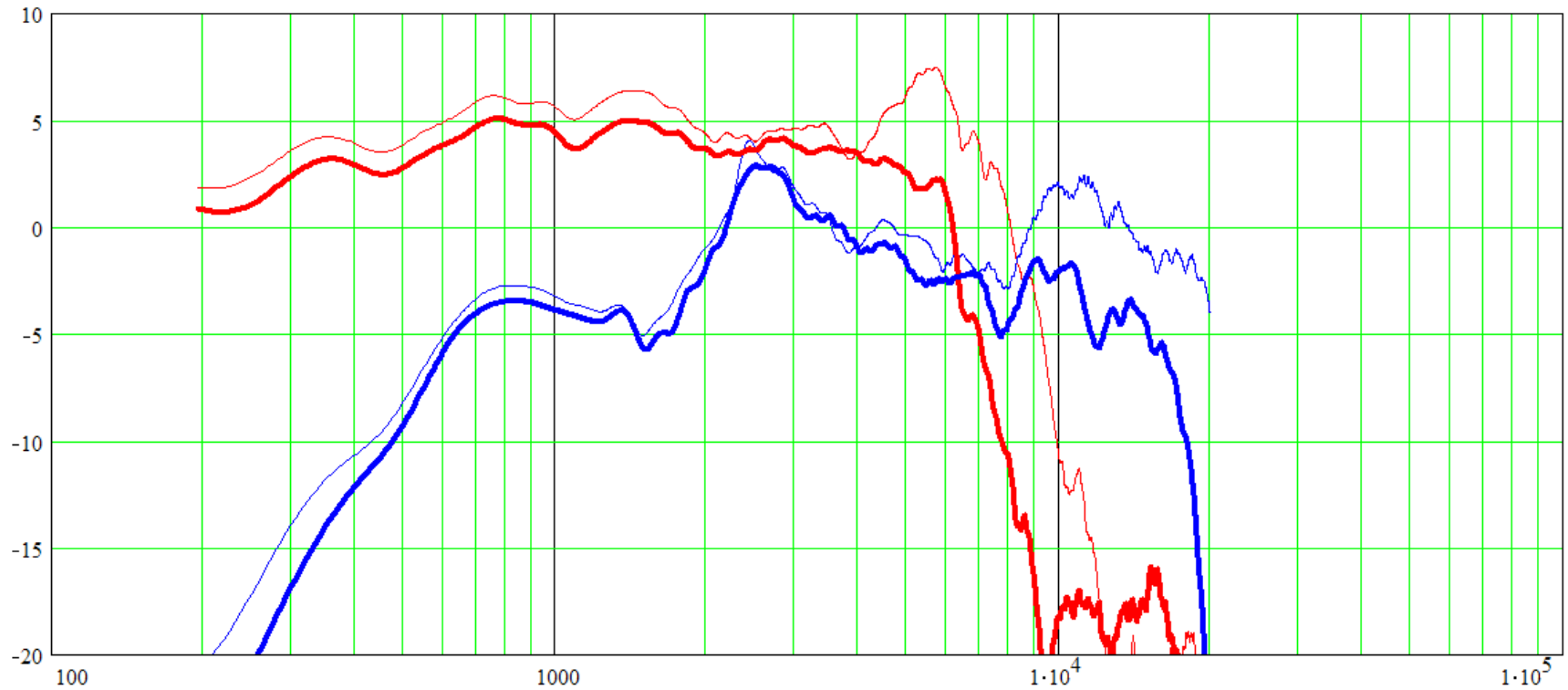


Note: some peaks/dips shift frequency!



# DSP Filters For Loudspeakers

## 30° Vertical Off-Axis Response

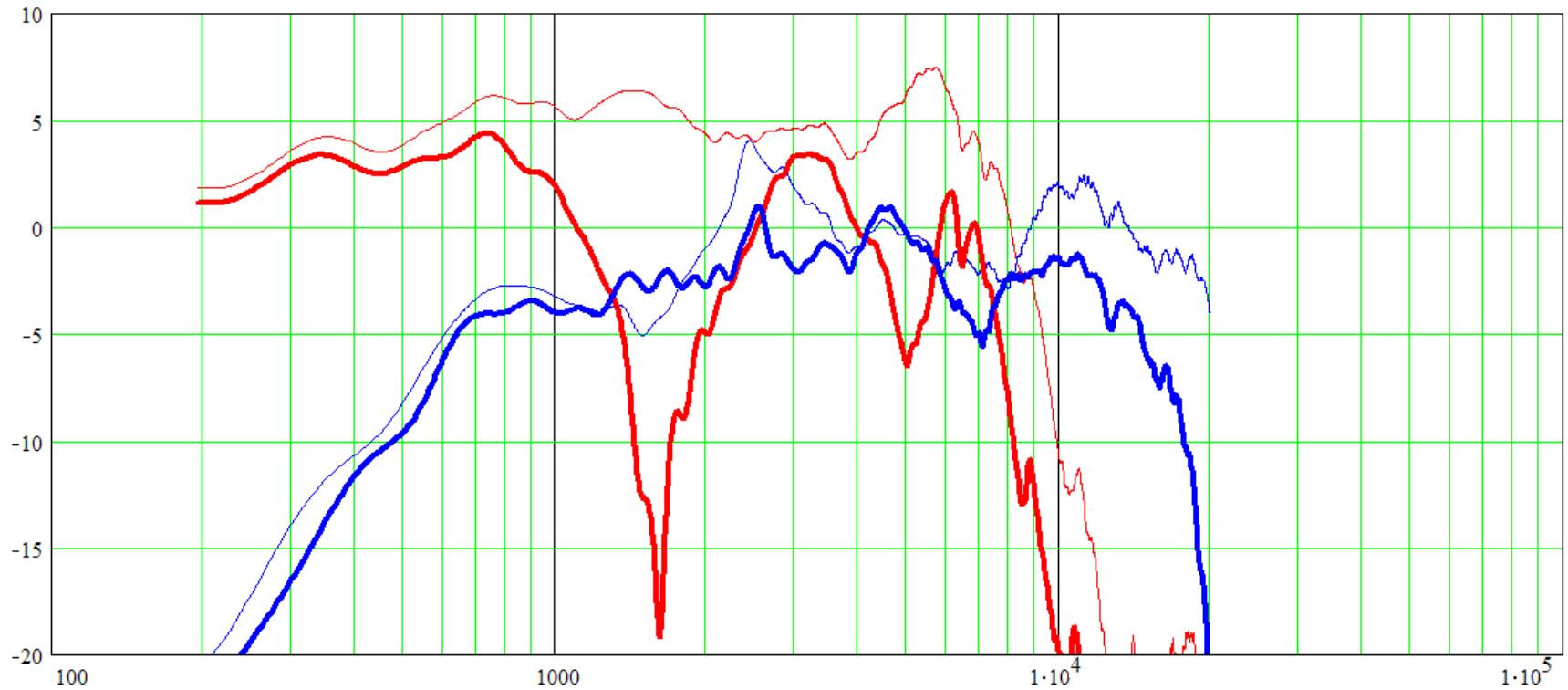

- Tremendous comb filter in LF response
- Other peaks/dips shift frequency!



# DSP Filters For Loudspeakers

Before we've even started...

- Worst irregularities are diffractions
  - Cabinet edges and woofer cones
- Virtual sources are far from drivers
  - Reflections change with listening position
  - Subverts response correction off axis


# DSP Filters For Loudspeakers
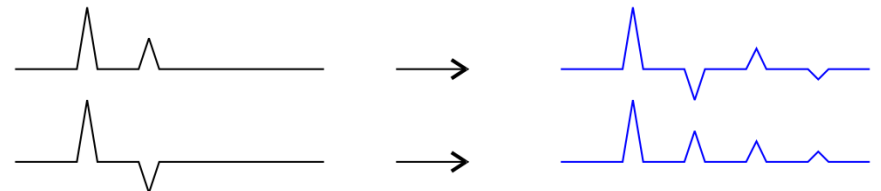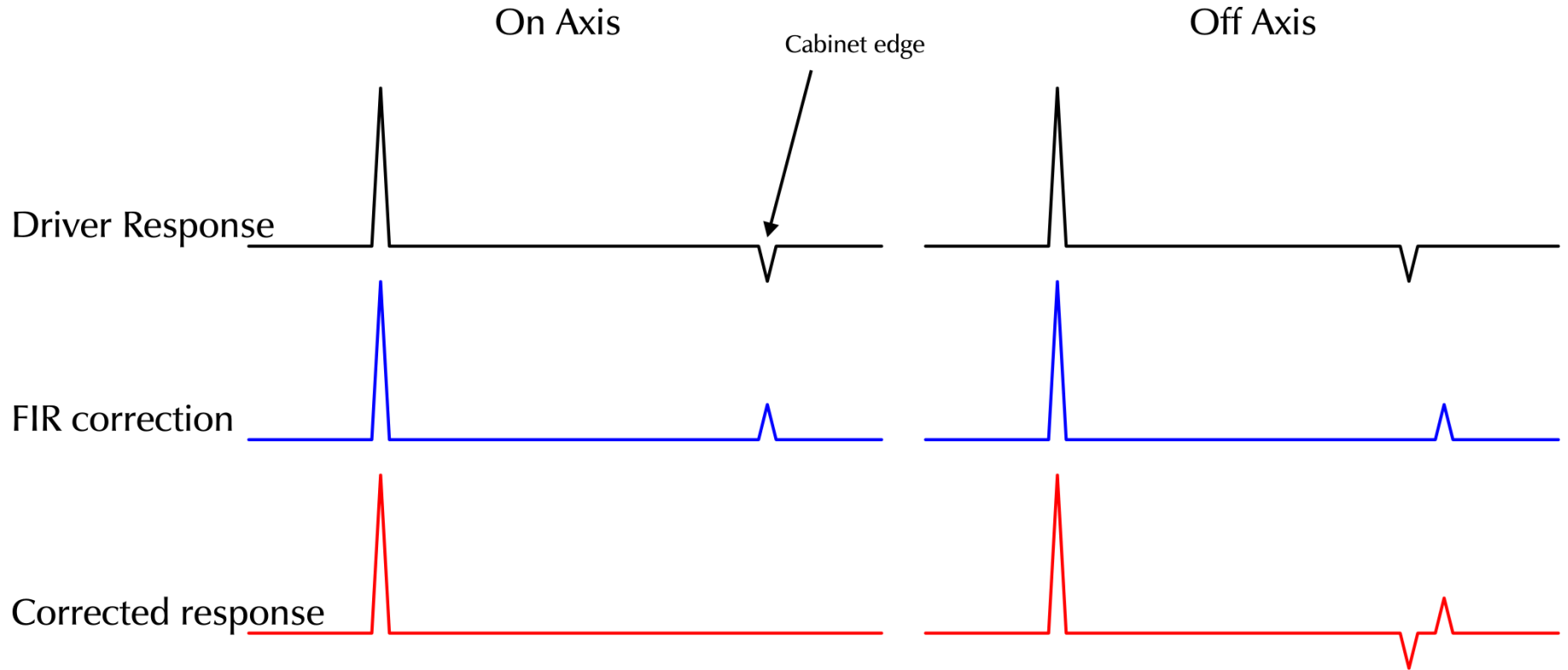
## Mis-correction of reflections and diffractions




# DSP Filters For Loudspeakers
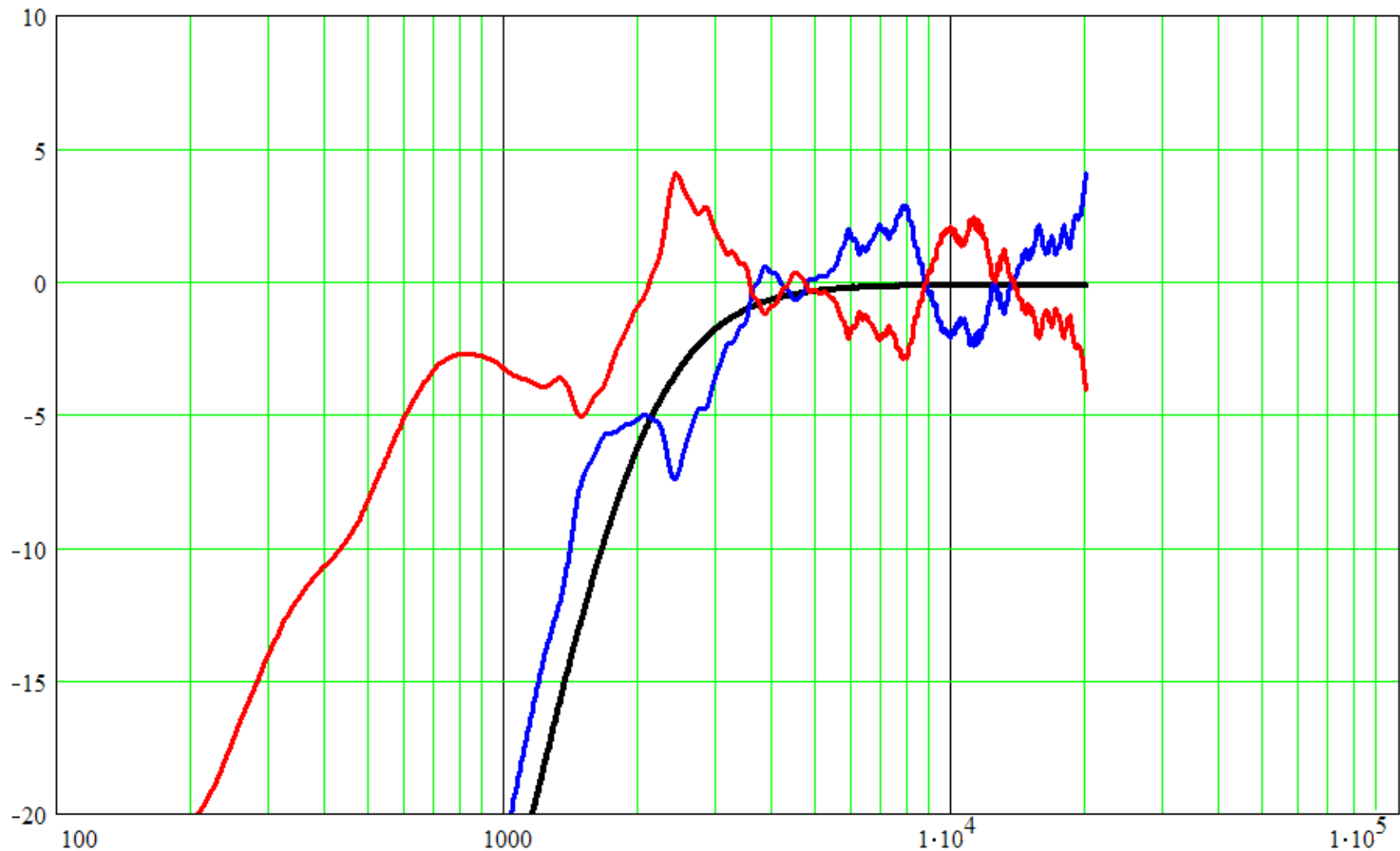
## Corrected and Filtered HF response (on axis)



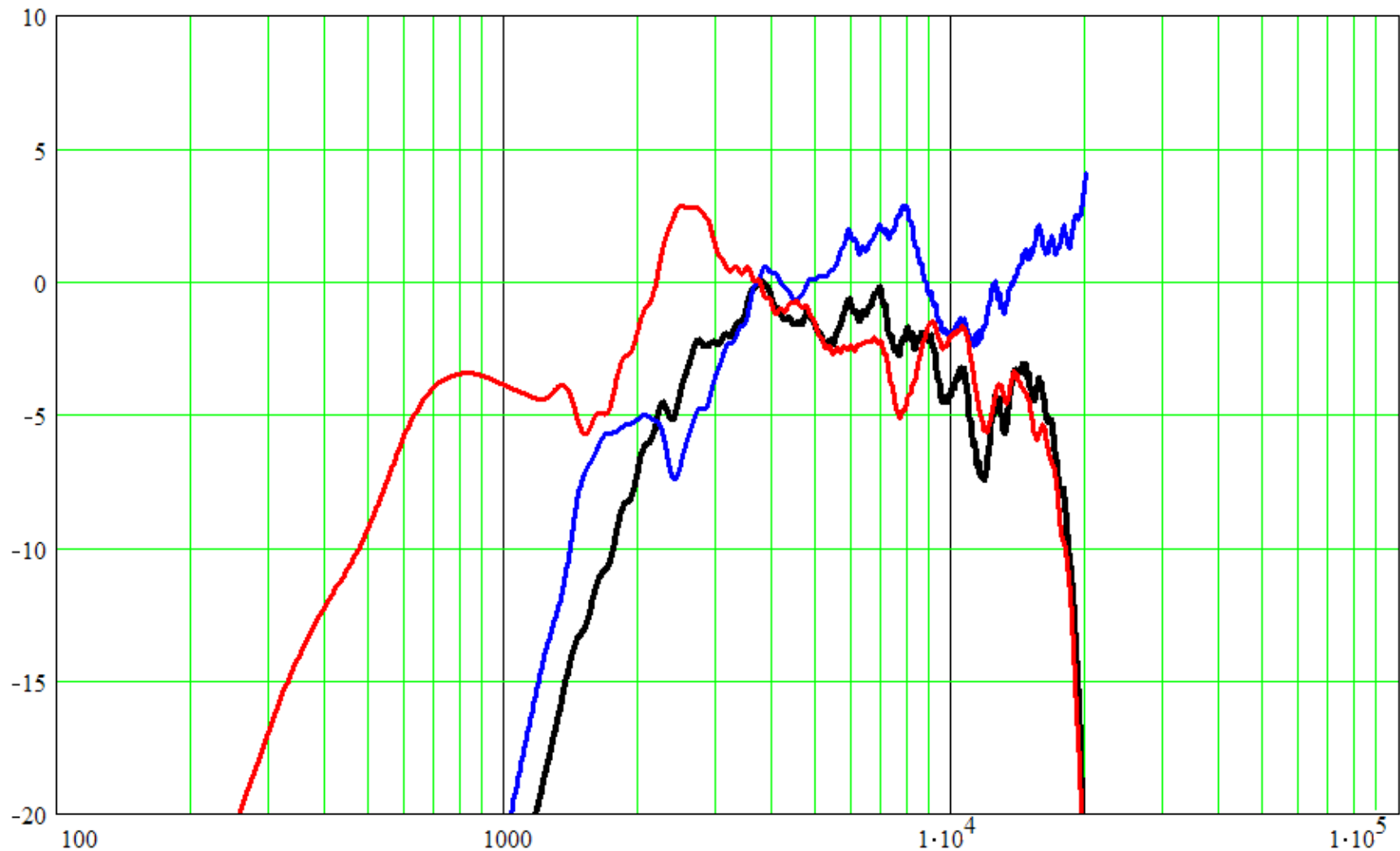
# DSP Filters For Loudspeakers

“Corrected” and Filtered HF response (30°H off axis)



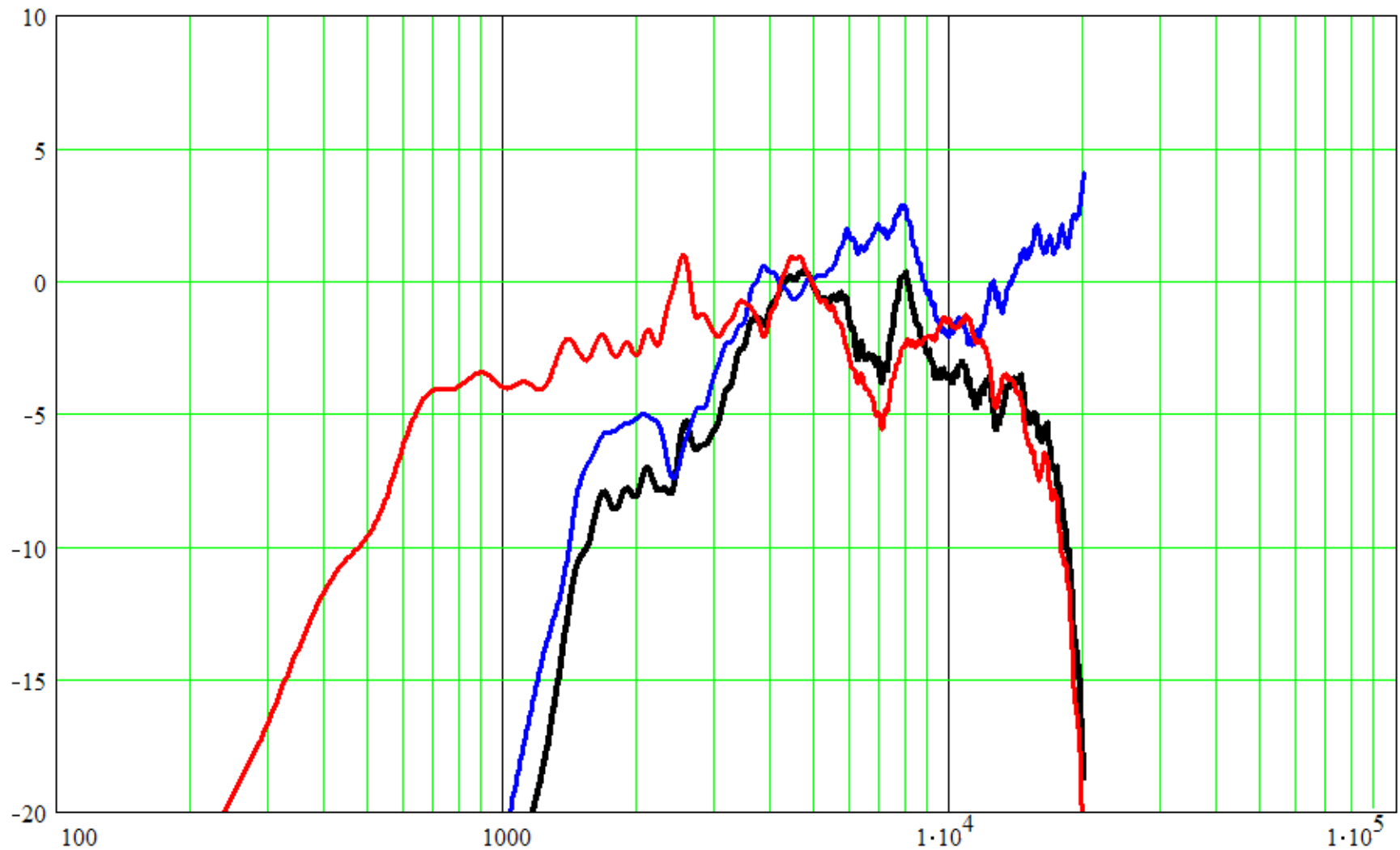
# DSP Filters For Loudspeakers

“Corrected” and Filtered HF response (30°V off axis)




# DSP Filters For Loudspeakers

## Sum Response (on axis)

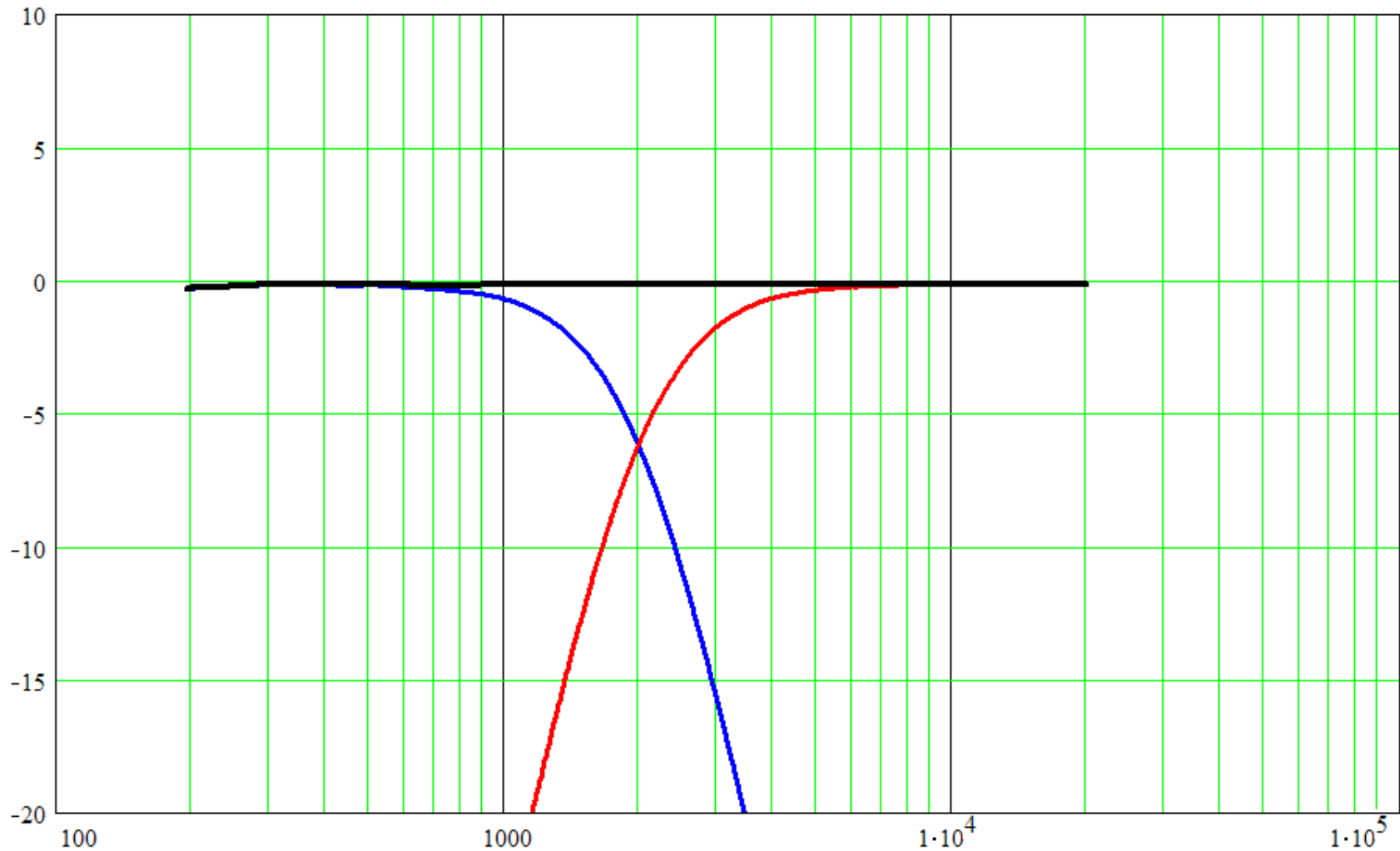

# DSP Filters For Loudspeakers


## Sum Response (30°H off axis)

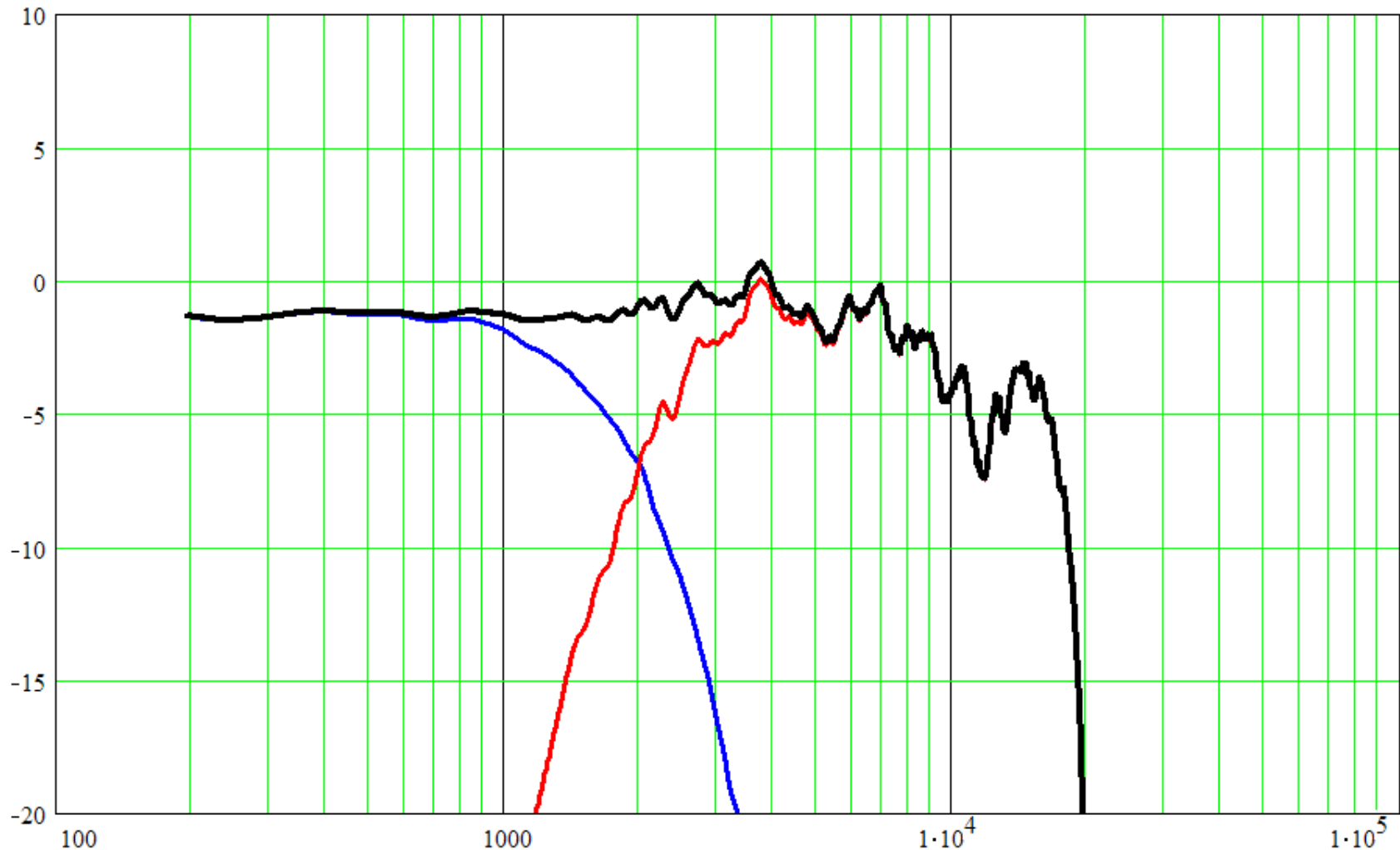




# DSP Filters For Loudspeakers

## Sum Response (30°V off axis)

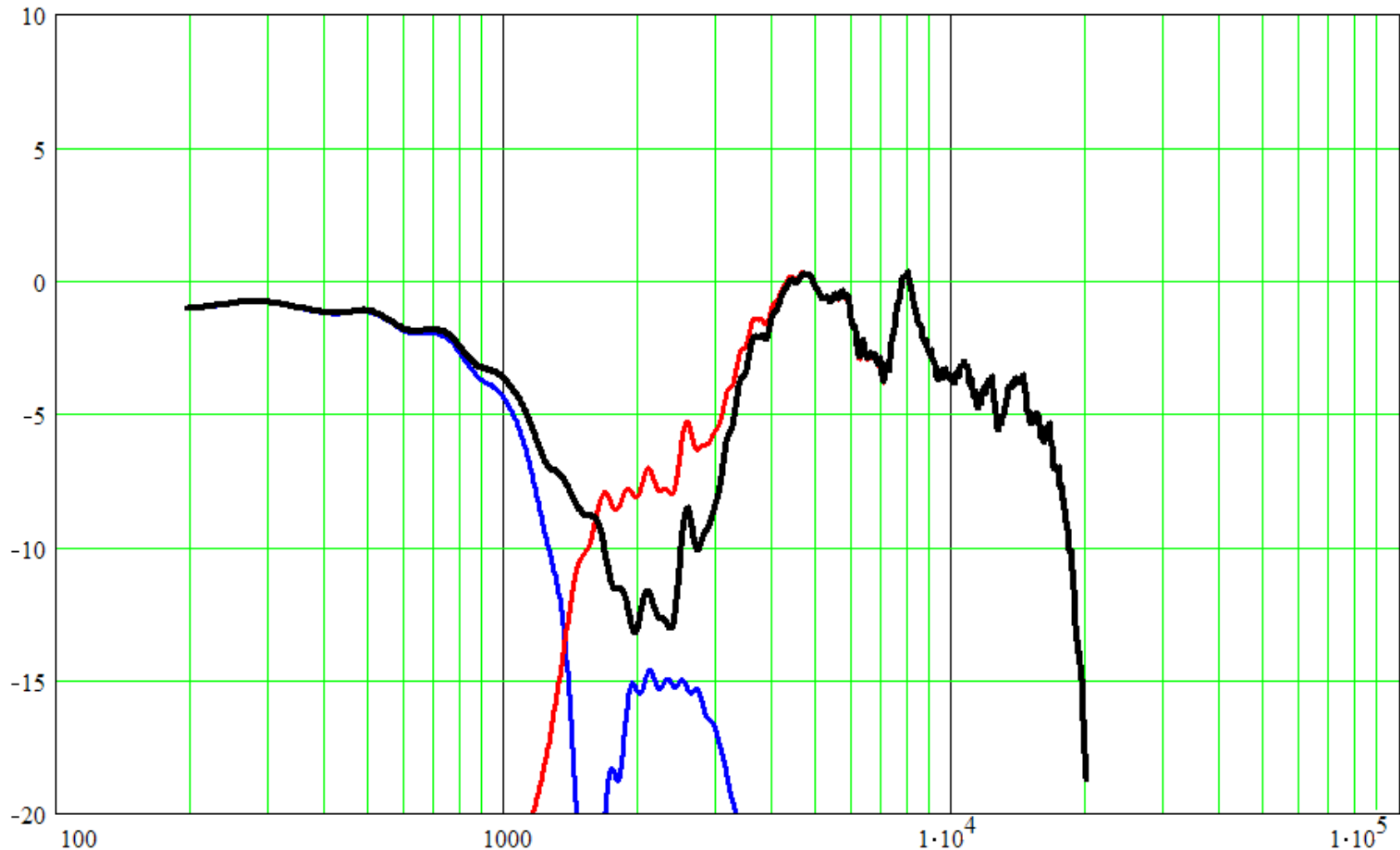


# DSP Filters For Loudspeakers

Impulse Response (on axis)

 


# DSP Filters For Loudspeakers

Impulse Response (30°H off axis)

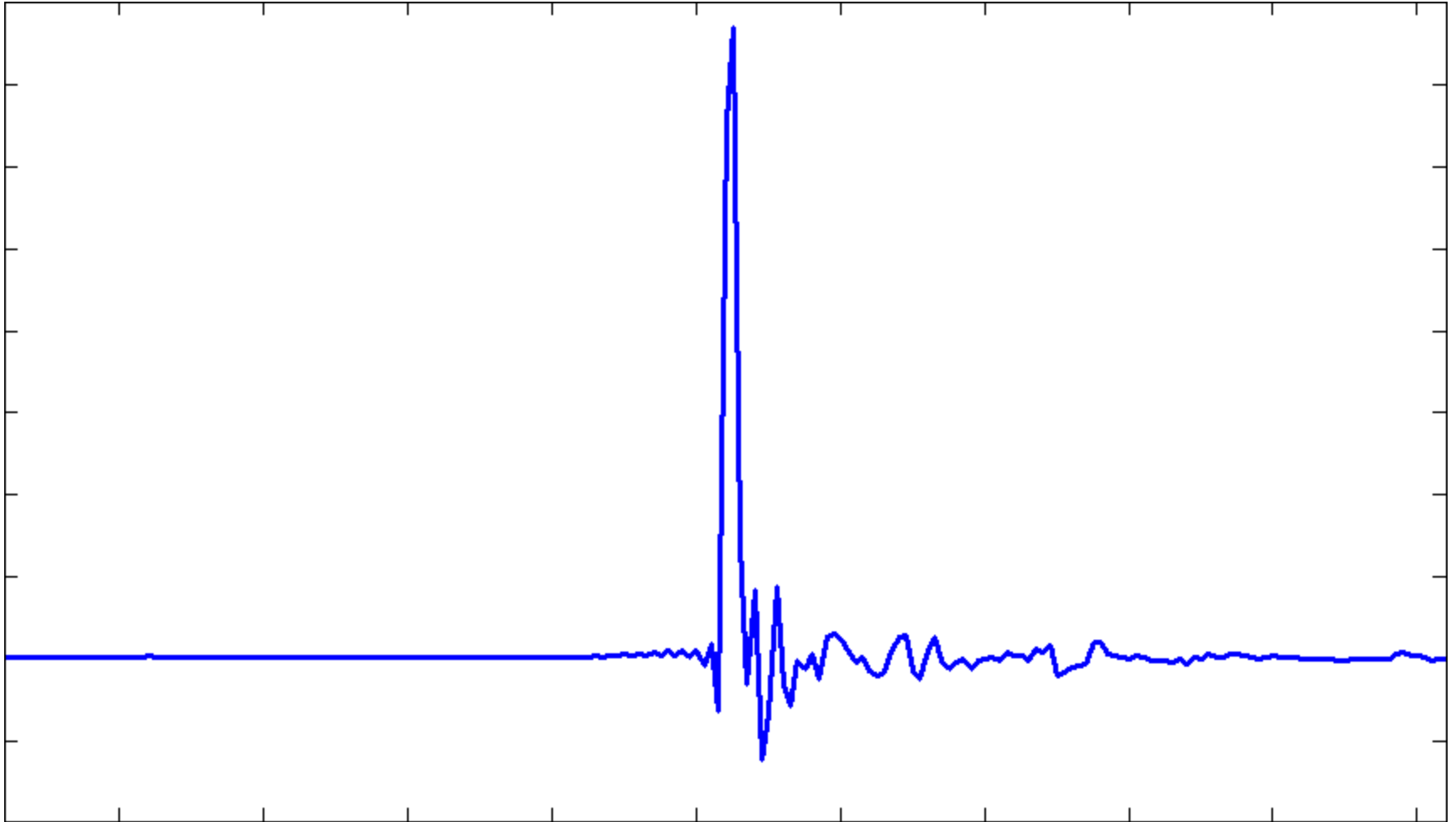


# DSP Filters For Loudspeakers

Impulse Response (30°H off axis, Y zoom)

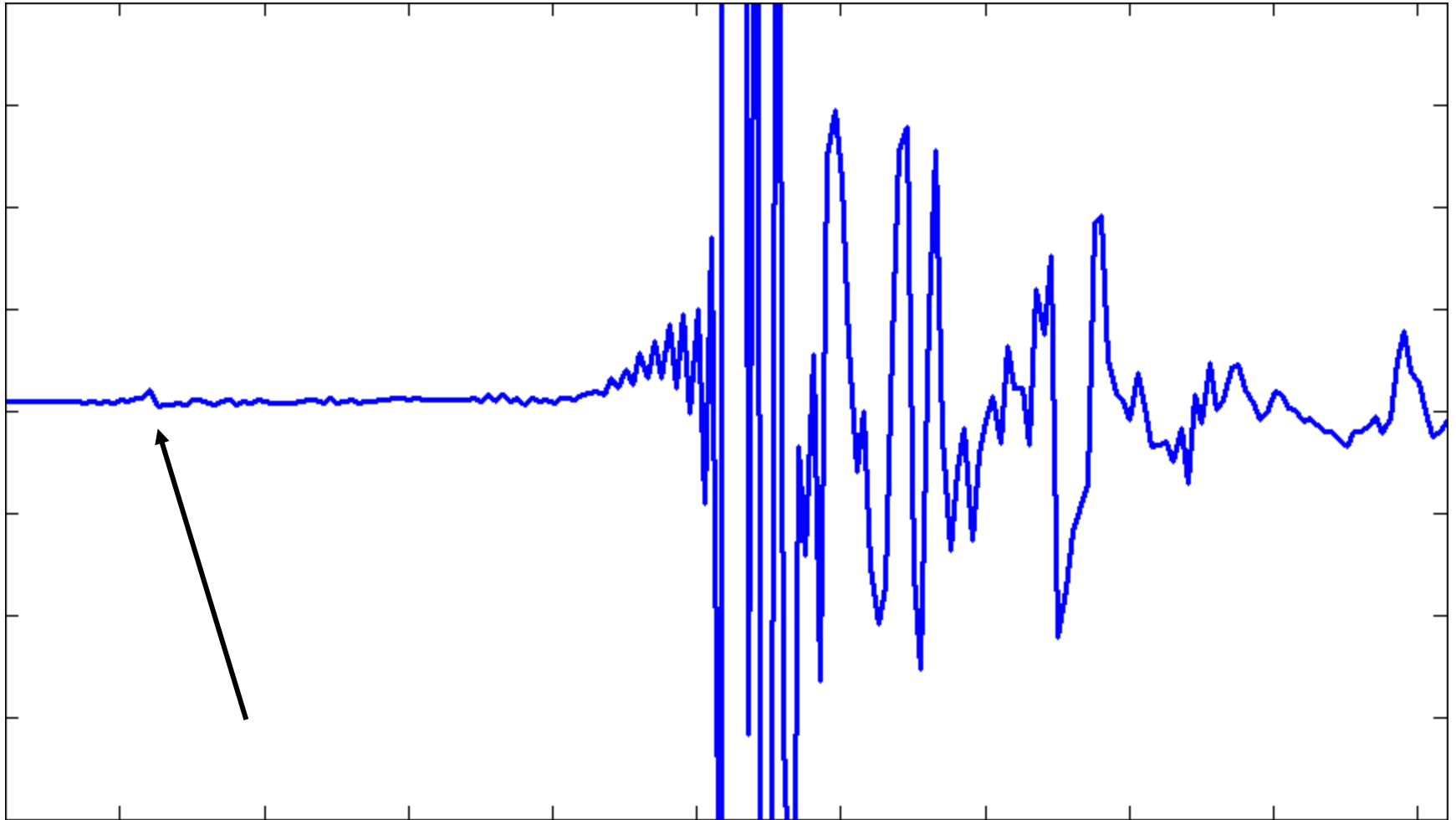


# DSP Filters For Loudspeakers

Impulse Response (30°V off axis)

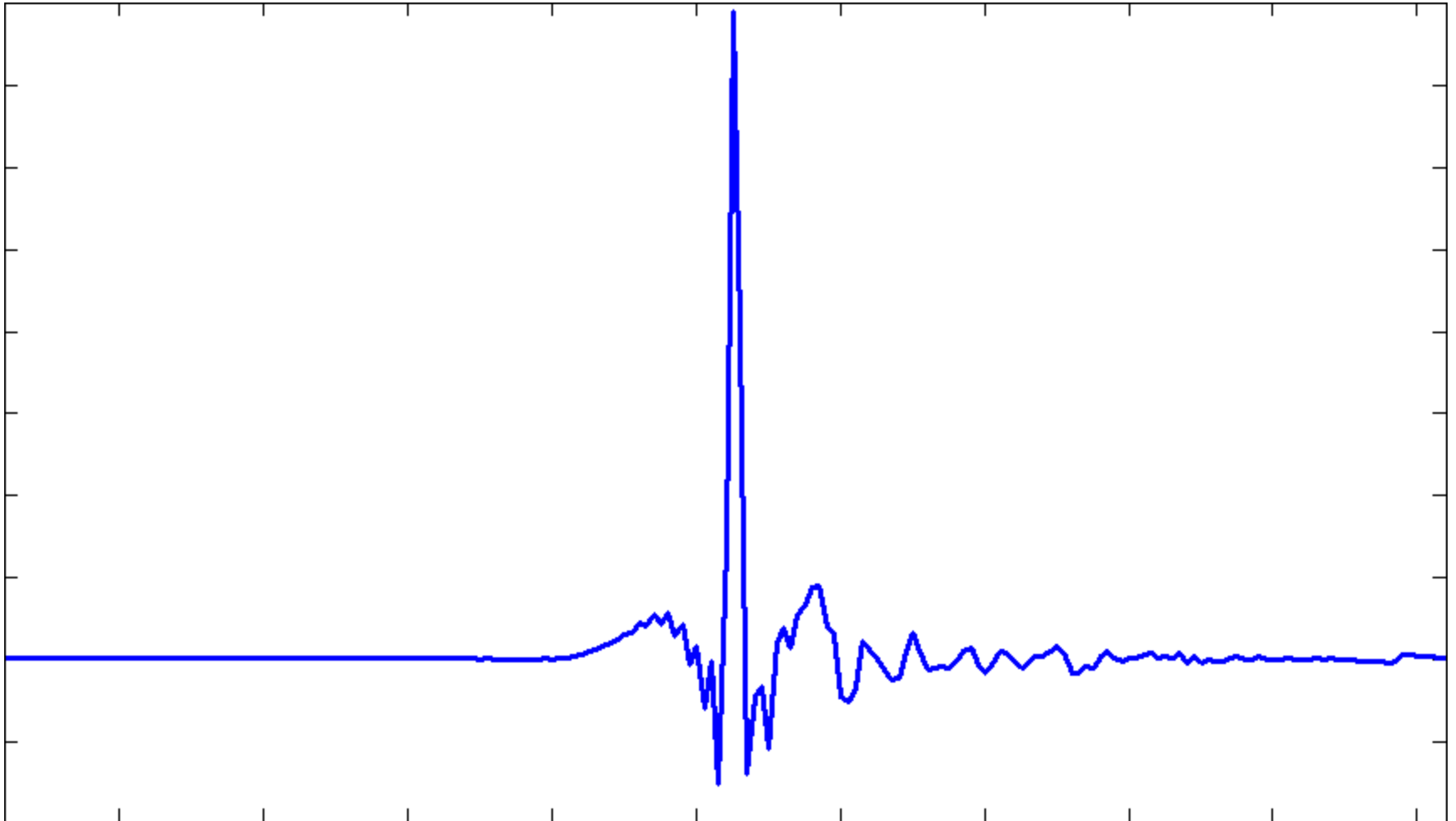
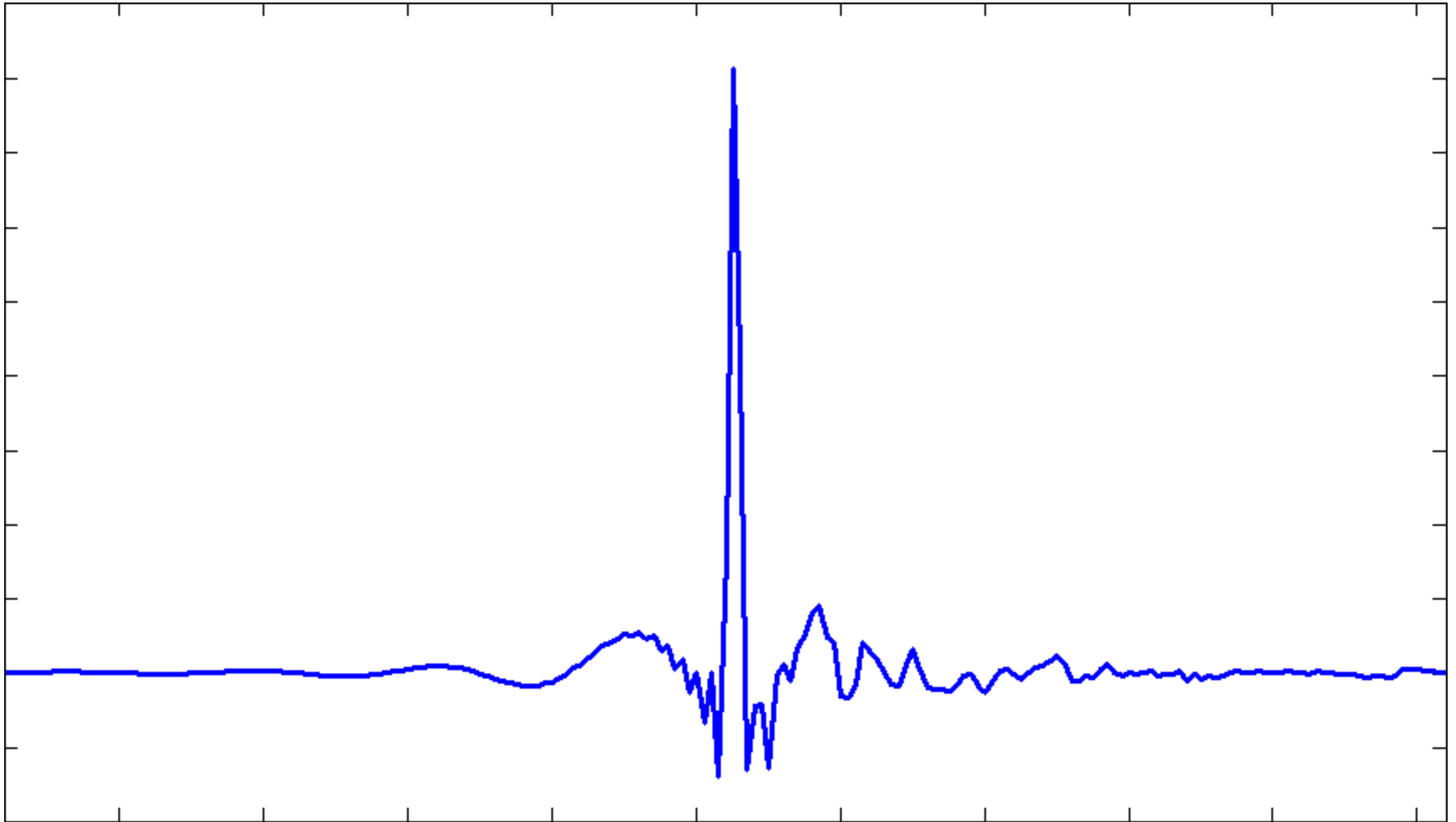
# DSP Filters For Loudspeakers

Impulse Response (30°V off axis, ultra-steep filter)



# DSP Filters For Loudspeakers

## Observations

- Heavy correction exacerbates acoustic problems
  - Steep, linear-phase filtering causes pre-ringing in off-axis response
  - Linear-phase target response invites pre-echos
- ⇒ Brute-force correction produces ugly, smeared sound

# DSP Filters For Loudspeakers

Sensible approach to correction:

- Don't Shave Off The Hair. It'll Grow Back.
  - Limit scope of correction to a few periods
- ⇒ *The subtler the correction, the wider the listening angle in which it still makes some sense.*



# DSP Filters For Loudspeakers

Even better approach to correction: manually!

- Forget FIR
- Of each bump and trough, find cause
  - If the driver is the source: correct ruthlessly
  - If the source is elsewhere: EQ gently
- Know your acoustics...

# DSP Filters For Loudspeakers

## Cross-over Filtering

- Use shallow slopes
- Target minimum phase sum
  - We really don't want linear phase HPF!
  - We only care about the sum, not the individual drivers.
- (...)

# DSP Filters For Loudspeakers



## Conclusion

- DSP does not exonerate you from doing your acoustical homework
  - You might even need to work harder
  - Some acoustic concepts really are “broken”
- Automated design procedure = pipe dream
- Impulse inversion method is naïve
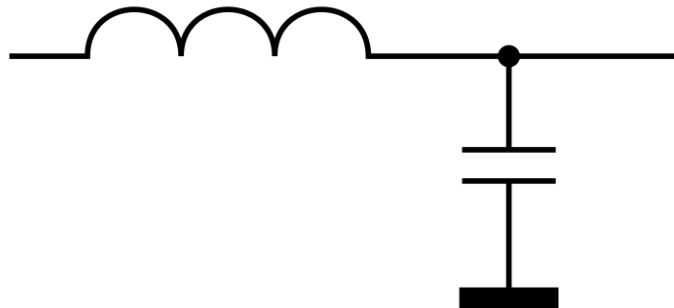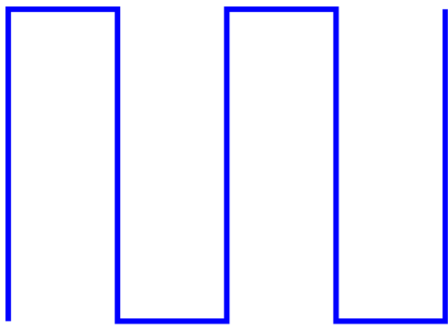
# Class D and EMI

Low-frequency EMI: Carrier and low harmonics.


- Close match with theory.
- Ripple cancelling possible.
- Not an EMI issue except for long cables
- Not a tweeter issue (come off it!)



# Class D and EMI
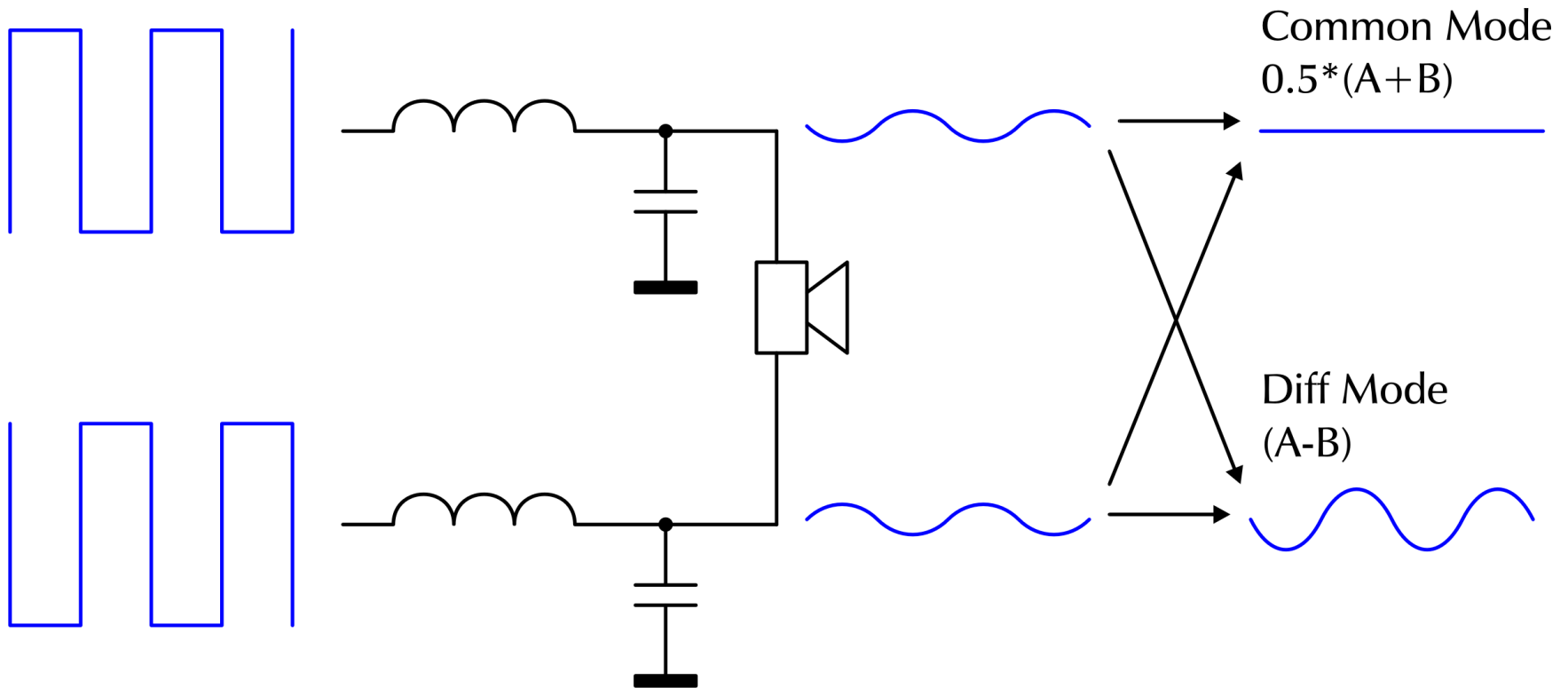
## Common and Differential Mode in H-Bridge Class D

- “Class AD”. Carriers and modulation are out of phase




Note: Common-mode is what radiates off cables.
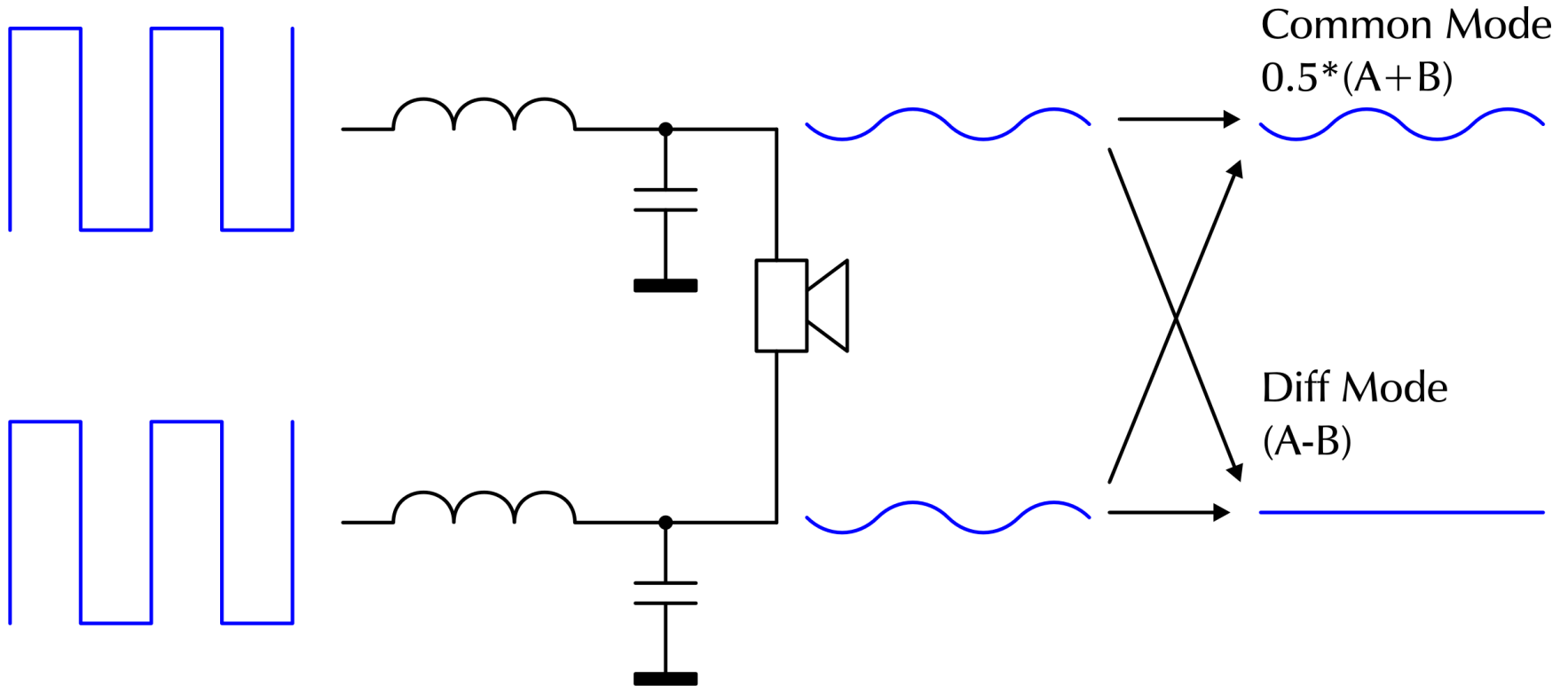
# Class D and EMI

“Class BD”.

- Carriers are in phase. Modulation is out of phase.



HF across load is reduced but CM increases.

# Class D and EMI


## Half bridge vs Full Bridge, Class AD vs BD

- Half-bridge
  - Can't cancel either CM or DM
  - Common-mode is half of differential mode
- AD
  - Common-mode voltage theoretically 0
  - Differential mode same as half bridge
- BD
  - Differential mode cancels at low modulation...  
...but that was not really a problem anyway.
  - Common-mode voltage same as half bridge

# Class D and EMI
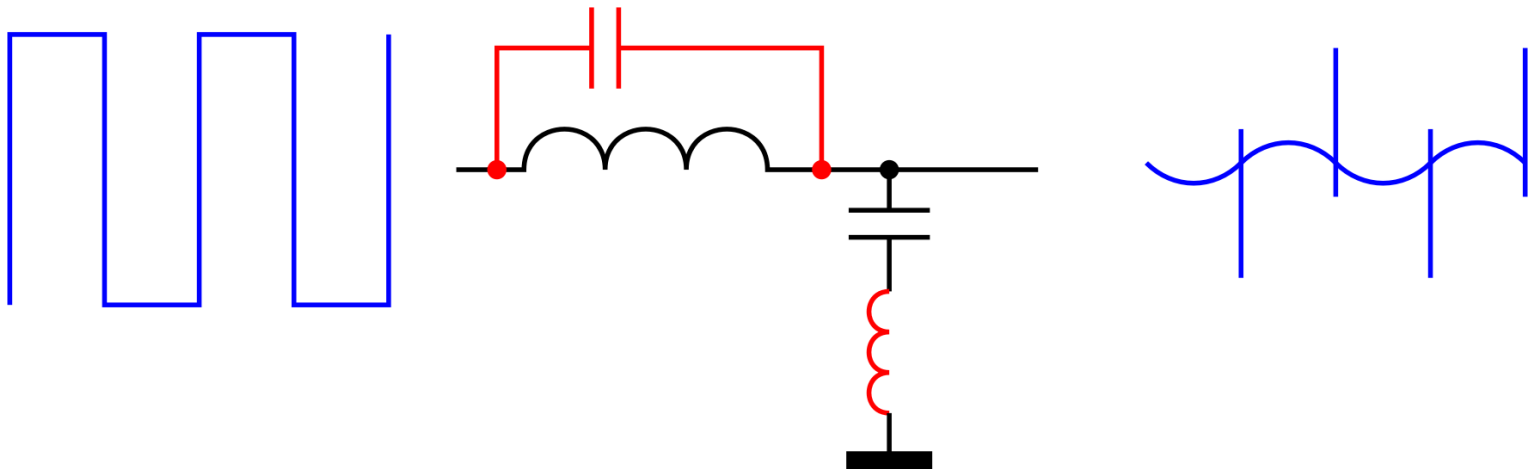
## High-Frequency EMI: Leaking switching transients

- Theoretical modeling is useless.
  - Capacitors become inductive
  - Inductors become capacitive
  - PCB becomes jumble of L's and C's.
- No tricks. Only good hardware design helps.
- Direct EMI problem under all circumstances.





# Class D and EMI

## Sensitive item 1: The capacitor.

- Myth of the “Low Inductance Capacitor”.  
(An Audiophile Favourite)
  - All modern film caps have sprayed end contacts.
  - Inductance is determined by geometry only (mostly size).



Bad.




Good.

Period.

# Class D and EMI

## Sensitive item 2: The inductor.

- Stray fields out of toroids

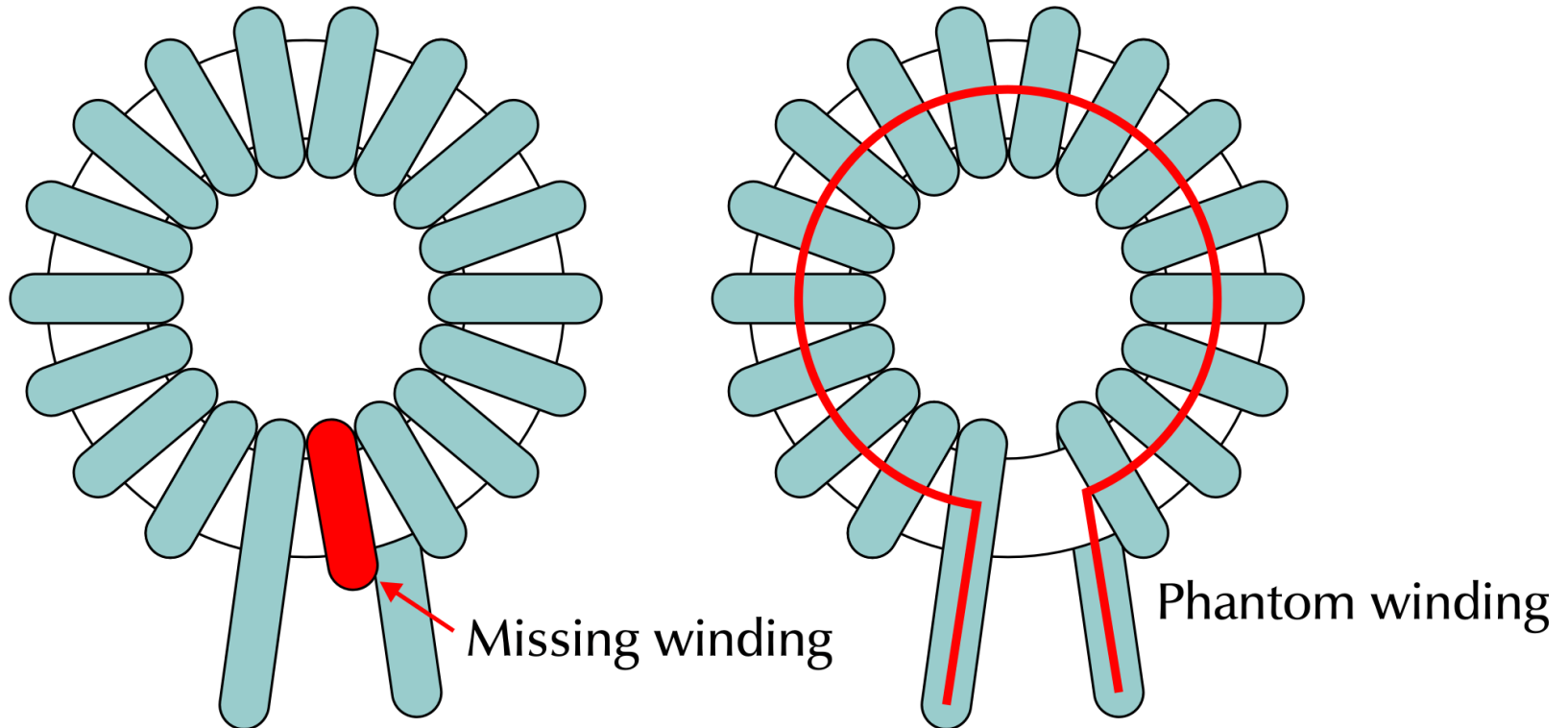


- Upright mounted toroids are worst.

# Class D and EMI
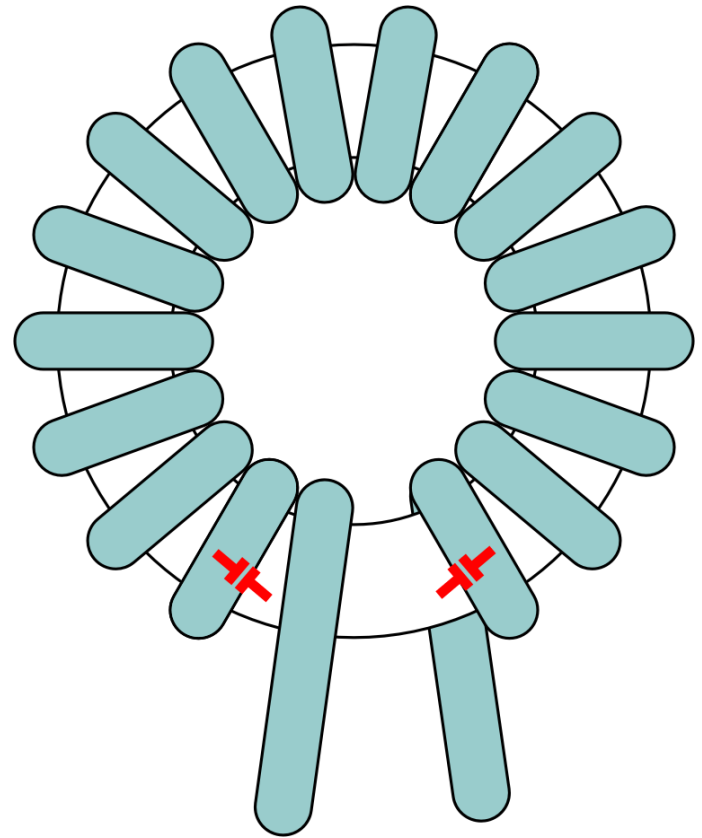
## Sensitive item 2: The inductor.


- Beware of indirect Capacitive Coupling through Core
  - Tight windings are better magnetically but worse electrostatically.
  - No external electrostatic shield: Capacitive coupling to chassis etc. can get significant.
- Toroids are not always optimal



# Class D and EMI
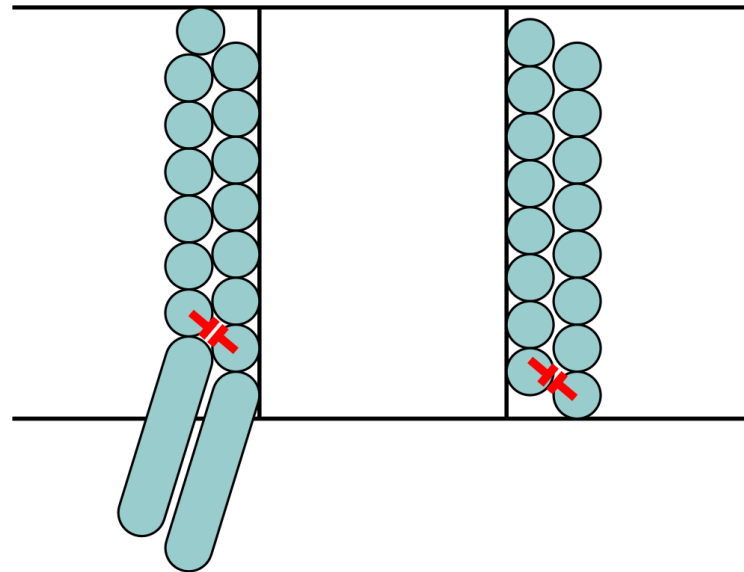
## Sensitive item 2: The inductor.

- Ferrite inductors: avoid direct capacitive coupling between windings




- “Hot” end sees “Cold” end
- 2 layers is worst case situation
- 1 layer is best

# Class D and EMI
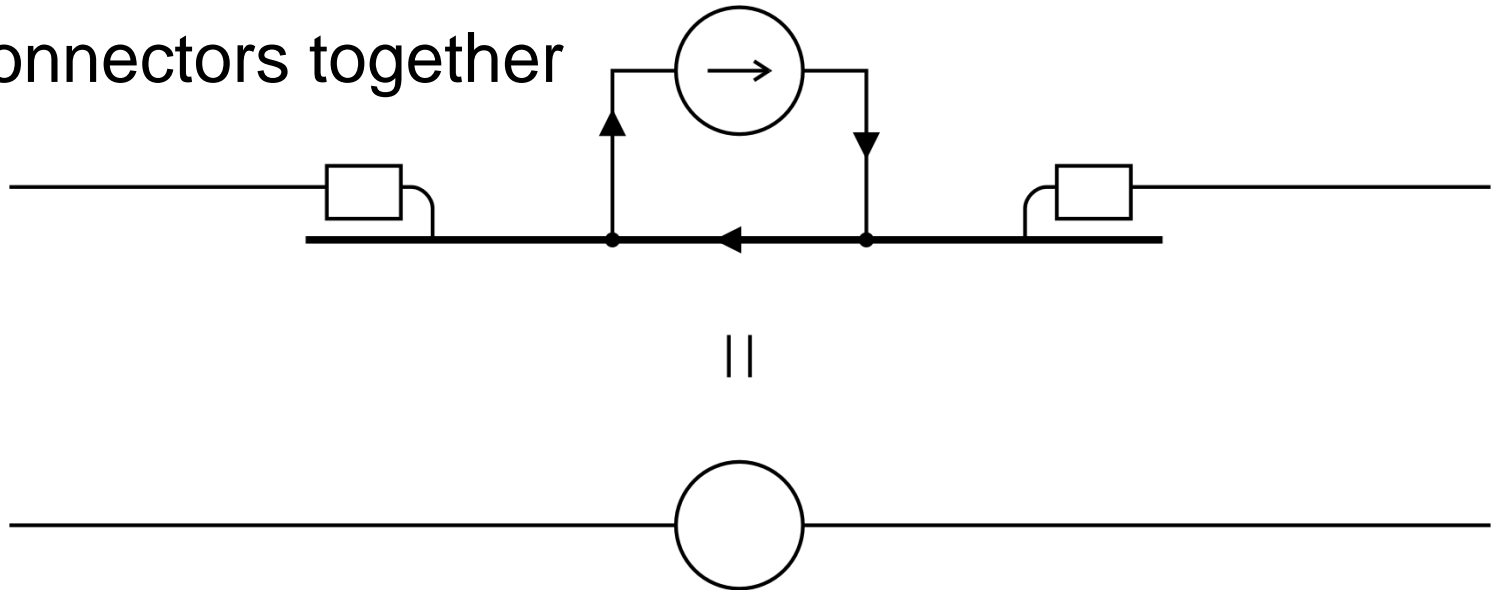
## Sensitive item 3: The PCB layout.

- Contiguous ground plane
- Keep connectors together



- Avoid capacitive coupling to external parts
- Minimize loop area (≠short traces)


# Class D and EMI

## Checking for EMI without Spectrum Analyser

- Just probe around the external connections with a scope!!!
- If you see rubbish, there is rubbish
- The higher the frequency, the more you should worry

# Class D and EMI


Example: Amplifier A, rated 160W

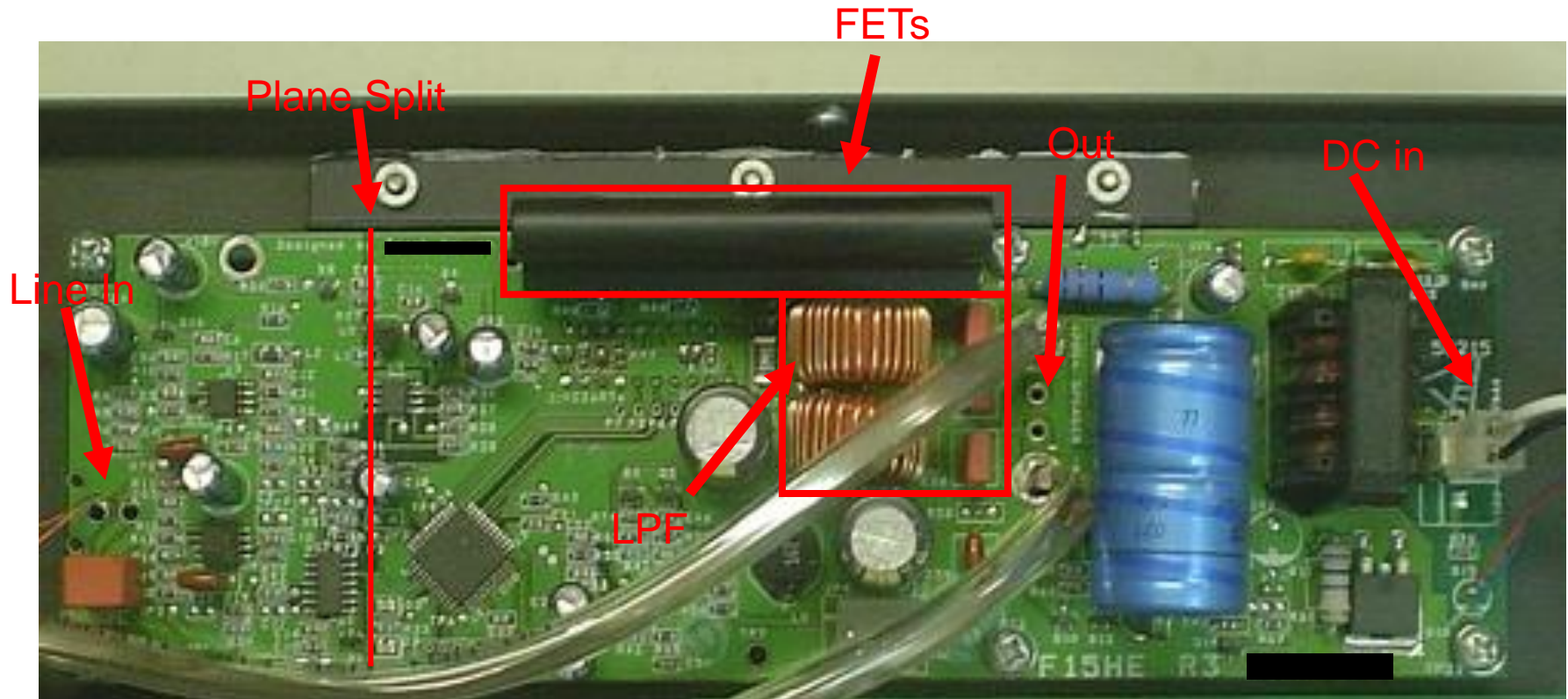

# Class D and EMI

Amplifier A, one output line

- 1V/div. Probe clip at RCA ground.

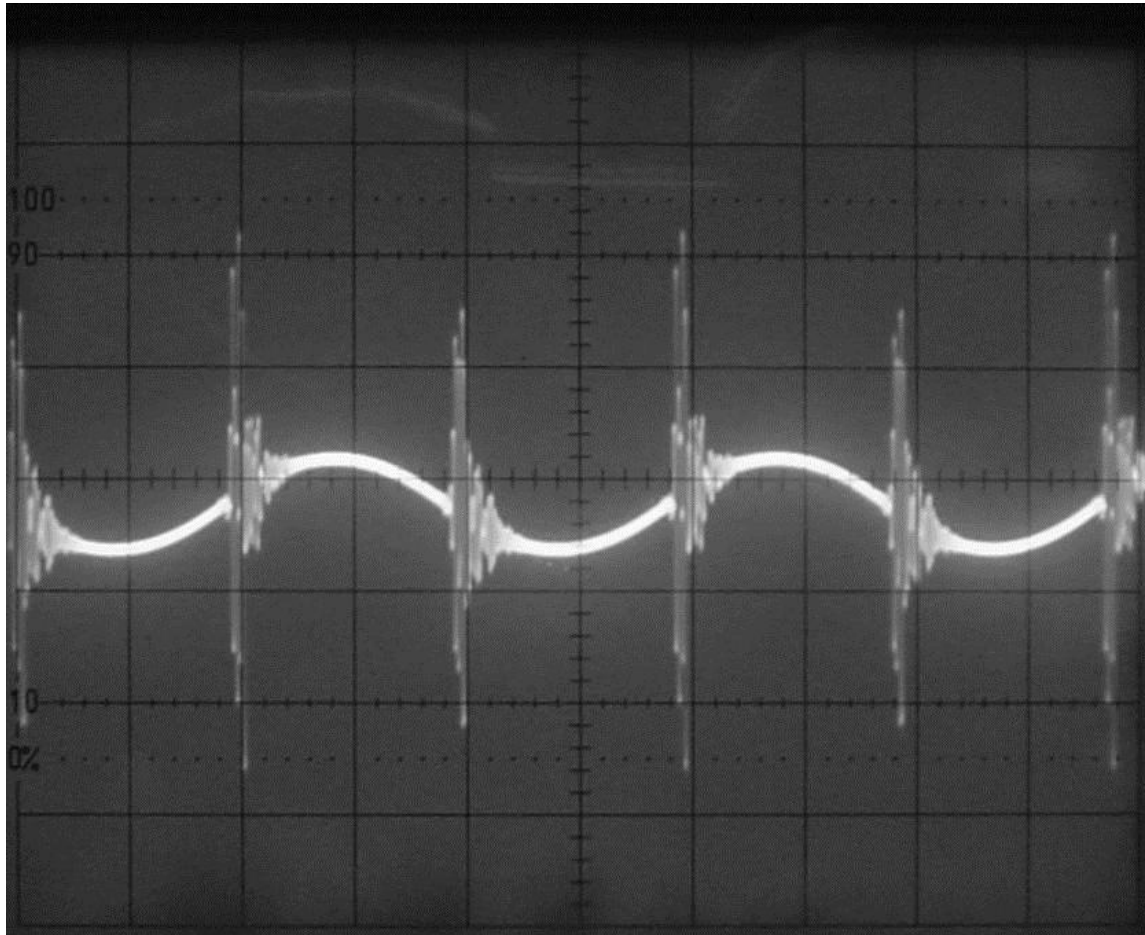




# Class D and EMI
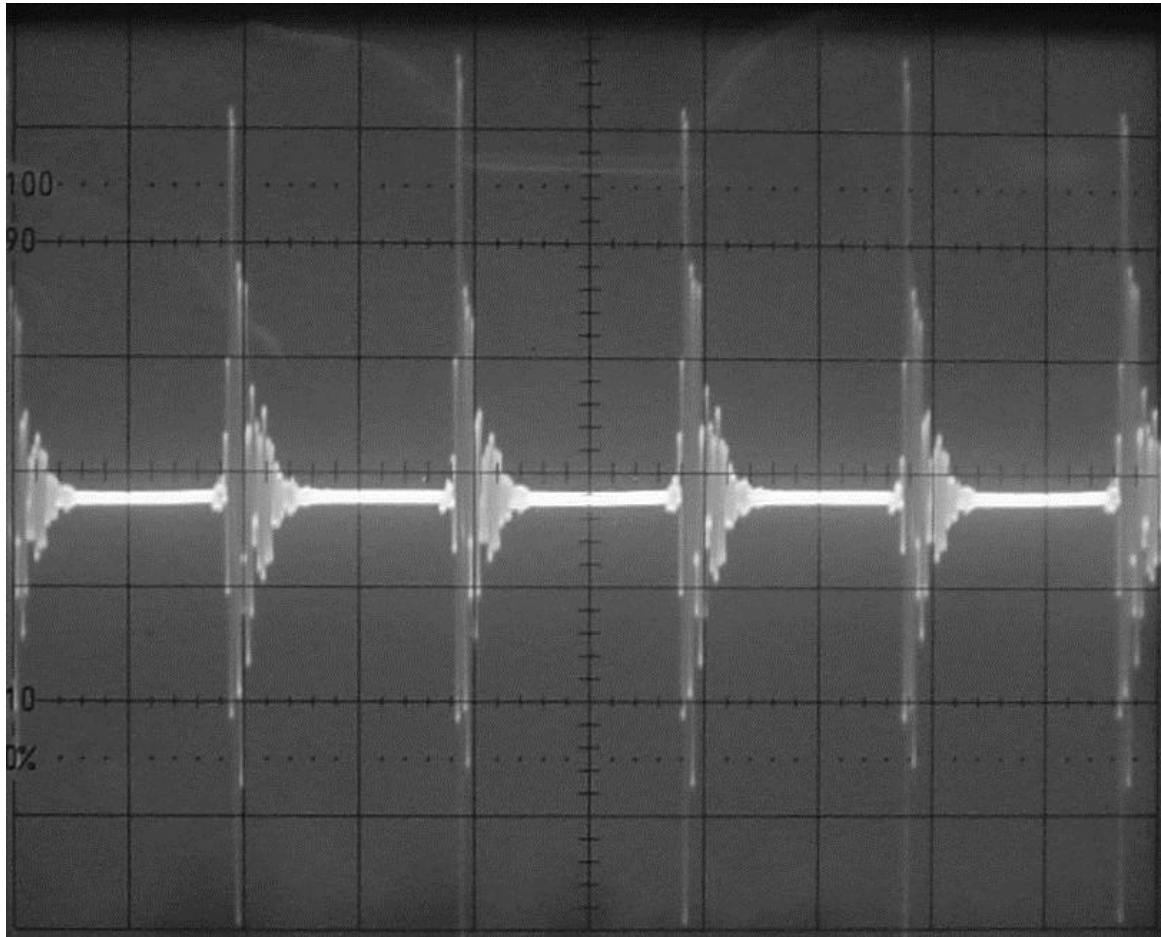
## Amplifier A, common mode


- 500mV/div. Amp is claimed to pass FCC???



# Class D and EMI


## Amplifier A, differential mode

- 500mV/div. Note: relatively clean.

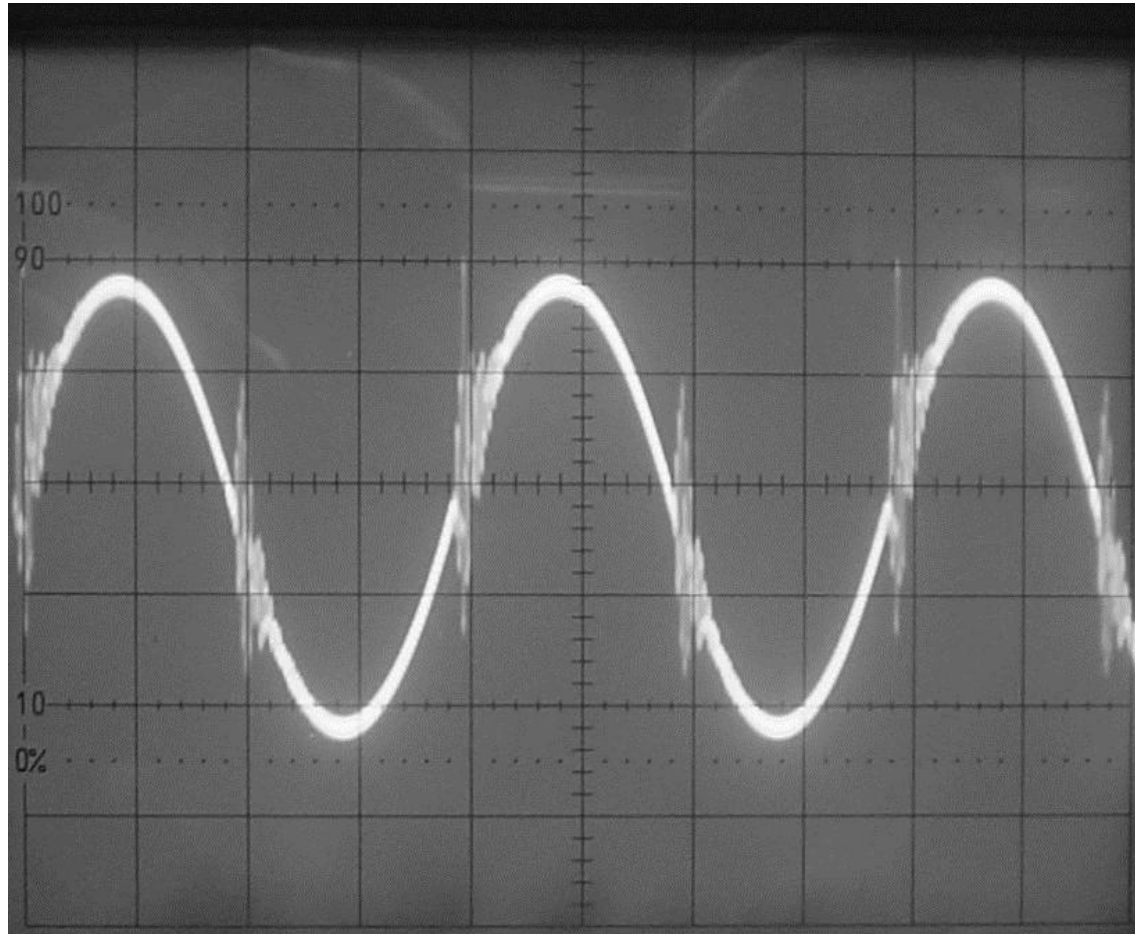

# Class D and EMI


Example: Amplifier B, rated 2kW

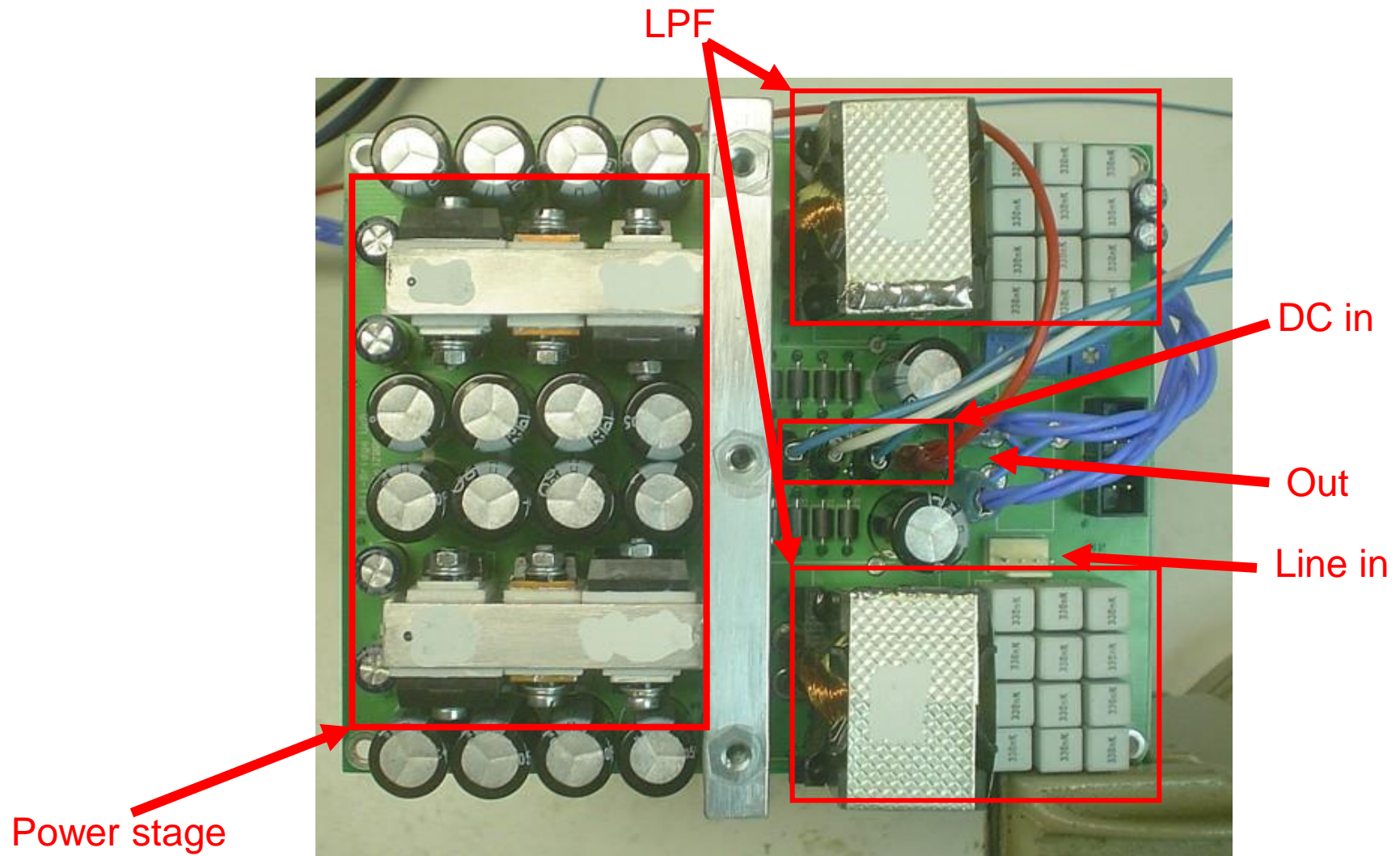

# Class D and EMI
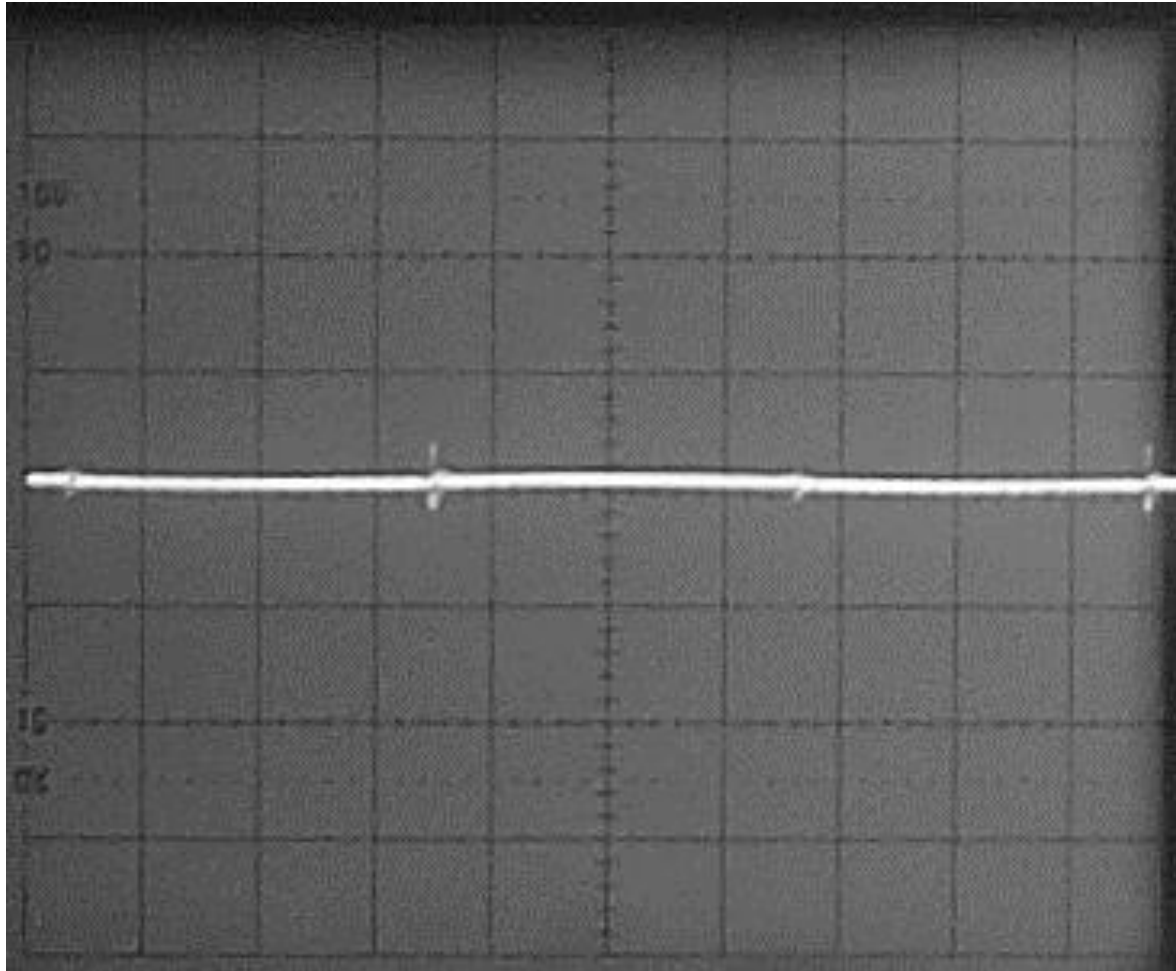
## Amplifier B, common mode

- 250mV/div. Probe clip at power GND faston tab






# Class D and EMI

## Amplifier B, differential mode

- 500mV/div.

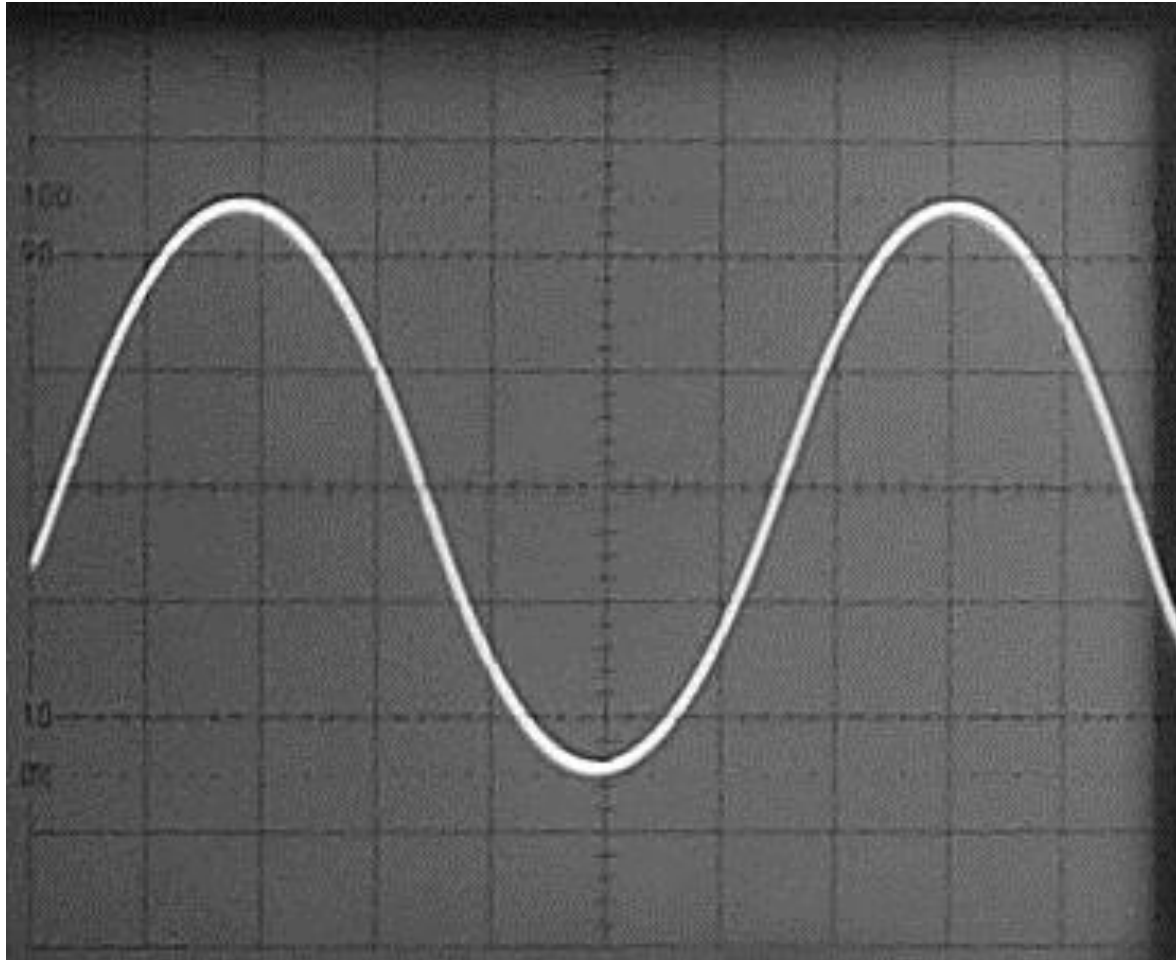

# Class D and EMI

## Class D EMI is no mystery

- Eyeballing components and PCB gives good indication
- Invest in an analogue scope
- Don't bother EMC testing if the scope pic isn't squeaky clean

# Specifying SMPS for Audio

## The complaint

- “I need a 2kW amp to do what a 1kW amp would do in the old days”
- “It sounds great with some sources and sux with others”

# Specifying SMPS for Audio

## Power Handling of COTS SMPS

- Protection limit = Peak Rating = DC rating
- Thermal design for rated output
- Protection = constant current, foldback or stop



# Specifying SMPS for Audio


## Power demand of resistive load

- Peak current/voltage =  $1.414 \times \text{RMS}$
- Peak power =  $2 \times \text{average ("RMS") power}$

# Specifying SMPS for Audio

## Power demand of reactive load


- Example impedance plot

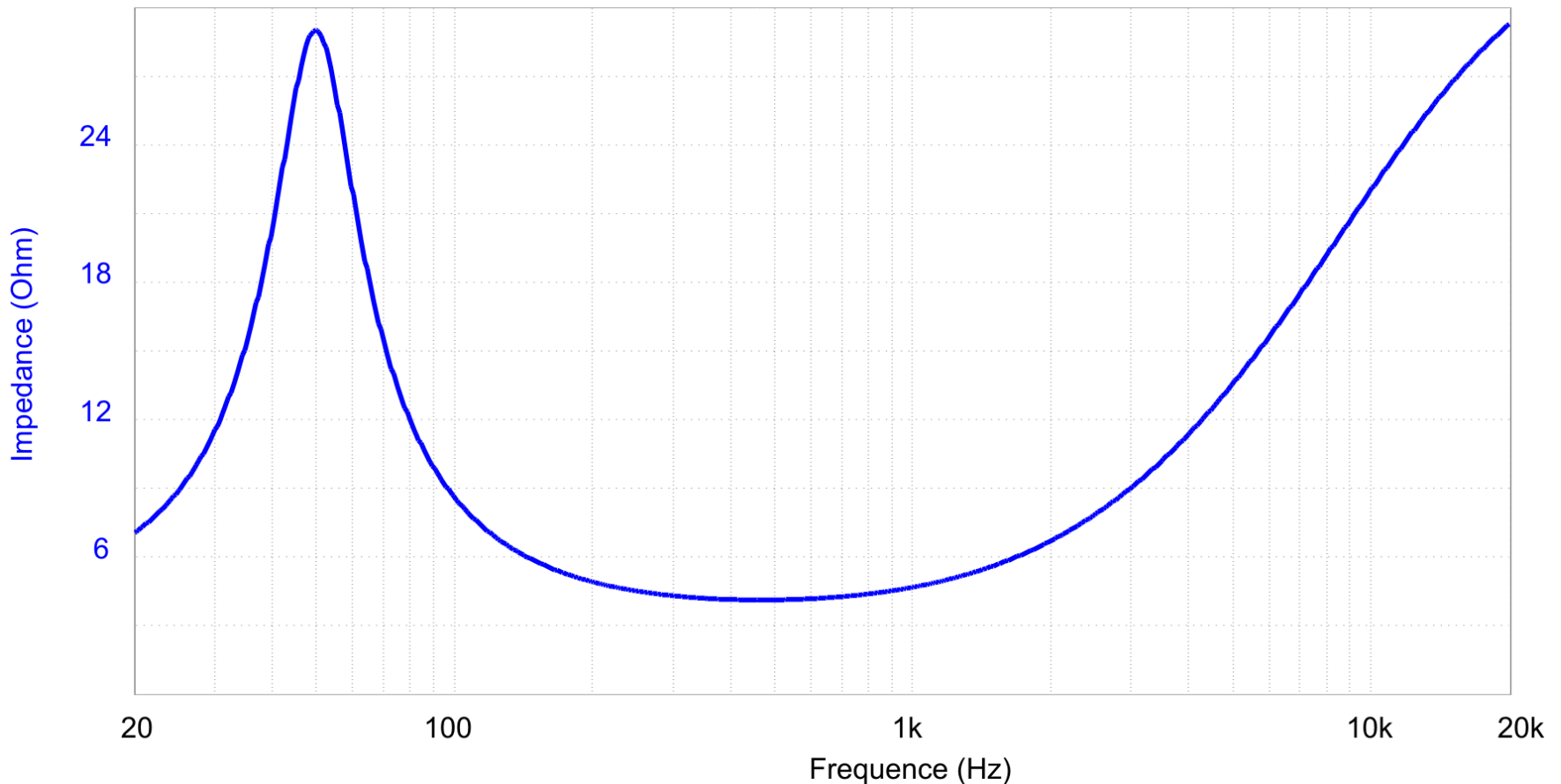

# Specifying SMPS for Audio

## Power demand of reactive load

- Worst case current pulse

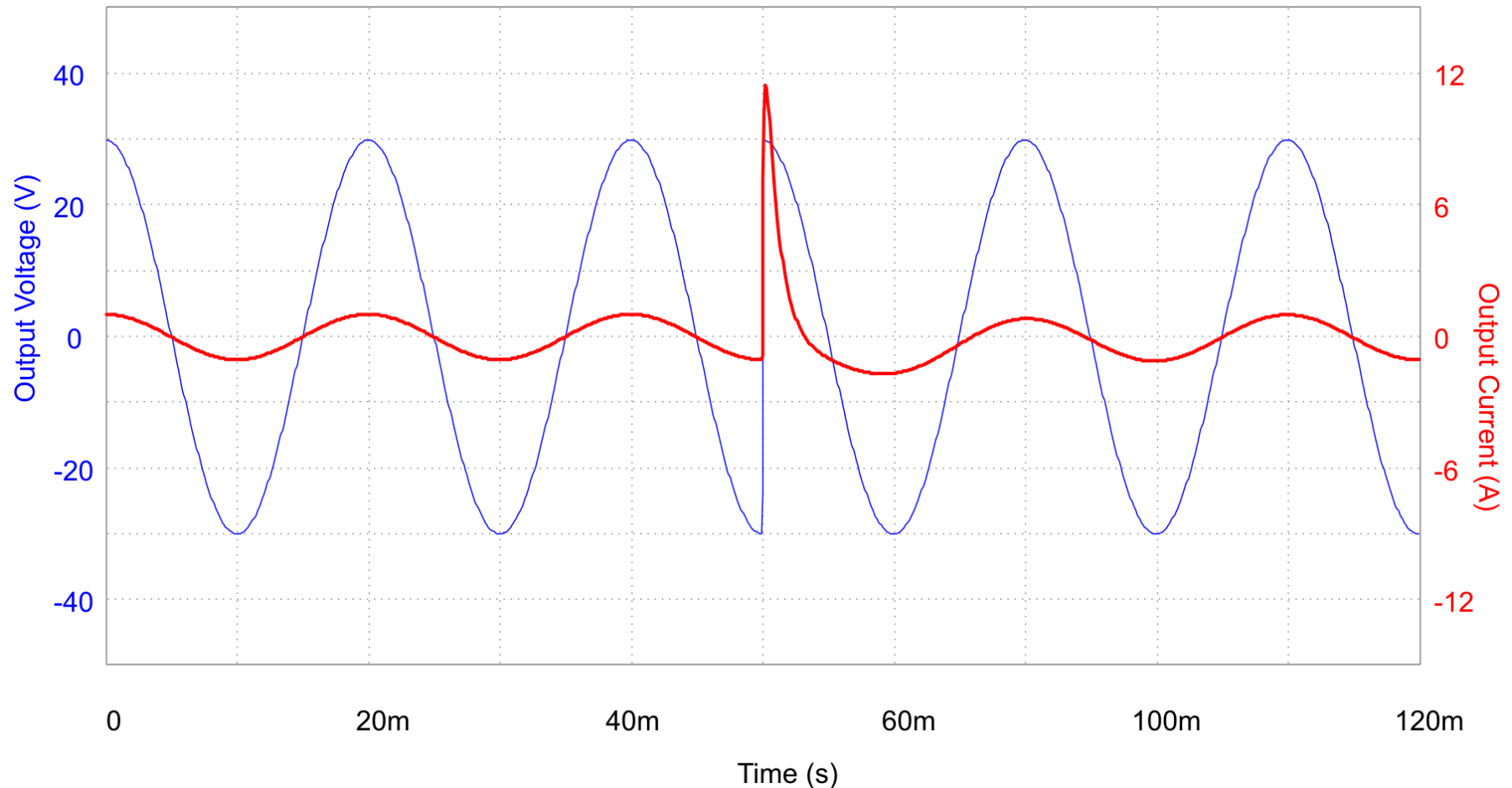

# Specifying SMPS for Audio

## Power demand of reactive load

- Maximum current pulse = 2x peak current in DC resistance!

## Reactive or resistive:

- SMPS rating = amplifier rating is inadequate

# Specifying SMPS for Audio


## Practical set of requirements

- Thermal design
  - $1/8P_r$  indefinitely (suggest  $1/3P_r$  for pro)
  - $P_r$  continuous for 5 minutes (IHF rating)
- Protection
  - Constant-Power at  $2x P_r$

# Specifying SMPS for Audio
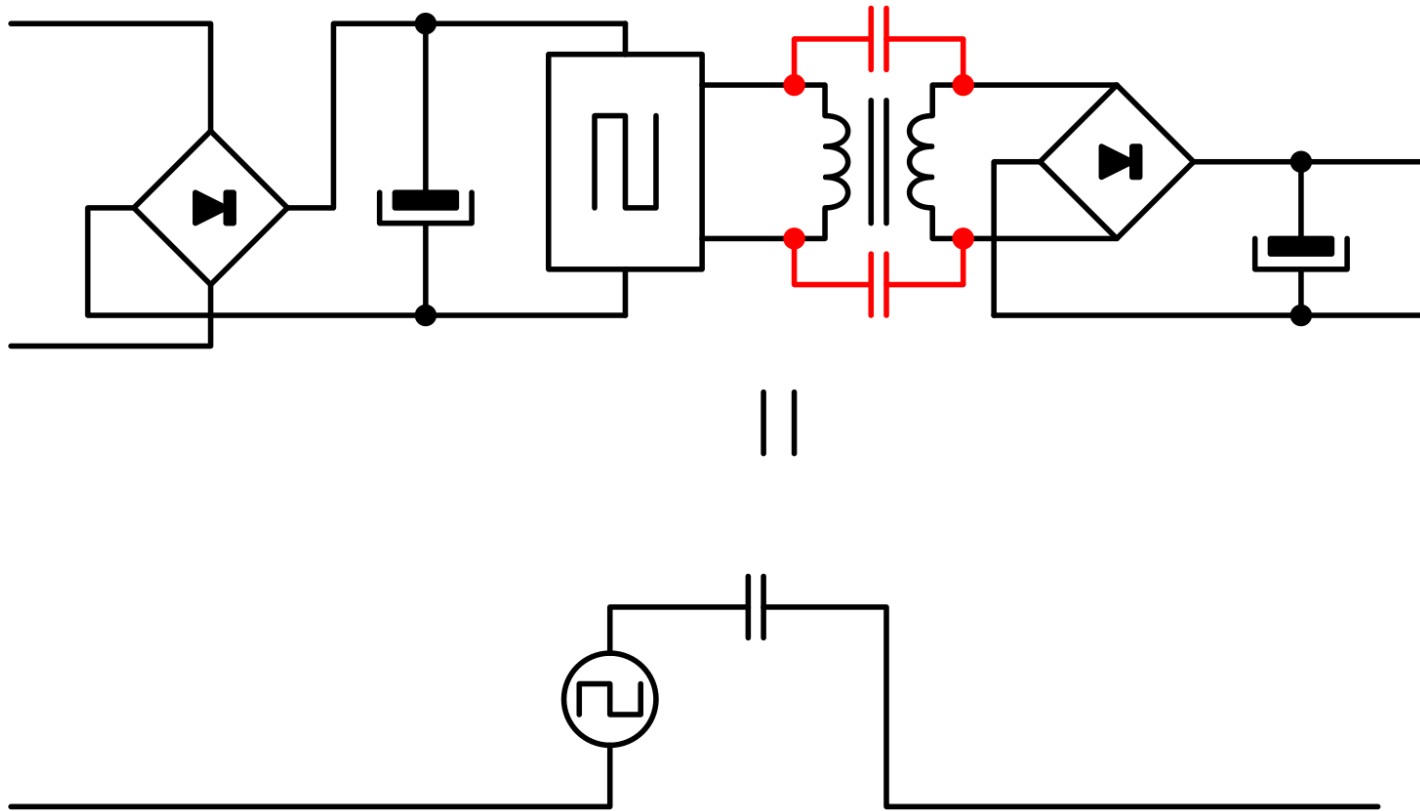
## EMI: Injected mains current



- Getting clean rails is easy (differential mode)
- Getting low CM noise is harder


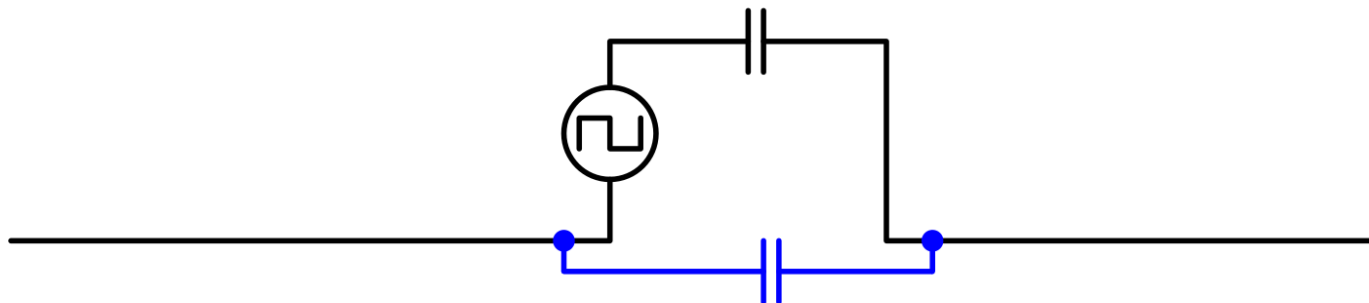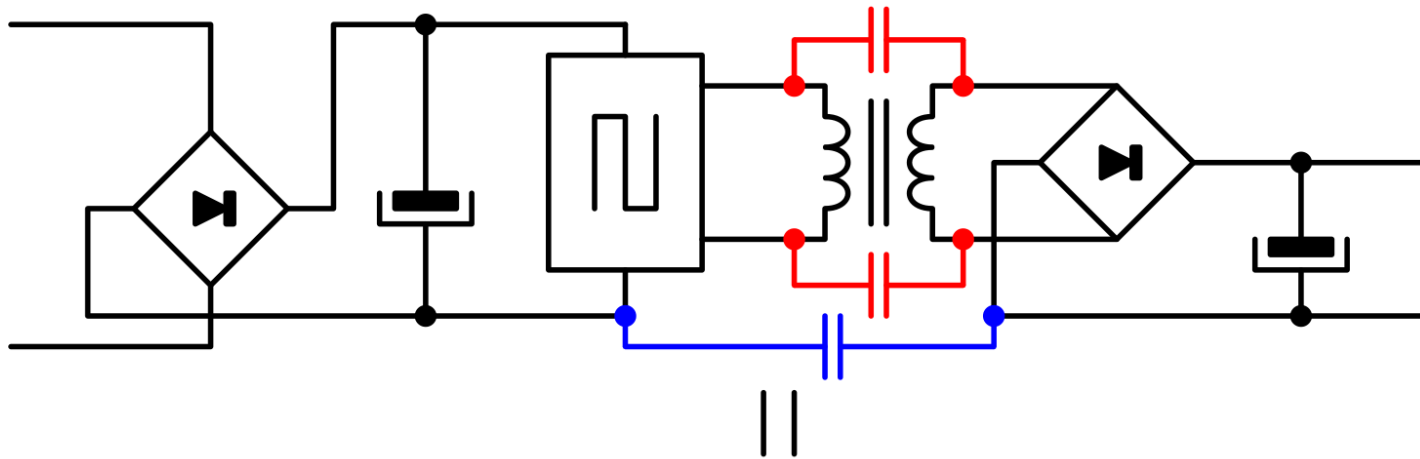
# Specifying SMPS for Audio

Y cap reduces CM noise voltage


- CM current reduction is indirect
- Increases coupling of mains-borne noise



# Specifying SMPS for Audio
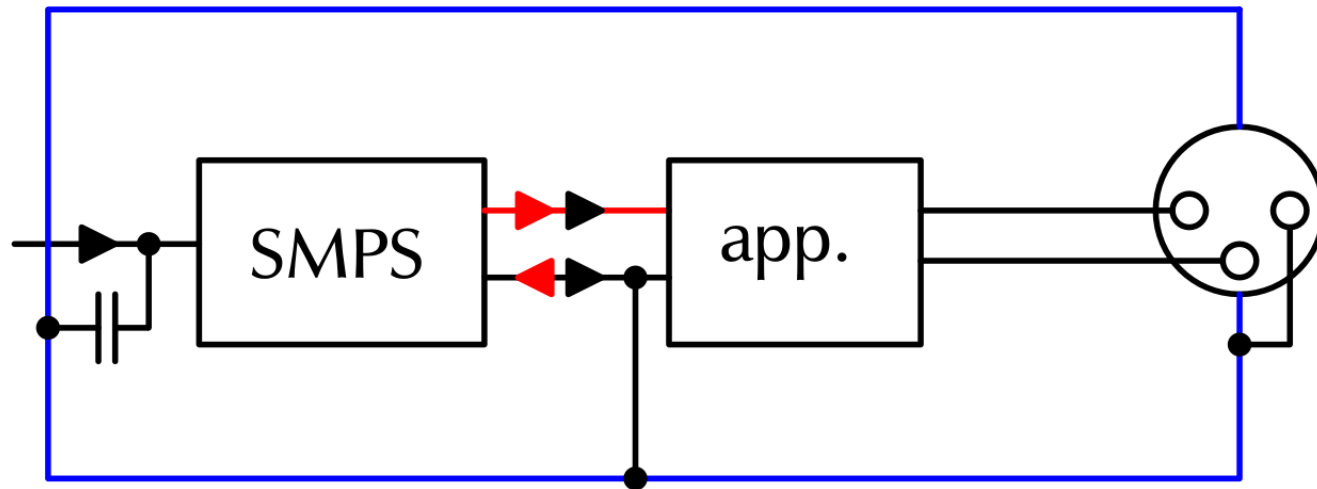
## Leakage current exacerbates Pin-1 problem

- Current enters circuit ground.
- Circuit ground current includes return
  - You can't just disconnect it (AES48 style).
  - Requires chassis connection at PSU output.
  - Creates additional layout challenges





# Specifying SMPS for Audio

## Additional EMI requirements for audio SMPS

- Common mode voltage/current noise
- Primary-to-secondary impedance

# “ID” in Audio: Successful Co-Development

## Nightmare story #1

- Customer wanted 100W class D solution
- Subcontracter had a fully working design that fit well
- C insisted on using “metal core” boards (hybrid)
- S made list of 8 technical issues that would definitely kill the project.
- C said all problems would get resolved
- All problems materialised, few got solved
- Project failed. C’s project manager resigned

What went wrong?

# “ID” in Audio: Successful Co-Development

## Nightmare story #1

- Customer wanted 100W class D solution
- Subcontracter had a fully working design that fit well
- C insisted on using “metal core” boards (hybrid)
- S made list of 8 technical issues that would definitely kill the project.
- C said all problems would get resolved
- All problems materialised, few got solved
- Project failed. C’s project manager resigned

Customer specified how, not what

# “ID” in Audio: Successful Co-Development

## Nightmare story #1

- Customer wanted 100W class D solution
- Subcontracter had a fully working design that fit well
- C insisted on using “metal core” boards (hybrid)
- S made list of 8 technical issues that would definitely kill the project.
- C said all problems would get resolved
- All problems materialised, few got solved
- Project failed. C’s project manager resigned

Customer specified how, not what

Customer could not justifiably make this judgment!

# “ID” in Audio: Successful Co-Development

## Nightmare Story #2

- C wants high-end class D amplifier...
  - that does not use feedback
  - that processes DSD...
  - ...with no alteration
- S produces a highly complex but working prototype
- C thanks S and starts product development cycle.
  - Layout gets changed
  - Clock distribution gets changed
- ...
- Project fails as C can't debug a buck regulator circuit...

What went wrong?

# “ID” in Audio: Successful Co-Development

## Nightmare Story #2

- C wants high-end class D amplifier...
  - that does not use feedback
  - that processes DSD...
  - ...with no alteration
- S produces a highly complex but working prototype
- C thanks S and starts product development cycle.
  - Layout gets changed
  - Clock distribution gets changed
- ...
- Project fails as C can't debug a buck regulator circuit...

**C specifies how, not what**

# “ID” in Audio: Successful Co-Development

## Nightmare Story #2

- C wants high-end class D amplifier...
  - that does not use feedback
  - that processes DSD...
  - ...with no alteration
- S produces a highly complex but working prototype
- C thanks S and starts product development cycle.
  - Layout gets changed
  - Clock distribution gets changed
- ...
- Project fails as C can't debug a buck regulator circuit...

C specifies how, not what

C overestimates self / underestimates problem

# “ID” in Audio: Successful Co-Development

## Outset

- Customer has needs
- Subcontractor has capabilities

## Potential problem

- Perceived overlap of competences  
(Real overlap of actual competences is not a problem)

## Failure modes

- Customer overestimates what they can do themselves
- Customer specifies implementation details
- Subcontractor meddles in customer's work.



# “ID” in Audio: Successful Co-Development

## Success Story

- C wants DSP/amplifier electronics for loudspeaker
- C and S agree “black box” spec
- S designs electronics
- C designs acoustics and filters
  - Politely refuses S’ spontaneous input (“that’s our problem”)
- Both parties finish in time, product is well received.

# “ID” in Audio: Successful Co-Development

## Critical steps for the Subcontractor:

- Agree and insist on responsibilities
- Avoid inept customers
- Refuse paper-only gigs
- Charge for spec changes once the design is underway

# “ID” in Audio: Successful Co-Development

## Critical steps for the Customer:

- Hire expertise, accept expertise.
- Write “black box” performance spec
  - Performance is judged with the box closed and the power on.
  - “Subjective sound quality” is a black box spec too.
  - Type of circuit or parts is not a performance spec.

# “ID” in Audio: Successful Co-Development

## The Two Roads

The Road To Hell:

Specify the Design, Accept the Performance.

The Road To Heaven:

Specify the Performance, Accept the Design.

Thank you!



Grimm | *AUDIO*

[recforums.prosoundweb.com](http://recforums.prosoundweb.com)