

Aleph Current Source Modifications
A W Newby
Mar 2007

Aleph Current Source Modifications

The Aleph controlled current source is a simple and effective circuit which provides the active load in the output stage of several Pass designs. The quiescent current in the output stage is set by a single sense resistor and is controlled by a bipolar transistor in a feedback loop. The current can be modulated by feeding an audio signal into the feedback loop. We examine the performance of the circuit at high signal levels; sufficient to cause clipping. It could be argued that the amplifier should not be driven so hard that clipping occurs. However, occasional peak transients may be hard to avoid and the modifications are both simple and effective. The observations have been with reference to Zen V4, but should be applicable to other designs using the Aleph CCS.

The Basic Circuit

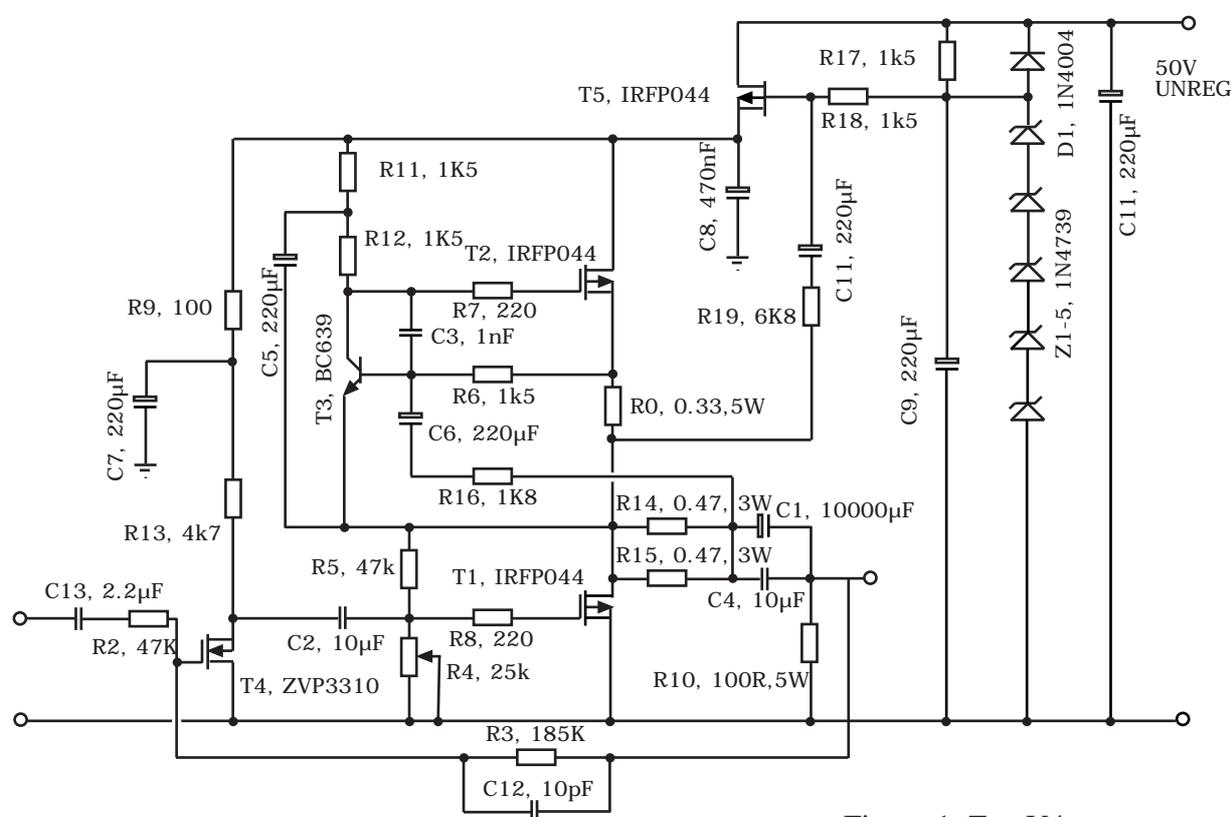


Figure 1. Zen V4

In Zen V4, the potential across R0 is sensed by transistor T3. A negative feedback loop controls the gate of T2 to maintain a constant drain current of $\sim 2 \text{ Amps} = V_{be}/R_0$. The current is modulated via C6 and R16. A bootstrap capacitor C5 provides a high impedance a/c load for transistor T3 by ensuring the voltage swing across R12 is low.

At low output signal levels, the voltage across transistor T3, $V_{c3} \sim V_{gs} + V_{R0} \sim 4.7 \text{ Volts}$. Just prior to clipping, the Aleph CSS will be supplying around $2A \pm 1A$. The potential dropped across VR0 will swing from 0.3 to 1.0 Volts and V_{c3} will vary from 4.35 to 5.05 Volts.

If the signal increases still further, clipping will occur and sharp peaks will occur in V_{c3} as transistor T2 switches hard on. Because of the voltage dropped across R0, the output cannot swing right up to the supply voltage. Given a symmetrical signal, positive clipping occurs before negative clipping. The output voltage starts to clip at 0.8 Volts above the ground rail and 2.0 volts below the positive supply rail. Relative to the 20V mid point, clipping occurs at -19.2 to +18 volts. Figure 2. shows the output and V_{c3} characteristic at the onset of clipping.

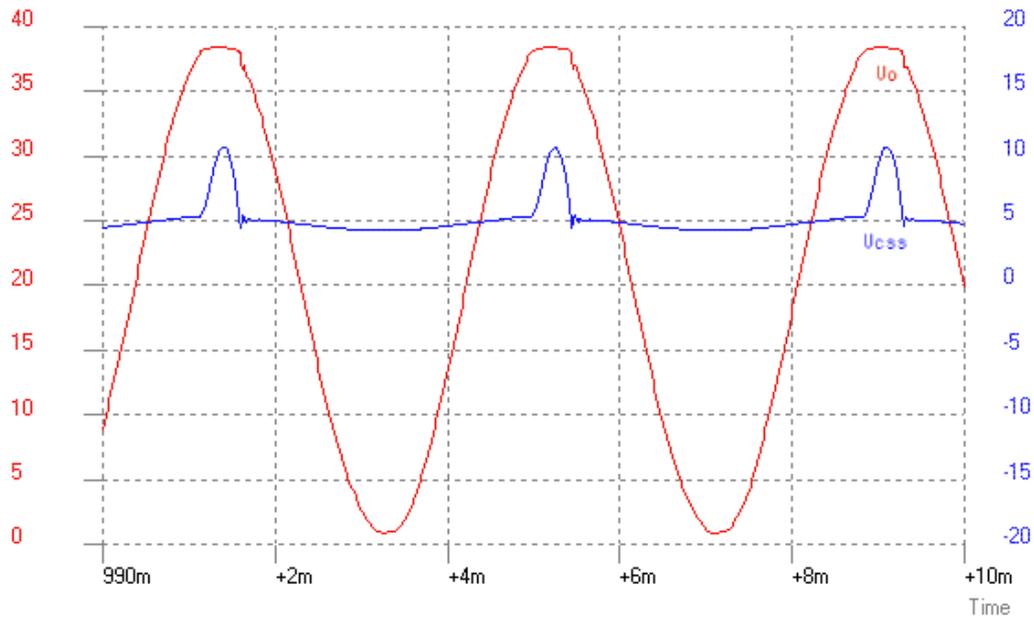


Figure 2. Output and V_{css} Characteristic at Clipping

The peaks in gate voltage of T2 exceed 10 volts whilst V_{ds} drops to near zero. During these peaks, the mosfet is well and truly in the linear region and behaves like a resistor of a few milli Ohms. Negative feedback around transistor T3, means that the peaks in transistor T2's drain current have a 'bite taken out'. This can be seen by looking at the voltage dropped across the sense resistor R_o , See Figure 3..

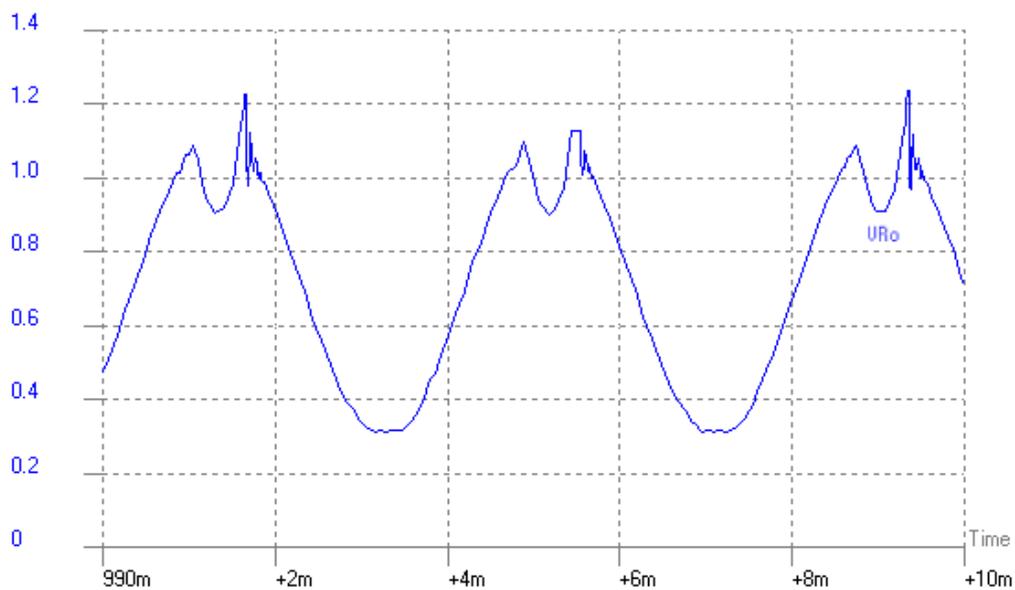


Figure 3. VR_o Characteristic at Clipping

The peaks in V_{css} are rather abrupt and the feedback arrangement, damped by R_6 and C_3 is a little slow to respond. The result is instability, particularly on the transition from clipping to normal operation. It takes 100 μ s or so for the instability to subside. This can be seen on V_{css} , VR_o and the amplifier output V_o . Relative to the 20V mid point, the distortion in the output is noticeable at a positive swing of just 16 volts. See Figure 4.

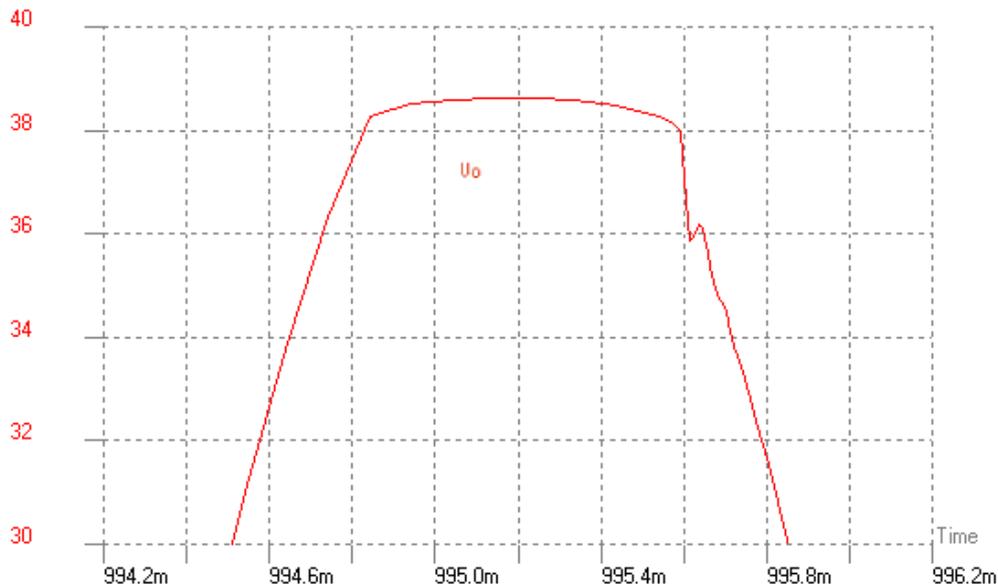


Figure 4. V_o Characteristic at Clipping

Note that the output voltage does not have a flat top. In the positive clipping state, the mosfet V_{ds} is near zero and the rounded top is the mirror of the 'bite taken out' of V_{R0} . The "ringing" can be minimised a little by reducing the value of $C3$ but doing so risks high frequency instability. The best solution is to limit V_{css} .

Aleph CCS with zener clamp

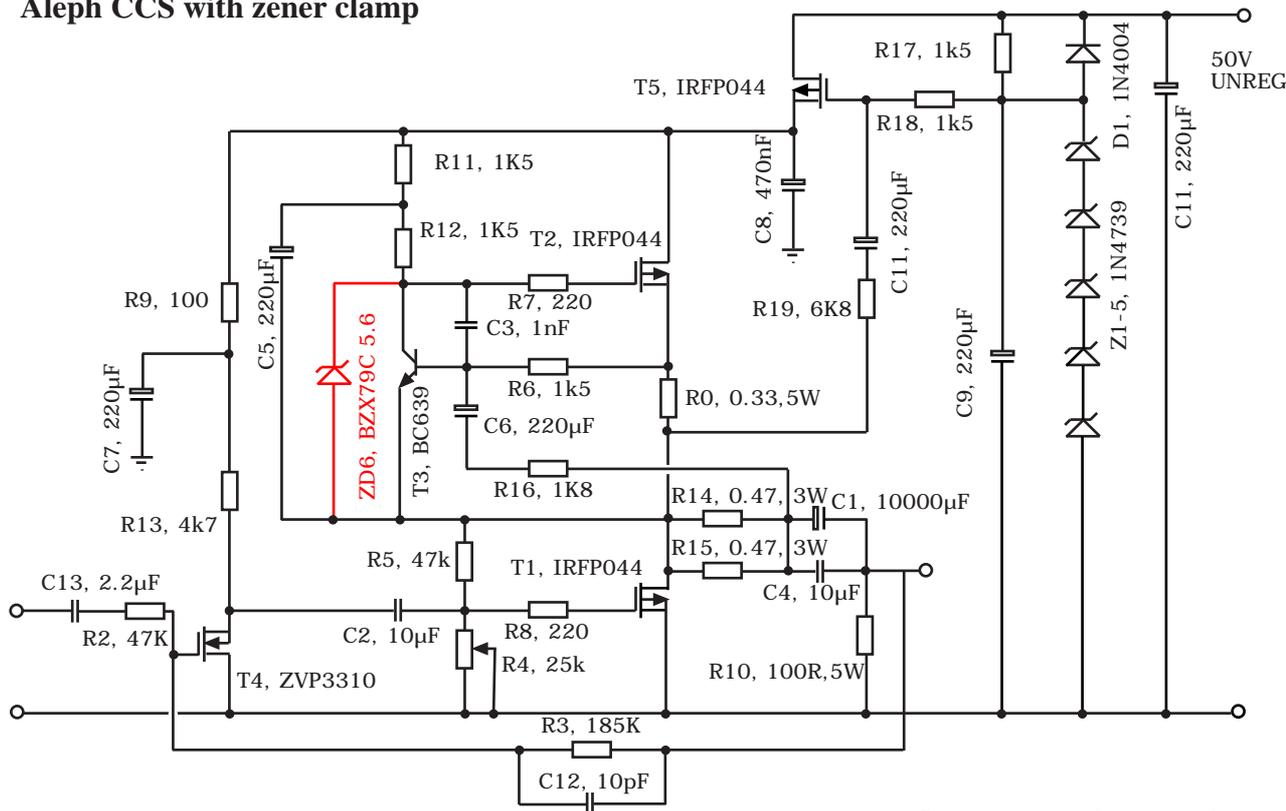


Figure 5. Zen V4 with zener clamp

The basic solution is as simple as it gets. A zener diode prevents V_{css} rising above the clamp voltage, which needs to be as close to the maximum normal swing of V_{css} . A 5.6 Volt zener should suffice and allows for part to part variation in the threshold voltage of $T2$.

Aleph CCS with current source and zener clamp

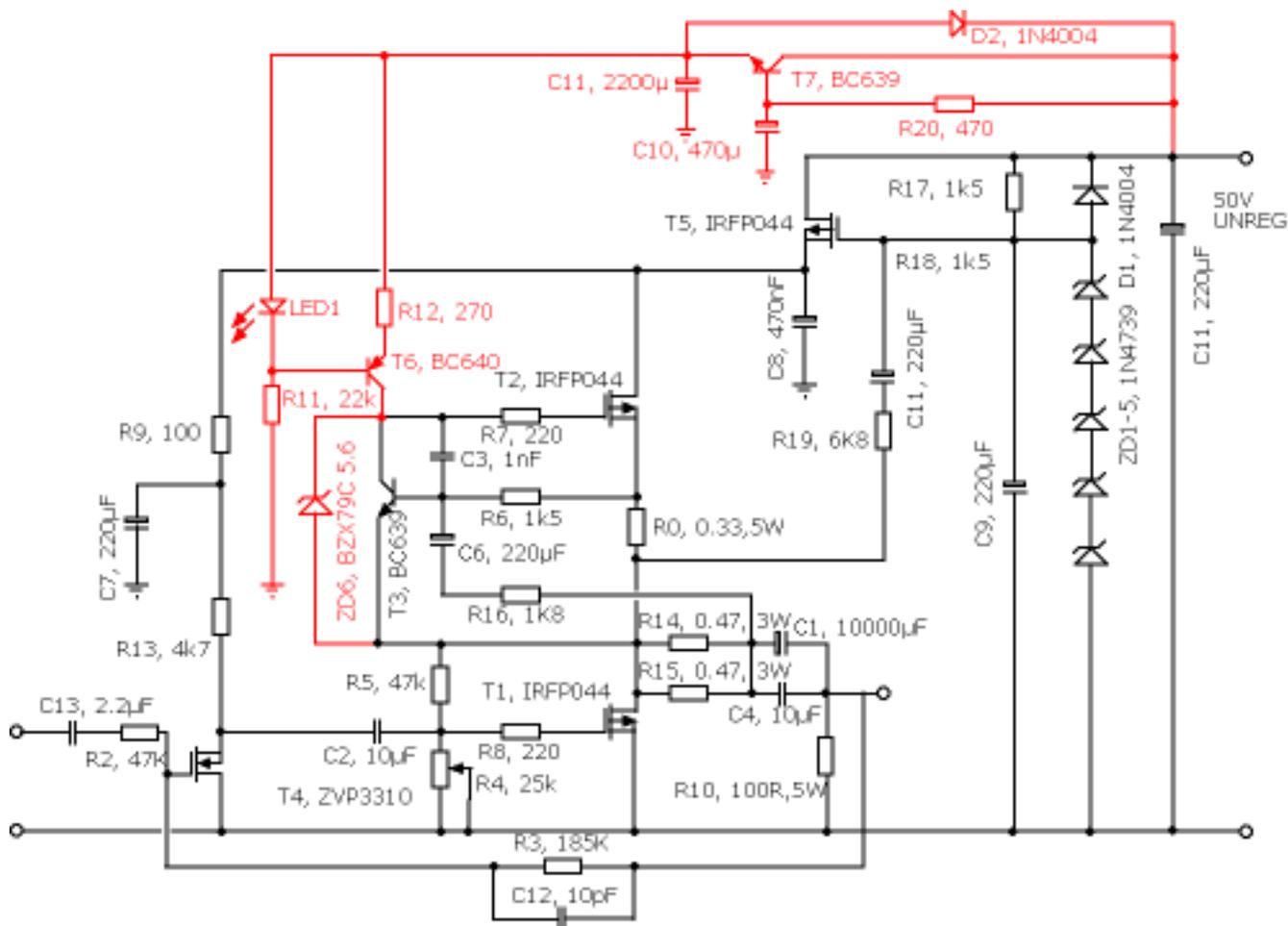


Figure 6. Zen V4 with current source & clamp

The basic circuit uses a bootstrap capacitor to provide a high impedance load for the feedback control transistor T3. For constructors who have built, or are interested in the Aleph CCS variant described in LTPZen, the circuit shown in Figure 6. uses a simple current source instead. The circuit exploits the forward voltage drop of a standard red LED. The current $= (V_f - V_{be})/R_{14}$ is set at 5 mA but is not critical. The current source requires an elevated supply voltage, provided by transistor T7 configured as a bipolar capacitance multiplier. As with the basic Aleph CSS clamp, the zener diode ZD6, clamps V_{css} to a maximum of 5.6 Volts.

Performance

The output characteristic with and without the clamp is shown in Figure 7. The zener clamp completely eliminates the post-clipping instability. As far as clipping is concerned, there is no difference in the performance between the basic circuit shown in Figure 5. and the variant shown in Figure 6.

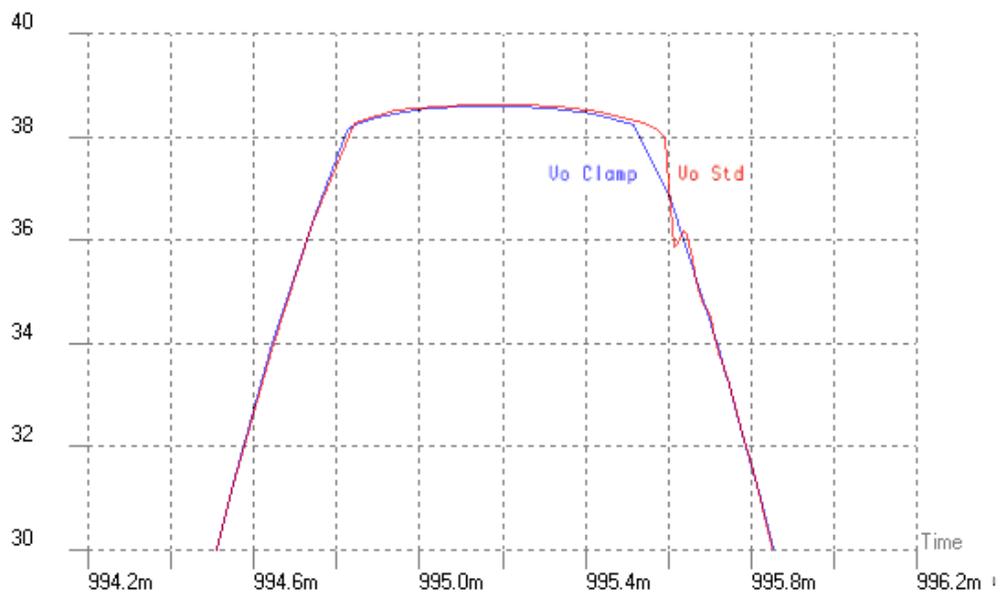


Figure 7. V_o Characteristic at Clipping; with / without clamp