

is approximately  $0.6\%/K^4$ . Maximum output current is determined by emitter current and the current gain of  $Tr_{9,11}$  or  $Tr_{10,12}$  respectively,

$$I_{O(max)} = \pm I_E h_{FE}^2 \quad (4)$$

It can be seen that, in contrast with many other designs, the maximum output current capability is symmetrical.

### Optimisation

Figure 2 shows the complete amplifier as used for our PSpice simulations. Adding  $Tr_5$  simplifies equation (3) to,

$$I_{C9} = I_{C10} = I_R \quad (5)$$

As a result, the quiescent current of the output stage is,

$$I_{C11} = I_{C12} = h_{FE} \times I_R \quad (6)$$

Note that the maximum available base current for  $Tr_8$  is increased with a factor square-root  $h_{FE}$  and the accuracy of the bias control loop is increased too.

Capacitors  $C_m$  and  $C_f$  perform frequency compensation. Capacitor  $C_m$  is a Miller capacitor, compelling the

open-loop transfer to a first-order frequency behaviour. Capacitor  $C_f$  forms feed-forward frequency compensation around the common-base connected level-shift transistor  $Tr_8$ .

Currents  $I_E$  and  $I_R$  are determined by

$V_{diode}/R_6$  and  $V_{diode}/R_7$  respectively. Emitter degeneration –  $R_1$  and  $R_2$  added to  $Tr_1$  and  $Tr_2$  respectively – is used to increase the amplifier's input voltage range to reduce transient inter-modulation distortion.

 


Fig. 8. Magnitude and phase plots of the output impedance.