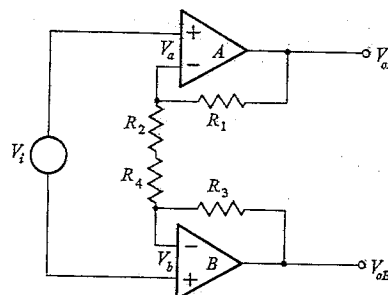


6-5 A DIDO system using two op amps is shown in the figure. DIDO stands for *differential input, differential output*. For minimizing offset and matching of parameters, the two op amps are fabricated on the same chip. Use  $V_{oA} = A_{vA} V_a$  and  $V_{oB} = A_{vB} V_b$ . Prove, for this system,

$$(a) \quad A_v(\text{diff}) = \frac{V_{oA} - V_{oB}}{V_i} = \frac{A_{vA}}{1 + A_{vA}[(R_2 + R_4)/(R_1 + R_2 + R_3 + R_4)]}$$


$$(b) \quad Z_i = \frac{V_i}{I_i} = 2R_{iA}(1 + A_{vA}K),$$

where  $R_{iA} = R_{iB}$ ,  $A_{vA} = A_{vB}$  and  $K = (R_2 + R_4)/(R_1 + R_2 + R_3 + R_4)$ .



Problem 6-5

6-6 The connection shown in the figure is referred to as a *voltage-follower* or *noninverting buffer*. Discuss the reasons why  $V_o = V_i$ , and comment upon the terminal impedance levels.

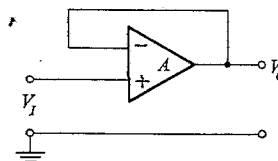

Problem 6-6

6-7 Show that when two parallel networks  $a$  and  $b$  are feeding  $\epsilon$  in Fig. 6-8 from voltages  $V_{ia}$  and  $V_{ib}$ , the relation between output and input is

$$V_o = - \left[ \frac{y_{21a}}{y_{21F}} V_{ia} + \frac{y_{21b}}{y_{21F}} V_{ib} \right].$$

6-8 Prove Eq. (6-21) for the bridged-T network.

6-9 Prove Eq. (6-22) for the twin-T network.

6-10 Prove Eq. (6-32) for inverting feedback.