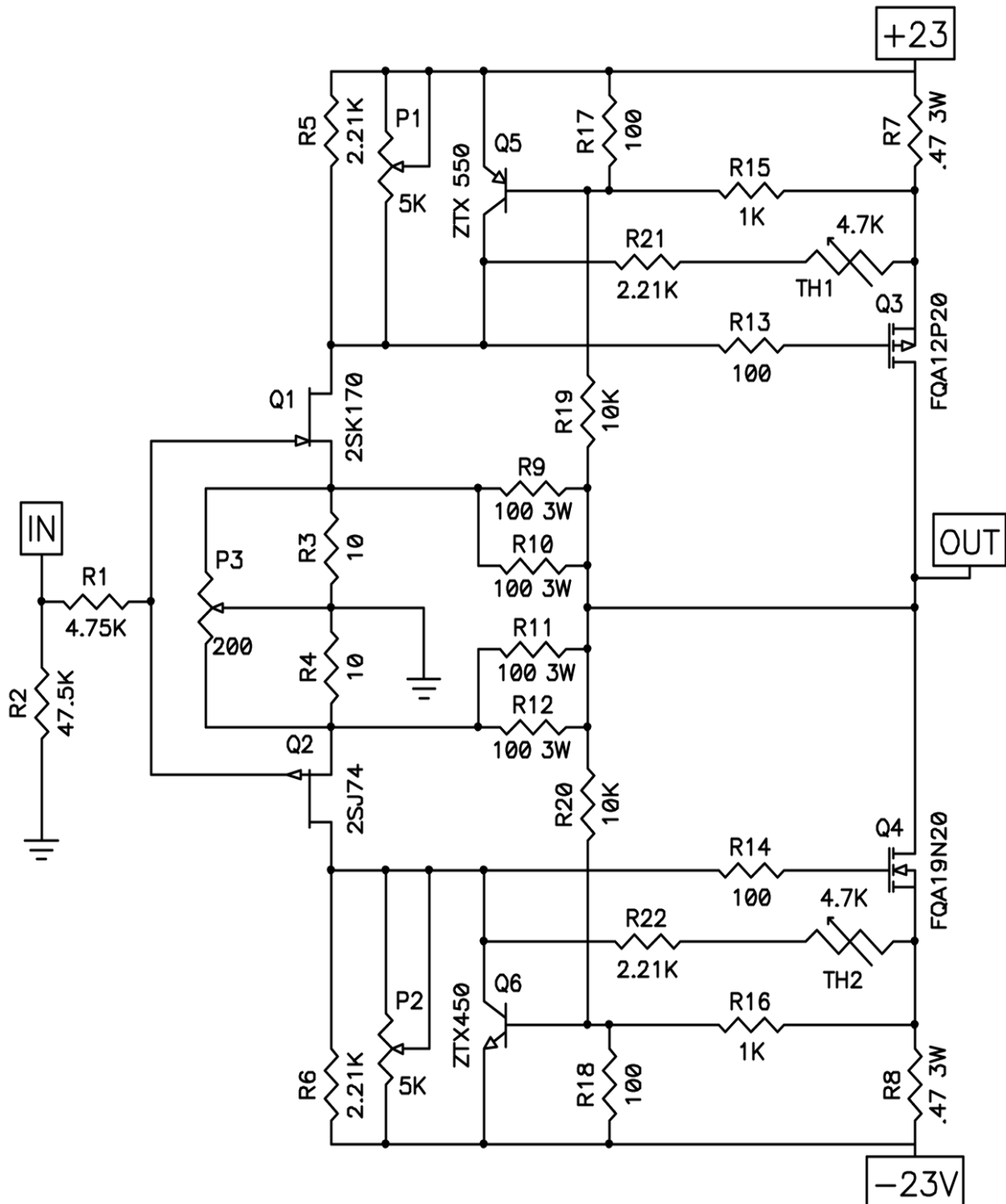


Assuming that you are already mostly familiar, here is the official DIY F5 schematic. It differs mostly from the original by the inclusion of P3, which aids in tweaking the symmetry of the circuit for the lowest possible distortion.



F5 AMPLIFIER

(C) 2008 NELSON PASS