

Walt's Blog 2014

REFERENCES AND REGULATORS, WHATS NEW

GLED431: AN ULTRA LOW NOISE LED REFERENCE CELL

DECEMBER 18, 2015 | WALT JUNG | 1 COMMENT

Looking for a low noise reference circuit for an audio regulator, at 2.5V? But you've found bandgap circuits too noisy? Read on!


Consider the simple circuit to the right, which I call the GLED431. Just 3 low cost parts, all easy to get. It acts like an extremely low noise 2.5V zener. On my setup, noise measures around $2\text{nV}/\sqrt{\text{Hz}}$, so if you take out the measuring system noise, the actual noise is likely below $1\text{nV}/\sqrt{\text{Hz}}$. Really quite good. We'll have more on this later on, in 2016.

While the GLED431 performance is very high for noise, you will need to apply about 5mA (or more) to make it work. Yes indeed, this current threshold is much higher than that of the TL431. But, it also has around 1/100 the noise! **Caveat(1): The voltage won't be as tight as typical bandgap ICs, nor as low for temperature drift. Those are conscious tradeoffs.**

Here are some V_{out} measurements on a sample set of 5 LTL-4231Ns, in the lab prototype shown, after 1 minute warmup:
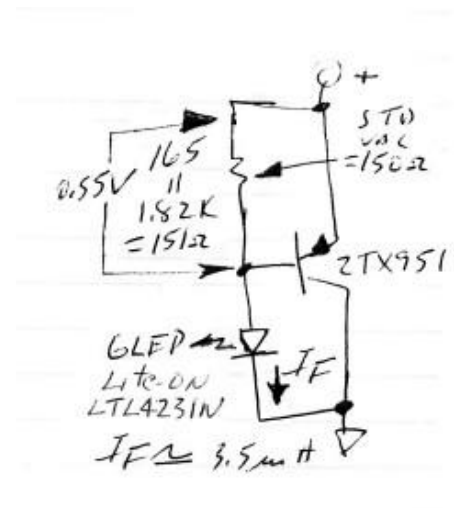
#1: 2.5094V, #2: 2.5093V, #3: 2.5069V, #4: 2.5019V, #5: 2.5062V

Not too shabby! In the schematic, the leftmost R values are just as shown from lab tests, as trimmed for the 2.500V target V_{out} . Obviously, just use a single 150Ω RN60D unit for this R. Note that the forward voltage of the **LTL-4231N** green LED (LiteOn) and the V_{be} of the **ZTX951** (Diodes Inc.) conveniently add,



This GLED431 circuit is very simple, and works as a 2.5V shunt reference with ultra low noise.

GO

DEC

JAN

MAR

20

2015

2016

2017

About this capture

9 captures

25 Dec 2015 - 29 Jun 2018

In use, if you are building say, a 5V regulator, select a series resistor so that 5mA is supplied to the GLED431 cell (499Ω). With this, also be sure to select a very low noise op amp, and reduce all the surrounding resistances, so as to minimize *their* noise contributions. Finally, be careful to minimize capacitive loading.

I am now releasing this simple version, as a Christmas present to the readers. Stay tuned for more, have fun with the GLED431, and have a great holiday!

Walt Jung

December 24, 2015



ONE THOUGHT ON “GLED431: AN ULTRA LOW NOISE LED REFERENCE CELL”



★ **Walt Jung**

JANUARY 18, 2016 AT 11:17 AM

From the [DIYaudio thread](#) by Jack Walton.

Quote: “Is there any particular reason to use ZTX951? How about BC560 low noise PNP?”

Response: Caveat 2 is the answer re the ZTX951 for the target Vout, plus the fact that it also offers lowest noise. This isn't just theory, it was tested.

Comments about dynamic Z aren't relevant to the cited application, where the GLED431 cell is operated within a regulator with the ref cell biased from the output (i.e., the example 5V reg, with a 499 ohm feed R from 5V).

COMMENTS ARE CLOSED.

