

Calculating voltages gives:
 $V_x = \frac{1}{3}[3 \cdot (V_x - V_0)] + \frac{2}{3} \cdot V_{in}$
 which leads to:
 $V_0 = 2 \cdot V_{in}$

