
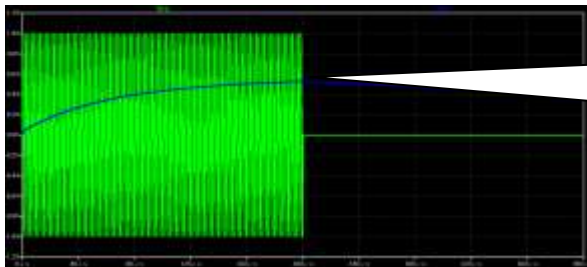


AC  
response

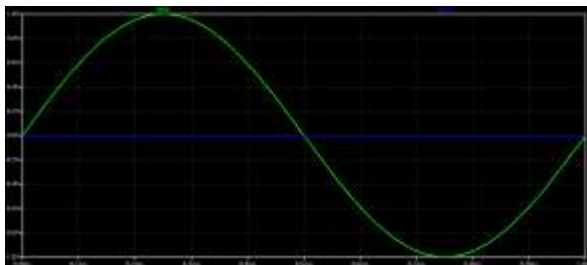

500KHz 1V pk-pk  
Oscillation gives  
0.5VDC output



At 1KHz, the detector  
output is zero. So, drive  
your circuit at 1KHz and  
then look with the  
oscillation sniffer –  
should be 0VDC reading  
on DVM.