

Use any rectifying diodes, can also fit TO220 package

For regulator you can use LM317, LM338, LT1083, LT1084, LT1085

