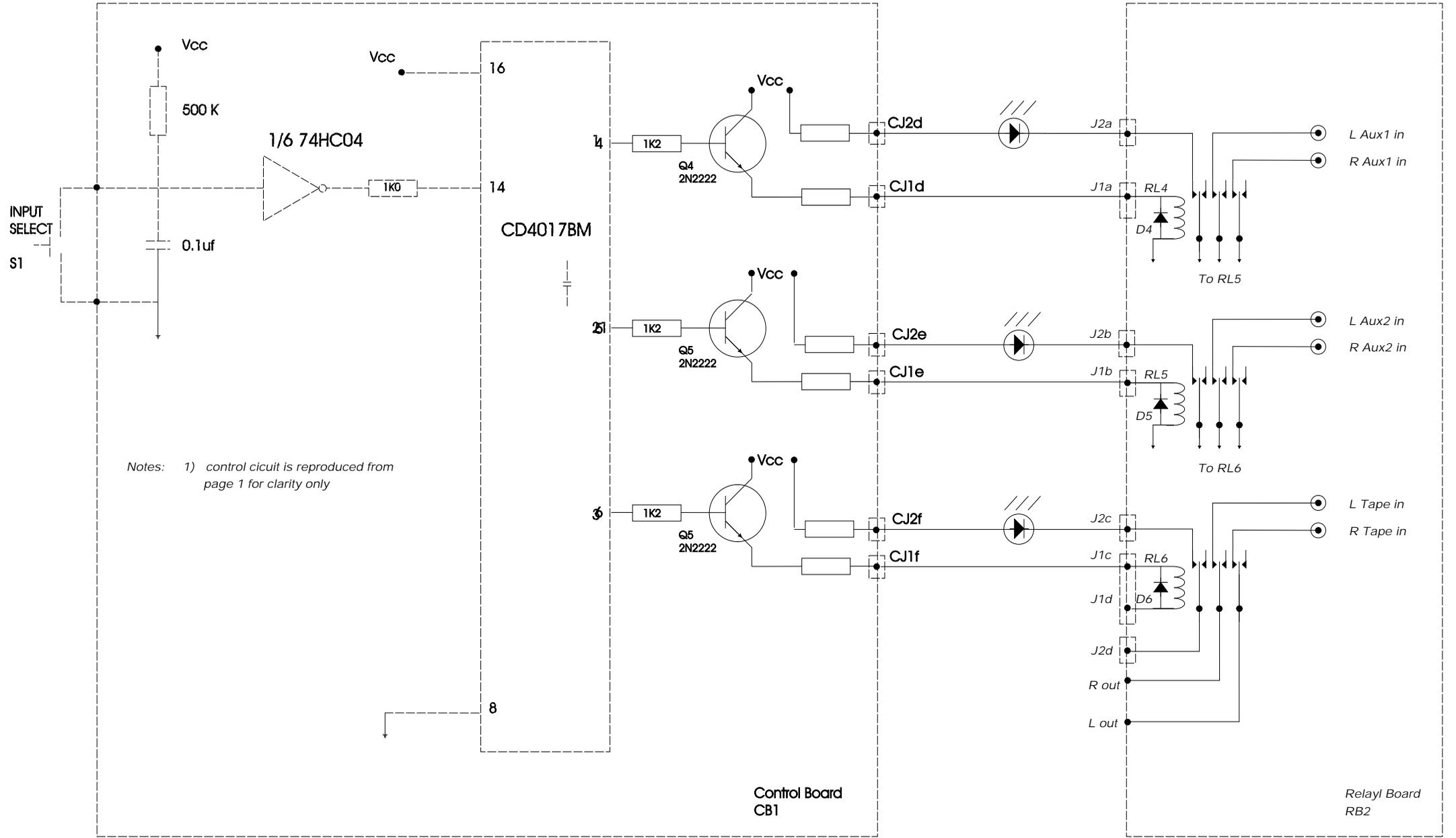



- Notes:
- 1) Vcc is 5-12 VDC
 - 2) R1-R8 is Aromat NF4EB-5V
 - 3) Select Rd1-8 to provide suitable LED current
 - 4) Select Rr1-8 to provide suitable relay coil voltage

Control Board
CB1

Relay Board
RB1



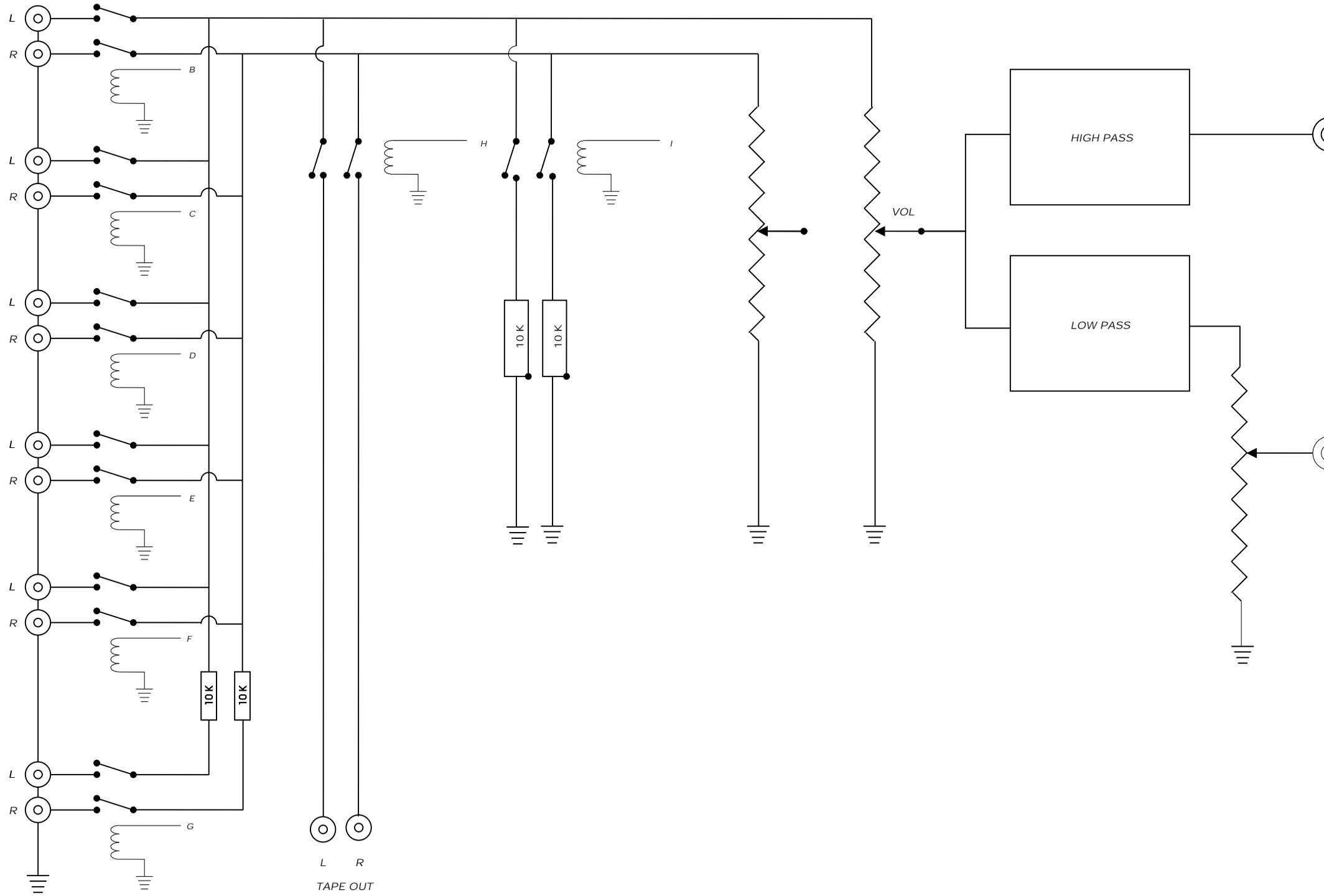PHONO IN
CD IN
TUNER IN
AUX1 IN
AUX2 IN
TAPE IN



L R
TAPE OUT