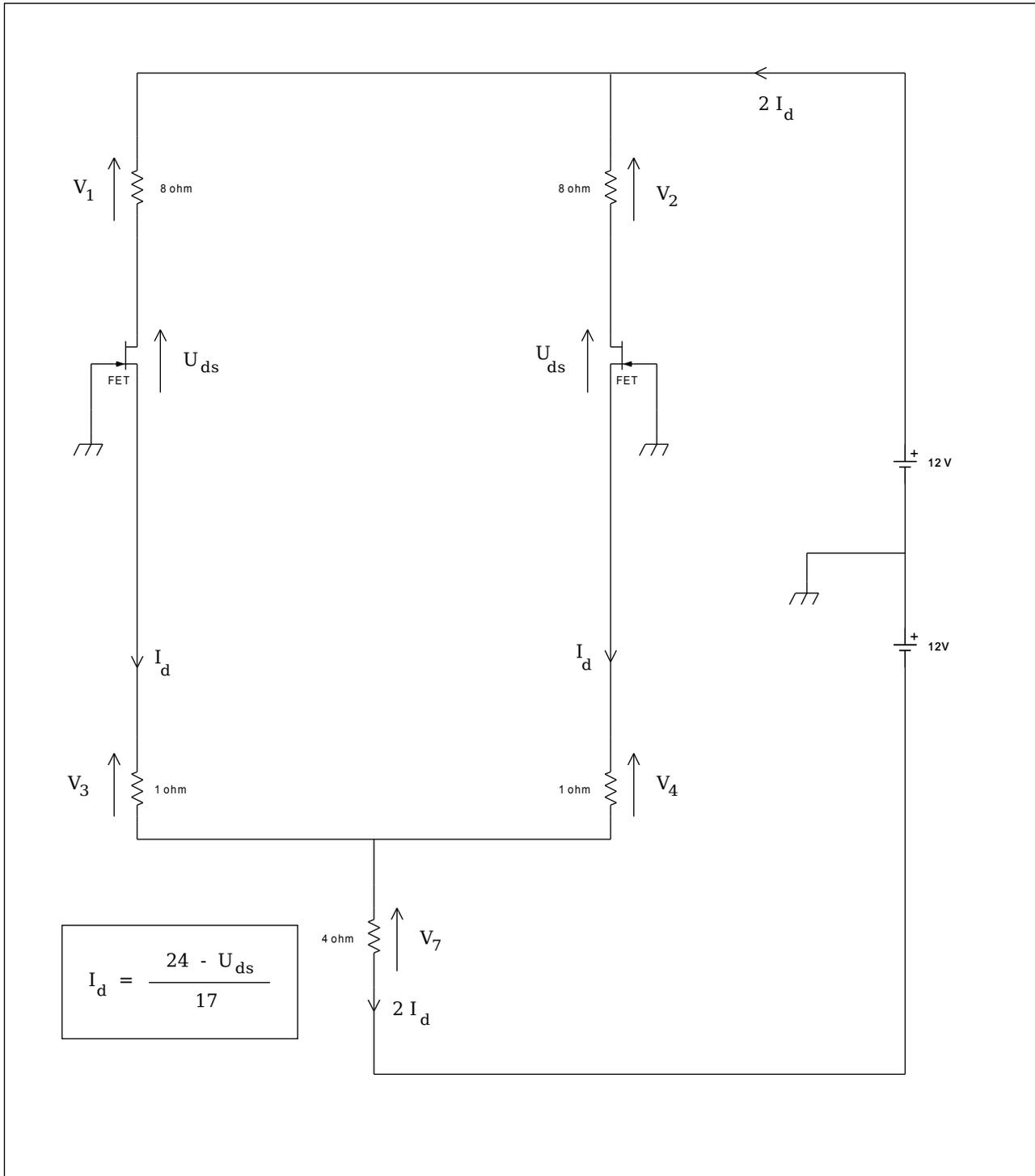




*The DC circuit*



For each branch the following applies:


$$(8 \times I_d) + U_{ds} + (1 \times I_d) + (4 \times 2 I_d) = 24$$

$$I_d = \frac{24 - U_{ds}}{17} \quad : \text{ the function of the DC load line for the fet}$$

When I switch on the circuit I measure a current flow of 0.902 A in each branch. This current is called the bias current(  $I_d = 0.902 \text{ A}$  ). From the equation above the bias current gives a voltage across the source and drain of  $24 - 17 ( 0.902 ) = 8.666 \text{ V}$ .

The point ( 8.666, 0.902 ) is also known as the operating point of the fet.

The AC circuit

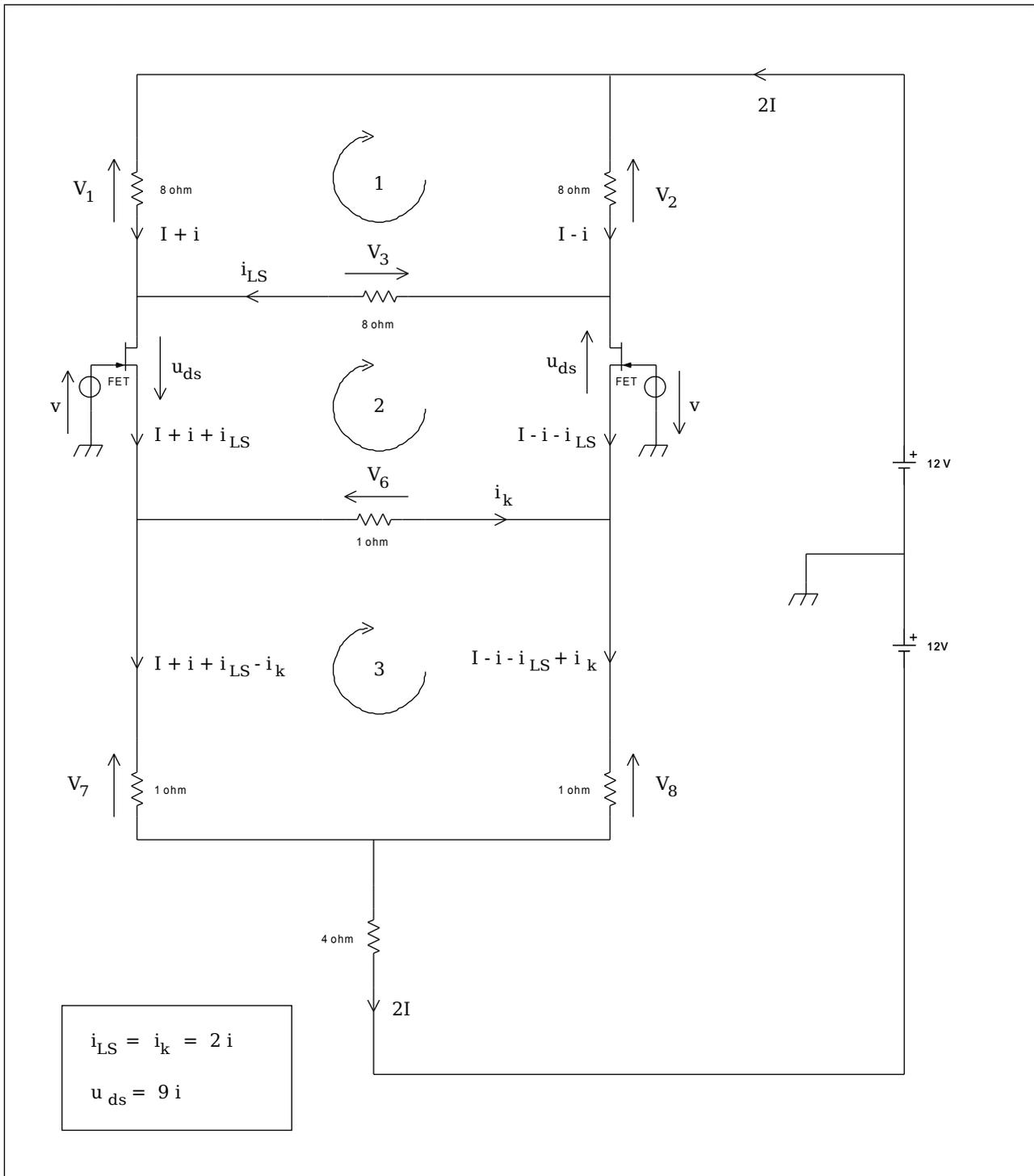

Applying Kirchoff's voltage law:

circuit 1:

$$V_1 - V_2 - V_3 = 0$$

$$8(I+i) - 8(I-i) - 8(i_{LS}) = 0$$

$$I+i - I+i - i_{LS} = 0$$

$$2i = i_{LS}$$

circuit 2:

$$-u_{ds} + V_3 - u_{ds} + V_6 = 0$$

$$-2u_{ds} + 8i_{LS} + i_k = 0$$

$$2u_{ds} = 8i_{LS} + i_k$$

circuit 3:

$$V_7 - V_6 - V_8 = 0$$

$$(I+i+i_{LS}-i_k) - (i_k) - (I-i-i_{LS}+i_k) = 0$$

$$2i + 2i_{LS} - 3i_k = 0$$

$$3i_k = 2i + 2i_{LS}$$

from circuit 1 and circuit 3:

$$3i_k = 2i + 2i_{LS} \quad \text{and} \quad 2i = i_{LS} \quad \text{give:} \quad i_k = i_{LS}$$

from circuit 2 and circuit 1:

$$2u_{ds} = 8i_{LS} + i_k \quad \text{and} \quad 2i = i_{LS} \quad \text{and} \quad i_k = i_{LS} \quad \text{give:} \quad u_{ds} = 9i$$

$$2i = i_{LS}$$

The current through an 8 ohm resistor is half of what flows through the loudspeaker.

$$i_k = i_{LS}$$

The current through the horizontal 1 ohm resistor also flows through the loudspeaker.

$$u_{ds} = 9i$$

By definition  $u_{ds}$  points upward when  $i_d$  comes down the drain.

Here the drain current  $i_d = 3i$ , and gives an impedance of  $u_{ds}/i_d = -3 \text{ ohm}$

$$i_d = -\frac{1}{3}u_{ds} \quad : \text{ the function of the AC load line for the fet.}$$