

## maneuvering room mic e

It is centered on the audio notebook homebrew

### Selected discrete components amplifier OP

For downsizing, this discrete amplifier OP wants to use the composite element anyway.

With a little research, the following two types of candidate dual N-ch J-FET of the first stage.

2SK2145 (SC-74A package = SC-59 5-pin)

2SK3320 (SC-88A package = SC-70 5-pin)

Toshiba is both. However, because the only available 2SK2145, you do not need to be selected.

But because there is only dual JFET of Toshiba N-ch, 2-stage differential amplifier is going to use a dual PNP transistor.

If there are several candidates for dual PNP transistor.

Candidate for SC-74A packages:

(Toshiba) 2SA1618

uPA501T (now Renesas NEC /)

Candidate for SC-88A packages:

(Toshiba) 2SA1873

RT2A00M / RT2A00AM1 (e Isahaya)

uPA571T (now Renesas NEC /)

For dual PNP differential amplifier and said, you do not come up with only 2SA798/2SA979 Mitsubishi, The final electronic chose RT2A00M Isahaya which inherited the business of Mitsubishi small signal transistor.

I think because it is very close to the specs of RT2A00M and Mitsubishi 2SA999, sound quality similar trend can be expected.



Subject: [Audio](#)

Genre: [Hobbies & Practical](#)


2011-06-02 (01:58): [OP amplifier](#) : 0 comments : 0 Trackbacks

[Top of page](#)
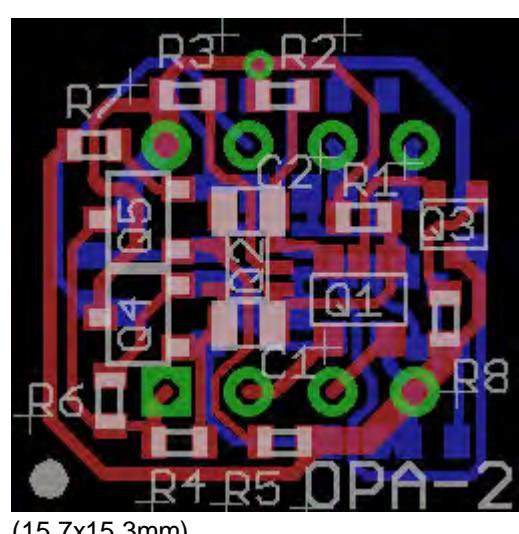
### Discrete OP amplifier (dual version)

The layout of the OP amp circuit containing two was completed safely.

So that it can be mounted on a wider range of equipment, this size was smaller than the previous single version.



Subject: [Audio](#)

Genre: [Hobbies & Practical](#)

2011-05-28 (01:52): [OP amplifier](#) : Comments 2 : 0 Trackbacks

[Top of page](#)

### Profile

Author: mic

### Recent Posts

[Ready to distribute Discrete Op-Amp Kit \(08/19\)](#)

[Discrete Op-Amp Kit in preparation distribution \(08/10\)](#)

[I purchased the Agilent U1733C LCR meter \(03/18\)](#)

[I'll try formed a discrete DAC \(1\) \(03/09\)](#)

[Discrete R-2R DAC \(02/03\)](#)

### Latest comments

[4ck: complete discrete amplifier OP \(04/20\)](#)

[bitstream: Discrete R-2R DAC \(02/09\)](#)

[mic: Discrete R-2R DAC \(02/08\)](#)

[bitstream: Discrete R-2R DAC \(02/05\)](#)

[mic: complete discrete amplifier OP \(02/02\)](#)

[kephis: complete discrete amplifier OP \(01/14\)](#)

[mic: complete discrete amplifier OP \(11/07\)](#)

### Latest trackbacks

### Monthly Archives

[2012/08 \(2\)](#)

[2012/03 \(2\)](#)

[2012/02 \(1\)](#)

[2011/12 \(1\)](#)

[2011/11 \(2\)](#)

[2011/09 \(3\)](#)

[2011/07 \(3\)](#)

[2011/06 \(7\)](#)

[2011/05 \(3\)](#)

[2011/04 \(4\)](#)

[2011/02 \(1\)](#)

[2011/01 \(1\)](#)

### Category

[OP Amp \(9\)](#)

[Power amplifier \(3\)](#)

[Parts \(5\)](#)

[\(6\) Power](#)


[Miscellaneous notes \(4\)](#)

[DAC \(2\)](#)


[Distribution board \(1\)](#)
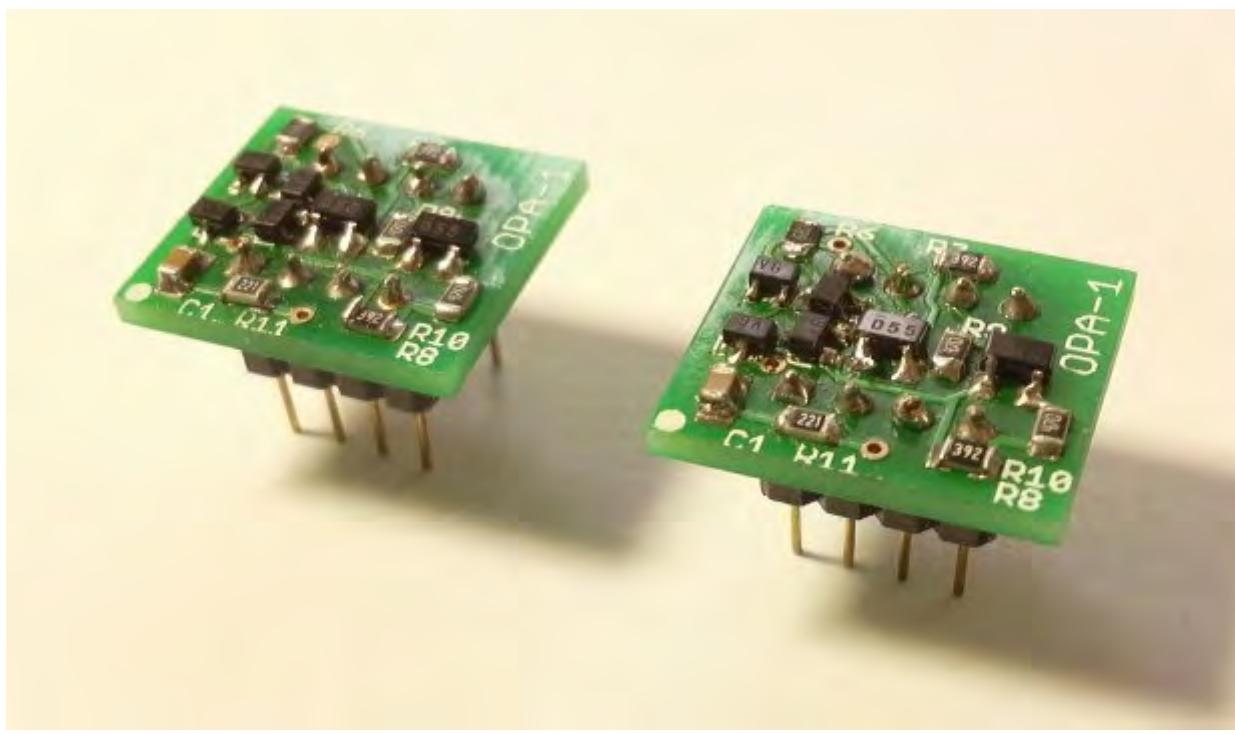
### I tried to DIP-8 amplifier Kaneda formula (completed)

Kaneda formula so tiny amplifier finished safely, we compared hear immediately attached to the DAC. A still sound better than IC, discriminator circuit is quite happy for the result. I made one because OP amp circuit pack is not used very often, but this time the circuit containing two of good luck.



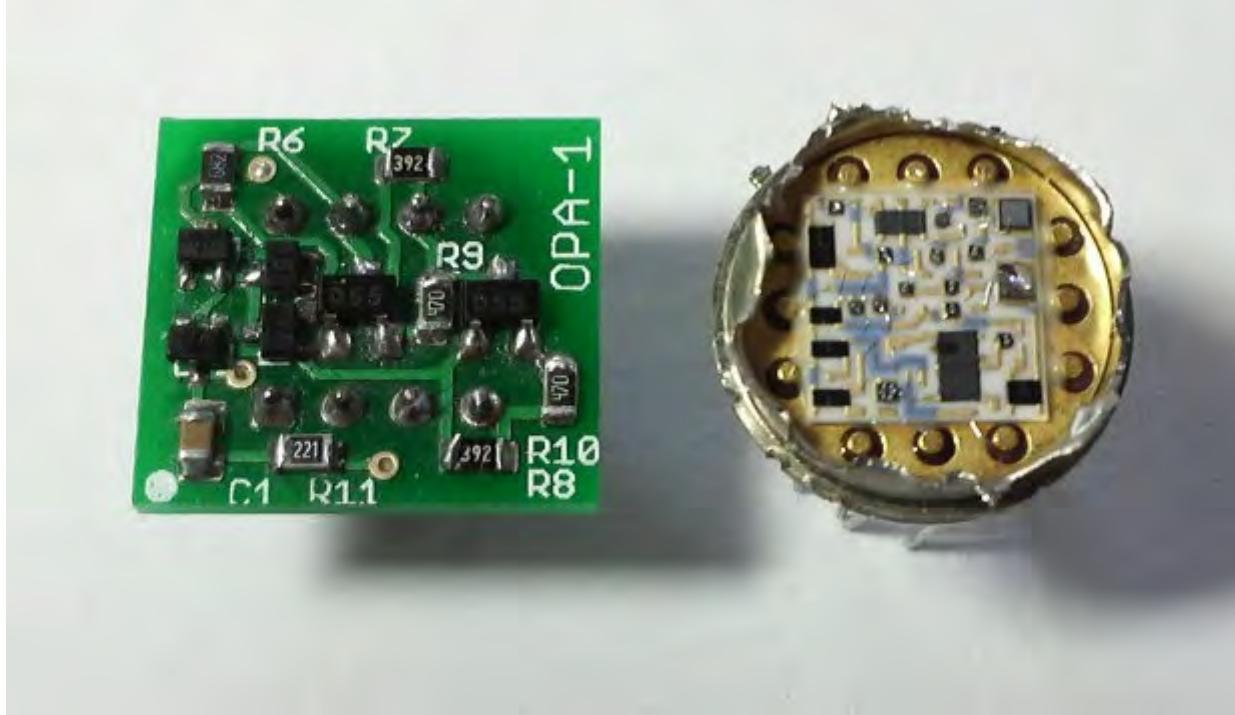Comparison between the hybrid LH0032: bonus. I can not compare with the LH0032 precision of course.



Subject: [Audio](#)

Genre: [Hobbies & Practical](#)

2011-04-23 (11:41): [OP amplifier](#) : 0 comments : 0 Trackbacks

[Top of page](#)

### [I tried to DIP-8 expression amp Kaneda](#)

### Search form

### Display RSS link.

[RSS of recent journals](#)

[RSS of the latest comments](#)

[RSS of the latest trackbacks](#)

### Link

[Management screen](#)

[Add the link to this blog](#)

### Powered By FC2 Blog




### Friend request form

[Want to be friends with this person](#)

### QR Code




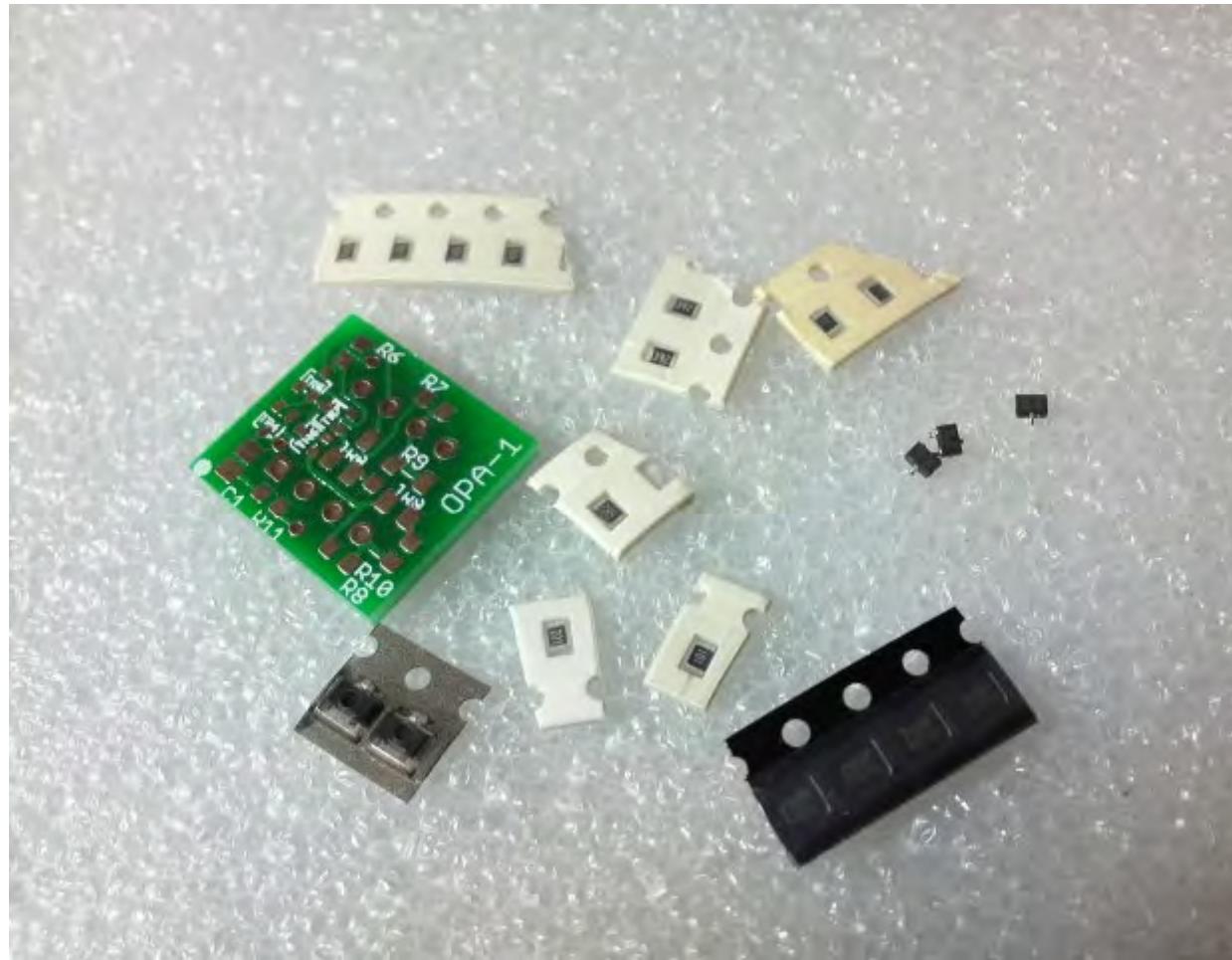

In order to compare under the same conditions as other amplifier OP, I teamed up on a substrate in an ultra-small amplifier Kaneda expression.

Conforms to the flat amplifier circuit of nearly No.198, 17.2x15.6mm slightly, all surface-mount components, board size element is used in the pseudo Will not say anymore Kaneda formula.

Actual circuit diagram is shown below.

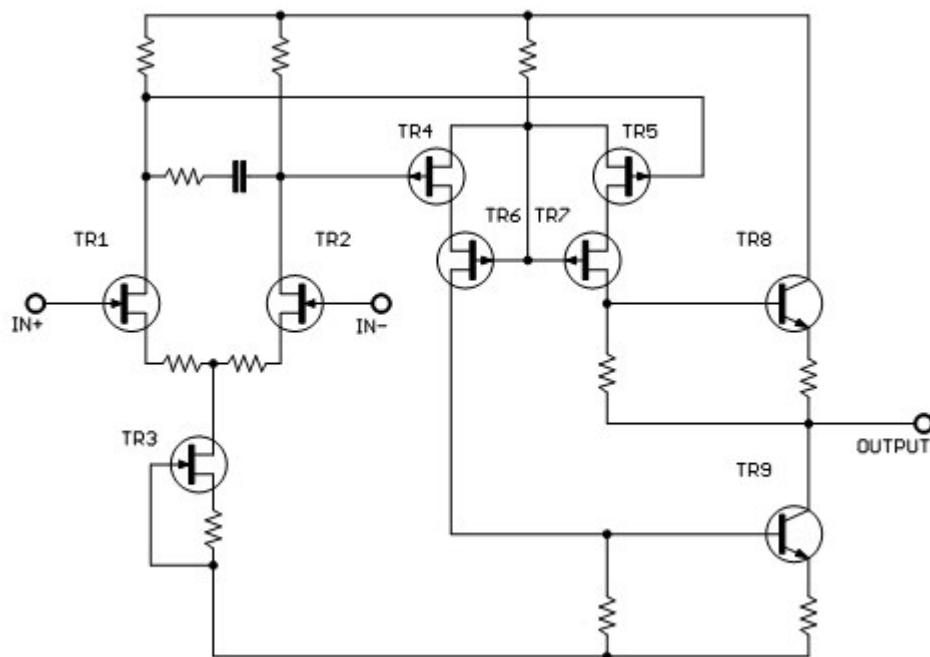


Tr1-3: 2SK880, Tr4-7: 2SJ144, Tr8-9: 2SD780A

At first glance is the same as No.198, is actually a N-Type.

2SC959 and 2SA606 because it is absolutely impossible into SMD at all, I was selected to be the most similar standard in the SC-59 package.

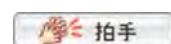So 200mW,  $P_c$  element of the final stage collector current is set to about 5mA. There is a possibility that the final stage elements and broken it more current.



Subject: [Audio](#)

Genre: [Hobbies & Practical](#)

2011-04-02 (13:14): [OP amplifier](#) : 0 comments : 0 Trackbacks

[Top of page](#)

[«Previous Page](#) [Home](#)

[Top of page](#)