

## A75 Mods


In the PC artwork of the original A75 boards in Audio Amateur, there are three resistors mis-labeled. The schematic is correct.

R22 on the PCB is R24 on the schematic

R26 on the PCB is R81 on the schematic

R24 on the PCB is R26 on the schematic

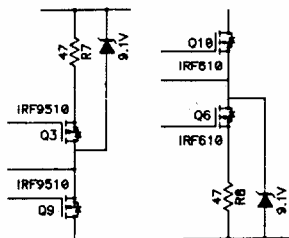In addition to this, it is worth noting that a modification was made to improve the reliability of the front end when the amp is overdriven. Two Zener diodes are added as seen in the diagram:



ZENER DIODES  
ADDED