

## Flyback Transformer Calculations

This is the Flyback Calculator work sheet. It is for the analysis of a Flyback Design operating Qr Mode Items in yellow are values that need/can be changed

V1.0 Initial Releas  
V1.1 Updated Wire selection

Input Data

Key Output Data

Authors:  
A. Brinlee

### Electrical Parameters

Vacmin:= 90 V	VrmsMinimum AC Input Voltage
Vacmax:= 264 V	Vrms Maximum AC Input Voltage
FacMainsMir:= 47 Hz	Minimum AC Mains Frequency
Vbrfd:= 0.9 V	Bridge Rectifier forward voltage drop
Vpkmin:= Vacmin: $\sqrt{2}$ = 127.2792 V	Peak Rectified voltage at the Vac min point
Vpkmax:= Vacmax: $\sqrt{2}$ = 373.3524 V	Peak Rectified voltage at the Vac max point
Vo1:= 12 V	Output Voltage
Io1:= 1.75 A	Output Current
Vfd1:= 0.45 V	Forward Voltage drop of the output rectifier
Vo2:= 14 V	Output Voltage
Io2:= 0.1 A	Output Current
Vfd2:= 0.9 V	Forward Voltage drop of the output rectifier
Cbulk:= 68 $\mu$ F	Nominal input bulk capacitance
TolCbulk:= 20 %	Bulk Cap Tolerance
thold:= 4 ms	Minimum Holdup requirements
tan $\delta$ := 0.24	Tan Delta of the Bulk Capacitor
Vbrownout:= 68 V	Bulk Cap DC Voltage the brownout protection circuit trips in
$\eta$ := 88 %	Expected PSU efficiency
Dmax:= 0.45	Maximum Dudty Cycle
Vacnom:= 115 V	Nominal AC Line voltage to consider the holdup time with
Fsw:= 45 kHz	Switching Frequency
LeakagePercent:= 1.2 %	Target ratio of Leakage Inductance to Primary Inductance

$$K_{\text{coupling}} = \sqrt{1 - \text{LeakagePercent}} \quad \text{Transformer Coupling Factor}$$

$$K_{\text{coupling}} = 0.994$$

$$P_o = V_{o1} \cdot I_{o1} + V_{o2} \cdot I_{o2} = 22.4 \text{ W} \quad \text{Output Power}$$

$$P_{\text{in}} = \frac{P_o}{\eta} = 25.4545 \text{ W} \quad \text{Estimated Input Power}$$

### Core Parameters PQ26/20 A-Core JPP-44

$$A_c = 119 \text{ mm}^2 \quad \text{Core cross sectional winding area}$$

$$MPL = 46.3 \text{ mm} \quad \text{Magnetic Path Length from core data sheet}$$

$$MLT = 56.55 \text{ mm} \quad \text{Mean Length per Turn from bobbin data sheet}$$

$$V_{\text{olfe}} = 5509.7 \text{ mm}^3 \quad \text{Core Fe Volume}$$

$$\text{CoreWid} = 19 \text{ mm} \quad \text{Core Width}$$

$$\text{CoreLen} = 26.5 \text{ mm} \quad \text{Core Length}$$

$$\text{CoreHt} = 20.15 \text{ mm} \quad \text{Core Height}$$

$$\text{WindowWidth} = 11.5 \text{ mm} \quad \text{Winding Window Width}$$

$$\text{WindowHt} = 5.25 \text{ mm} \quad \text{Window Winding Height (B-jC)/2}$$

$$\mu = 2400 \quad \text{Core Permeability}$$

$$W_a = \text{WindowWidth} \cdot \text{WindowHt}$$

$$W_a = 0.6038 \text{ cm}^2$$

$$\text{BobbinWidth} = \text{WindowWidth} - 2.2 \text{ mm} \quad \text{Use this equation or enter from bobbin mfg data sheet.}$$

$$\text{BobbinWidth} = 0.93 \text{ cm} \quad \text{Use 2.2mm when using tripple insulated wire and 8.2mm}$$

$$\text{BobbinWidth} = 8.03 \text{ mm} \quad \text{Measured when using margin tape.}$$

$$A_p = W_a \cdot A_c \quad \text{Power Handling ability of the core}$$

$$A_p = 0.7185 \text{ cm}^4$$

$$A_t = 2 \cdot \text{CoreLen} \cdot \text{CoreWid} + 2 \cdot \text{CoreLen} \cdot \text{CoreHt} + 2 \cdot \text{CoreWid} \cdot \text{CoreHt}$$

$$A_t = 28.4065 \text{ cm}^2 \quad \text{Surface Area for heat dissipation}$$

For EE/ER style transformers use the above but substitute for Core Height the following:  $\text{CoreHt} + 2 \cdot \text{WindowHt}$

### Constants

$$K_i = 0.0388 \quad \text{Gap Loss Coefficient}$$

$$K_u = 0.32 \quad \text{Window utilization factor use 40\% for most cases}$$

$$K_f = 4 \quad \text{Waveform coefficient use 4 for a square wave or 4.4 for a sinewave}$$

**Bulk Capacitor Calculations**

$$C_{bulkmin} = \frac{2 \cdot P_{in} \cdot t_{hold}}{(V_{pkmin} - 2 \cdot V_{brfd})^2 - (90 \text{ V})^2} = 26.6364 \mu F$$

Choose CBulk &gt; than this value

90V is the expected min  
Bulk Cap Voltage-Will be calculated  
Later

$$D_{LC} := 0.2 \quad \text{Bulk Cap conduction Dutycycle}$$

$$C_{esr} := \frac{\tan \delta}{2 \cdot \pi \cdot 2 \cdot \text{FacMainsMin} \cdot C_{bulk} \cdot (1 - \text{Tol}C_{bulk})}$$

$$C_{esr} = 7.4697 \Omega$$

$$V_{BulkMin} = \sqrt{2 \cdot V_{acmin}^2 - \frac{P_{in} \cdot (1 - D_{LC})}{C_{bulk} \cdot \text{FacMainsMin}}} = 99.1383 \text{ V}$$

$$V_{BulkMin} = 90 \text{ V} \quad \text{Choose } V_{BulkMin} < \text{ that Voltage Above}$$

$$V_{acNomPk} = V_{acnom} \cdot \sqrt{2} - 2 \cdot V_{brfd} = 160.8346 \text{ V}$$

$$V_{ref1} = \frac{D_{max} \cdot V_{BulkMin}}{(1 - D_{max})} = 73.6364 \text{ V} \quad \text{Reflected voltage on the primary}$$

$$V_{BulkPk} = V_{pkmax} - 2 \cdot V_{brfd} = 371.5524 \text{ V} \quad \text{Peak Voltage on the Bulk cap}$$

$$V_{dsref} = V_{BulkPk} + V_{ref1} = 445.1887 \text{ V} \quad \text{Peak Plateau voltage seen by the FET}$$

Does not include the leakage inductance spike

**Transformer Design**

$$\Delta \beta_m = 2700 \text{ G} \quad \text{Peak Flux Density in Tesla}$$

$$n := \frac{V_{ref1}}{V_{o1} + V_{fd1}} = 5.9146 \quad \text{Turns ratio}$$

$$V_{rr\_opd} := \frac{V_{BulkPk}}{n} + V_{o1} + V_{fd1} = 75.2699 \text{ V} \quad \text{Reverse Recovery on the output rectifier}$$

$$I_{pk} := \frac{P_{in}}{V_{BulkMin} \cdot D_{max}} \cdot 2 = 1.257 \text{ A} \quad \text{Peak Current during the switch On time}$$

$$L_p := \frac{V_{BulkMin} \cdot D_{max}}{I_{pk} \cdot F_{sw}} = 715.9821 \mu H \quad \text{Required Inductance}$$

$$I_{spk} := \frac{P_o}{V_{o1} \cdot (1 - D_{max})} = 3.3939 \text{ A} \quad \text{Secondary Side peak current}$$

$$N_p := \text{round} \left( \frac{I_{pk} \cdot L_p}{\Delta \beta_m \cdot A_c}, 0 \right) = 28 \quad \text{Adjust } D_I \text{ and } D_{bm} \text{ above to get a whole number}$$

$$N_{s1} := \text{round} \left( \frac{N_p}{n}, 0 \right) = 5 \quad \text{Number of Secondary turns}$$

$$l_g := 0.1569 \text{ mm} \quad \text{Adjust } l_g \text{ (Core Gap) until } L_{gapped} = L_p$$

$$FFlux := 1 + \frac{l_g}{\sqrt{A_c}} \cdot \ln \left( \frac{2 \cdot \text{WindowWidth}}{l_g} \right) = 1.0717 \quad \text{Fringing Flux Caused by gapping the core}$$

$$L_{gapped} := \frac{\left( 0.4 \frac{H}{m} \cdot \pi \cdot 10^{-6} \right) \cdot N_p^2 \cdot FFlux \cdot A_c}{l_g + \frac{MPL}{\mu}}$$

$$L_{gapped} = 713.1417 \mu H \quad \text{This needs to equal } L_p \quad L_p = 715.9821 \mu H$$

$$B_{max} := \frac{0.4 \frac{H}{m} \cdot \pi \cdot N_p \cdot FFlux \cdot (I_{pk}) \cdot 10^{-6}}{l_g + \frac{MPL}{\mu}} = 2690.3648 \text{ G} \quad \text{Double Check this against your input requirement}$$

$$\text{Energy} := \frac{L_p \cdot I_{pk}^2}{2}$$

Energy in W-S

$$\text{Energy} = 0.0006 \text{ J}$$

Available energy storage in the gap

$$\text{Energy} \cdot F_{sw} = 25.4545 \text{ W}$$

Max Power available at that frequency and inductance

$$A_{Le} := \frac{L_p}{N_p^2} = 0.9132 \text{ } \mu\text{H}$$

Effective ALe gapped uH/turn

$$H := \frac{0.4 \cdot \pi \cdot N_p \cdot I_{pk}}{MPL} = 12.0043 \text{ Oe}$$

Oersteds Check this against data sheet curves

$$P_g := K_i \frac{10^4 \text{ W}}{\left( \frac{m^2}{T^2} \right) \text{ Hz}} \cdot \text{WindowWidth} \cdot l_g \cdot F_{sw} \cdot \Delta \beta m^2$$

McLyman - Transformer and Inductor design Handbook

$$P_g = 2.2966 \text{ W}$$

$$N_{s2} := \text{round} \left( \frac{V_{o2} + V_{fd2}}{V_{o1} + V_{fd1}} \cdot N_{s1}, 0 \right) = 6$$

Number of Aux turns

$$V_{o2Actual} := \frac{N_{s2}}{N_{s1}} \cdot (V_{o1} + V_{fd1}) - V_{fd2} = 14.04 \text{ V}$$

### Skin Depth and Wire Selection

$$\rho = 1.7241 \cdot 10^{-6} \text{ } \Omega \text{ cm}$$

Nema M1000 pdf

$$\alpha = 0.0039$$

Temperature Compensation for Cu

$$\text{TempW} = 100$$

Degree C Operating Wire temperature

$$\text{Tambient} = 20$$

Ambient Wire Temperature the Cu constant was derived from

$$\rho_e := \rho \cdot (1 + \alpha \cdot (\text{TempW} - \text{Tambient}))$$

$$\rho_e = 2.262 \cdot 10^{-6} \text{ } \Omega \text{ cm}$$

Adjusted electrical Resistivity

$$K_{cu} := \sqrt{\frac{\rho_e}{\rho}}$$

$$\delta := \frac{6.62}{\sqrt{F_{sw}}} \cdot K_{cu} \cdot \sqrt{\text{Hz}} \text{ cm}$$

$$\delta = 0.0357 \text{ cm}$$

Skin Depth in cm

$$\text{MaxWireDia} = 2 \cdot \delta$$

$$\text{MaxWireDia} = 0.7149 \text{ mm}$$

Maximum wire Diameter that uses 100% of the Cu area at the fundamental switching frequency

## Primary Wire Selection

$W_p := 0.32 \text{ mm}$  Furikawa TEX-E 0.32mm or Rubadue 28AWG Tripple Insulated

$W_{priOD} := 0.54 \text{ mm}$  OD with Insulation

Target is Low Leakage and innerwinding C on the primary so use a Split winding for the primary and sandwith the secondary between them.

$Pri_{windingfit} := \frac{BobbinWidth}{W_{priOD}} = 14.8704$  this should be  $< N_p/2$  for a split winding

$I_{priRMS} := I_{pk} \cdot \sqrt{\frac{D_{max}}{3}} = 0.4868 \text{ A}$  Primary Side RMS current

$R_{pdc} := \frac{\rho_e \cdot MLT \cdot N_p}{\left(\frac{W_p}{2}\right)^2 \cdot \pi} = 0.4453 \Omega$  Power Dissipation at 100C

$P_{priwire} := I_{priRMS}^2 \cdot R_{pdc} = 0.1056 \text{ W}$

## Secondary Side Wire Selection

$W_s := 0.1 \text{ mm}$  Litz Wire

$Strands_{sec} := 100$  Uses 100x0.1mm Stranded Litz Wire

$W_{secaarea} := \left(\frac{W_s}{2}\right)^2 \cdot Strands_{sec} \cdot \pi = 0.7854 \text{ mm}^2$

$Litz_{od} := 0.125 \text{ mm}$

$Wire_{bundleod} := 2 \cdot \sqrt{\left(\frac{Litz_{od}}{2}\right)^2 \cdot Strands_{sec}} = 1.25 \text{ mm}$

$Sec_{windingfit} := \frac{BobbinWidth}{Wire_{bundleod}} = 6.424$  Must be  $<$  than  $N_s/1$

$I_{secpk} := \frac{I_o \cdot 1.2}{(1 - D_{max})} = 6.3636 \text{ A}$  Assumes QR mode and disregars time for the transformer winding dead time between cycles as the winding rings to the next state.

$I_{secRMS} := I_{secpk} \cdot \sqrt{\frac{(1 - D_{max})}{3}} = 2.7247 \text{ A}$  RMS Current through the coil

$R_{sdc} := \frac{\rho_e \cdot MLT \cdot N_s/1}{W_{secaarea}} = 0.0081 \Omega$

$P_{secwire} := I_{secRMS}^2 \cdot R_{sdc} = 0.0605 \text{ W}$

## Auxillary Winding Selection

$W_{ns2} := 0.25 \text{ mm}$  Auxillary Wire Se;ection TEX-E Furikawa

$W_{ns2maxOD} := 0.467 \text{ mm}$

$W_{vertfit} := W_{ns2maxOD} + Wire_{bundleod} + 2 \cdot W_{priOD} = 2.797 \text{ mm}$  Adjust  $W_{vertfit} <$  BobbinHeght