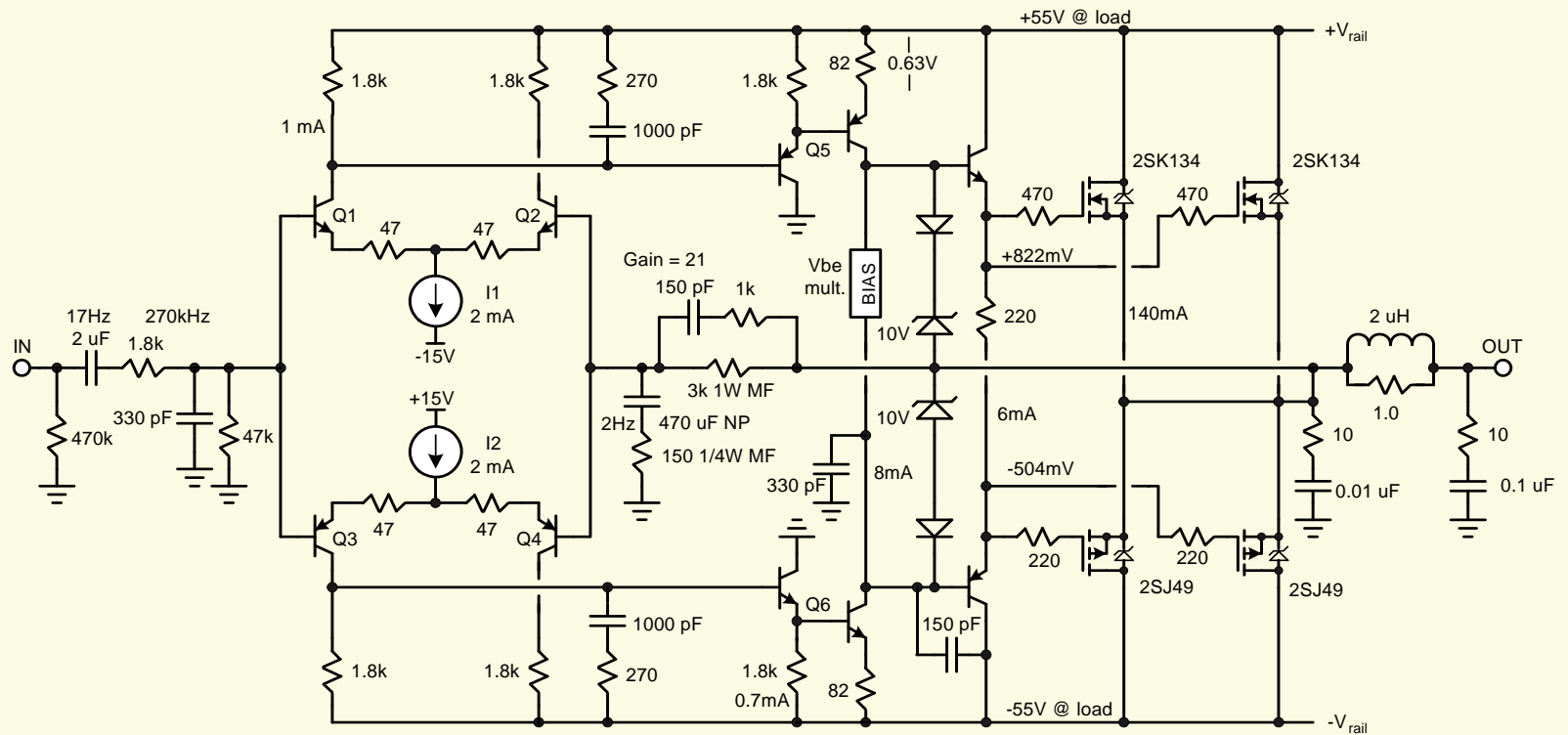


The DH-220C Audio Amplifier Design

- 📄 The Hafler DH-220
- 📄 N-channel JFET input stages
- 📄 DC servos and advantages
- 📄 Full complementary input stages and P-P VAS
- 📄 LSK489 and LSJ689 dual monolithic JFETs
- 📄 Bias spreader and gate protection
- 📄 Lateral MOSFET output stage & distortion
- 📄 DH-220C performance

Bob Cordell


Hafler DH220 (simplified)



Bob Cordell

Basic JFET Input Stage

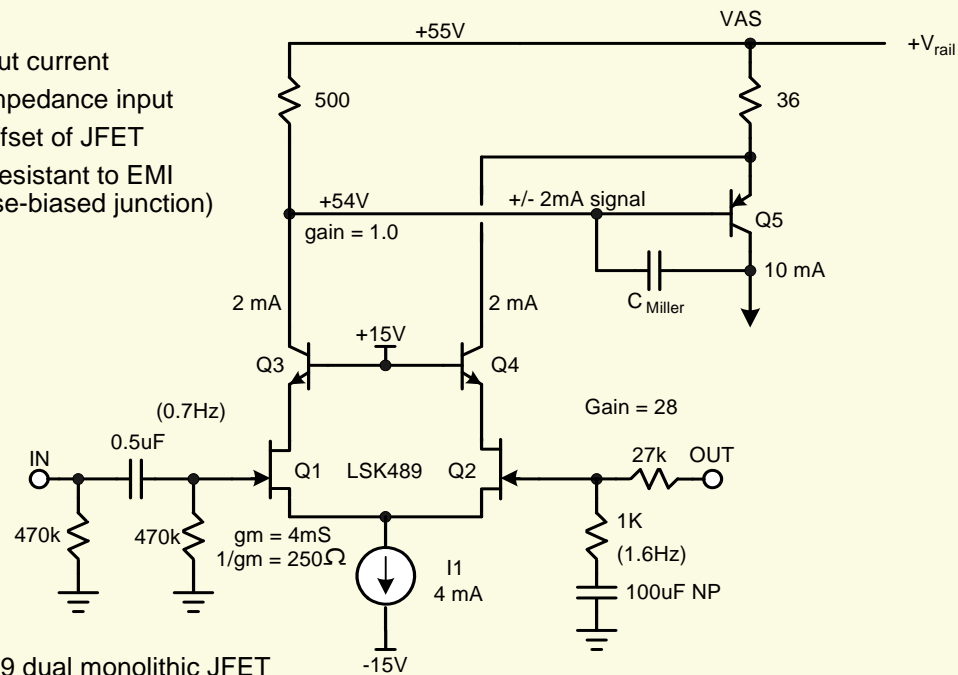- no input current
- high impedance input
- only offset of JFET
- more resistant to EMI (reverse-biased junction)




- LSK489 dual monolithic JFET
- low dc offset
- low noise
- low capacitances: $C_{iss} = 4\text{pF}$, $C_{rss} = 2\text{pF}$

Bob Cordell

JFET IPS with 2EF VAS

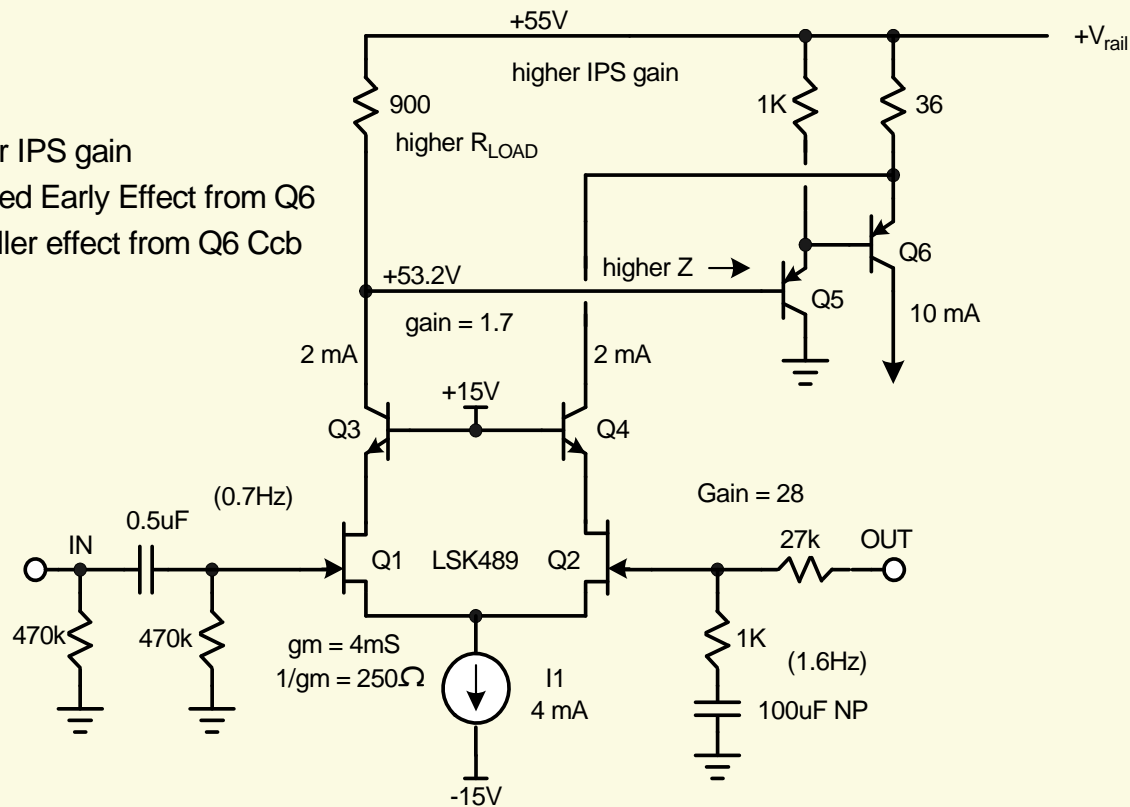
- higher IPS gain
- reduced Early Effect from Q6
- no Miller effect from Q6 Ccb



Bob Cordell

JFET IPS with Current Mirror

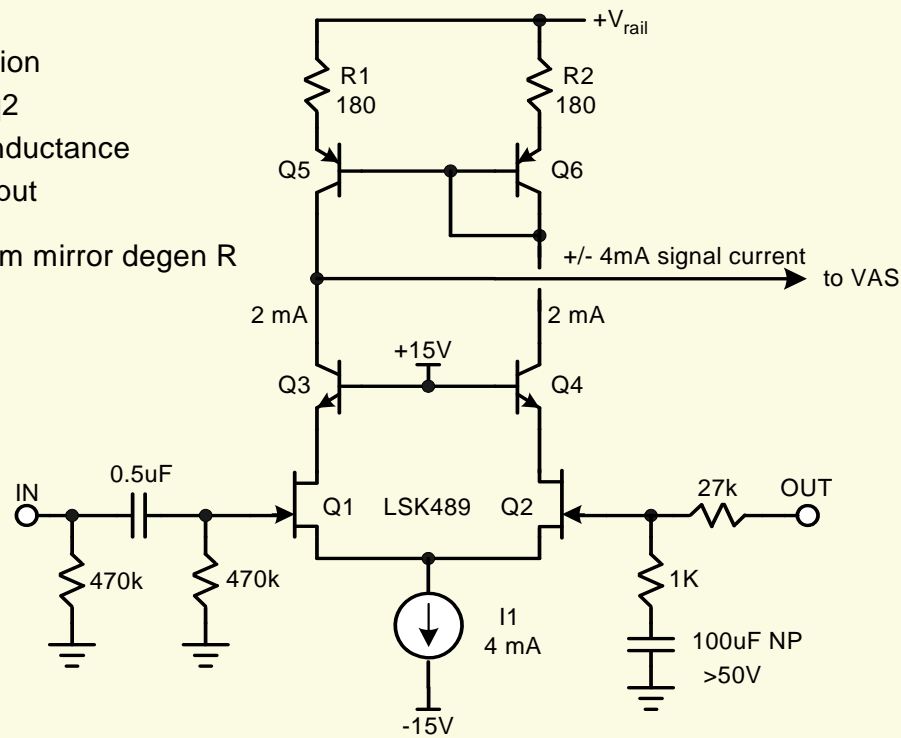
- very high Z IPS load
- common mode rejection
- I_{q1} forced to equal I_{q2}
- doubles IPS transconductance
- doubles max IPS output signal current
- potential for noise from mirror degen R



Bob Cordell


JFET IPS with LSK389

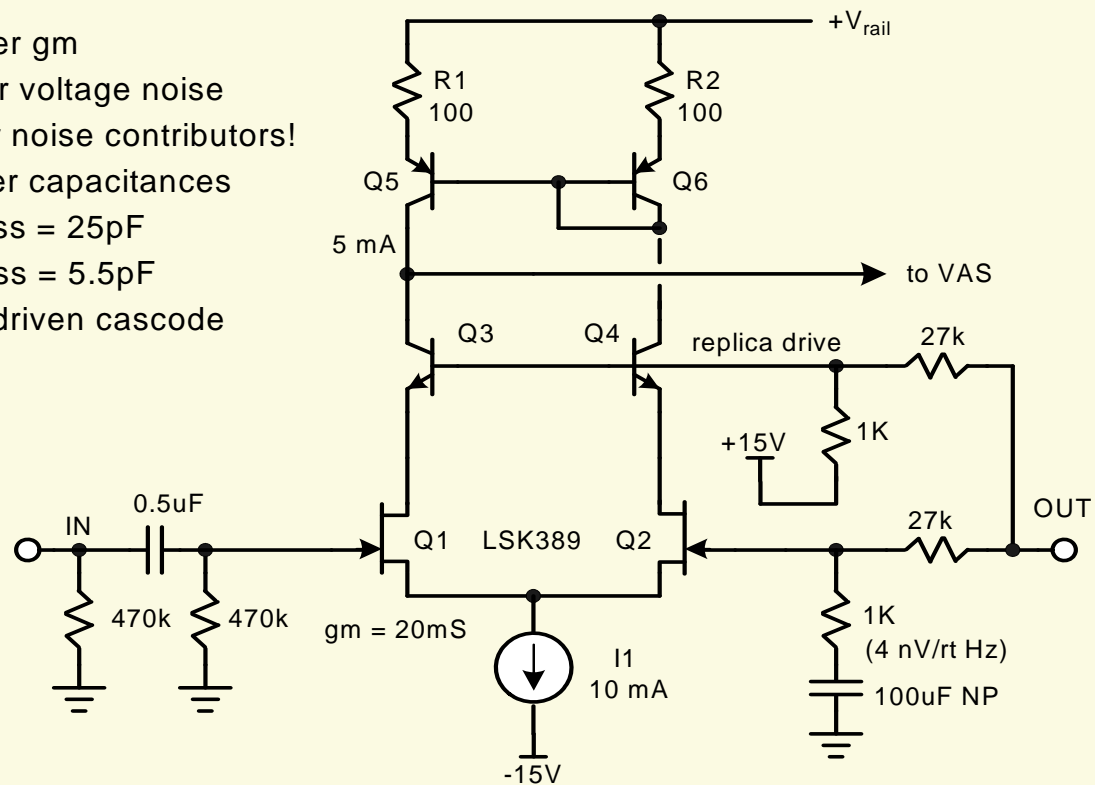- higher g_m
- lower voltage noise
- other noise contributors!
- higher capacitances
 - $C_{iss} = 25\text{pF}$
 - $C_{rss} = 5.5\text{pF}$
- use driven cascode



Bob Cordell


JFET IPS with Helped Current Mirror

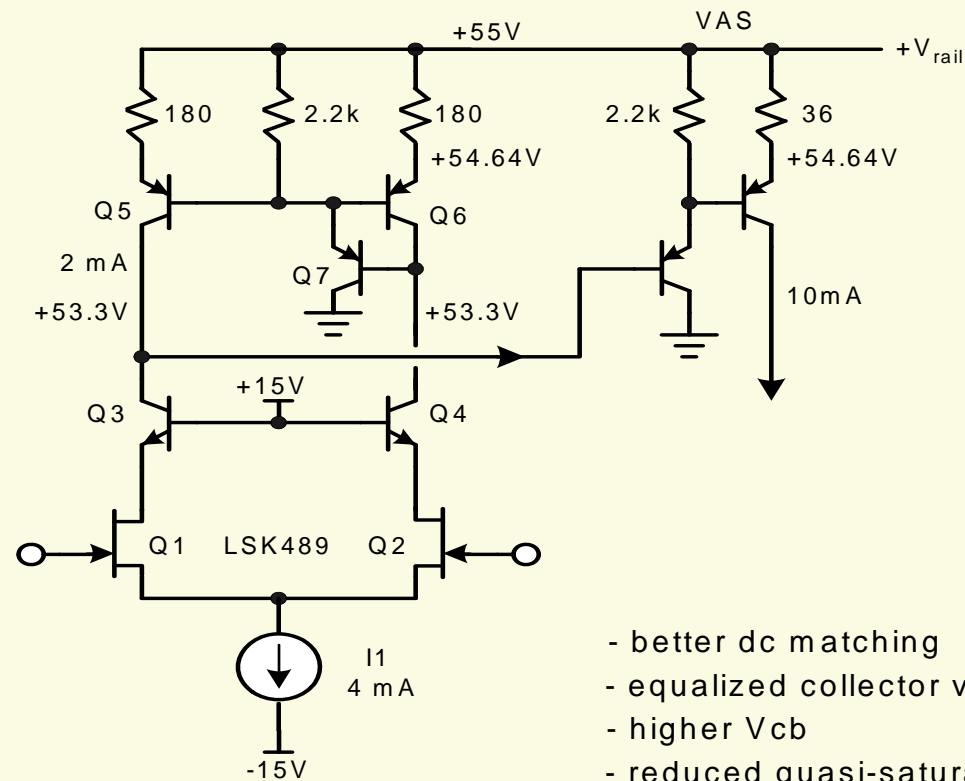

- better dc matching
- equalized collector voltages
- higher V_{cb}
- reduced quasi-saturation

Bob Cordell

JFET IPS with DC Servo

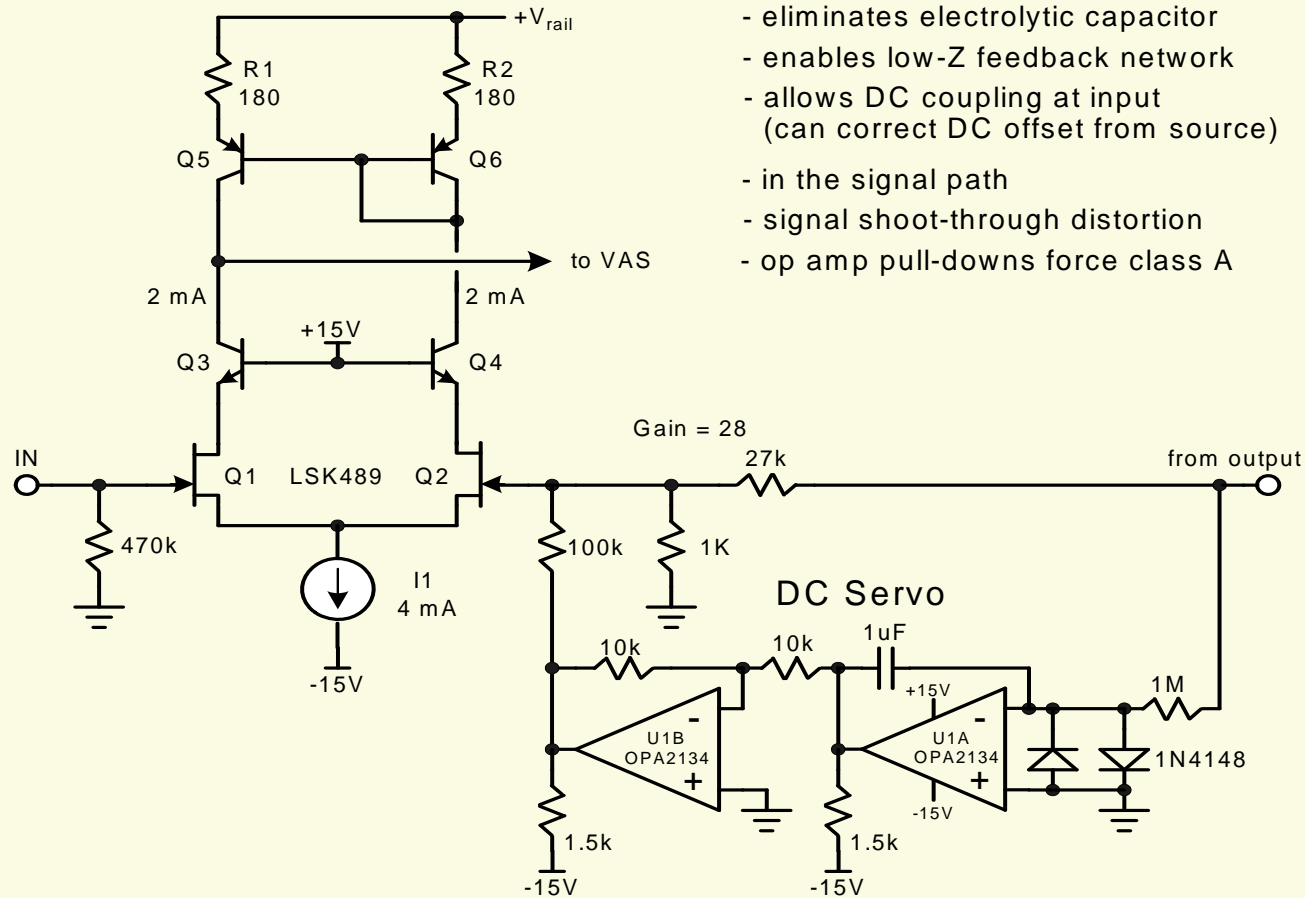


- eliminates electrolytic capacitor
- enables low-Z feedback network
- allows DC coupling at input (can correct DC offset from source)
- in the signal path
- signal shoot-through distortion
- op amp pull-downs force class A

Bob Cordell


JFET IPS Folded Cascode

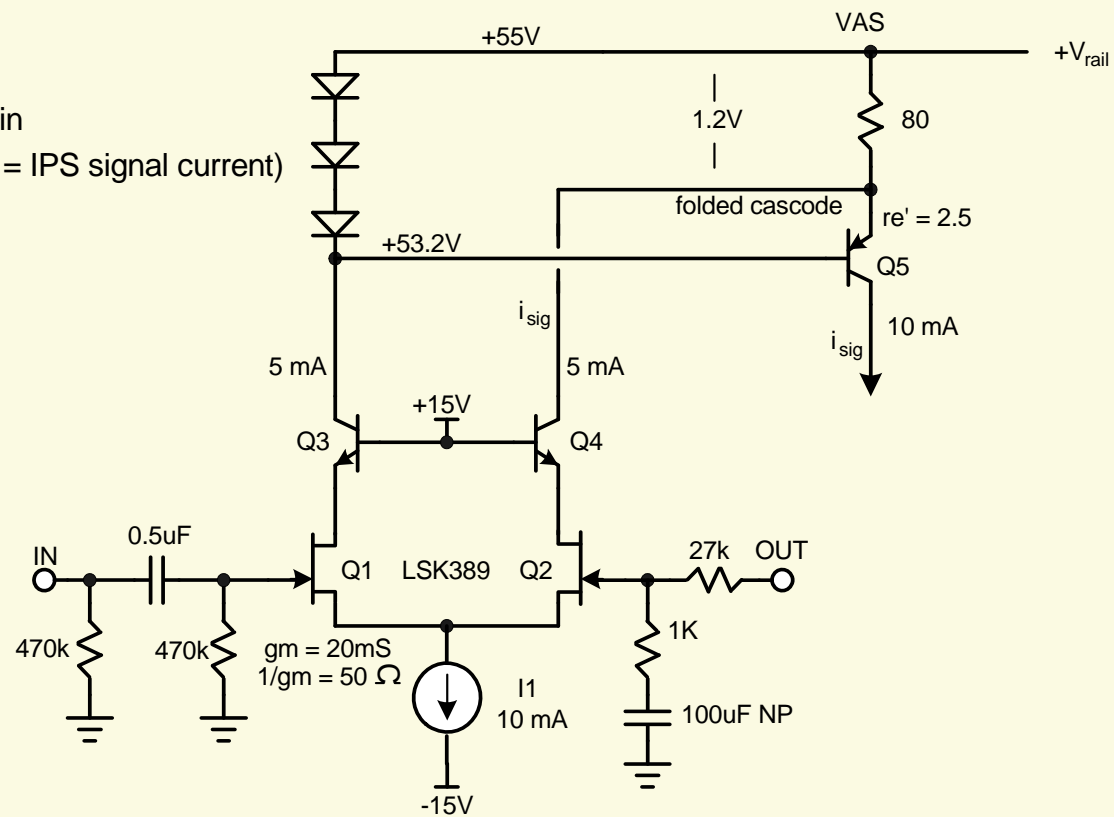- fast
- no signal current gain
(VAS signal current = IPS signal current)
- watch noise



Bob Cordell

JFET IPS Folded Cascode with Imirror

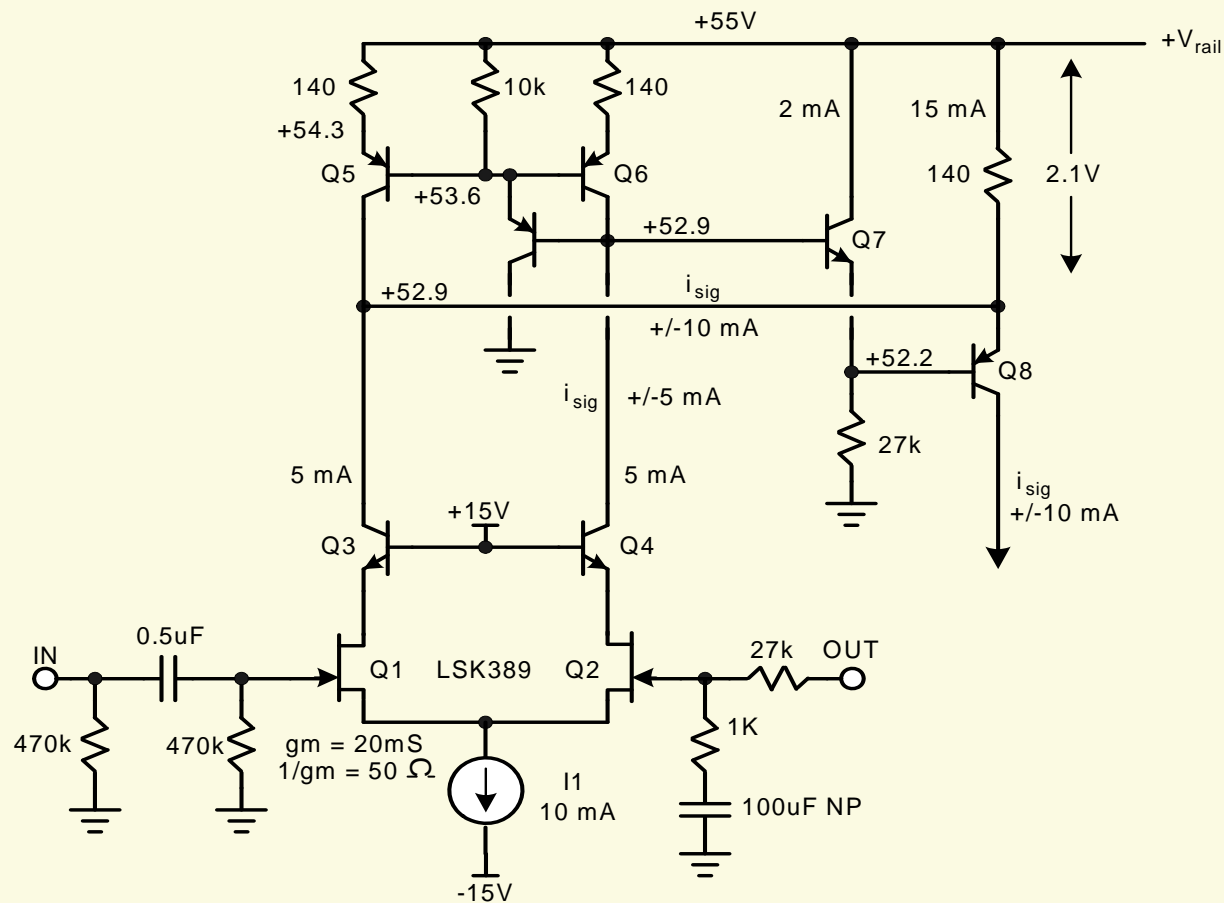


Bob Cordell

BJT Full Complementary IPS

- enables push-pull VAS
- twice signal current output
- 3dB lower noise
- some input bias current cancellation
- VAS bias current sensitive to IPS current (S = 2.6:1)
- matching within pairs important

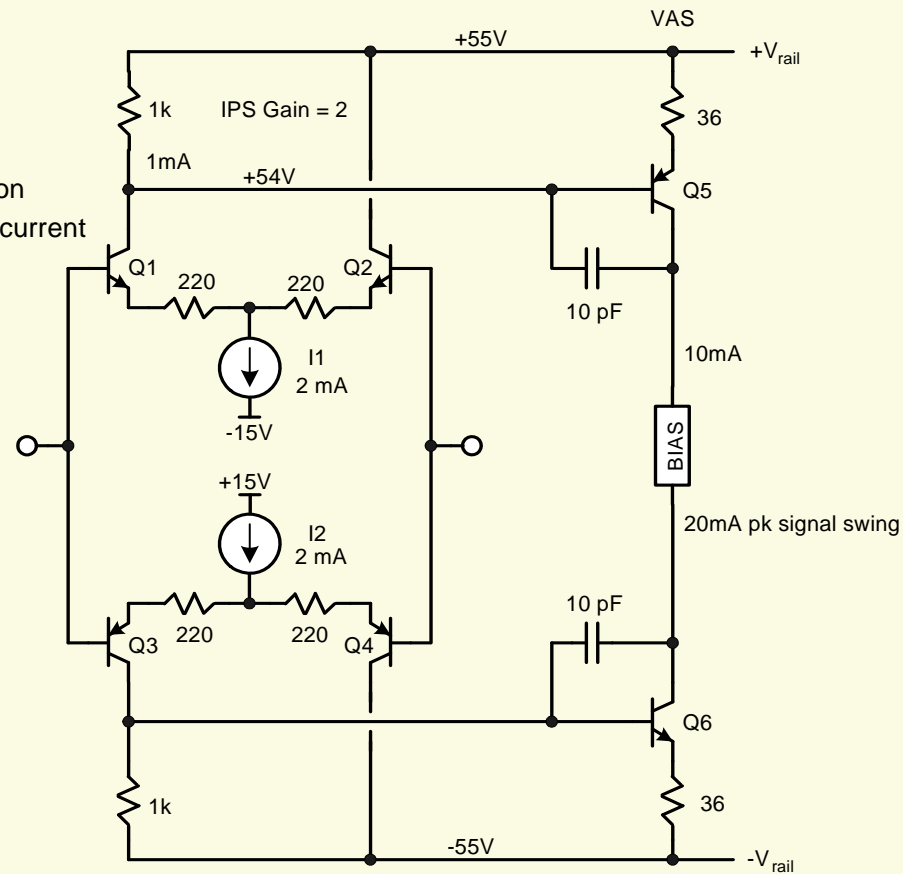
- Miller compensation
- ULGF = 1 MHz for CLG = 28
- ~100 V/us slew rate



Bob Cordell

BJT Full Complementary IPS with Mirrors

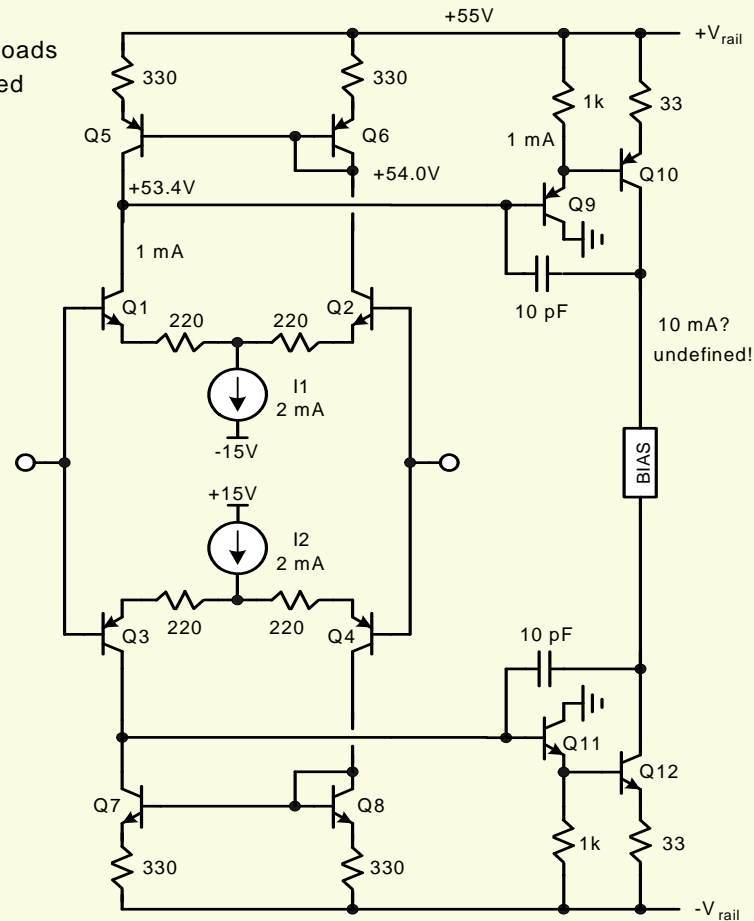
- benefits of current mirror loads
- BUT VAS current undefined



Bob Cordell

Complementary IPS with Loaded Mirrors

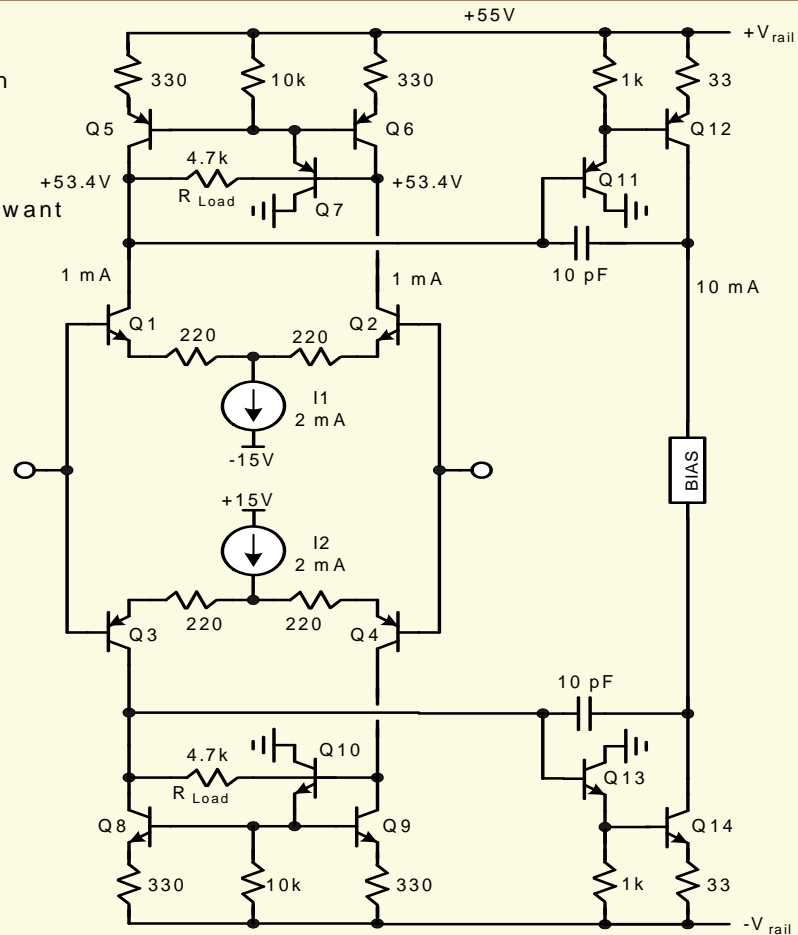
- 0V across R_{Load}
- stabilized and defined IPS DC gain
- defined VAS operating current
- reduced loop gain at VLF
- but plenty of OLG in VAS
- choose R_{Load} to be whatever you want
- IPS gain = 10 (good)



Bob Cordell

Complementary JFET IPS

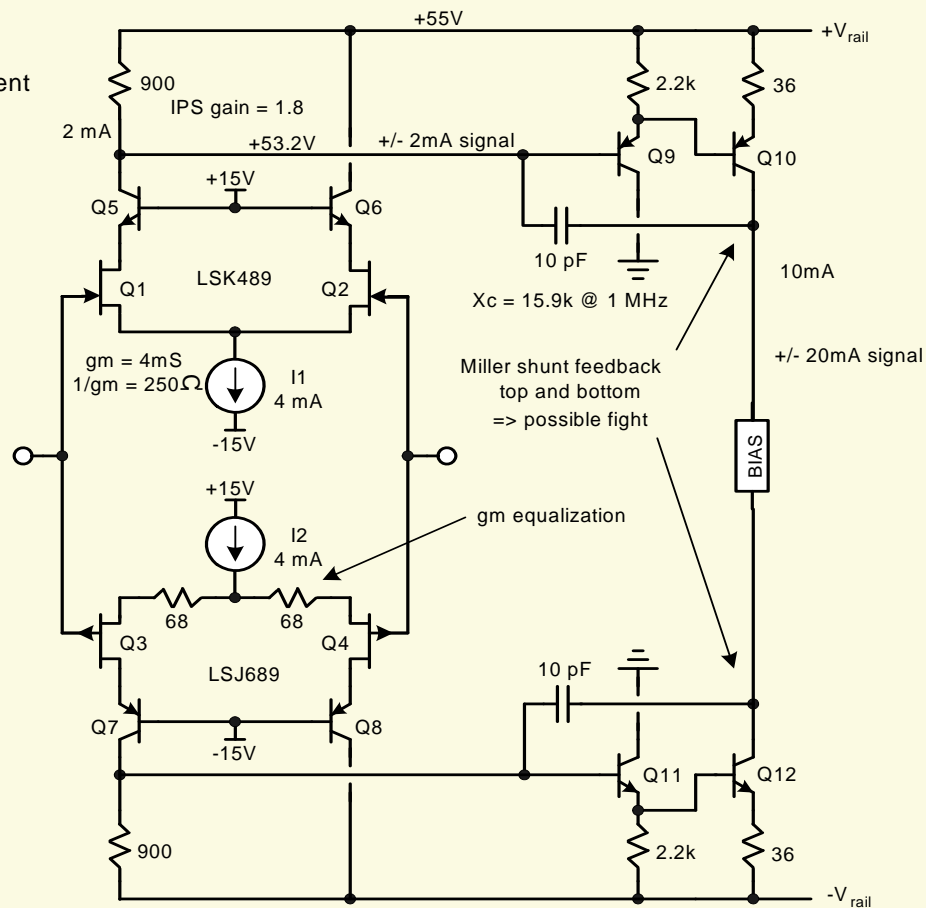
- gm equalization desirable
- DC offset in each pair affects VAS current
- use dual monolithic JFETs
- ULGF = 1 MHz @ CLG = 28
- slew rate = 2mA/10pF = 200V/us



Bob Cordell

JFET IPS with Current Mirrors

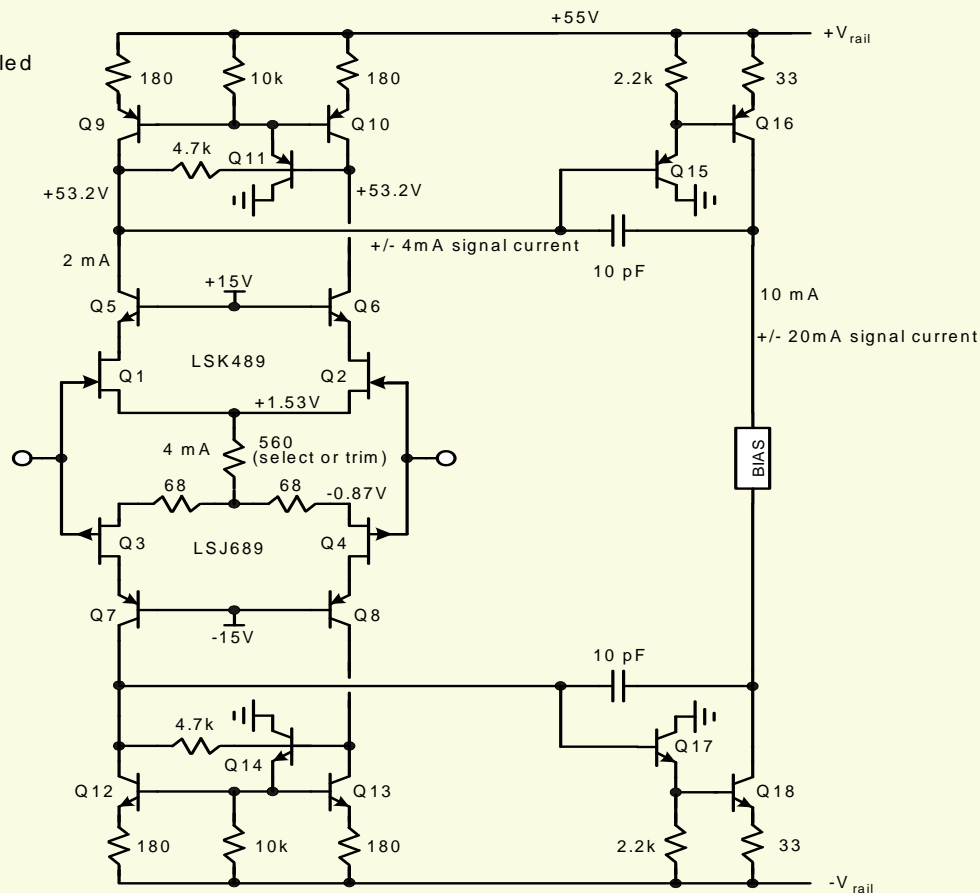
- IPS transconductance doubled
- loaded current mirror



Bob Cordell

Clamped Current Mirror and VAS

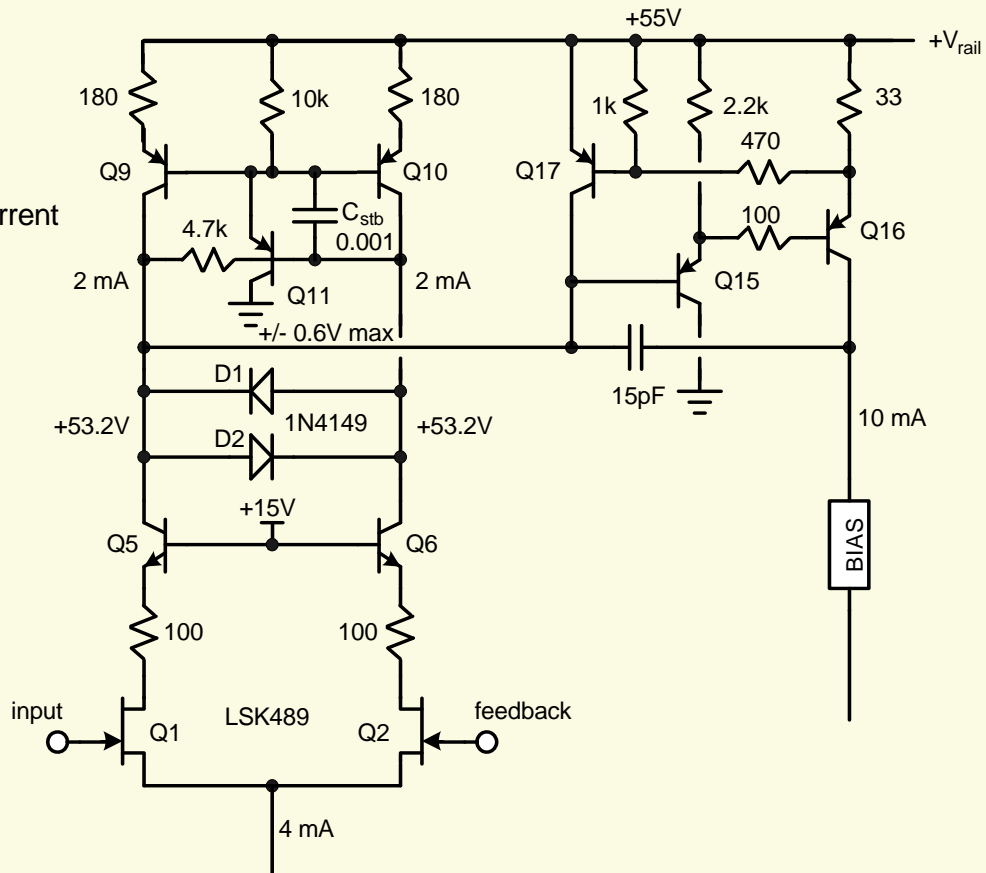
- D1, D2 clamp IPS output swing
- controlled swing when clipping
- Q16 base resistor limits Q15 current
- C_{stb} helps VHF stability
- Q5, Q6 REs help VHF stability
- Q17 limits Q16 to 20mA



Bob Cordell


IPS and VAS (top half)

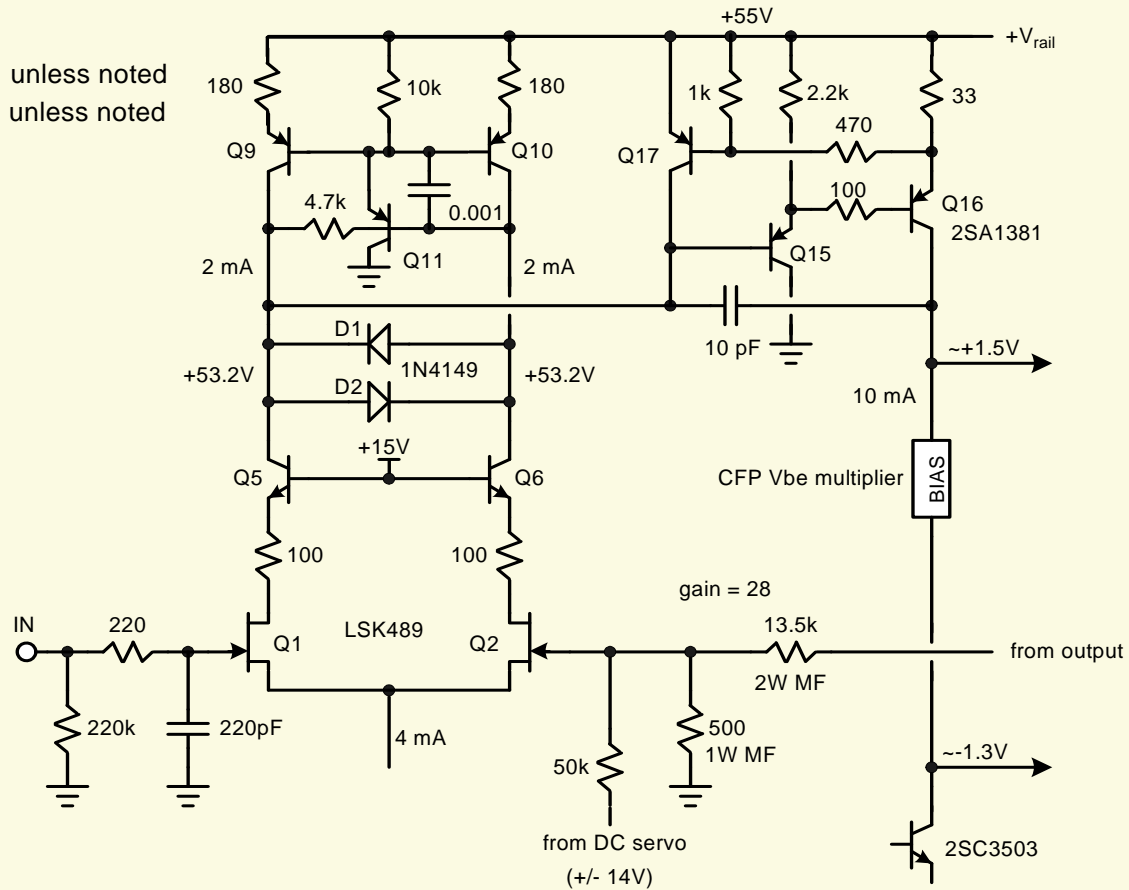- all NPN 2N5551 unless noted
- all PNP 2N5401 unless noted




Bob Cordell

Bias Spreader and Gate Protection

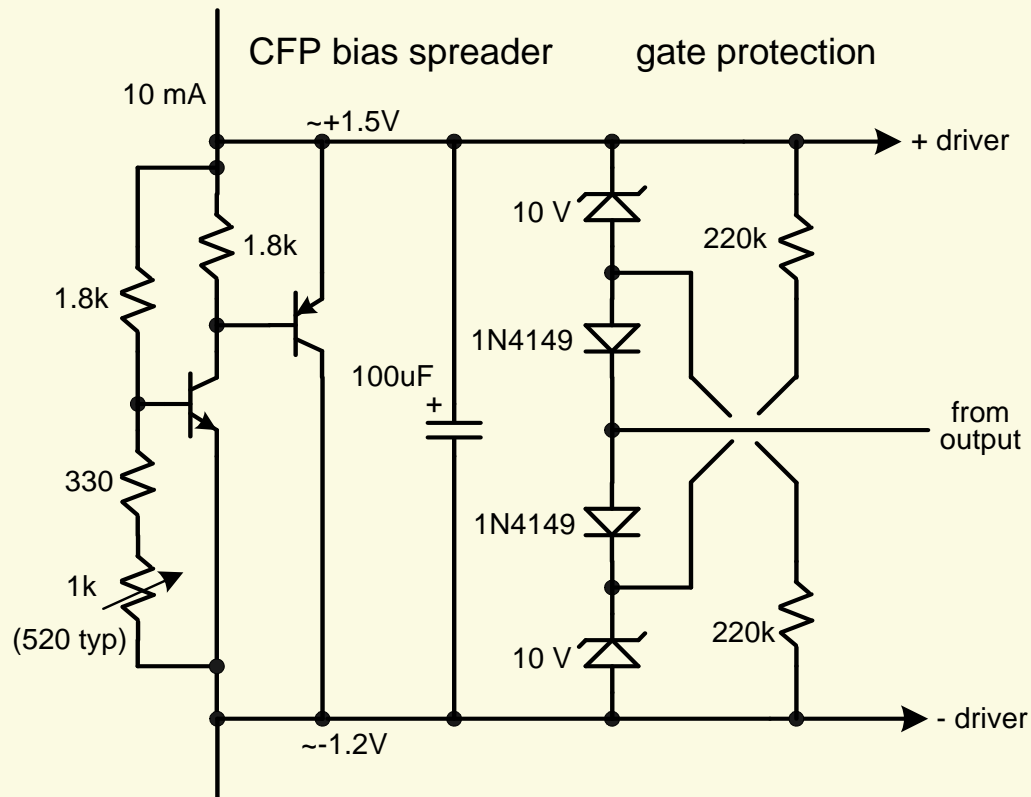


Bob Cordell

Lateral MOSFET OPS THD-1

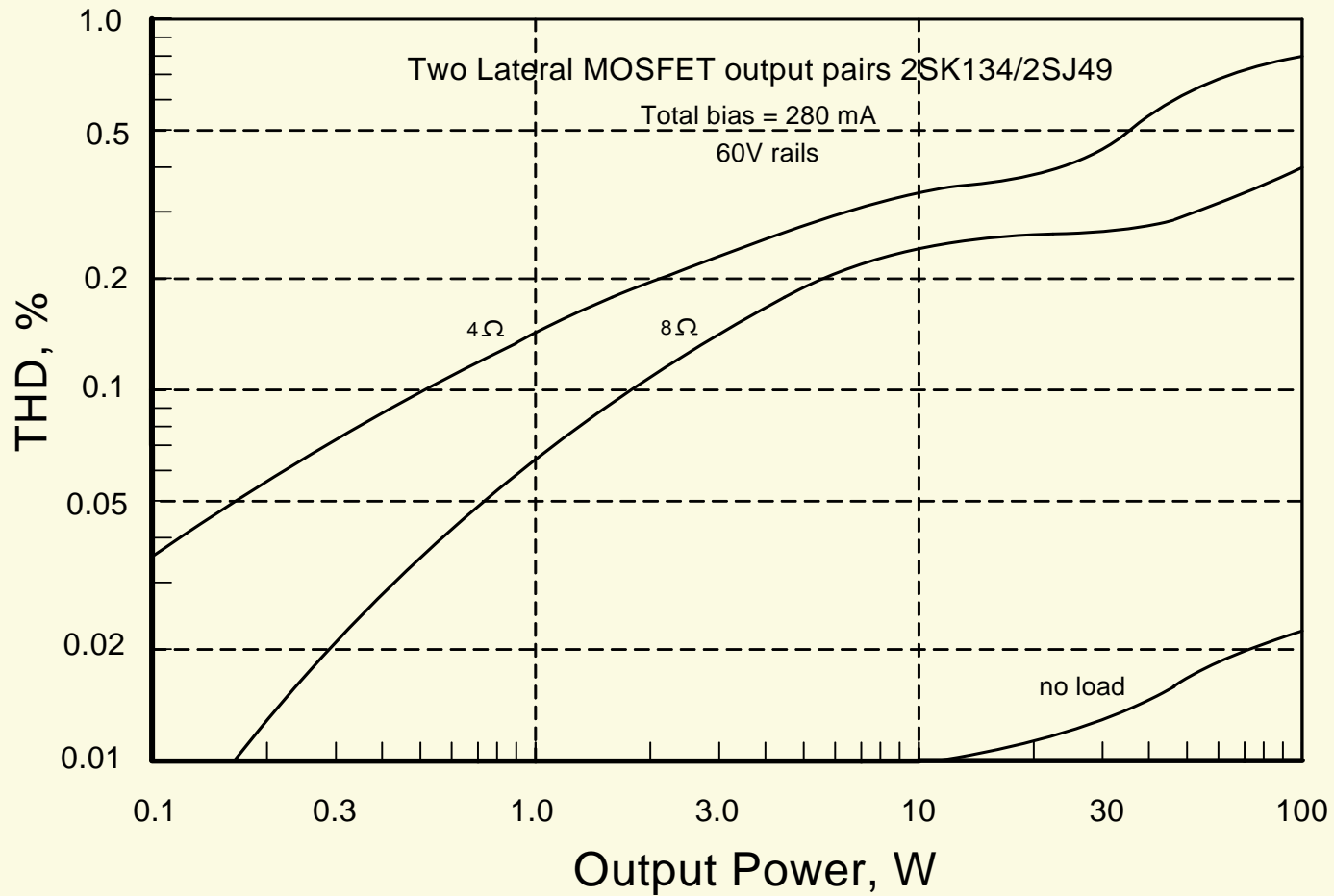


Bob Cordell

MOSFET OPS THD-1 Spectrum @ 1W

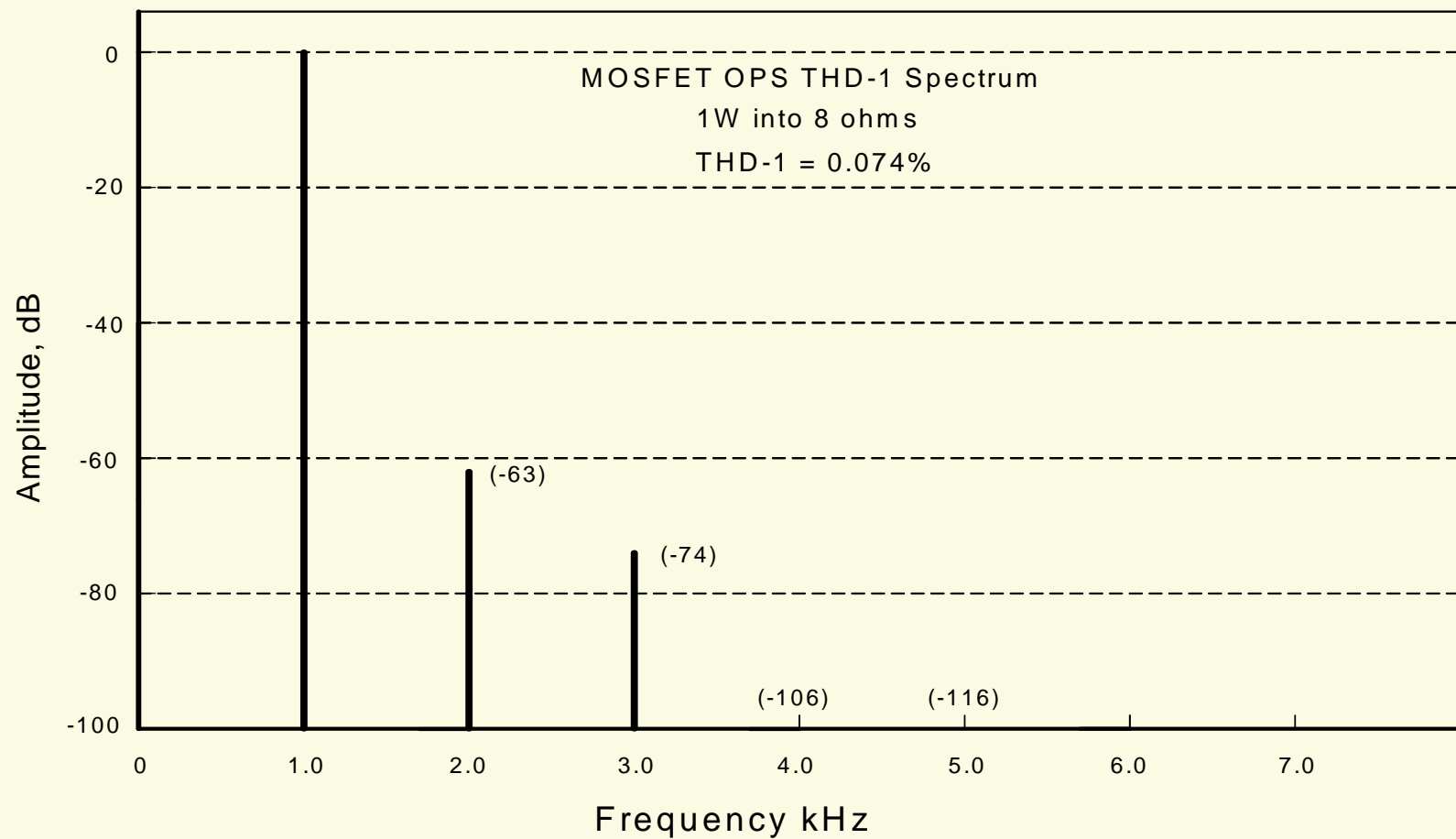


Bob Cordell

MOSFET OPS THD-1 Spectrum @ 8W

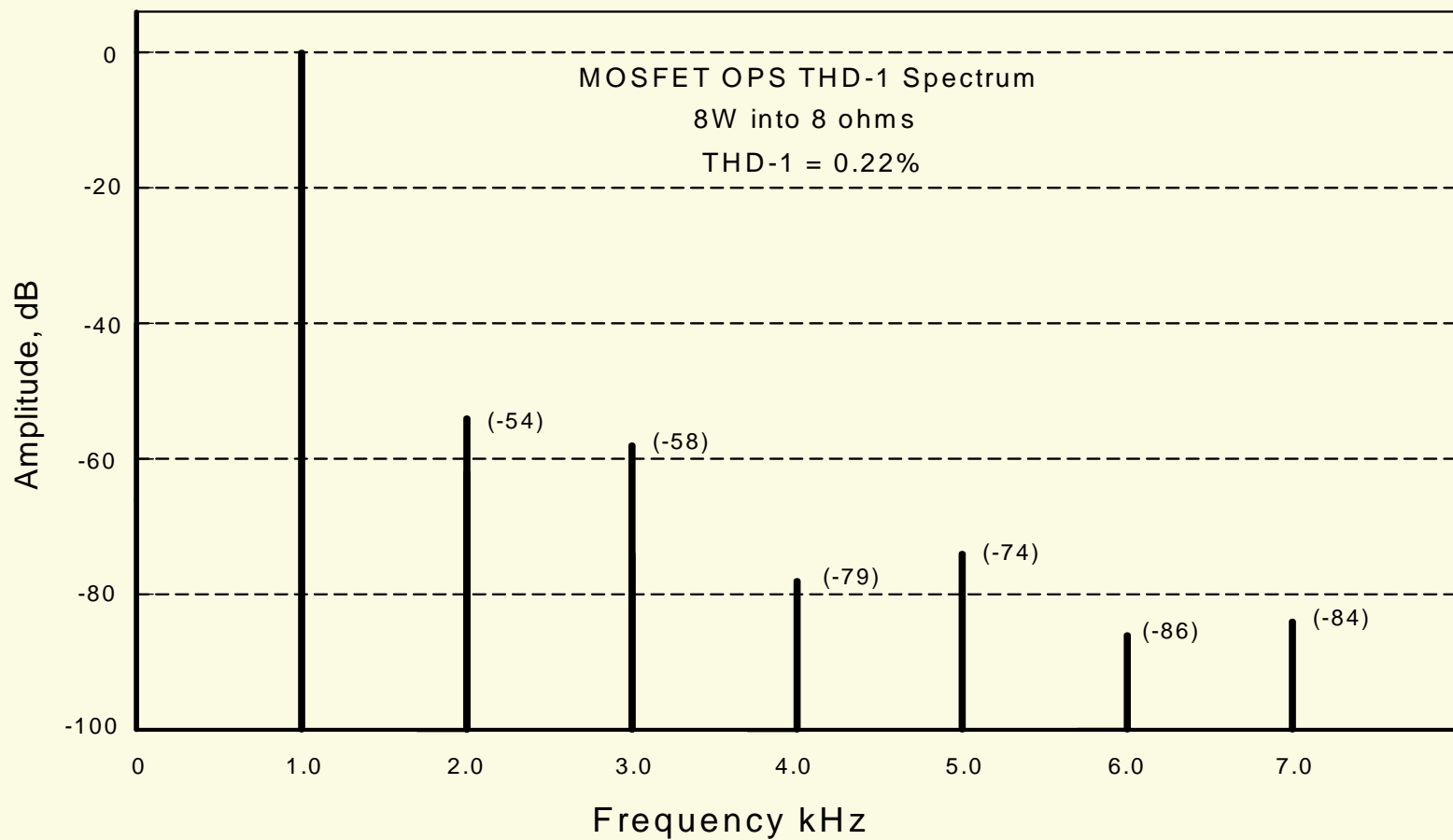


Bob Cordell

MOSFET OPS THD-1 Spectrum @ 50W

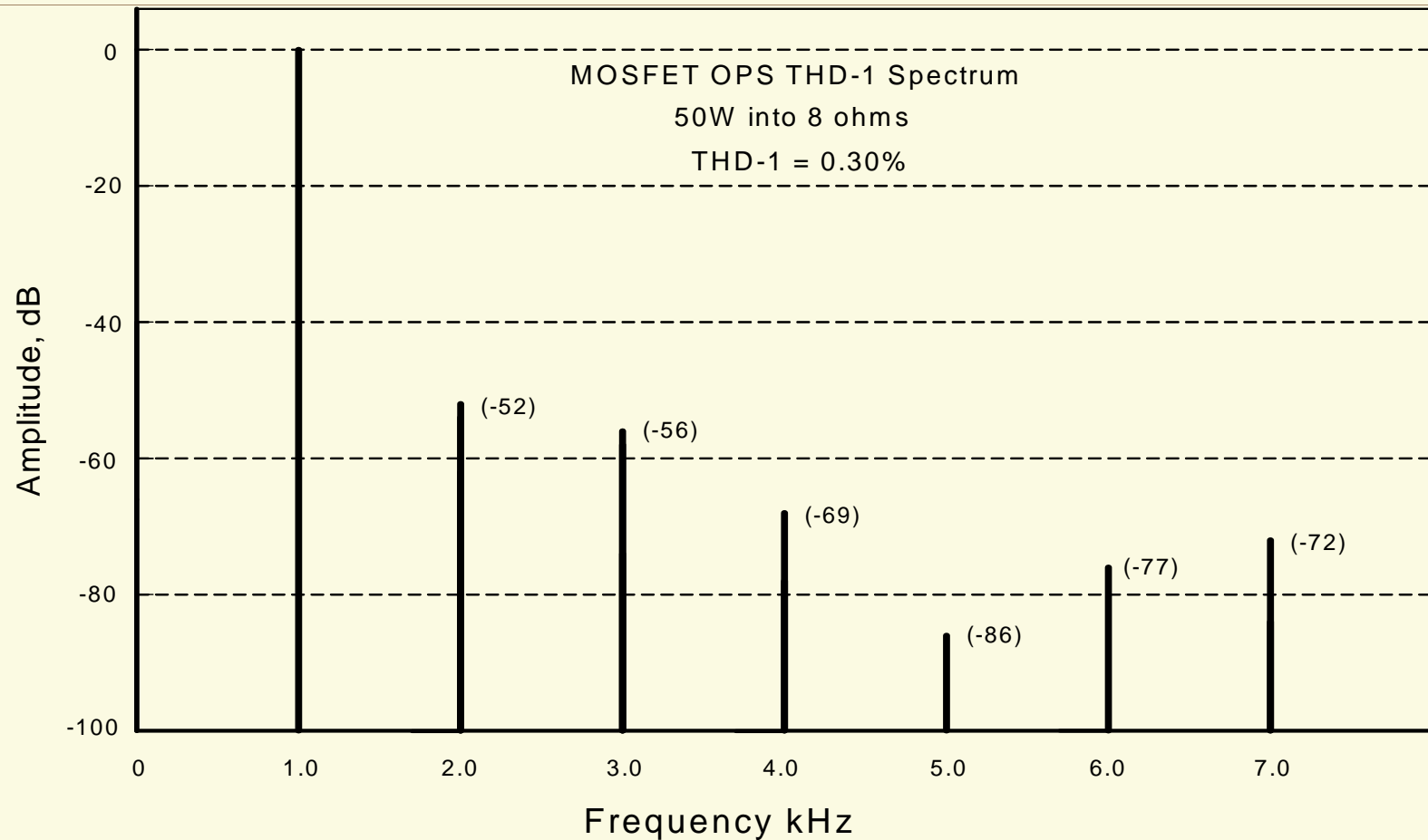


Bob Cordell

DH-220C THD + N vs Power

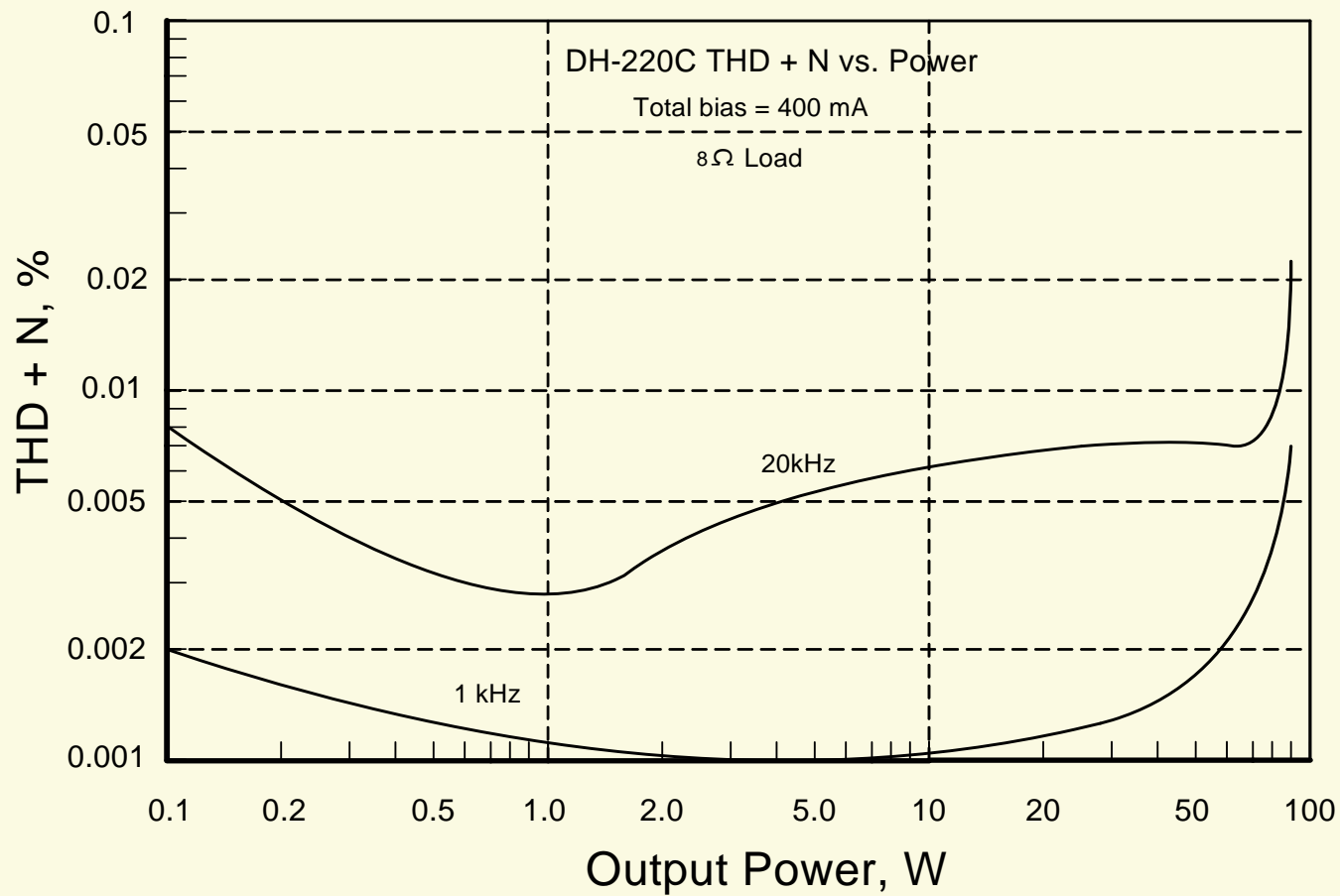


Bob Cordell

DH-220C THD + N vs Frequency

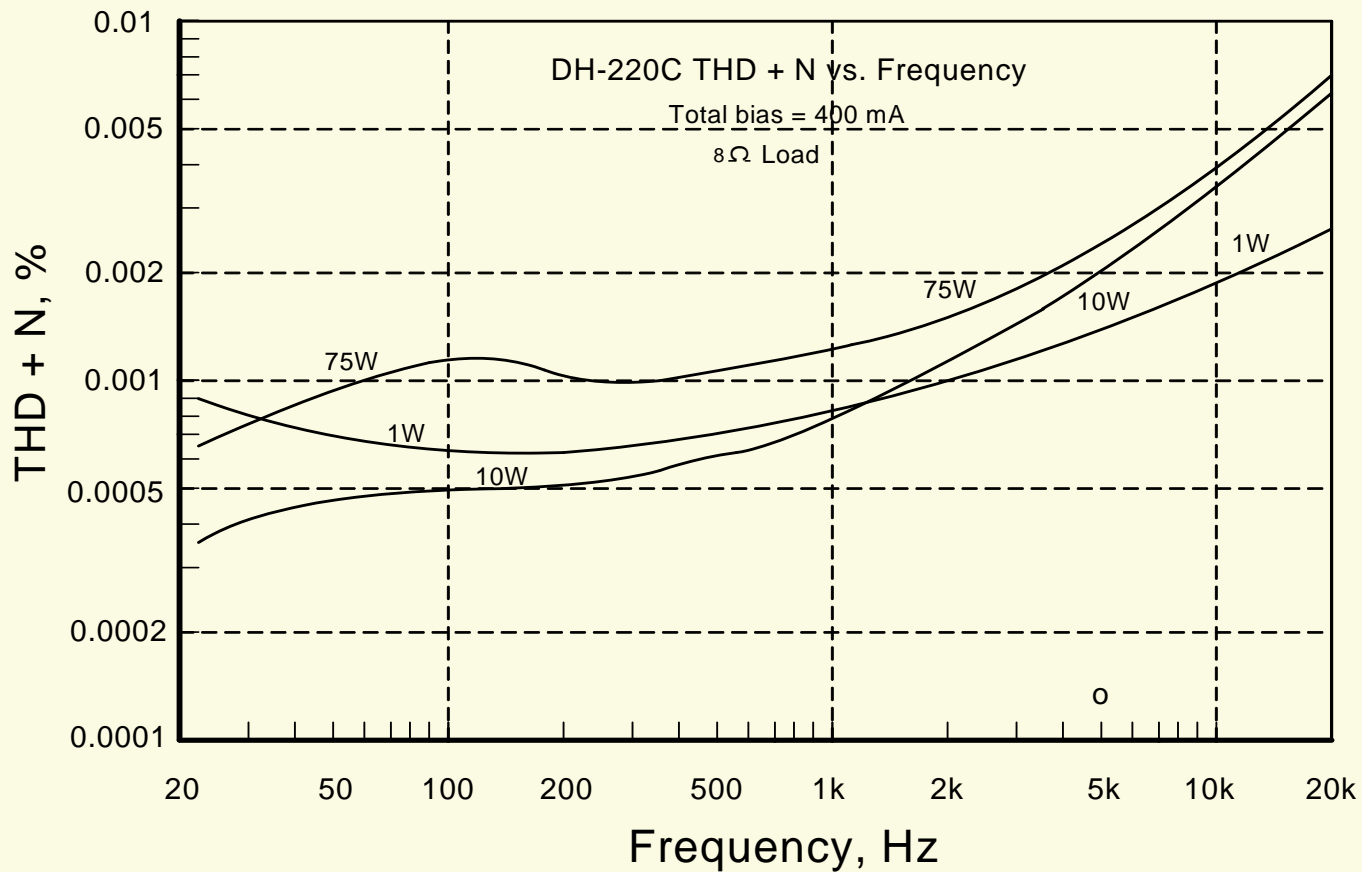

Bob Cordell

Input Power vs Output Power

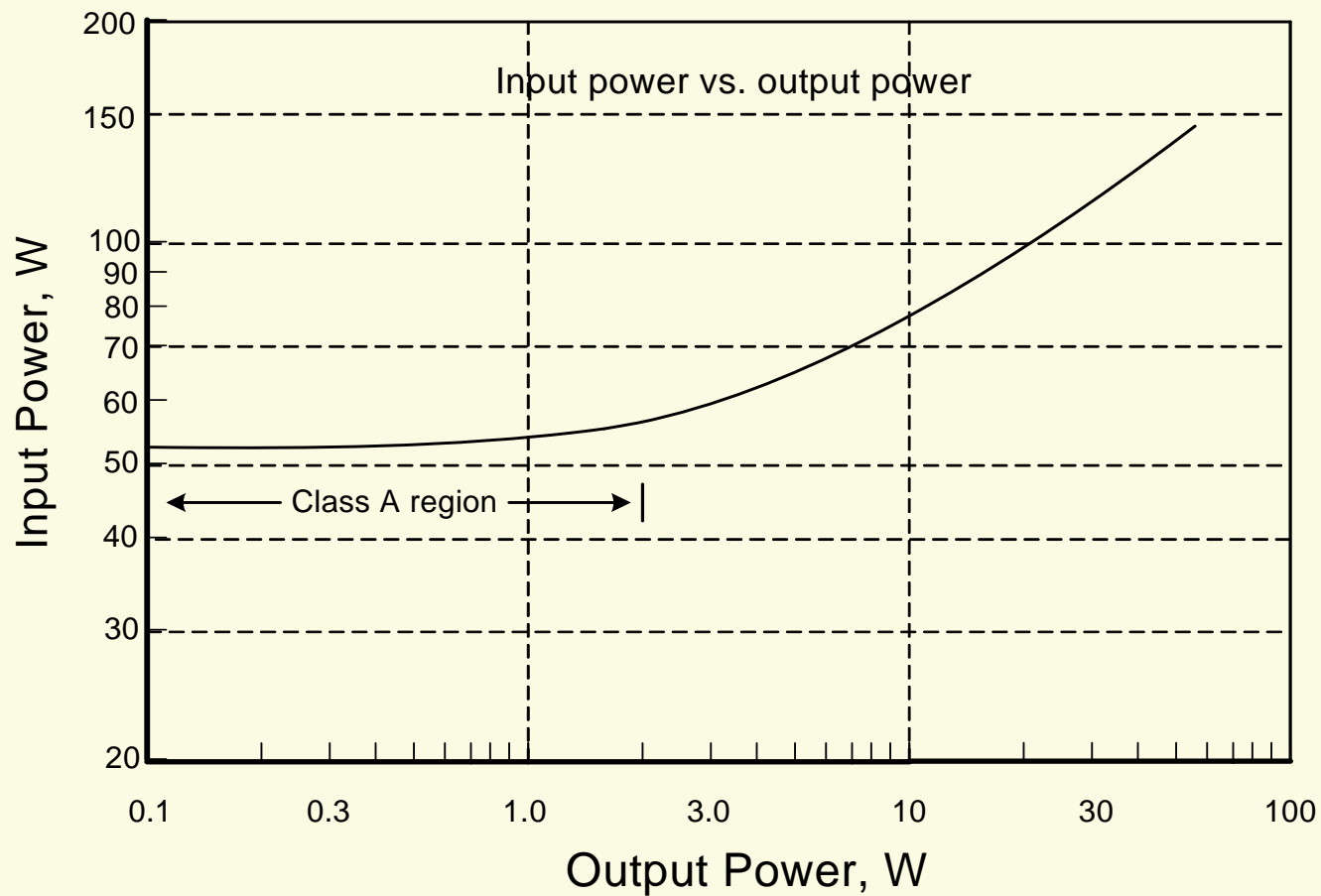


Bob Cordell

Performance

- Very low THD-1 and THD-20
- THD-1+N 0.001% @ 2w, 8 ohms
- THD-20+N 0.007% @ 75w, 8 ohms
- Very low noise – 5 nV/rt Hz
- 104 dB A wtd S/N re 1w, 8 ohms
- Large class A region – 400mA bias

The DH-220C Breadboard

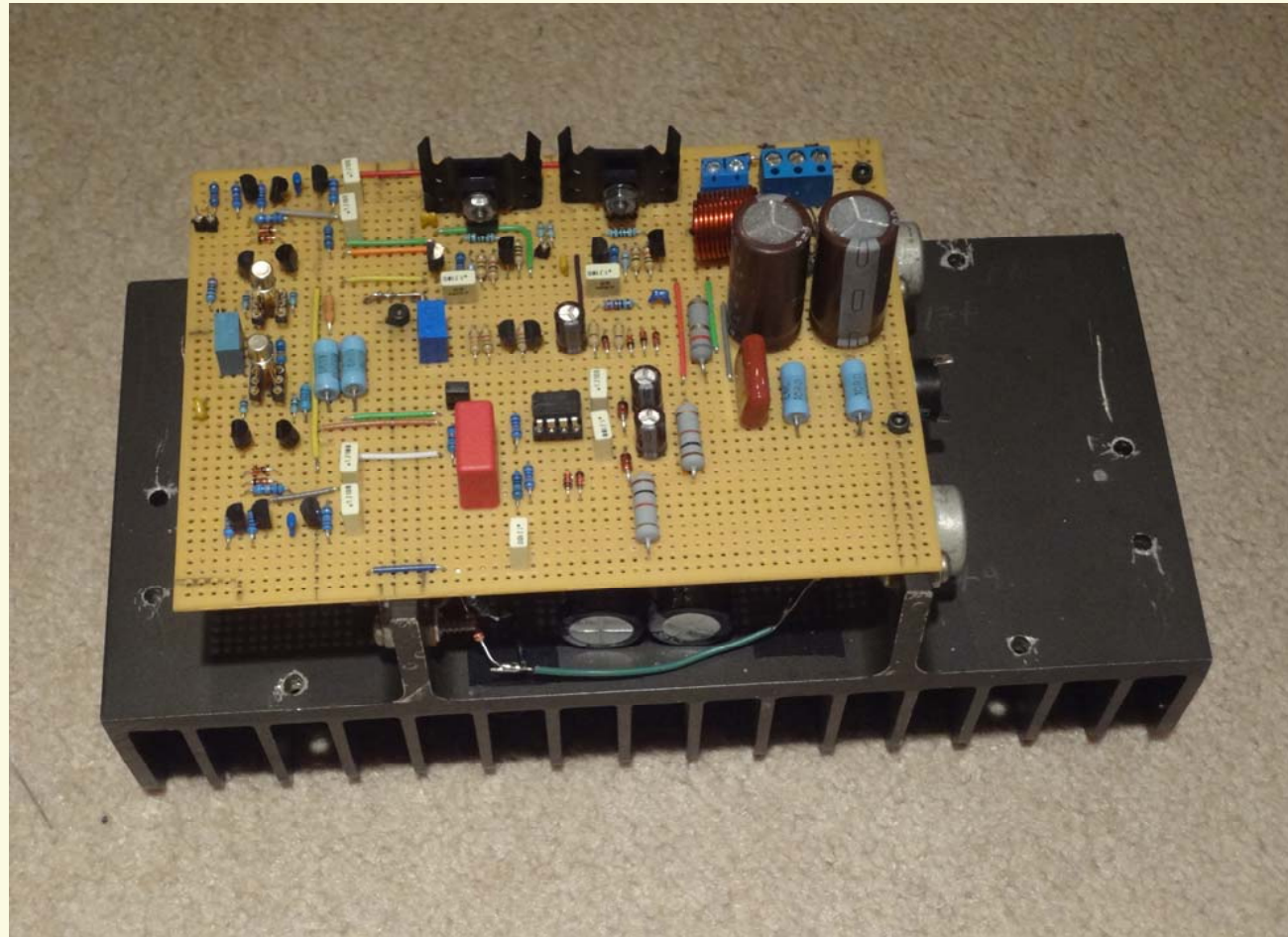

Bob Cordell

Summary

- 📄 Re-designed DH-220 with JFET Complementary Input Stage
- 📄 Linear Systems LSK489 and LSJ689
- 📄 Lateral MOSFET output stage
- 📄 Large class A region – good “First Watt”
- 📄 Very low distortion
- 📄 Very low noise – 104 dB A wtd re 2.83V