

High-fidelity Main Amplifier

By J. Haskell

THIS UNIT PROVIDES A GOOD QUALITY 10W OUTPUT

THE increasing number of hi-fi enthusiasts who wish to start a hi-fi system from scratch will welcome this article about a hi-fi amplifier capable of providing up to 10W of good quality reproduction with negligible distortion, and good frequency response.

Circuit

The main amplifier is usually built separately and can be stored away from the control unit if desired. An obvious choice for the output section in an amplifier of good quality is a push-pull one. The output stage consists of two EL84's in push-pull, under normal or low-loading conditions as required. Distributed loading was considered but due to the lack of peak power handling this arrangement was discarded. The normal loading condition for the output valves results in a distortion figure of about 0.3% at 10W over a power response of better than 30--15,000c/s within one decibel. This response is more than adequate for even the most critical of listeners, and only very expensive speaker systems can reproduce below

30c/s at the rated output. The frequency response is 10c/s to 20kc/s \pm 1dB or better.

The valves are cathode-biased under both loading conditions. A balance control is included in the cathode circuit of V2 and V3.

Low-loading

Under this loading, the distortion content at 10W is approximately 0.1% over the specified range, and is therefore more suitable for music and speech reproduction in the home than normal loading. The anode to anode load for EL84's, in normal and low-loading conditions is 8,000 Ω and 6,000 Ω respectively. The usual "grid stopper" resistors are included in the circuit to prevent any parasitic oscillations from taking place.

The Phase Inverter

The phase inverter circuit is designed around a high-gain double-triode valve type ECC83, the first section of which acts as a driver and the second section as the phase inverter proper. This type of circuit gives good reproduction and is quite popular, the only disadvantage being that the overall gain is slightly more than unity (1.8). Since the cathode resistors of the phase inverter are not by-passed, there is heavy negative feedback, giving good transient response and also

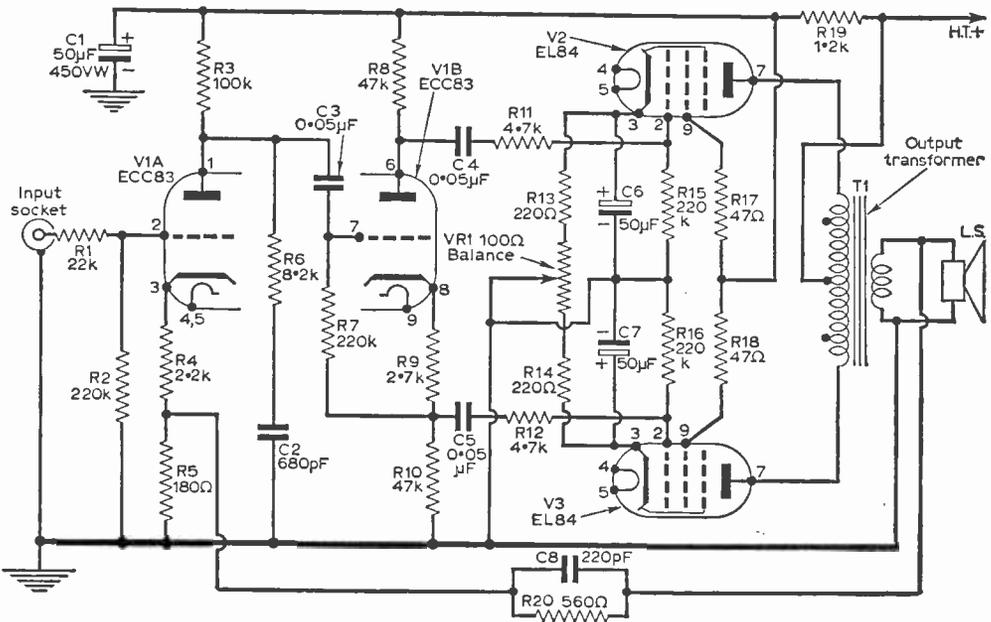


Fig. 1—The circuit diagram.

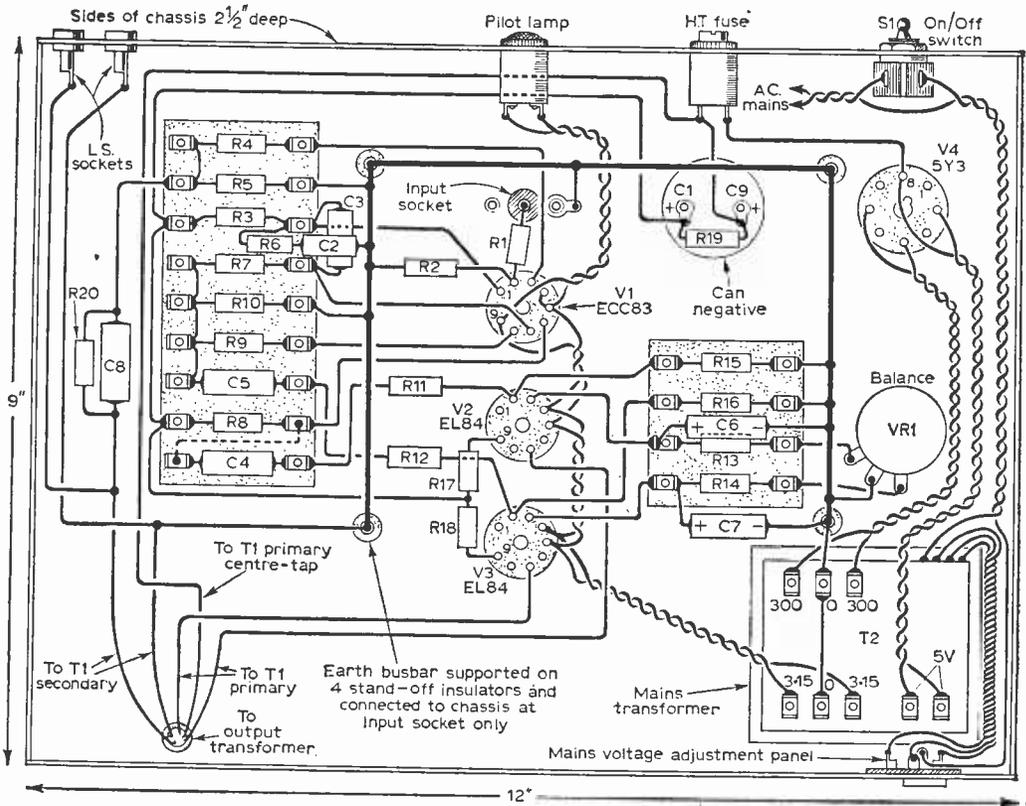


Fig. 3—The complete underchassis wiring diagram.

will be obtained if this amplifier is used in conjunction with the pre-amplifier designed by the author (June issue, 1961), as this was used with the prototype. The basic sensitivity is about 600mV and any high quality pre-amp capable of this output may be used.

Assembly

The components are first mounted on the group boards as shown in Fig. 3. When resistors R8 and R10, R15 and R18 are being soldered, a heat shunt should be used. Only one wire goes beneath the group boards, this is from C3 to R6 and is shown dotted in Fig. 3. When the group boards are assembled, they may be bolted into place with a spacer located between the board and the chassis, to allow for the wiring underneath.

All earth connections are soldered to the busbar, which may be held insulated from the chassis by means of two tagstrips: this busbar should be earthed to chassis at the input socket only.

An output socket may be included if desired, and should be insulated from chassis if possible.

Wiring

The heater and power supply should be wired in first. Tightly twisted wires are used for all A.C. circuits, and this wiring should be kept away from signal circuits and positioned as close to the chassis as possible.

Feedback

For negative feedback to take place, the amplifier output secondary winding must be correctly phased in relation to the input. If in phase with the input, violent oscillations will take place, which may damage a high-grade speaker suspension; hence, it is best to use a low-grade speaker to secure the correct phase relation.

Output Stage Balance

The output stage is next balanced and is a very simple procedure. The balance control VR1 should be slotted with a file for screwdriver adjustment only. Before switching on, check for an H.T. short with the meter. After switching on, if positive feedback occurs, then switch off immediately and reverse the anode connections on the output transformer primary. After about thirty seconds the set should have warmed up and a very slight hum only should be present (the hum level is approximately 80dB below full output).

A D.C. voltmeter is next connected across the anodes of the EL84's and the balance control VR1 is adjusted until no reading is obtained (ignore random fluctuations). The valves are now balanced from the D.C. aspect, which is usually the same for signal input. If a balance cannot be obtained, the valves should be switched over and the procedure carried out again: if a balance is still not obtained, then the valves should be checked for emission. Usually a balance is easily obtained. ■