


## Part1

I had to split it in to parts because of the 100kb upload limit.

This is a simple procedure to calculate “by hand” a third order Bessel or Butterworth filter in a MFB topology. I couldn’t find it in any book. (well...perhaps I could use some more reading) There is some work at the horizon but not as much as it may seem. You may want to use a pocket calculator able to solve 3<sup>rd</sup> order equations (and with a few ‘memories’ to store partial results) - like a Casio fx-991MS....

Two good advices: always run a simulation of the circuit to check for any catastrophic errors. (experience talks here ☺) and use a bridge to match the components values and check DF vs. freq. of capacitors.

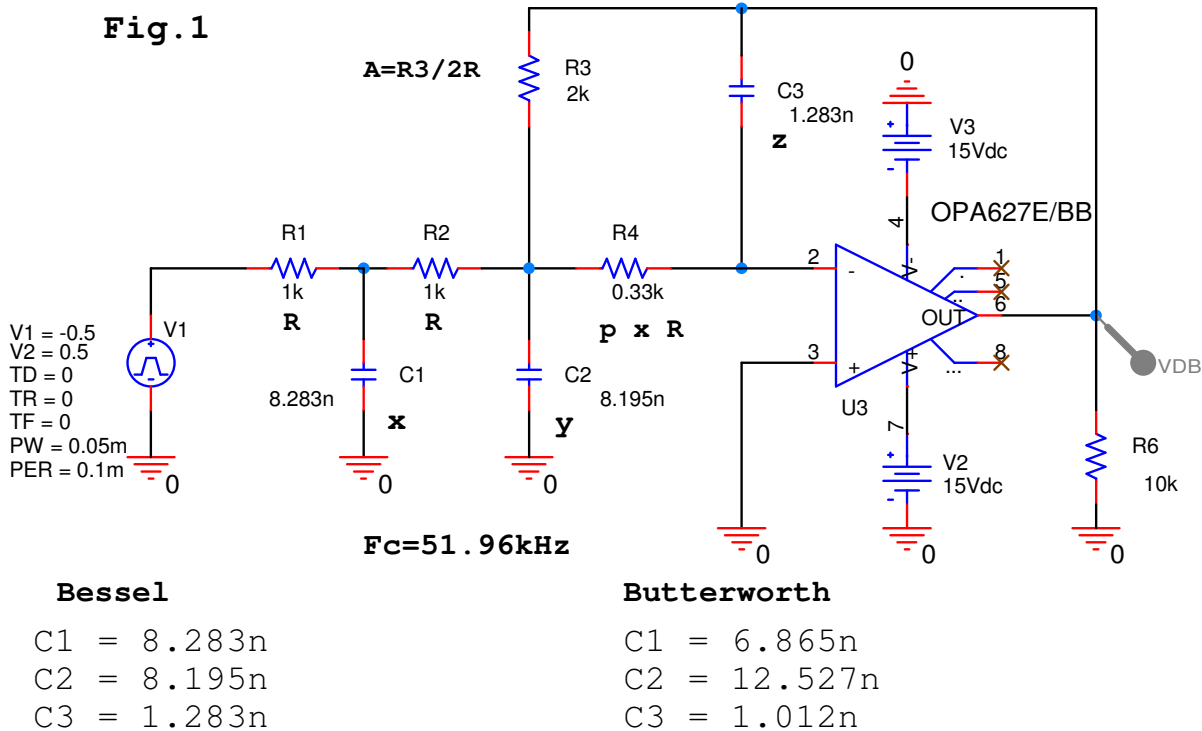I’ll start with a single ended example and in Part2 I’ll show how to go for a differential configuration.



Some general formulas that apply to the 3<sup>rd</sup> order filter in Fig.1:

$$G = -\frac{A}{s^3 + a*s^2 + b*s + 1}; \text{ where } s = j*2*\pi*f_c$$

$$|G| = -\frac{A}{\sqrt{(1-a*t^2)^2 + t^2*(b-t^2)^2}}; \text{ where } t = \frac{\omega}{\omega_c} = \frac{f}{f_c}; \varphi = \pi \mp \arctg \frac{t*(b-t^2)}{1-a*t^2};$$

Now comes some “heavy” stuff. The generalized form for Bessel polynomials is:

$P_n = \sum_{k=0}^n \frac{(n+k)!}{(n-k)!*k!} * \left(\frac{x}{2}\right)^k$  - don’t ask me any other details please, my maths... RIP (☺). So the first polynomials of interest for implementing electronic filters are:

$$P_1 = x + 1$$

$$P_2 = 3 * x^2 + 3 * x + 1 \xrightarrow{\text{OR}} t^2 + \sqrt{3} * t + 1$$

$$P_3 = 15 * x^3 + 15 * x^2 + 6 * x + 1 \xrightarrow{\text{OR}} t^3 + \sqrt[3]{15} * t^2 + \frac{6}{\sqrt[3]{15}} * t + 1 ; x \longrightarrow \frac{t}{\sqrt[3]{15}} \text{ to match the transfer function of the circuit.}$$

$$P_4 = 105 * x^4 + 105 * x^3 + 45 * x^2 + 10 * x + 1 \dots \text{etc.}$$

The filter coefficients are **a** and **b**. For a Bessel response  $a = \frac{6}{\sqrt[3]{15}} = 2.432881$  and  $b = \sqrt[3]{15} = 2.466212$ . For a Butterworth response  $a = b = 2$ .

For the Bessel the cut-off frequency ( $f_c$ ) is defined as the frequency at which the phase response reaches half of its maximum (or  $-\frac{n * \pi}{4}$ , where  $n$  is the filter order). The  $-3\text{dB}$  point occurs earlier (for a third order  $f_{-3\text{dB}} = 0.711887 * f_c$ ).

$$f_c = \frac{1}{2 * \pi * \sqrt[3]{R_1 * R_2 * R_3 * R_4 * C_1 * C_2 * C_3}} = \frac{1}{2 * \pi * R * \sqrt[3]{A * p * C_1 * C_2 * C_3}} ;$$

$$\text{For simplifying things: } R_1 = R_2 = R ; A = \frac{R_3}{R_1 + R_2} = \frac{R_3}{2 * R} ; p = \frac{R_4}{R_1}$$

Further on I made some notations:  $K_1 = A * p$ ;  $K_2 = 2 * A + p$  and also for the unknowns ( $x, y, z$ ) that we have to find:

$$C_1 = \frac{x}{2 * \pi * f_c * R} ; x = \frac{C_1}{\sqrt[3]{A * p * C_1 * C_2 * C_3}}$$

$$C_2 = \frac{y}{2 * \pi * f_c * R} ; y = \frac{C_2}{\sqrt[3]{A * p * C_1 * C_2 * C_3}}$$

$$C_3 = \frac{z}{2 * \pi * f_c * R} ; z = \frac{C_3}{\sqrt[3]{A * p * C_1 * C_2 * C_3}}$$

Tip: at the end if you want to check quickly for errors, you can use this relation:  $x * y * z = \frac{1}{A * p}$  (don't

use it as part of the solving 3 equations system indicated bellow!)

Actually after writing the circuit eqn. and using the notations I made until now the following three equations will give us the solutions. I avoided the boring calculations to reach down to this point. (Huh! - imagine a few pages of this stuff edited in Word) You can use either mesh method or Y to  $\Delta$  (and back) transformations...so after solving (1) it is easy to obtain  $x$  and then  $y$  from two simple 1<sup>st</sup> order equations:

$$z^3 - \frac{2 * b}{K_1 + K_2} * z^2 + \left[ \frac{a}{(K_1 + K_2) * (K_2 + 2 * K_1)} + \left( \frac{b}{K_1 + K_2} \right)^2 \right] * z - \frac{a * b - 1}{(K_1 + K_2)^2 * (K_2 + 2 * K_1)} = 0 \quad (1)$$

$$2 * b = x + 2 * (K_1 + K_2) * z \quad (2)$$

$$2 * a = 4 * K_1 * y * z + (K_2 + 2 * K_1) * x * z \quad (3)$$

Here usually I choose “p” as number smaller than unity from the 1% resistor tolerance series. By choosing “p” we force the ratio between R1(R2) and R4. Just a few examples: if p= 0.475 then at the end you will have plenty of pairs to choose from: (1.21k, 0.576k), (1k, 0.475k), (931, 442), (820, 390) etc.

Then you may want to choose A=1 (0dB gain => R3= 2R) as it is often the case and we can finally solve for z. We retain only the real solution of course. There’s a risk of getting negative values for x or y or even z. Anyway a 3<sup>rd</sup> order equation has always at least one real solution. The problem is to get a positive one. Usually for  $p \leq 0.9$  and for A reasonably small you’ll get valid solutions.

The same equations if A= 1 can be written:

$$z^3 - \frac{b}{p+1} * z^2 + \left[ \frac{a}{2 * (p+1) * (3 * p + 2)} + \frac{1}{4} * \left( \frac{b}{p+1} \right)^2 \right] * z - \frac{a * b - 1}{4 * (3 * p + 2) * (p+1)^2} = 0$$

$$x = 2 * b - 4 * (p+1) * z$$

$$y = \frac{2 * a - (3 * p + 2) * z * x}{4 * p * z}$$

You can tune the filter by choosing ( $f_c, \mathbf{R}$ ) and then fine-tune it by choosing ( $f_c, \mathbf{C}_x$ ). Then you can go down in tighter tolerances series and reiterate the calculations if you feel that you’re getting close to some nice standard available values.