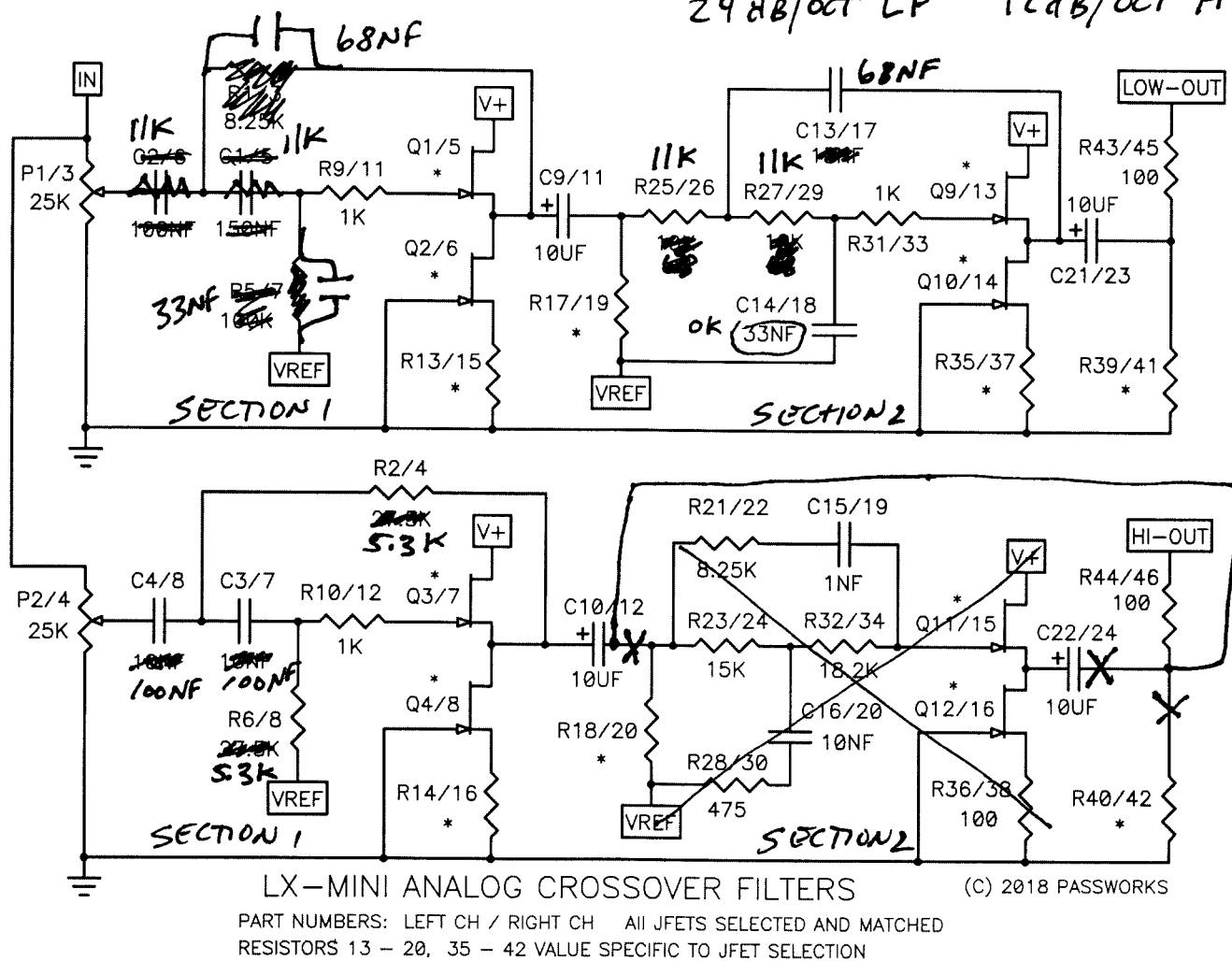


So here's the actual circuit of the analog LX-mini crossover: **300 Hz**
24 dB/OCT LP **12 dB/OCT HP**



And here is the power supply filtering for the external switching 24 volt power supply. The crossover draws about 75 ma current, and I recommend a quiet wall-wart rated at 500 mA or more. The inexpensive Triad WSU240-0500-13 gives excellent results, but you are free to use something else, including regulated linear supplies.

