

### Base Spreading Resistance $r_{bb'}$ – Measurement Approach<sup>23</sup>

The  $r_{bb'}$  measurement set-up is given in Fig. 3.28. The device under test is operated at about 1mA. The total gain  $G_1$  of the circuit is about 50 dB, with  $S_2$  closed. With  $S_2$  open total gain  $G_2$  will be

$$G_2 = G_1 + 20 \log \frac{R_6 + R_7 + R_8}{R_5}$$

$$= G_1 + 2.997 \text{ dB} \quad (3.114)$$

<sup>23</sup> Tom McCormick 1992 in a letter to Wilfried Adam – as a follow-up of Mr Adams 1989 EW&WW article on “Designing low-noise audio amplifiers”

All capacitors should have a value large enough to ensure a flat frequency response in  $B_{20k}$ . For NPN devices power supply should be +15 V and all capacitors reversed.

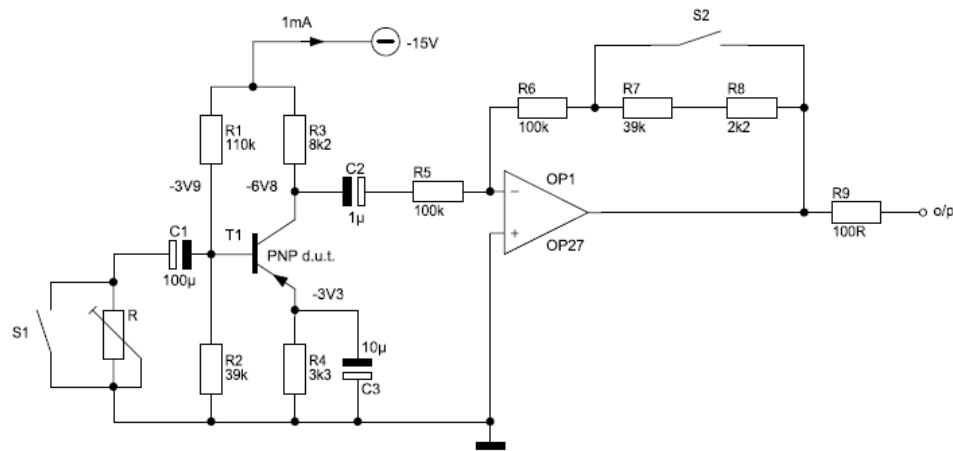


Fig. 3.28 McCormick  $r_{bb'}$  measurement set-up

The measurement approach goes like follows:

- Step 1: measurement of noise in  $B_{20k}$  at the output of OP<sub>1</sub> with  $S_1$  closed and  $S_2$  opened, resulting in a total gain of  $G_2$  and an output noise voltage of  $e_{N.out.1}$
- Step 2: decrease of circuit gain to  $G_1$  by opening of  $S_1$  and closing of  $S_2$
- Step 3: adjustment of  $R$  as long as the test circuit produces the Step 1 output noise voltage  $e_{N.out.1}$
- Step 4: measurement of  $R$ : this will be the value of  $r_{bb'}$  of the d.u.t.

The principal method behind this measurement result comes from Eqs. (3.17–3.19) that describe the noise voltage sum of two resistors – in our case of equal valued  $R$  (after adjustment) and  $r_{bb'}$ .