



This inexpensive, yet effective, AGC amplifier has a dynamic range greater than 50 dB and is built using only half of an LM358 dual 8 pin op-amp package.