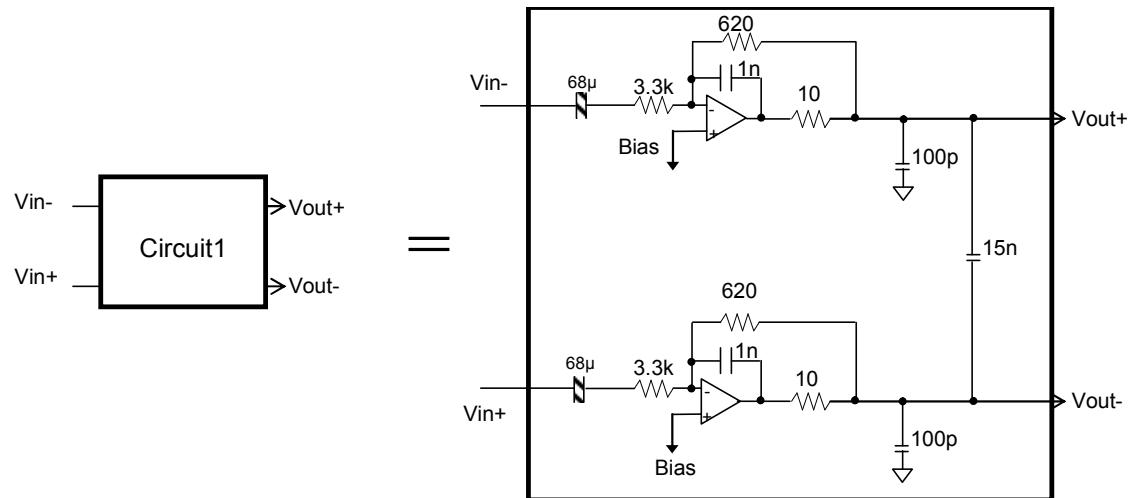


AK5574 analog input circuit example


May 2016

ASAHI KASEI MICRODEVICES CORPORATION
Mixed Signal Products Division
Audio & Voice business Unit


Circuit 1) Analog circuit for differential input



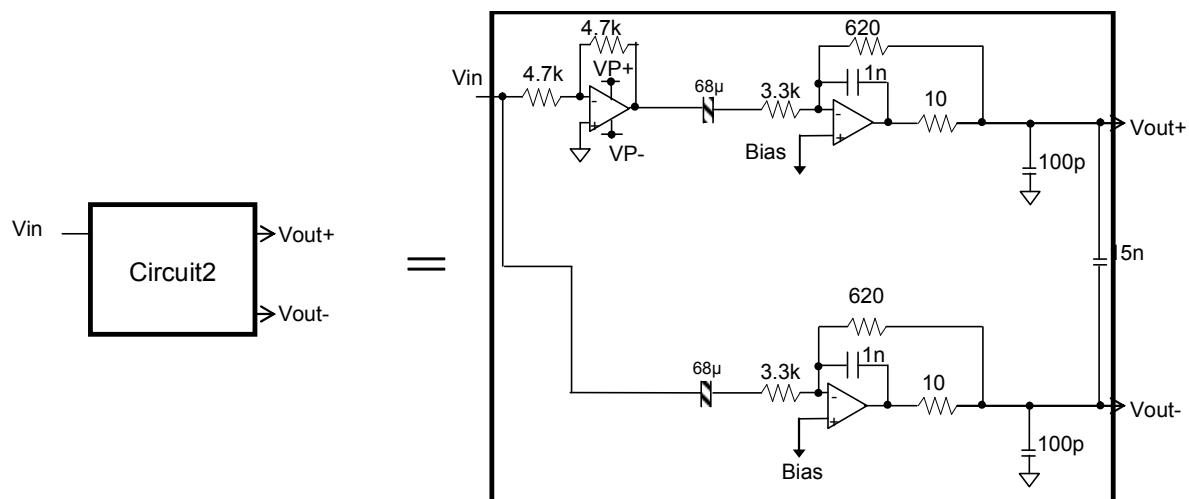
Circuit 2) Analog circuit for single-ended input



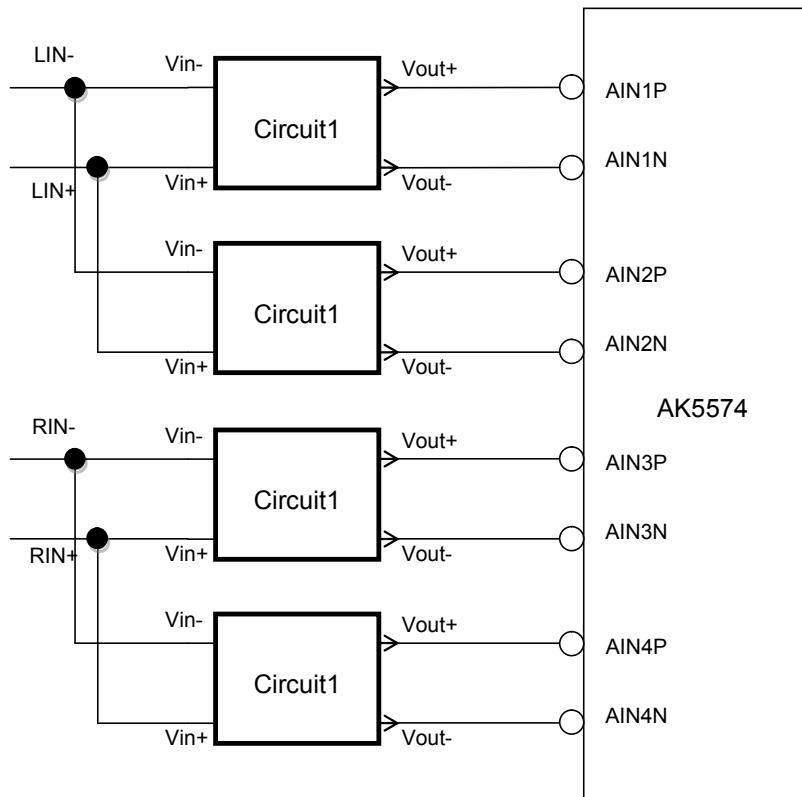
2ch summation mode for differential input



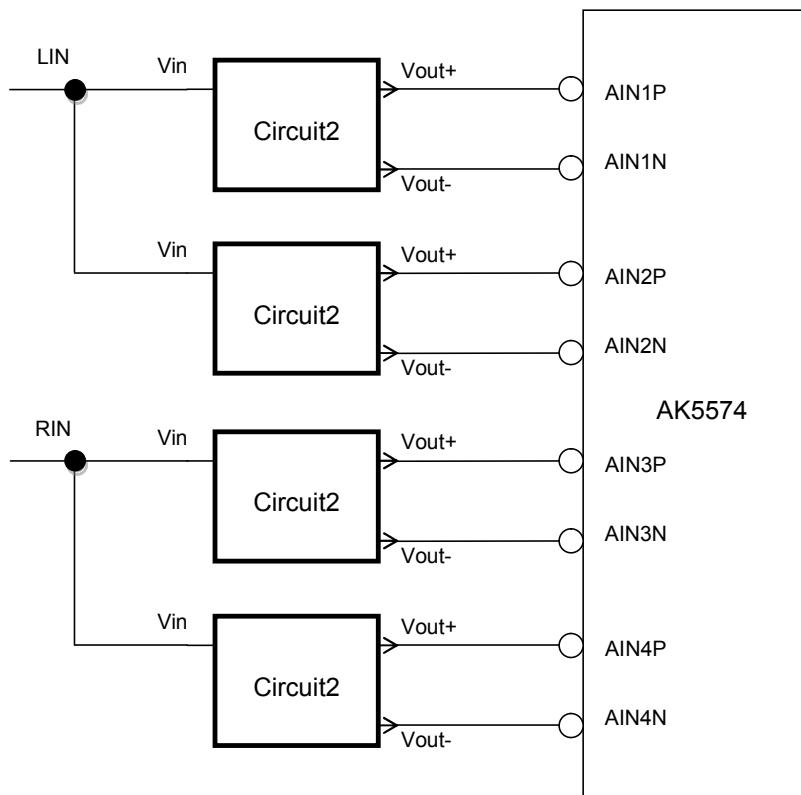
2ch summation mode for Single-ended input



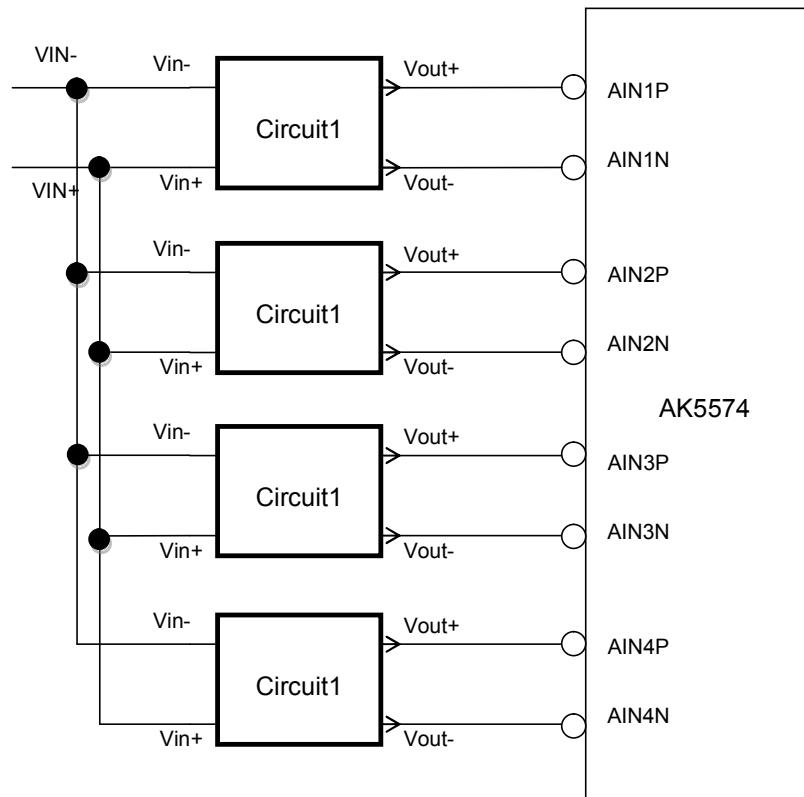4ch summation mode for differential input



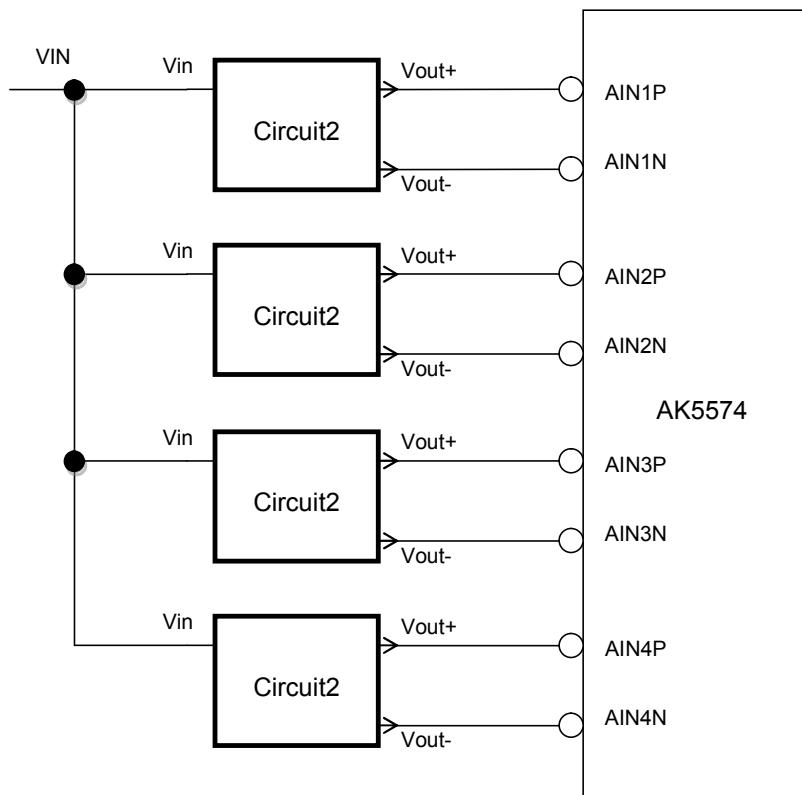4ch summation mode for Single-ended input



End of document