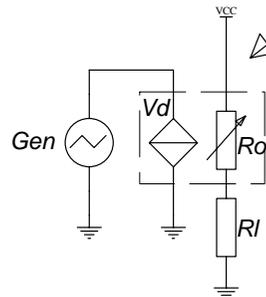


Two LM1875s working in parallel will provide more power, why?




This is a simple model to introduce why
 Gen: signal for driving the output stage
 this signal comr from the section in front,
 generally it should be the drive section

Vd+Ro:power BJT model
 this is the typical model.in class ab and class a etc,
 Ro is a variable resistor,which value is decided by Vd

RI:load(your speaker)

But we only disscus the clipping power this time.
 $P_{max} = U \cdot U / R = VCC \cdot (RI / (RI + Ro)) / 1.414 \cdot VCC \cdot (RI / (RI + Ro)) / 1.414 / RI$
 $= 25 \cdot (8 / (8 + Ro)) / 1.414 \cdot 25 \cdot (8 / (8 + Ro)) / 1.414 / 8$

so if reduce Ro,Pmax will increase

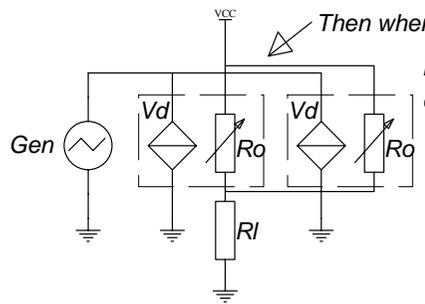

Then when we make 2 lm1875s working in parallel the model will like this
 it is obvious that the source resistor up on the RI becomes into Ro/2,
 one time less than before,so the clipping power out is more