

unit's design is fully pushpull from input to output, modulation noise is totally absent at low frequencies. Overall noise, too, is diminished since there is no ground loop. Measurements made with an r-f filter to eliminate r-f contamination yield a noise figure of -112 dB.

About the Circuit. Since most amplifiers employ a single differential input circuit, they are essentially single-ended designs. Virtually all power amplifiers can accurately reproduce sine waves fed into their inputs. However, it is not necessarily true that all amplifiers will accurately


reproduce music and voice signals that are generally nonsinusoidal and rarely have positive and negative peaks that are equal in amplitude. The obvious solution to accurately amplifying music and voice signals, of course, is to use separate amplifiers for the positive and the negative half cycles. If the amplifiers are identical, it is then possible to obtain a virtually "perfect" amplifier.

Due to its unique mirror-image design, Ampzilla is an almost perfect amplifier. The positive and negative half-cycle amplifiers in Ampzilla share a common feedback loop, an advantage for any source that must drive

the amplifier.

The biasing system in Ampzilla employs a unique integrated circuit (IC1 in Fig. 2) that contains five operational amplifiers. The op amps in this IC track the quiescent output current in such a way as to make thermal runaway impossible.

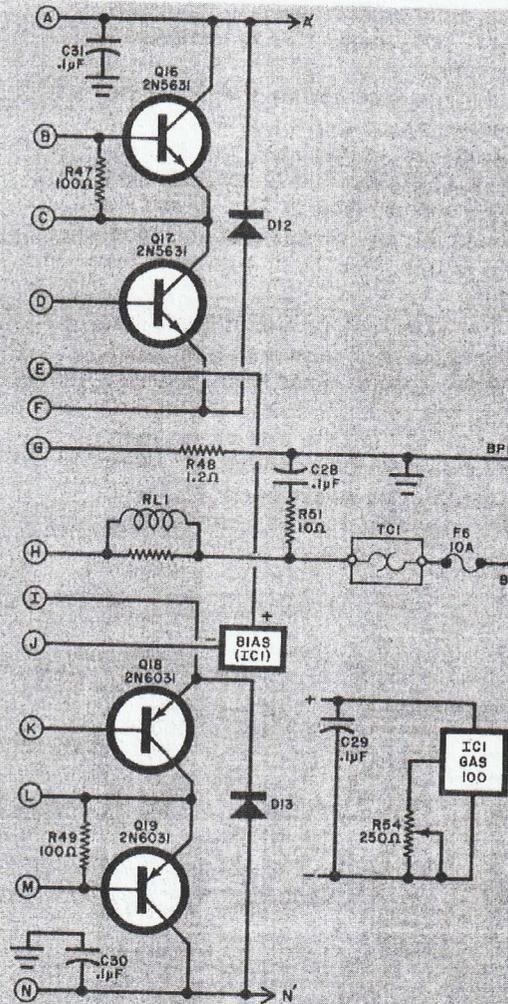The output stage of Ampzilla operates in a quasi-class-A mode, while the driver and slave output stages are driven class A for the full cycle. Only the driven output transistors, Q17 and Q18, are operated class B. However, Q17 and Q18 do not switch from positive to negative. Rather, they traverse back through the class-A region at



PARTS LIST

(For power supply and **one channel**)

- BP1, BP2—Five-way binding post (one red, one black)
 C1—200-pF, 100-volt ceramic capacitor
 C2, C3, C10, C11, C20, C21—100µF, 10-volt electrolytic capacitor
 C4, C24, C29—0.1-µF, 16-volt ceramic capacitor
 C5-C8—330-µF, 10-volt electrolytic capacitor
 C9—100-µF, 50-volt electrolytic capacitor

- C12, C14—22-pF, 500-volt, 10% ceramic capacitor
 C13, C15—47-pF, 500-volt, 10% ceramic capacitor
 C16-C19, C28, C30, C31—0.1-µF, 100-volt ceramic capacitor
 C22, C26, C27—0.001-µF, 500-volt, 10% ceramic capacitor
 C23, C25—220-µF, 16-volt electrolytic capacitor
 C32, C33—16,800-µF, 75-volt computer-grade electrolytic capacitor
 D1-D4, D15, D16—1N4148 diode
 D5—1N5878C 51-volt, 5% zener diode
 D6-D9—1N4938 diode
 D10, D11—1N5823 diode (do not substitute)
 D12, D13—1N4004 diode
 D14—MV5022 (Monsanto) diode
 F1-F4—AGC 6-ampere fuse
 F5—MDL 10-ampere slow-blow fuse
 F6—AGC 10-ampere fuse
 IC1—GAS100 op amp integrated circuit
 J1—Phono jack
 L1, L2—1-mH r.f.c. (12-ohm dc resistance) (Do not substitute for following transistors.)
 Q1, Q2, Q5, Q8—MPSU06 transistor (Motorola)
 Q3, Q4, Q6—MPSU56 transistor (Motorola)
 Q7, Q11—MJ3584 transistor (Motorola)
 Q9, Q10—2N3584 transistor
 Q12, Q13—2N6316 transistor
 Q14, Q15—2N6318 transistor
 Q16, Q17—2N5631 transistor
 Q18, Q19—2N6031 transistor
 R1—2.2-ohm
 R2—1-megohm
 R3—1000-ohm
 R4, R6, R16, R17—7500-ohm
 R7, R8, R23, R24—150,000-ohm
 R9-R12, R31, R33, R35, R36, R47, R49—100-ohm
 R14, R15—1800-ohm
 R18, R22, R25—620-ohm
 R21, R26, R46—62-ohm
 R29, R30—36,000-ohm
 R32—390-ohm
 R34—470-ohm
 R48—1.2-ohm
 R52, R53—10-ohm
 R5—1000-ohm, linear-taper trimmer potentiometer
 R13—200-ohm, ½-watt, 1% resistor
 R19, R20, R28—3900-ohm, 1-watt, 10% resistor
 R27—4990-ohm, ½-watt, 1% resistor

All resistors ½ watt, 5%

- R43, R44—0.39-ohm, 5-watt, 10% resistor
 R55—2000-ohm; 5-watt, 10% resistor
 R50—2.2-ohm, 2-watt, 5% resistor
 R51—10-ohm, 2-watt, 5% resistor
 R45—0.125-ohm, 10-watt, 3% resistor
 R39, R40—300-ohm, 1-watt, 2% resistor
 R37, R42—1000-ohm, 2-watt, 2% resistor
 R38, R41—750-ohm, 2-watt, 2% resistor
 R54—250-ohm, linear-taper trimmer potentiometer
 RECT1—200-PIV, 25-ampere bridge rectifier
 RL1—32 turns #16 enameled wire wound on R50
 S1—Dpdt 15-ampere switch (Cutler-Hammer No. 7241K2 or similar)
 T1—106-volt center-tapped, 12-ampere transformer (1500 volt/ampere)
 TC1—70° C thermal cutout (Elmwood Sensors)

Misc.—Suitable heavy-duty alum. chassis; mounting bracket for RECT1 and fuse block; 1000-sq.-in. finned heat sink; fuse block for four fuses; fuse holder for F5; fuse holder for F6; "Boxer" fan (IMC Magnetics Corp.); 3½-in. long L bracket with ½-in. and 1-in. legs for small heat sink; silicone paste; insulators for transistors; insulating fish paper (goes between large pc board and chimney); shielded cable; No. 16 or No. 14 stranded and solid hook-up wire; heavy-duty ½-in. (minimum) tall hard plastic feet; No. 6 solder lugs (3); No. 6 crimp ring-type solderless lugs; small rubber grommet; heavy-duty three-conductor line cord; shoulder fiber washers (2) for J1; machine hardware; rubber washers (4) for mounting power transformer; solder; etc.

Note: The following items are available from the Great American Sound Co., Inc., 8780 Shoreham Dr., West Hollywood, CA 90069: Complete stereo amplifier kit, including assembly manual for \$340, plus shipping for 65 lbs. (specify fan speed: slow, medium or fast.); factory-wired for \$475; with wattmeters for \$525 (plus shipping); Set of four etched, drilled, screened, and staked pc boards for \$20; Special power transformer for \$100, plus shipping for 45 pounds; Chimney and L brackets, \$50; Special GAS100 operational amplifier IC for \$1.50. A power-reading wattmeter system with 2 meters and with a range selector switch is also available for \$35 in kit form or \$50 factory wired and tested.