



Fig. 8.5 Multiple-feedback bandpass filter.

Active Filters

DESIGN PROCEDURE

Given: H_0 , $Q = \frac{1}{\alpha}$, $\omega_0 = 2\pi f_0$.

Choose: $C = C_3 = C_4$

Calculate: $Q = \frac{1}{\alpha}$

$$R_1 = \frac{Q}{H_0 \omega_0 C} = \frac{R_5}{2H_0}$$

$$R_2 = \frac{Q}{(2Q^2 - H_0) \omega_0 C}$$

$$R_5 = \frac{2Q}{\omega_0 C}$$

$$f_0 = 1 \text{ kHz}$$

$$H_0 = 1$$

$$Q = 5$$

$$C = C_4 = C_5 = 0.1 \mu\text{F}$$

$$R_5 = \frac{2.5}{2\pi \cdot 10^3 \cdot 10^{-7}} = 15,915 \Omega$$

$$R_2 = \frac{5}{(2 \cdot 5^2 - 1) \cdot 2\pi \cdot 10^3 \cdot 10^{-7}} \approx 162 \Omega$$

$$R_1 = \frac{R_5}{2} = 7,958 \Omega$$