

Autobias for mosfet audio output stages

It's said that biasing vertical d-mosfets in a class-AB output stage is less critical than biasing their bipolar counterparts. So many designers are content with the classical V_{BE} multiplier as bias generator. However, the accuracy needed for utmost performance (in terms of cross-over distortion and quiescent dissipation), cannot be provided by such a circuit, even when it is thermally coupled to one of the output devices. Edmond Stuart explains

Several factors may contribute to the lack of accuracy:

- 1) Mismatch between relative temperature coefficients of mosfets and bjts as consequence of the variability of the gate threshold voltage as well as the temperature coefficient of V_{GS}
- 2) Thermal delay and attenuation of the coupling between output device and sensing element.
- 3) Drivers - if included - that operate at a different temperature.
- 4) Long-term drift of threshold voltages as a result of aging¹.
- 5) Errors in adjusting the bias level

for each individual amplifier.

So it seems natural to replace the V_{BE} multiplier - which in fact provides a kind of error feed forward² - by a control loop based on feedback of the bias current itself. In the past, several attempts has been undertaken in this direction, but none of them seem to me suitable for high-end applications, as they are intrusive also on other parts of the amplifier. This could raise distortion^{3,4}, complicate HF compensation^{5,6} or be incompatible^{3,4,5} with a complementary source follower arrangement (which I prefer), or


could be too complex⁷. Nevertheless, reference 5, ingenious in its own right, inspired me to a re-design that overcomes these shortcomings.

The new design comprises three sections: a bias current sensor, an isolator and an integrator. Each of them will be discussed below in detail.

Bias sensor

The bias sensor's purpose is to detect any deviation from the nominal bias level without being influenced by the current distribution over the output transistors, i.e. independently of the

Fig. 1. Circuit diagram of the autobias generator connected to a typical mosfet output stage

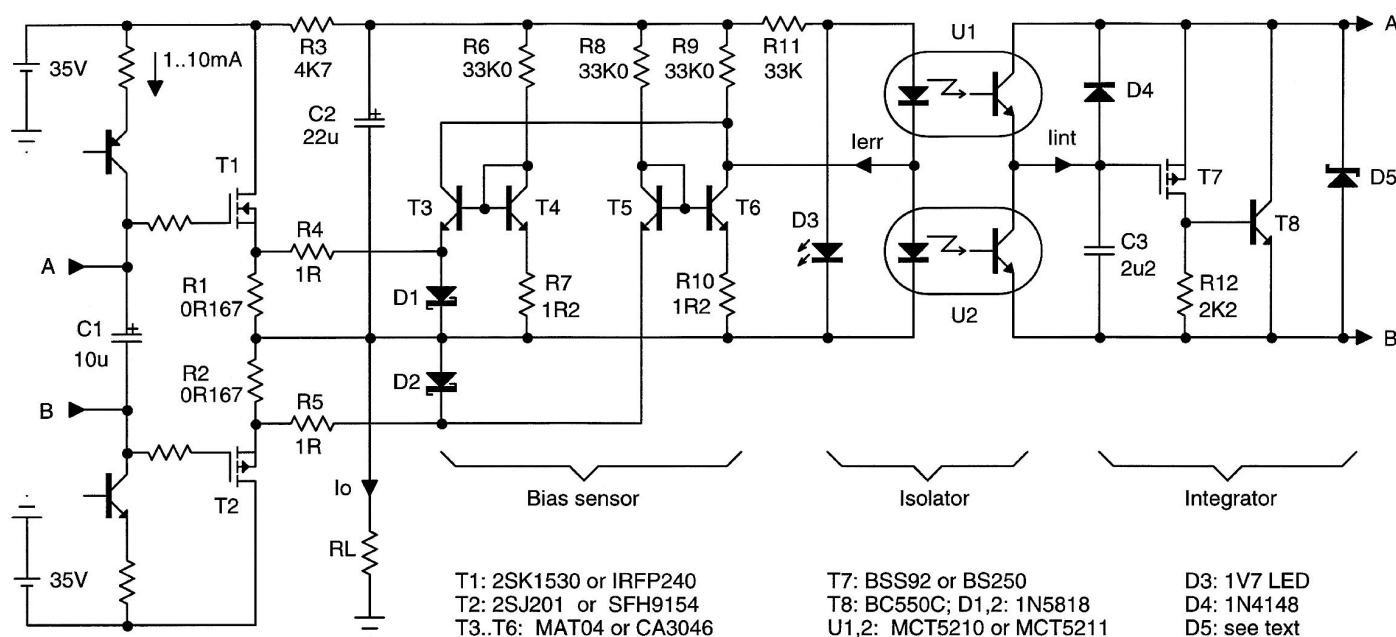

current delivered to the load (R_L). This is accomplished by sensing the voltages across the source resistors of the output stage and passing them to a non-linear network, comprising two current mirrors (transistor pairs $T_{3,4}$ and $T_{5,6}$ respectively). Two equal reference currents are supplied to the inputs of the mirrors via R_6 and R_8 . Since the voltage across each source resistor adds an off-set to V_{BE} of T_3 and T_6 , the currents reflected by them will be lower than the reference.

Under quiescent conditions, this offset is such that each mirror reflects only 50% of the reference current. As dictated by the laws of physics*, this condition is met if the offset voltage is 18mV (at room temperature). Together with R_1 and R_2 , this 18mV defines the quiescent current of the output stage (e.g. 100mA if

$R_1=R_2=0.18\Omega$). To maintain this condition the reflected currents are summed together and subtracted from a third reference current supplied by R_9 . The resulting difference, I_{ERR} , tells us whether the output stage is under, correct or over biased, thus I_{ERR} can be used as a feedback signal, **Fig. 2**.

Next, what happens in the presence of small or medium signals? This is illustrated by the middle curve of **Fig. 3**. It shows the relationship between error signal and output current at the nominal bias level. As one can see, the crux is that *the error signal stays very close to zero*. Apparently, the non-linear behaviour of the mosfets, in particular in their weak and moderate inversion region, matches the characteristics of the bias sensor quite well. The other curves show the error signal if the output stage is forced to

an under - or over biased state. Beyond output currents of ca. 0.6A the error signal is pinched off. This looks like a disadvantage, but it turned out to be beneficial, as explained below.

Finally, what happens in the presence of large signals? Suppose T_1 carries a large current and T_2 is turned off. In this case the reflected current in T_3 is zero, while in T_6 it is 100%. Summed together and subtracted from the third reference, the resultant error signal is again zero. This is exactly what we want, as an output stage operating in class B provides no information about the quiescent current, thus the error signal has been pinched off in order to preserve the charge of the integrator's capacitor (C_3).

Since music has a high peak/average ratio - some 20dB - the average signal level - even at maximum volume - is well within the capture range of the bias sensor. Sine waves at full power give no trouble either, as the relative time traversing the capture region is long enough to let the control loop do its work. However, a large square wave pushes the output stage continuously in class B and no error signal is produced at all, leaving the integrator in an undefined state.

Isolator

To avoid any adverse interaction between common mode and differential signals at the gates (node A and B), an isolator has to be inserted somewhere inside the servo loop. Putting it between bias sensor and integrator greatly simplifies the circuit, as the integrator can now simply use the bias voltage as supply. Given the bipolar nature of the error signal, two opto-couplers (U_1, U_2) are needed, one for charging, the other for discharging C_3 . They are specified for operating at low currents (<1mA). Apart from their primary task (isolation), they serve one more purpose: masking the tiny deviations of the error signal, as can be seen at the middle curve of **fig. 3**. The reduced transfer ratio at very low currents from which any opto-coupler suffers (see **Fig. 4**), meets this purpose nicely. R_{11} delivers the supply voltage to U_1 , while being limited by LED D_3 reducing V_{CE} of T_3 and T_6 to approximately the same level of T_4 and T_5 and preventing simultaneous conduction of U_1 and U_2 .

Integrator

Depending on the mosfets actually used, bias voltage can vary from 2 to 10V. To handle this range it leads

 


Fig. 2. Simulated error signal as function of bias current
($I_{REF}=1mA$, $R_{1,2}=0.167\Omega$, $R_L=\infty$).

 


Fig. 3 Simulated error signal as function of output current at bias levels (from top to bottom) of 60, 90, 120, 150 and 180mA. Notice that at 120mA this signal stays close to zero.

almost automatically to the kind of topology, as shown in fig. 1. In spite of its simplicity, this integrator, or to be more precise - integrating shunt regulator, exhibits a dynamic output impedance that is low enough ($<2\Omega$) to cope with AC currents from the driver stage. In order to exclude interaction at AF, integrator capacitor C_3 is rated such that the unity gain frequency of the servo loop falls below the audio spectrum, somewhere between 1 and 10Hz, depending on transfer ratio of the opto-couplers. D_4 discharges C_3 during switch off and protect the gate of T_7 . For reliable operation, low leakage at the integrator input is essential, so D_4 should be protected from light. Zener diode D_5 is rated at the maximum expected bias voltage plus a small margin and should be adapted to fit a particular design. If some component fails or if nasty test signals have been applied, this diode protects the output stage against excessive common mode currents.

Accuracy

The bias level is very sensitive to mismatches of the transistors pairs and reference currents. Base-emitter voltages T_3 and T_4 respectively T_5 and T_6 should match at least within 0.5mV. A quad transistor like a MAT04 or CA3086, selected on low V_{os} , meets this requirement. For the same reason, R_6 , R_8 and R_9 should match at least within 0.5% as well as the equivalent emitter series resistors; hence R_7 and R_{10} are rated slightly higher than R_4 and R_5 . Since a MAT04 is equipped with small reverse connected diodes between base and emitter, Schottky diodes D_1 , D_2 are added to protect them.

Now we come to a moot point: the voltage of 18mV across R_1 and R_2

which all relies upon, varies linear with the absolute ambient temperature*. Of course, it varies much less than the junction temperature of the output devices and thermal runaway is precluded, but still it is not constant. It is not yet clear to me whether this should be regarded as flaw or feature, as one could argue that the decreased transconductance of mosfets at elevated temperatures just needs an increased bias level. Interestingly, a bias control IC from Linear Technology⁶ shows the same temperature dependence, which could not be explained by an inherent shortcoming of the basic circuit. So I concluded that this property has been added on purpose. Asking why, Linear Technology was unable to give a satisfactory explanation. If anybody could shed light on this

* $V_{BE} = V_T \ln 2$, where $V_T = kT/q$, the thermal voltage (25.86mV at 300K).

matter, please let me know.

Experimental results

To see if the circuit is generally applicable, I tested it on several combinations of mosfets, all capable of delivering 12 to 20A, but of different types and brands. To minimise temperature effects, measurements were done at a reduced supply voltage of 2x16V, the mosfets mounted on a large heatsink with forced air cooling and at a frequency of 1kHz. Static measurements were done at an even lower voltage, 2x7.5V. Since these were very time consuming, I have done this only in case 1 and 2.

In the first instance, dynamic behaviour of bias current was observed by means of an oscilloscope, but changes at various output levels were hardly visible and difficult to quantify, except in case 1, which showed an increase of 5% at maximum output power. Instead, I

 


Fig. 4. Transfer function of the isolator.

Ripple amplitude of the error signals measured at $V_O = 8V_{pp}$ and 1kHz as well as estimated ripple on bias voltage (V_{RPL}) at 20Hz.

Case	Type	Manufacturer	$R_L (\Omega)$	$I_{ERR} (\mu A_{eff})$	$I_{INT} (\mu A_{eff})$	$V_{RPL} (mV_{eff})$
1	IRFP240 IRFP9240	Int. Rectifier Idem	4 ∞	15.9 62.4	3.3 157.0	12.9 568
2	2SK1530 2SJ201	Toshiba Idem	4 ∞	4.9 3.2	<0.1 <0.1	<0.4 <0.4
3	IRFP240 FQA12P20	Intersil Fairchild	4 ∞	14.2 5.0	1.3 <0.1	4.7 <0.4
4	IRFP240 SFH9154	Intersil Fairchild	4 ∞	7.2 5.6	0.2 <0.1	0.8 <0.4
5	FQA19N20 FQA12P20	Fairchild Idem	4 ∞	11.6 5.1	0.7 <0.1	2.5 <0.4

used a DVM to measure the ripple amplitude of the error signal before and after the isolator under load and no load conditions. Next, I estimated the ripple-on-bias voltage at 20Hz, according to $V_{RPL} = I_{INT} / (2 \pi f C_3)$, instead of a direct measurement at 20Hz, because thermal modulation could be disturbing. See table for results.

The first trial was rather disappointing, not to say confusing. The error-function, **Fig. 5**, is heavily skewed and ripple currents are high (see table, case 1). Transconductances were reasonably matched - within 20 %, so something else spoiled it. It appeared that the output conductance (G_{OS}) of the IRFP9240 was the culprit. At a drain current of 125 mA, G_{OS} is about 5mA/V, while the IRFP240 shows a G_{OS} of only 0.4mA/V (corresponding to an Early voltage of 25V and 312V

respectively). So an increase of output voltage of 1V -without load- will increase the quiescent current by 4.6mA. No wonder that the error function is skewed. At higher drain currents the IRFP9240 behaves better: at 1A for instance, the Early voltage raises to ca. 75V. This explains why the ripple on I_{ERR} becomes much smaller when the output stage is loaded with a low impedance.

However, speaker impedances are not always that low - at resonance up to tenfold, so a no load condition has also to be taken into account. Without blaming the manufacturer, I cannot recommend this mosfet pair. After all, these devices were designed for switching, not for driving loudspeakers.

In the next trial I used a complementary pair from Toshiba, especially intended for linear applications: 2SK1530 and 2SJ201.

Due to closely matched transconductances (within 5%) and high Early voltage (over 300V) for both N- and P-channel parts, the results were far better. The error function, **Fig. 6**, is in accordance with the simulation, although skew is slightly higher and in the opposite direction. Ripple currents were hardly measurable.

In the last three cases I tested several other samples (courtesy of Fairchild) which are less expensive, but, as in case 1, primarily targeted for fast switching. Results were almost as good as in case 2 and I see no reason not to use these mosfets, except that the higher gate threshold voltage reduces the maximum output power somewhat, that is, without using a boosted power supply for the drivers.

I have also investigated a few combinations of two 20A N-channel and three 12A P-channel devices. Because no improvements were seen, I will not discuss them any further. Using bjts instead of mosfets will probably not work at all, as Spice simulations were very discouraging. For lack of Spice models, lateral d-mosfets have not been investigated.

Conclusion

Provided that output devices are selected with some care, in particular with regard to trans- and output conductance, the proposed circuit comes up to all expectations. Since the circuit acts only on the bias voltage and is not intrusive on any other part of the amplifier, it should be easy to incorporate into new or existing designs like mentioned in ref. 8 and 9.

References

1. Finnegan, T, 'Going linear with power mosfets, part 2', *EW*, Sept. 1992, p.781.
2. Self, D, 'Thermal dynamics in audio power', *EW*, May 1996, pp. 410-415.
3. Roehr, W., 'The autobias amplifier', *JAES*, April 1982, pp. 208-216.
4. Siliconix, 'Mospower Application Handbook', Chapter 6, pp.105-110
5. Gevel, M. van de, 'Audio power with a new loop', *EW*, Feb. 1996, pp.140-143.
6. Datasheet LT1166, Automatic bias system, Linear Technology.
7. Brown, I., 'Opto-bias basis for better power amps', *EW+WW*, Feb. 1992, pp. 107-109
8. Hitachi Mosfet Handbook, Section 6.1, pp. 143-151.
9. Stochino, G., '300V/ μ s power', *EW*, April 1997, pp.278-282

Fig. 5. Same as fig. 3, but measured on a IRFP240/IRFP9240 pair at bias levels of 57, 85, 118, 142 and 171mA.

 


Fig. 6. Same as fig.5, but measured on a 2SK1530/2SJ201 pair.

