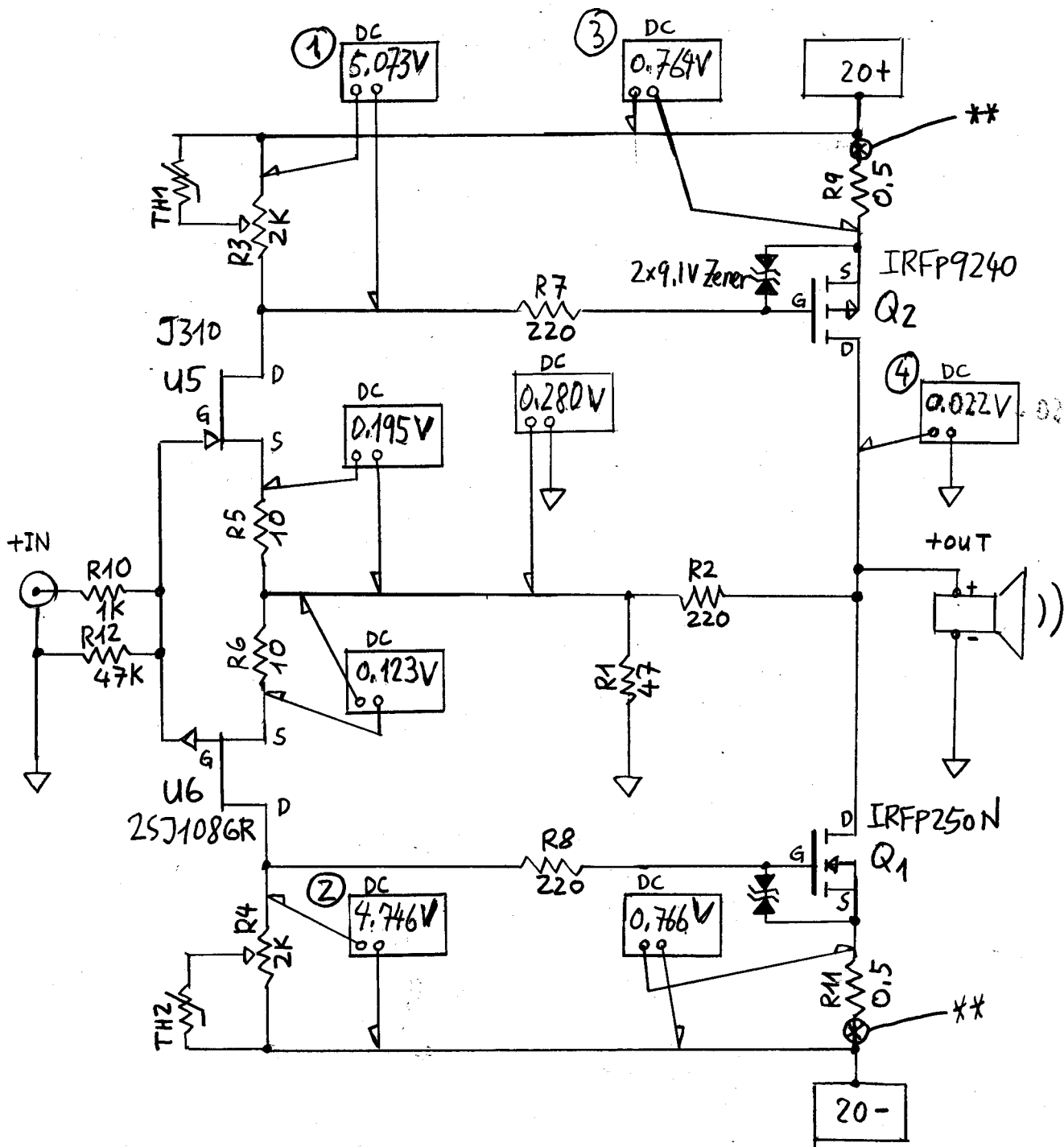


» Babo Zen «
Nelson Pass - ZV5 w. JFET Inputs

✓KY 25 Mar 2007



NB,
-R9&R11 5W wire-wound

- Open the points marked "x"

Adjust R3 & R4 to get about 4V at ① & ②

Connect the points marked "x".

Adjust R3 & R4 to get about 4V at ① & ②
Connect the points marked "x x"
Adjust R3 & R4 to get 0,75V at ③ and ~0V at ④

Adjust R3 & R4 to get 0.75V at ③ and ~0V at ④