

Active Speakers and Amplifiers

COMPONENTS

-  Amplifiers
-  Active Crossover
-  Control Circuits

Active Speakers and Amplifiers

Most people own an active speaker system

 Subwoofer

 Computer Speakers



Active Speakers and Amplifiers

ADVANTAGES

- Too many to list
- Dynamic range, peak power
- Efficiency
- Small, inexpensive XO components
- Greater control of driver dynamics
- No speaker cables
- Absence of XO interactions

Active Speakers and Amplifiers


The Gain Clone

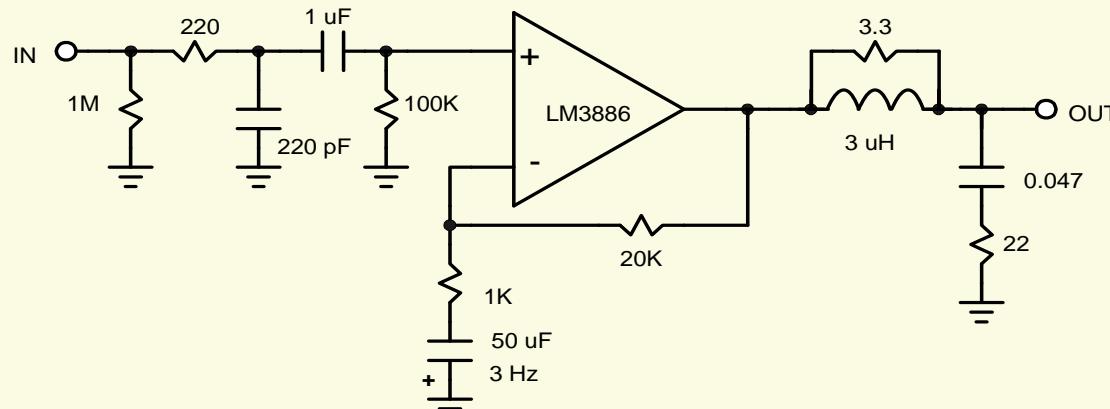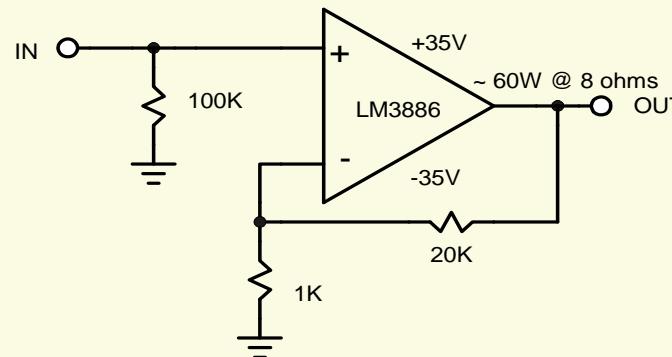

R. R. Cordell 05/14/04


Active Speakers and Amplifiers

INVERTING GAIN CLONE WITH SMALL CAPS

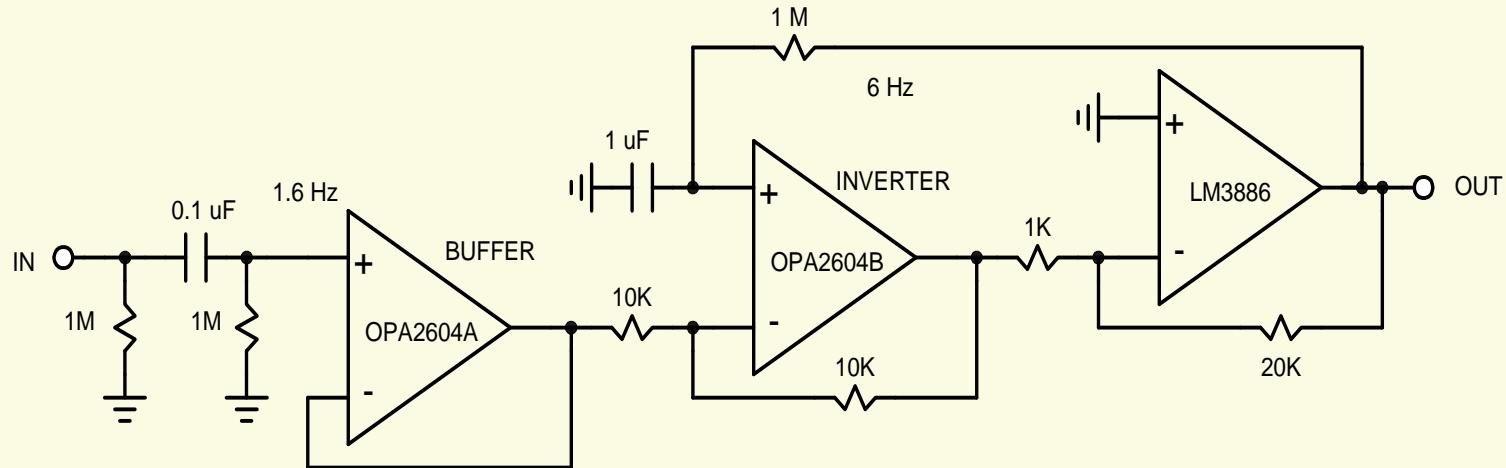

Active Speakers and Amplifiers


INVERTING SUPER GAIN CLONE

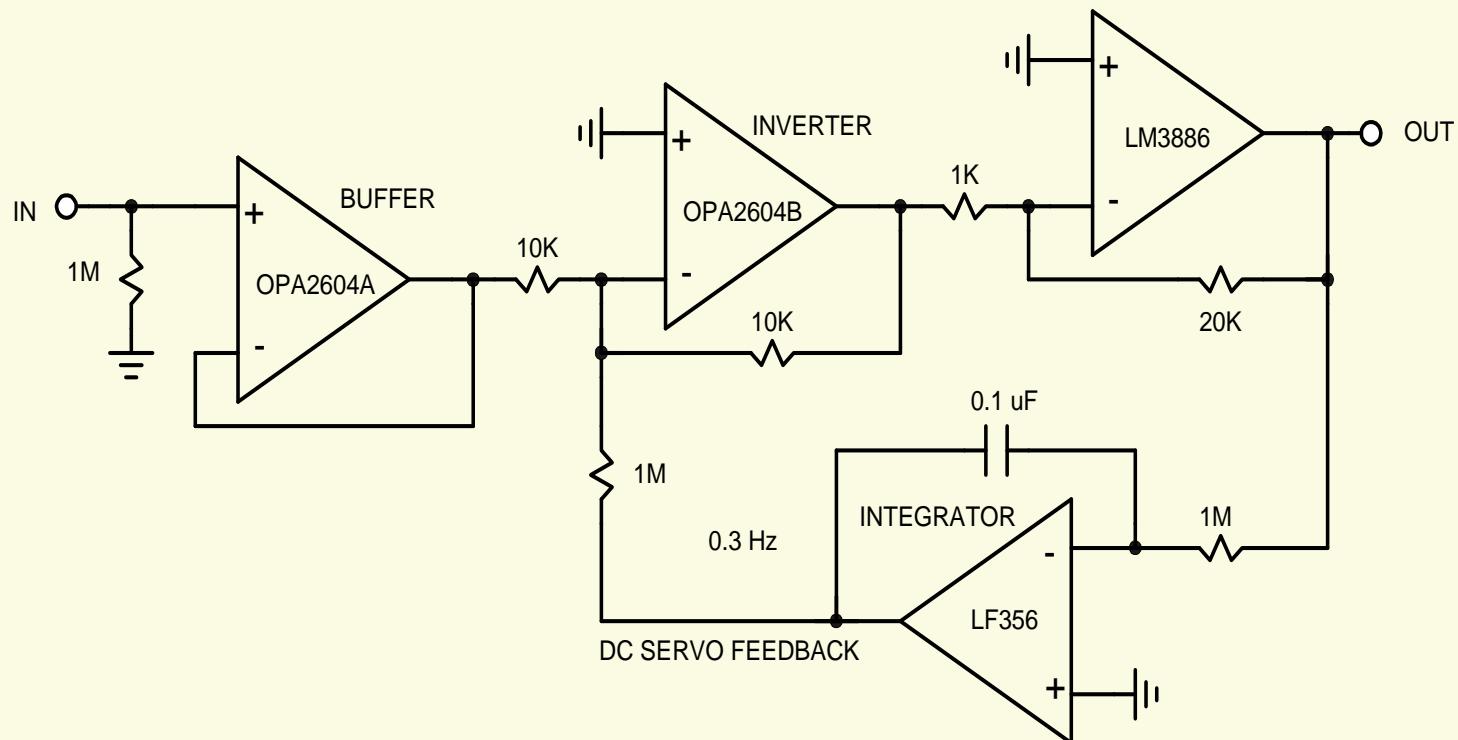


R. R. Cordell 05/14/04

Active Speakers and Amplifiers

NON-INVERTING SUPER GAIN CLONE



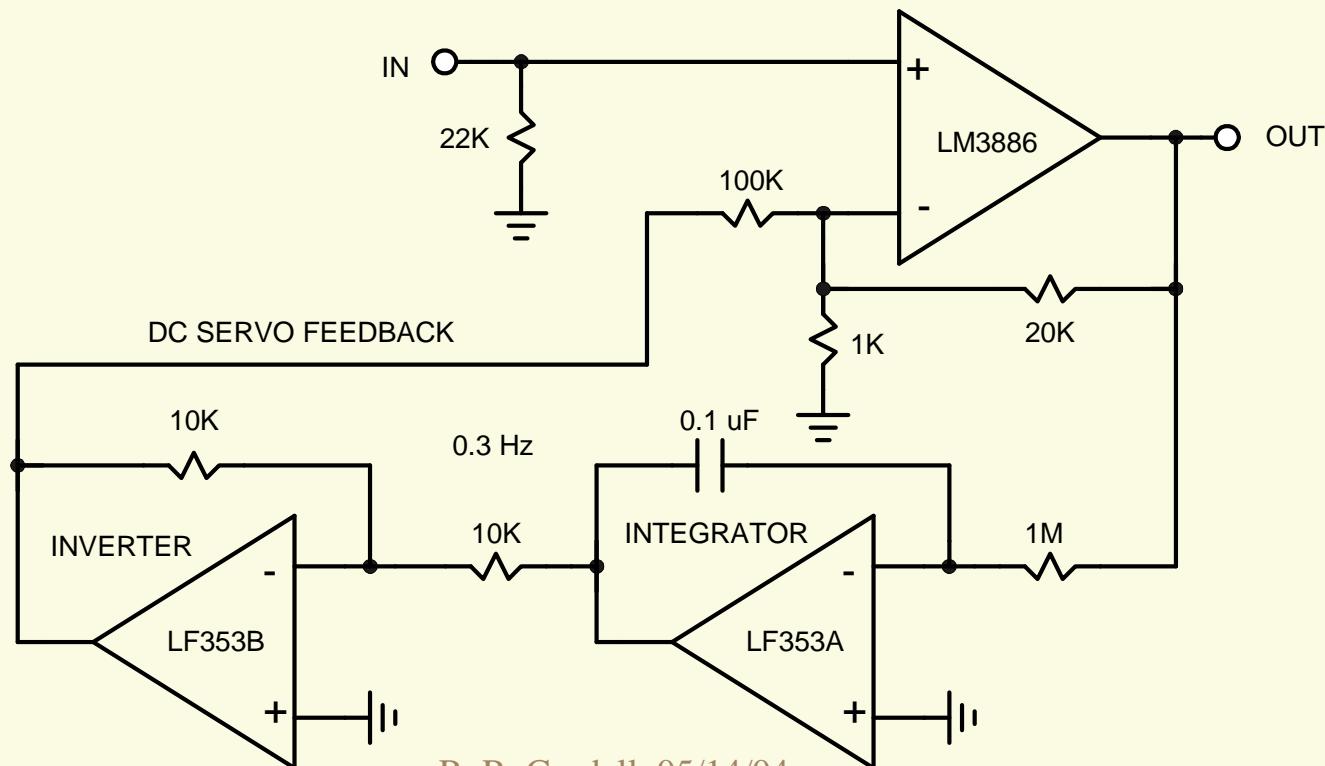


Active Speakers and Amplifiers

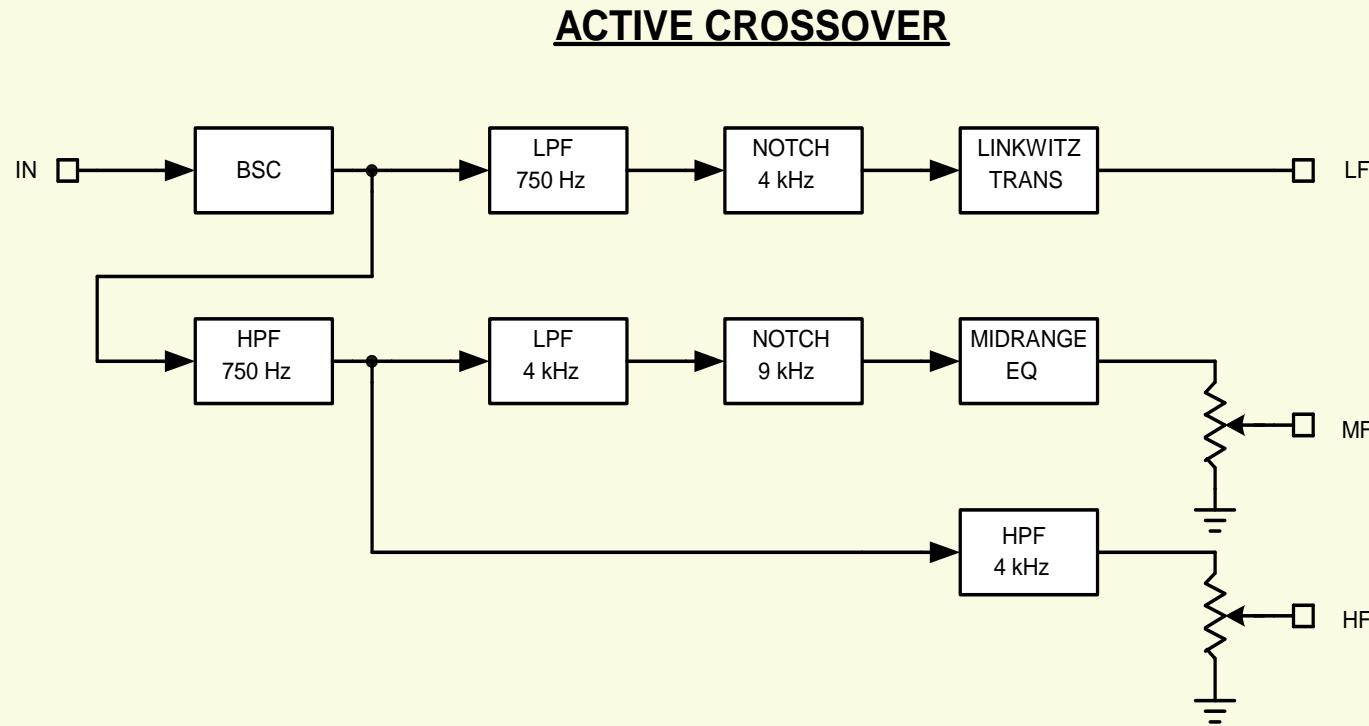


Active Speakers and Amplifiers

Voltage Follower Filters

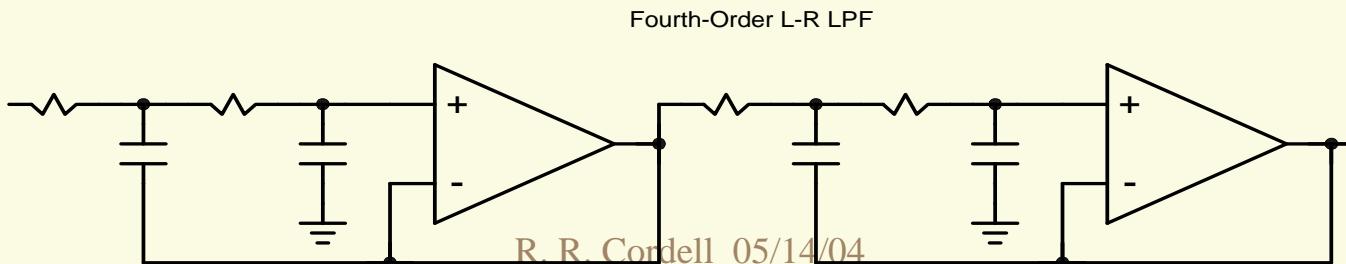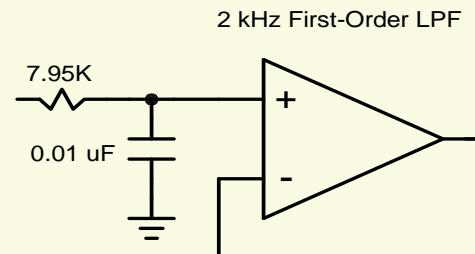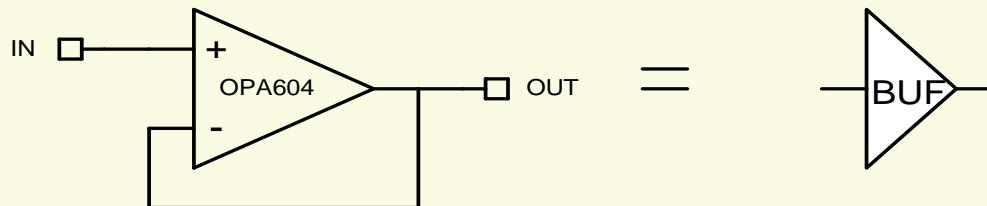

Active Speakers and Amplifiers


Voltage Follower Filters

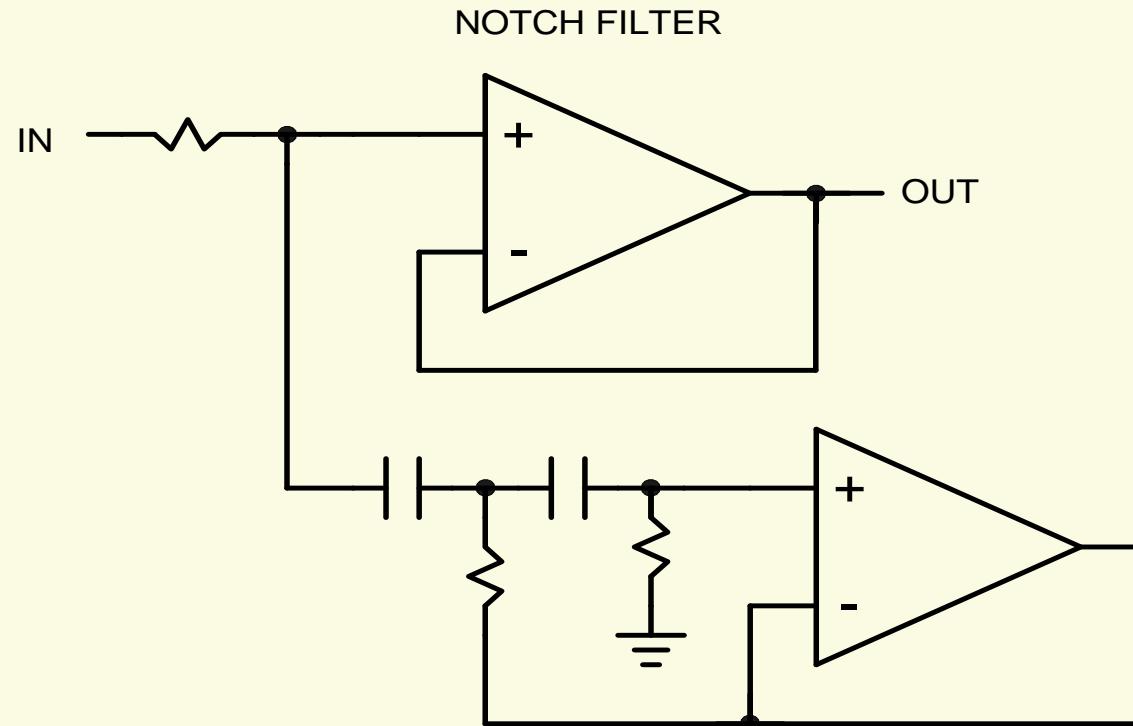

R. R. Cordell 05/14/04

Active Speakers and Amplifiers


ACTIVE BAFFLE STEP COMPENSATION

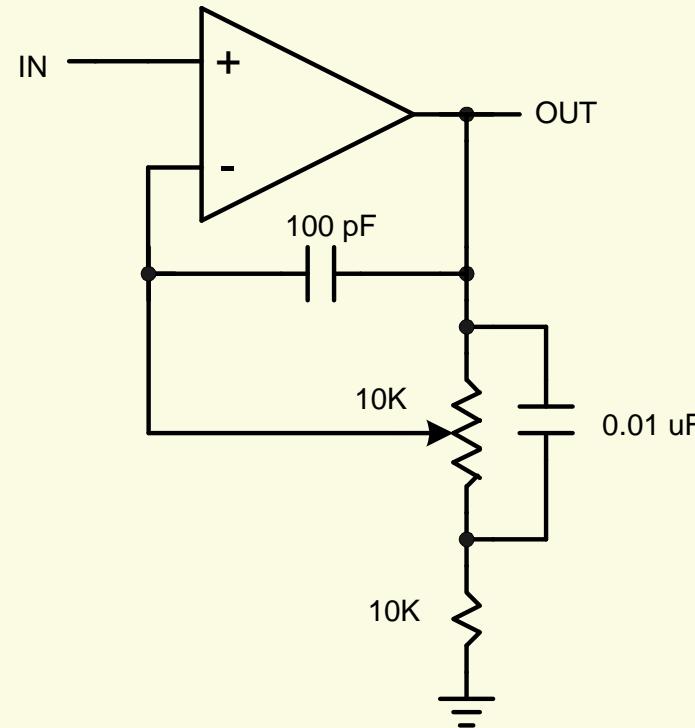

R. R. Cordell 05/14/04

Active Speakers and Amplifiers

Linkwitz Transform

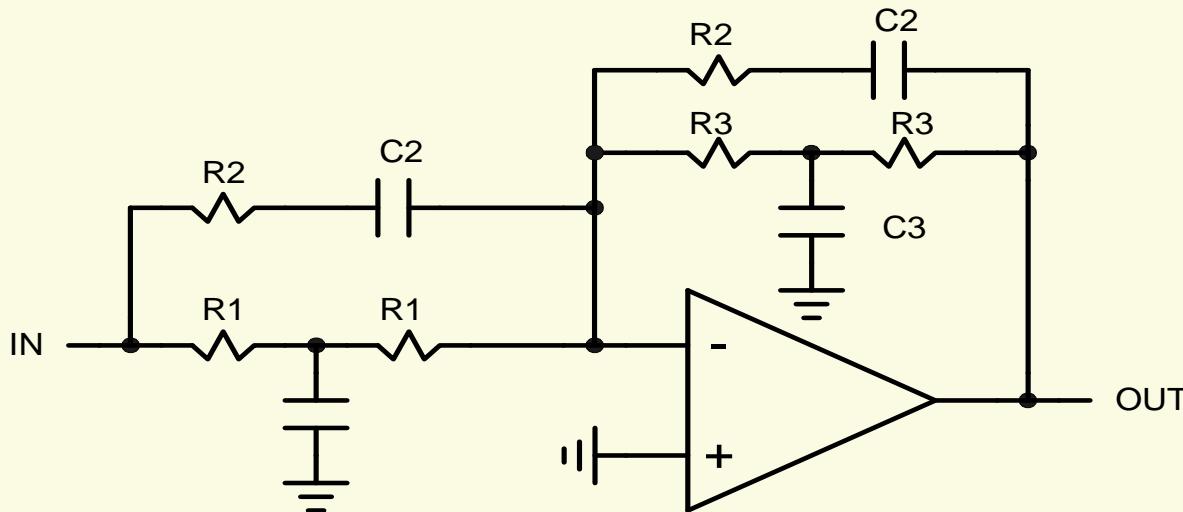

47 Hz, 0.56 → 20 Hz, 0.6

R1 = 14K C1 = 1.0 uF

R2 = 79K C2 = 0.056 uF

R3 = 79K C3 = 0.18 uF