



Build a Distortionless Preamplifier

PREPARING FOR FOUR CHANNEL?
YOU MAY WANT TO USE THIS PREAMP

BY JAMES BONGIORNO

THE ADVENT of four-channel stereo need not necessarily obsolete your present hi-fi system. Regardless of which four-channel system is finally agreed on as a standard, we feel that it's a safe bet that the conventional two-channel front end will remain and the four-channel decoding will take place after this stage. Therefore, it is more important than ever that the two-channel

front end be of the best quality available. In essence, what you need is a noise-free, distortionless, nonoverloading amplifier that will follow the RIAA curve faithfully.

The phono preamplifier whose schematic is shown in Fig. 1 (only one channel is shown) comes as close to this "perfect" preamp as the state of the art permits. It is virtually impossible to overload this unit with

PARTS LIST PREAMPLIFIER

Components common to both channels:

C10—68- μ F, 3-volt 20% tantalum capacitor

D1,D2—1N914 diode

R18—43,000-ohm resistor

S1—Dpdt slide switch

Duplicate components in each channel:

C1,C4—22- μ F, 60-volt, 20% tantalum capacitor

C2—56-pF, 5% polystyrene capacitor

C3—33-pF, 5% polystyrene capacitor

C5—0.47- μ F, 100-volt, 10% Mylar capacitor

C6—330-pF, 5% polystyrene capacitor

C7—5600-pF, 2% polystyrene capacitor

C8—1650-pF, 2% polystyrene capacitor

(1500 and 150 in parallel)

C9—17-pF, 5% polystyrene capacitor

J1,J2—Phono jack

Q1,Q3—2N4250 transistor

Q2—2N5089 transistor

R1,R14,R16—47,000-ohm, 2% resistor

R2,R3—390-ohm, 10% resistor

R4—1-megohm, 10% resistor

R5—62,000-ohm, 5% resistor

R6—Selected (see text)

R7—22,000-ohm, 5% resistor

R8,R17—470-ohm, 2% resistor

R9—681,000-ohm, 1% resistor

R10—3900-ohm, 5% resistor

R11—2700-ohm, 5% resistor

R12—1000-ohm, 10% resistor

R13—2.2-megohm, 1% resistor

R15—2200-ohm, 1% resistor

Note—For miscellaneous items and availability of parts see Parts List for Power Supply. (All resistors are 1/2 watt.)