

Bandpass 2. Another multiple-feedback circuit uses an additional active element to overcome some of the disadvantages of the single-amplifier circuit, especially the bandpass realization for Q 's roughly between 10 and 50. High Q 's realized with bandpass 1 have large spreads of element values and high Q sensitivities to element value changes. The multiple-feedback circuit with positive feedback is shown in Fig. 8.6. The voltage transfer function is

$$\frac{E_o}{E_1}(s) = \frac{s(K/R_1C_4)}{s^2 + (s/R_5C_4)(1 + C_4/C_3 - KR_5/R_6) + (1/C_3C_4R_5)(1/R_1 + 1/R_2 + 1/R_6)}$$

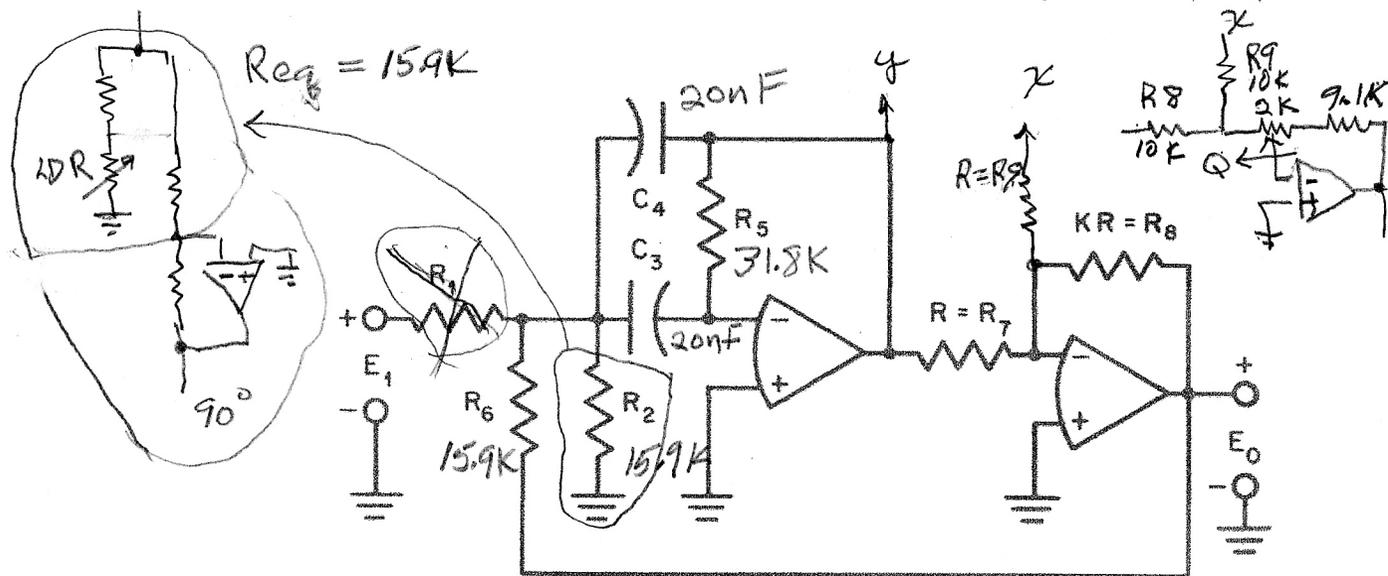


Fig. 8.6 Multiple-feedback bandpass circuit with positive feedback.

$$\frac{y}{x} = \frac{K H_0}{1 - K H_0} \cdot \frac{s \alpha \omega_0 (1 - K H_0)}{s^2 + s \alpha \omega_0 (1 - K H_0) + \omega_0^2}$$

$$H_0' = \frac{K H_0}{1 - K H_0}$$

$$Q' = \frac{1}{\alpha'} = \frac{1}{\alpha (1 - K H_0)}$$