
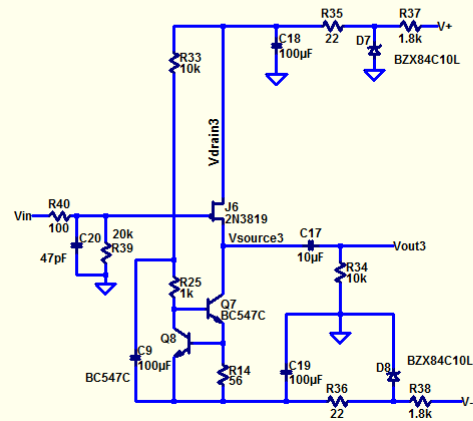



## JFET Basic Buffer

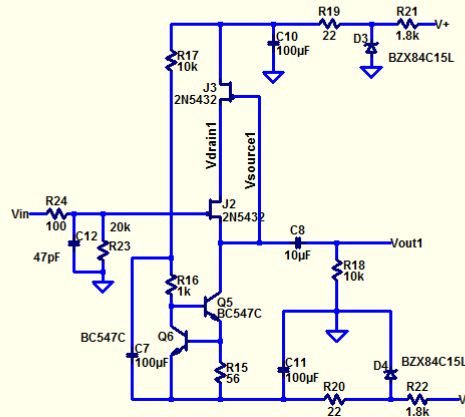



## JFET with JFET Cascode



## JFET with BIP Cascode

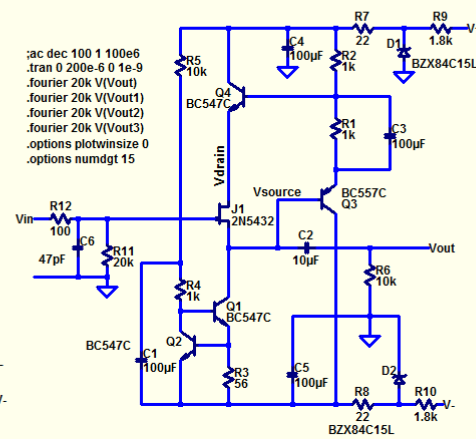

## Reference Buffer

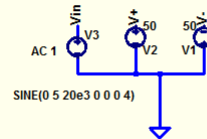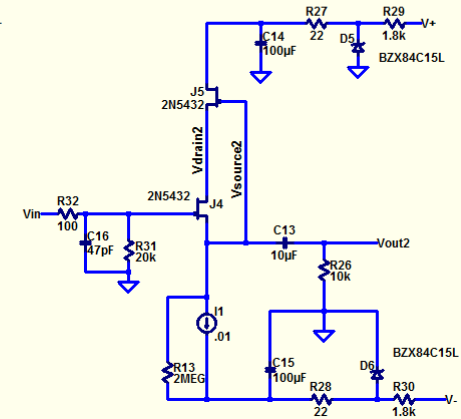

Upper figures 2 V pk into 10k at 20 kHz; lower figures for 5 V pk into 10k

Total Harmonic Distortion: 0.001016%

Total Harmonic Distortion: 0.000522%

Total Harmonic Distortion: 0.000233%

Total Harmonic Distortion: 0.000302%

Total Harmonic Distortion: 0.002549%

Total Harmonic Distortion: 0.001410%

Total Harmonic Distortion: 0.017154%

Total Harmonic Distortion: 0.000853%



Frequency response