
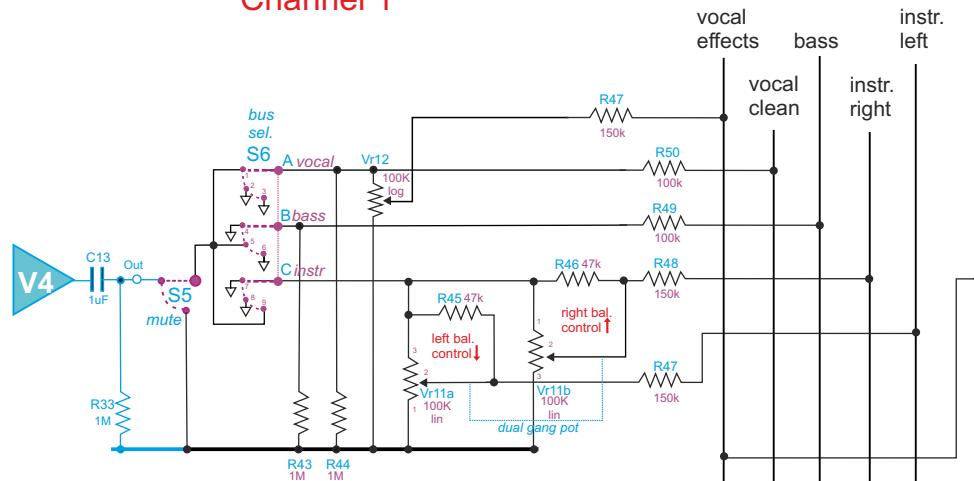


Bus amplifiers


Channel 1

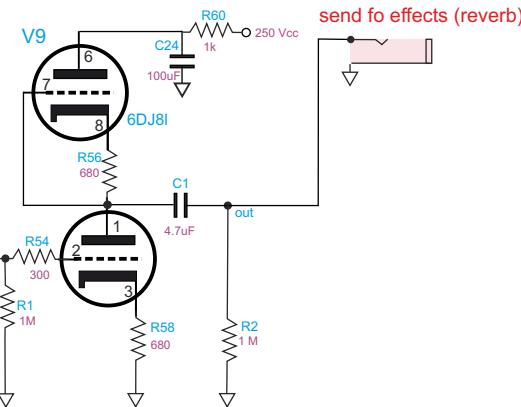

Vocal effects




Vocal clean

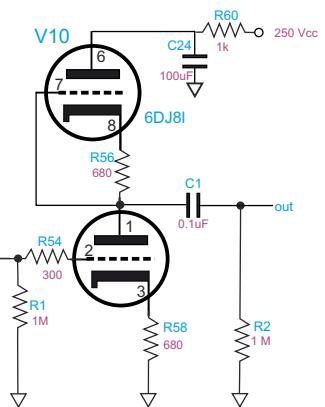


Channel 10


Instrument right

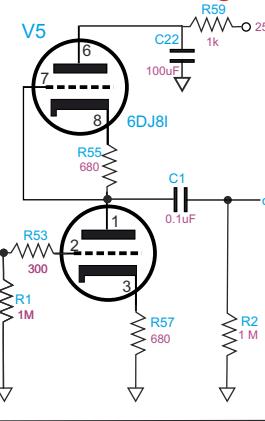

Instrument left

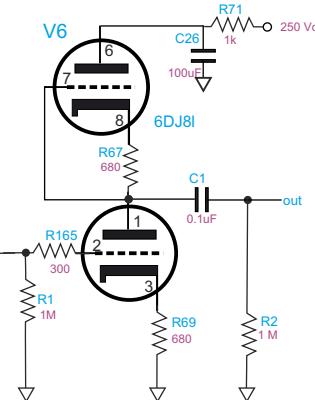

Bass

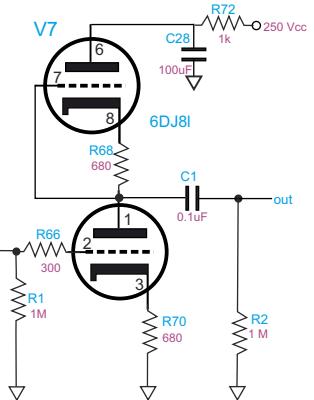

SIMULATION TESTS

Rload of Vocal bus (Vr12 on max) -> 41.7 Kohm (gain= -4.6; 1 V -> 0.218V)
 Rload of Vocal bus (Vr12 on min) -> 52.6 Kohm (gain= -5.7; 1 V -> 0.175V)

Rload of Instr bus (Vr11a on max and Vr11b on min) -> 20.8 Kohm (gain= -8.8; 1 V -> 0.114V)
 Rload of Instr bus (Vr11a and Vr11b on the middle position) -> 30.6 Kohm (gain= -12.7; 1 V -> 0.079V)