



FIGURE 13

The benefits of C_2 are better maintained when the film bypass capacitors are located as close as possible to the amplifier circuit. The slower, low frequency capacitor (C_1) may be located further away because of L 's reduced influence at lower frequencies.