

And here are the schematics. You may adjust the highs to your preference by either increasing or decreasing the 6 ohm tweeter series resistor by an ohm or two. Make sure you reverse the tweeter polarity as shown. The little resistors shown in series with the woofer inductor and the final tweeter series inductor are not real--they are just the suggested dcr of the inductors. All other resistors are really there. You will probably have to order a .10 inductor for the last element in the tweeter circuit, and then unwind a little less than half of the wire. The value is not critical.

