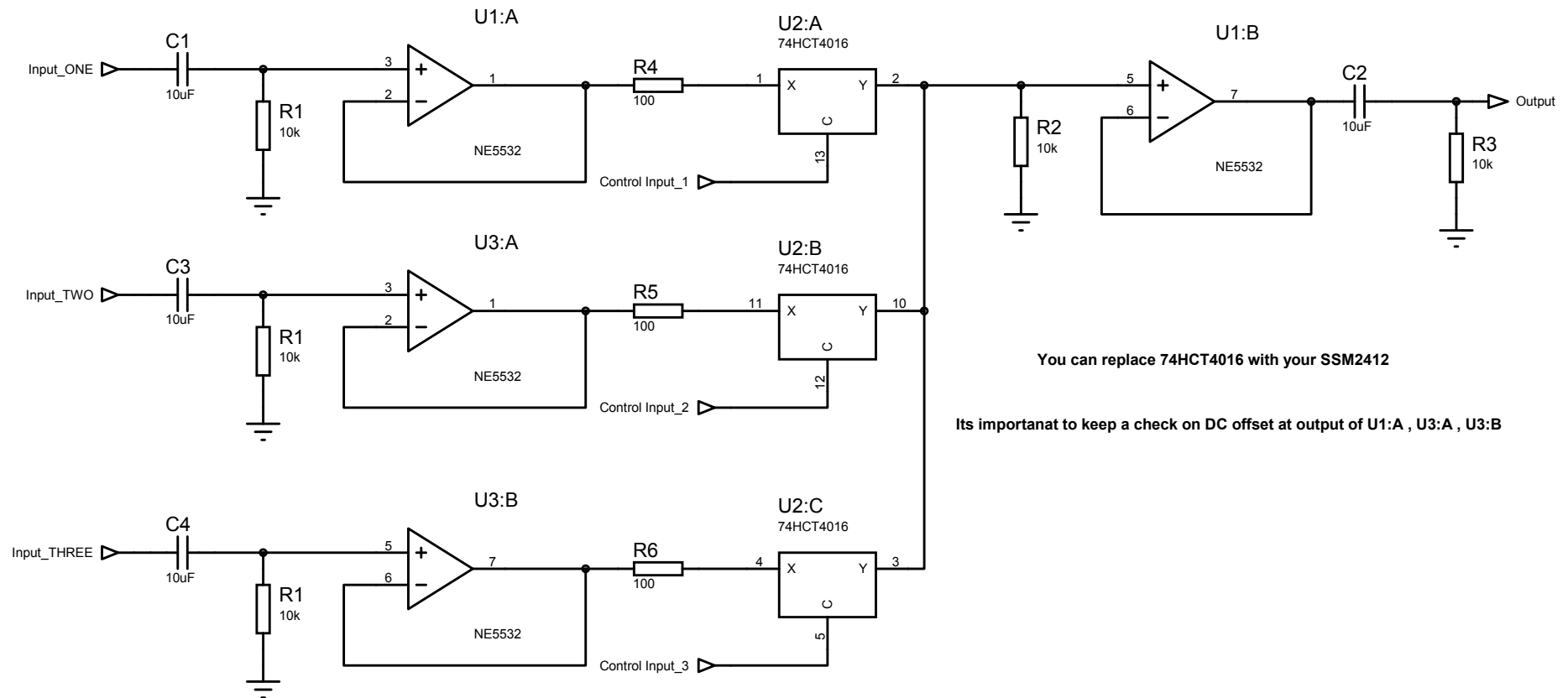


Typical Channel Selector



You can replace 74HCT4016 with your SSM2412

Its important to keep a check on DC offset at output of U1:A , U3:A , U3:B