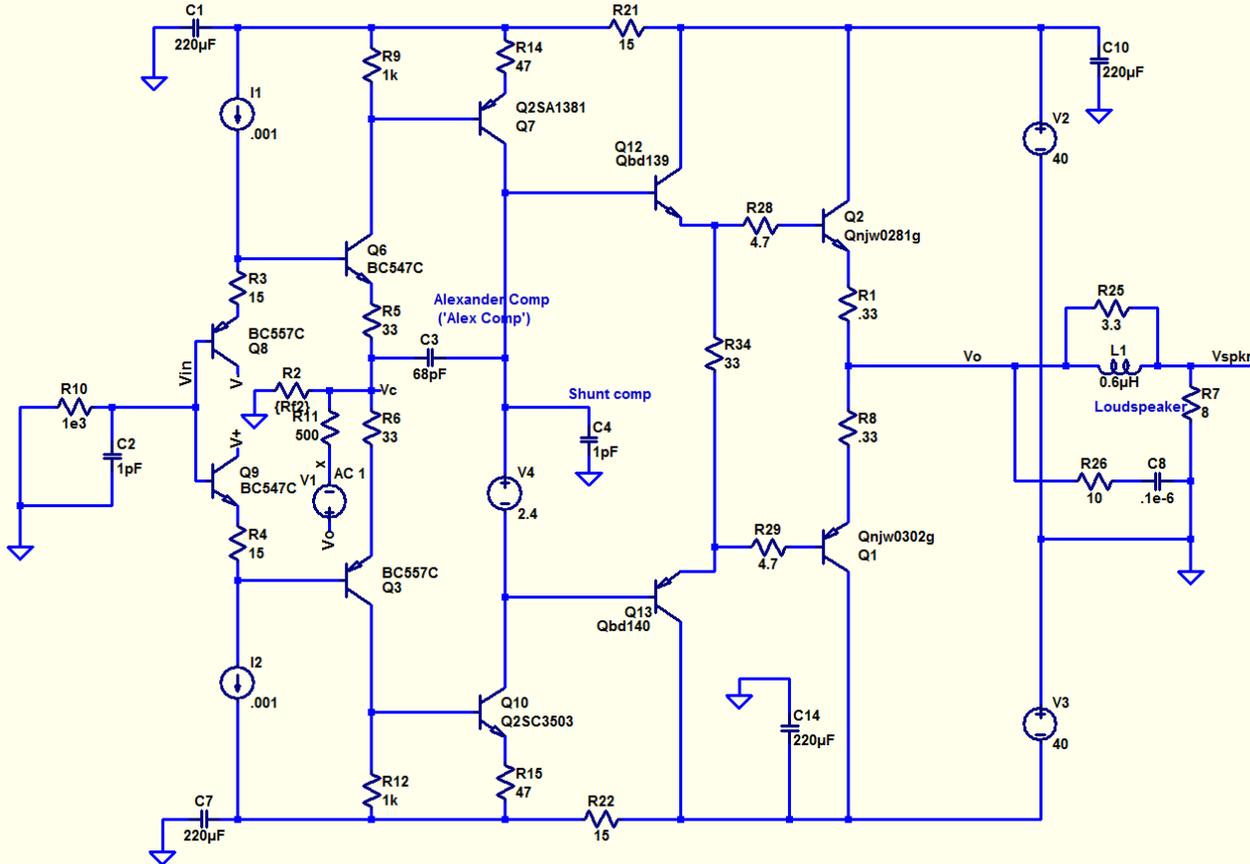


# CLF Study 2

# Basic CFA




## Loop Gain

```
.ac dec 100 1 100e6
.options plotwinsize = 0
.fourier 20k V(Vo)
.tran 0 200e-6 0 1e-9
.options numdgt = 8
.step temp list 0 20 80
```

```
.step param Rset 200 1e6 999800
.options it1=1000
.options it6=1000
.options gshunt 1e16
```


```
.step param Rf2 list 5 10 15 20 25 30
```

# Basic CFA Loop Gain plot

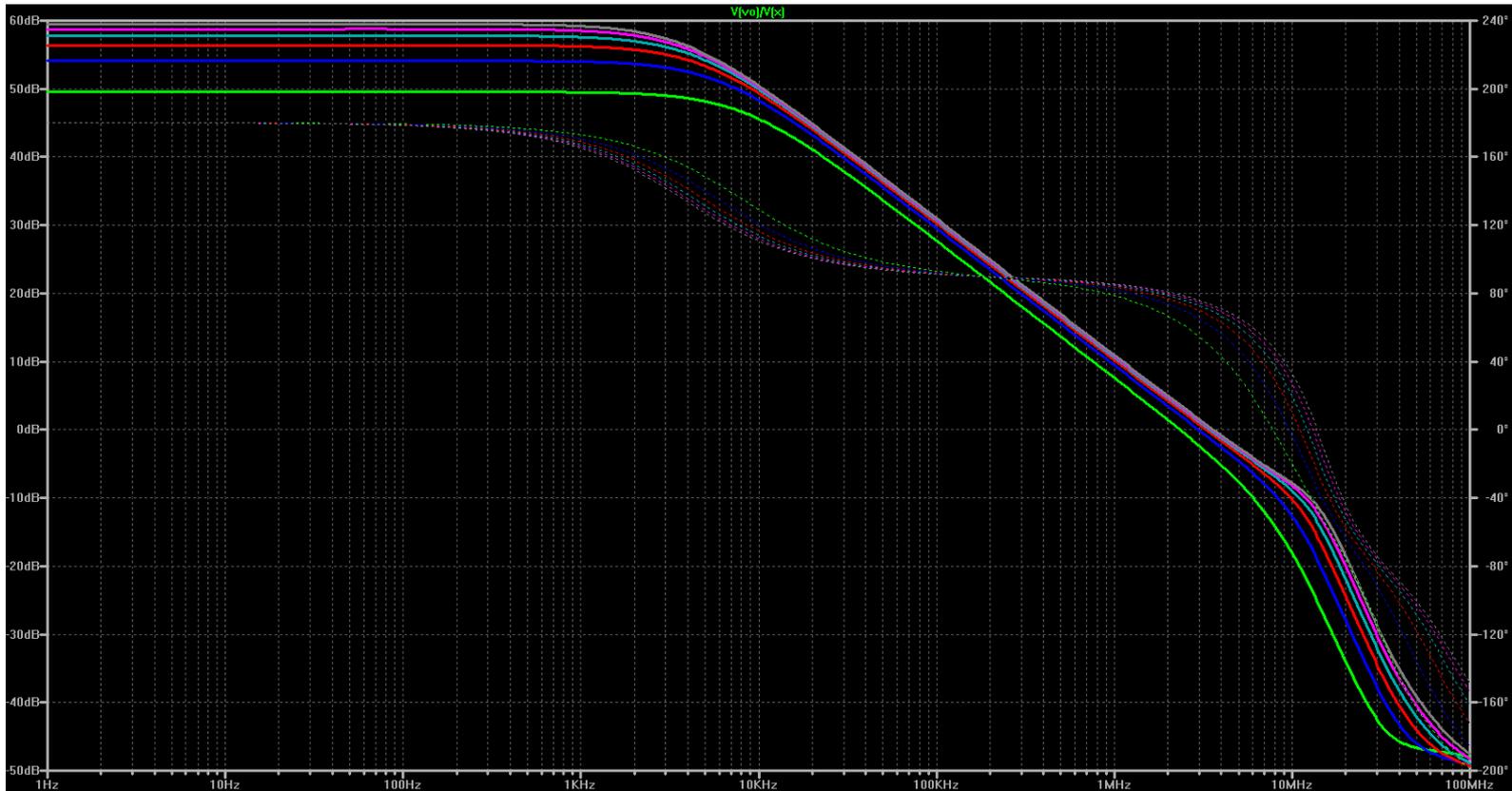

- CL gain stepped from 18x to 101x
- ULGF c. 3 MHz established by selecting C3; R11 could also be used for this purpose, but my view is in a practical discrete audio power amp, its easier to adjust C3

# 'Quick 'n Dirty' CFA with TPC

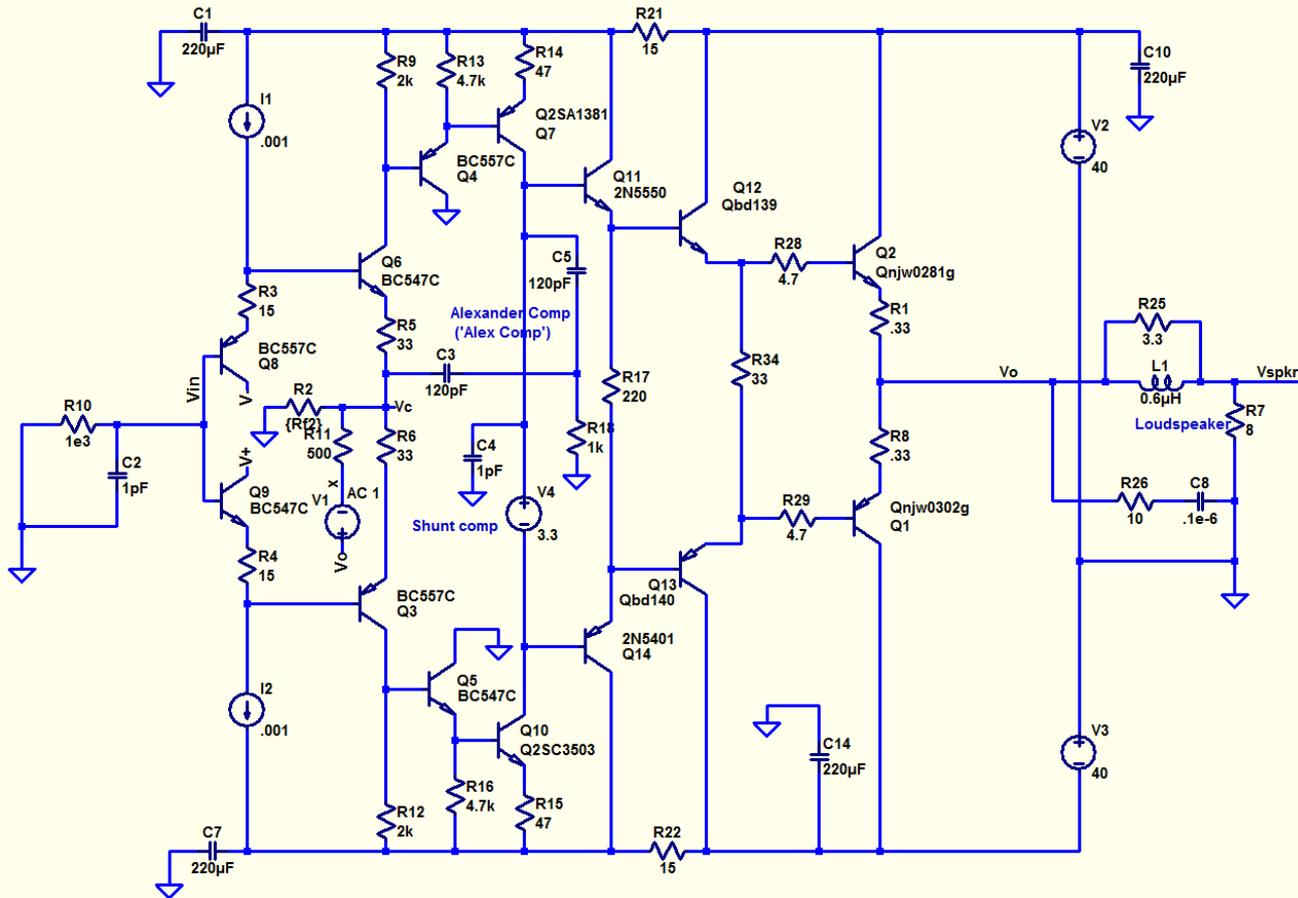

## Loop Gain


```
.ac dec 100 1 100e6
.options plotwinsize = 0
.fourier 20k V(Vo)
.tran 0 200e-6 0 1e-9
.options numdgt = 8
.step temp list 0 20 80

.step param Rset 200 1e6 999800
.options itl1=1000
.options itl6=1000
.options gshunt 1e16

.step param Rf2 list 5 10 15 20 25 30
```

- Added beta enhancers and EF3 (together adding 25 dB loop gain)

# 'Quick 'n Dirty CFA TPC LG Plots

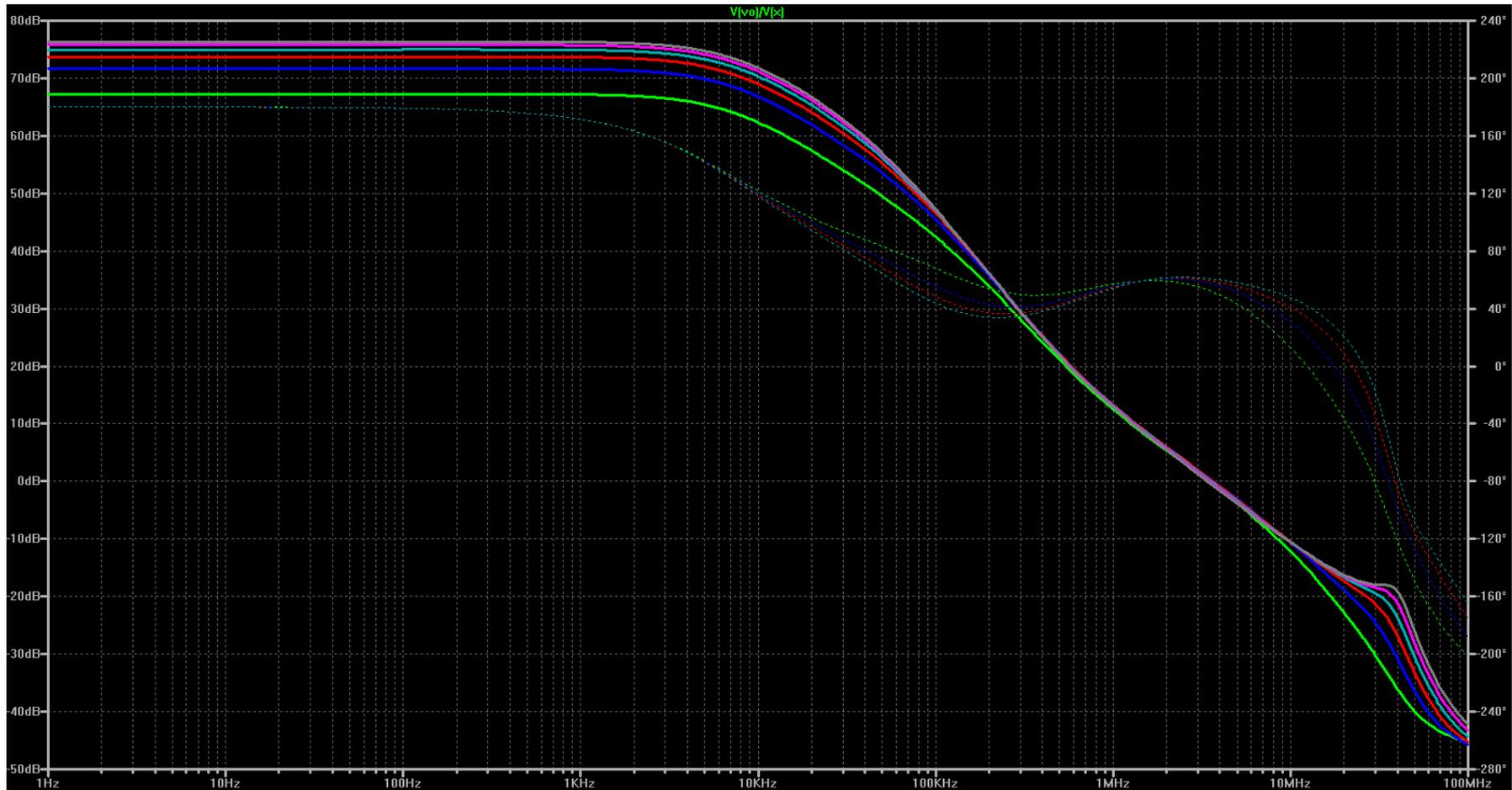

- Even with TPC, -3dB LG point remains fairly constant