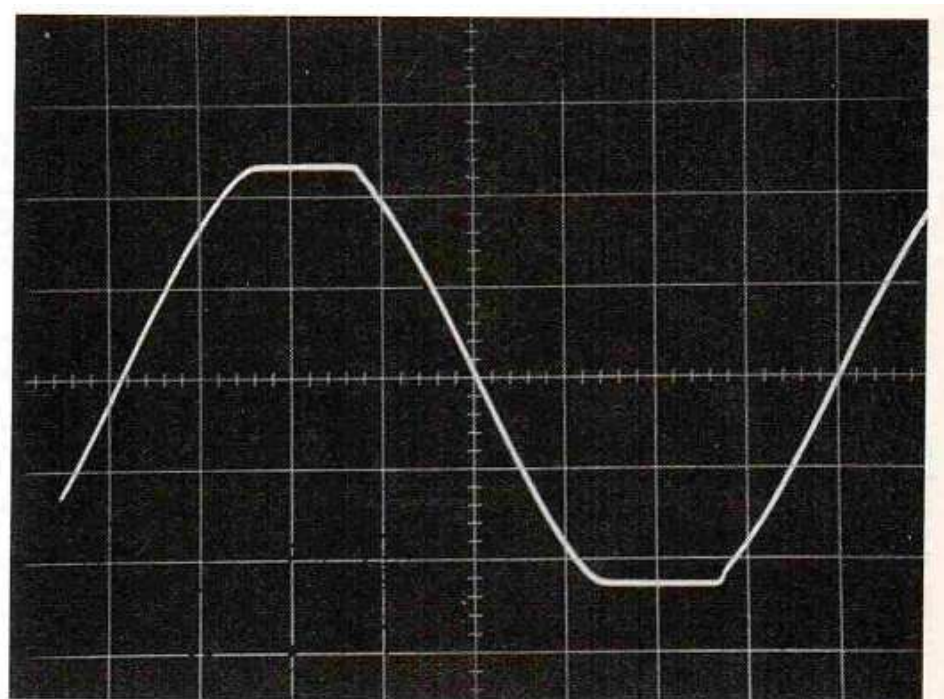


*Fig. 13. Waveform resulting from driving the amplifier at 30W with a 20kHz sine wave illustrates the absence of switching distortion.*



*Fig. 14. Overdrive and recovery waveforms using a 5kHz input signal.*