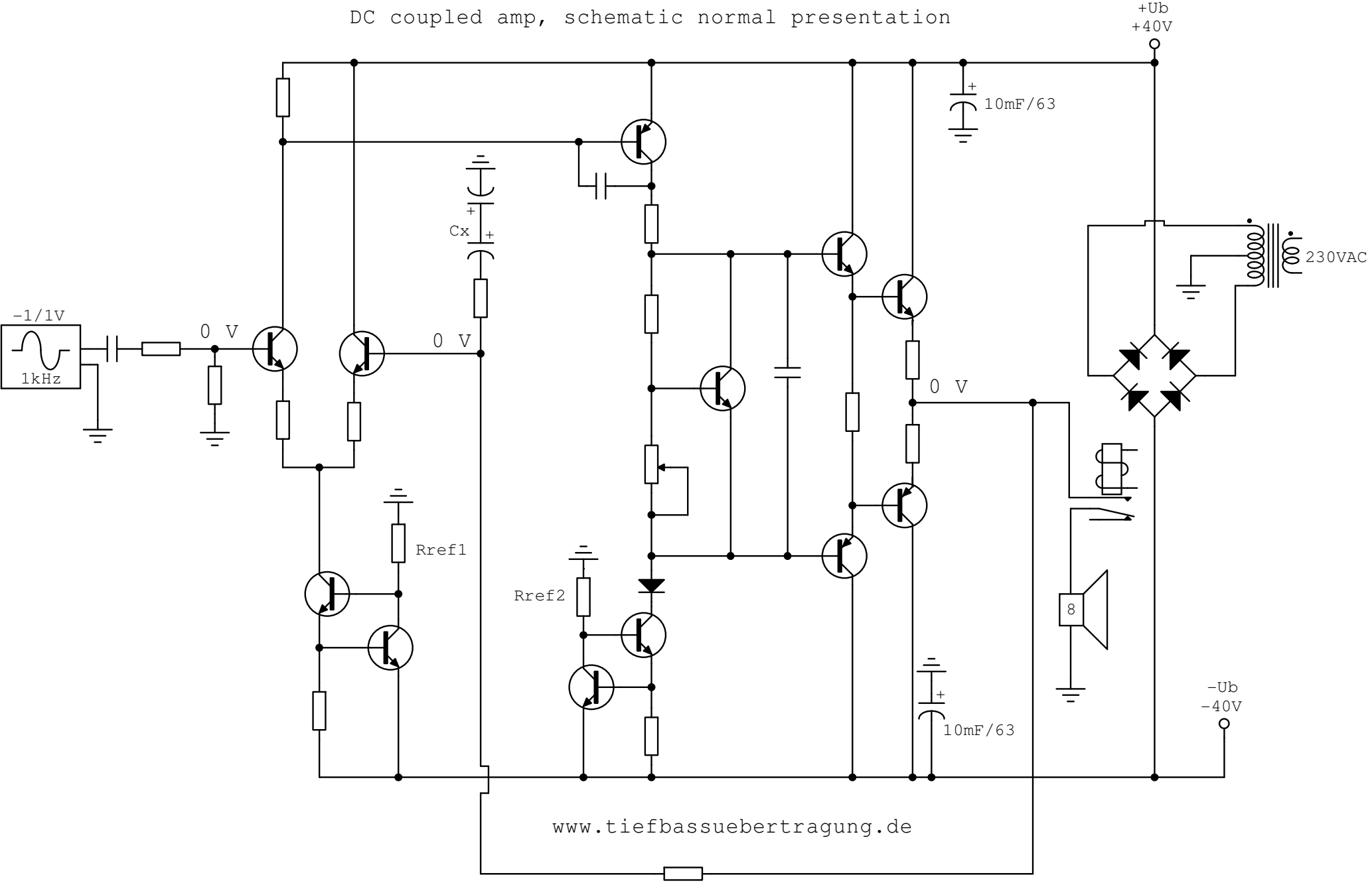
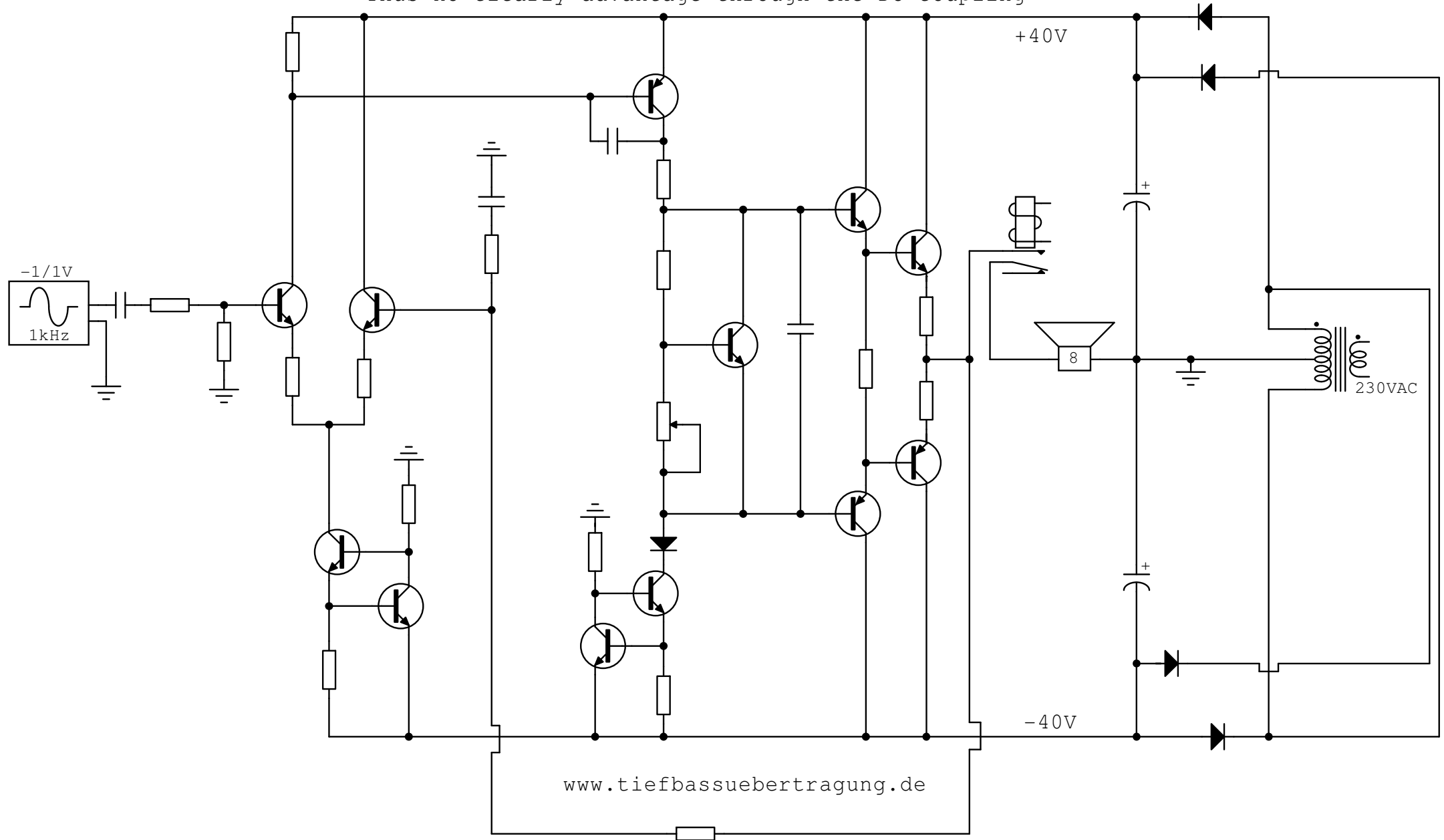


DC coupled amp, schematic normal presentation



DC coupled amp, schematic - presentation for better understanding.
Frequency range between 0 Hz (DC) and the - 3db frequency limit through
the high pass character of the power supply capacitors undefined.
Thus no clearly advantage through the DC coupling



Elimination of the DC-coupling and simultaneously produced DC protection
for existing amplifiers. By the capacitors twice of the voltage essential !!!

