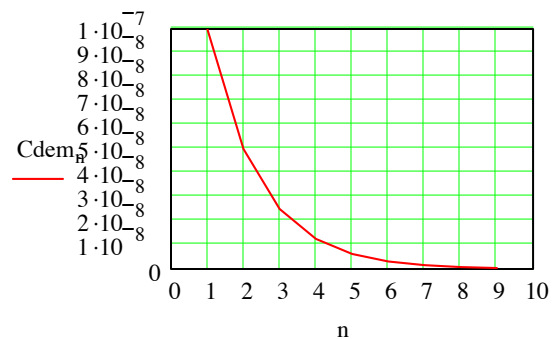


bit := 14	number of DAC bits (TDA1541A=16 TDA1540 = 14)
Iref := 2·mA	current DAC reference
VdvCmsb := 10.5·V	voltage across Cmsb (TDA1541A=7.5V TDA1540 = 10.5V)
wc_percent := 14.2·%	worst case %
Fdem := 176.4·KHz	DEM frequency
DEMbits := 10	number of DEM bits (TDA1541A=7 TDA1540 = 10)

$\text{Bit} := \left\lceil \frac{1}{2^{(\text{bit}+1)}} \right\rceil$	$\text{Bit} = 3.052 \times 10^{-5}$	bit constant
$\text{Iwc} := \left(\frac{\text{Iref}}{4} \right) \cdot \text{wc_percent}$	$\text{Iwc} = 71 \mu\text{A}$	worst case p-p ripplea current for given %
$\text{Vwc} := \text{Bit} \cdot \text{VdvCmsb}$	$\text{Vwc} = 3.204 \times 10^{-4} \text{V}$	
$\text{Zwc} := \frac{\text{Vwc}}{\text{Iwc}}$	$\text{Zwc} = 4.513 \Omega$	
$\omega_{\text{dem}} := 2 \cdot \pi \cdot \text{Fdem}$		
$\text{Cmsb} := \frac{1}{\omega_{\text{dem}} \cdot \text{Zwc}}$	$\text{Cmsb} = 0.2 \mu\text{F}$	
$\text{Cdem}_0 := \text{Cmsb}$		
$n := 1 \dots (\text{DEMbits} - 1)$		
$\text{Cdem}_n := \frac{\text{Cmsb}}{2^n}$		

	0	
0	0.2	
1	0.1	
2	0.05	
3	0.025	
4	0.012	
5	$6.247 \cdot 10^{-3}$	
6	$3.124 \cdot 10^{-3}$	
7	$1.562 \cdot 10^{-3}$	
8	$7.809 \cdot 10^{-4}$	
9	$3.905 \cdot 10^{-4}$	

Cdem = μF



Cmsb = 1 x 220 nF	demFo=176.4KHz	15.7%	For Zwc = 1 wc_percent = 64% Cmsb=0.9uF
Cmsb = 2 x 100 nF	demFo=176.4KHz	14.2%	
Cmsb = 1 x 100 nF	demFo=176.4KHz	7.2%	