



- Combination 2 stg preamp (AA764), with no tone stack & 2 gain pots ① & ②
- ⓑ is preamp supply (last in line)
- 3 stages of cathode-biased 12AX7 gain!
- Cathodyne PI to 6V6's (or 6Y6, 6K6's)
- Xtra gain stage from unused 2nd input (on 5E3)
- 3rd gain stage on PI 12AX7
- ②nd vol pot added to control sig to PI
- Tone stack removed to keep design simple, to get PI working...

2nd Design - Dec 2013

"Cut'n Paste" Deluxe

- one input (get xtra gain stage)
- 2 gain pots & grid stoppers
- 3 stages gain preamp
- Cathodyne / 6V6 P-P
- NO Tone Stack
- ⓖ lower power P-P tubes

& possible "stoppers"