



- ① Looking out of the emitter of  $Q_1$ , find the small-signal Thevenin equivalent circuit.
- ② Now, assuming  $v_{i2} = -v_{i1}$ , what does the emitter of  $Q_1$  "see"? Is this different from the Thevenin circuit in ①?