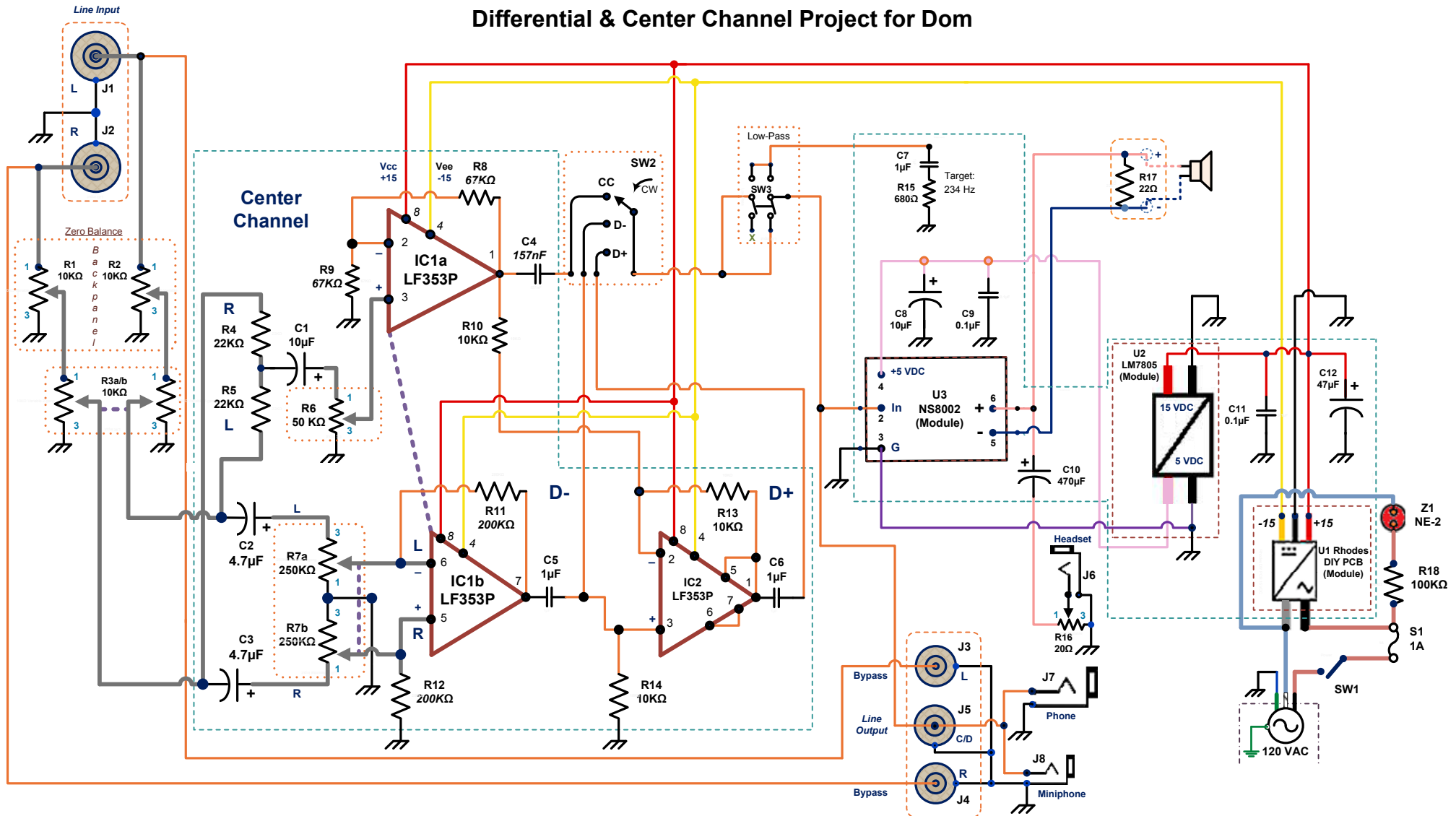


## Differential & Center Channel Project for Dom



R8, R9: 47K + 2 x 10K  
 R11, R12: 2 x 100KΩ  
 C4: 3 x 470nF