



R3 may need to be adjusted for your supply voltage. Aim for around 5mA to keep the resistor cool. Current limit is adjusted with R4. Raising R4 value will raise current limit