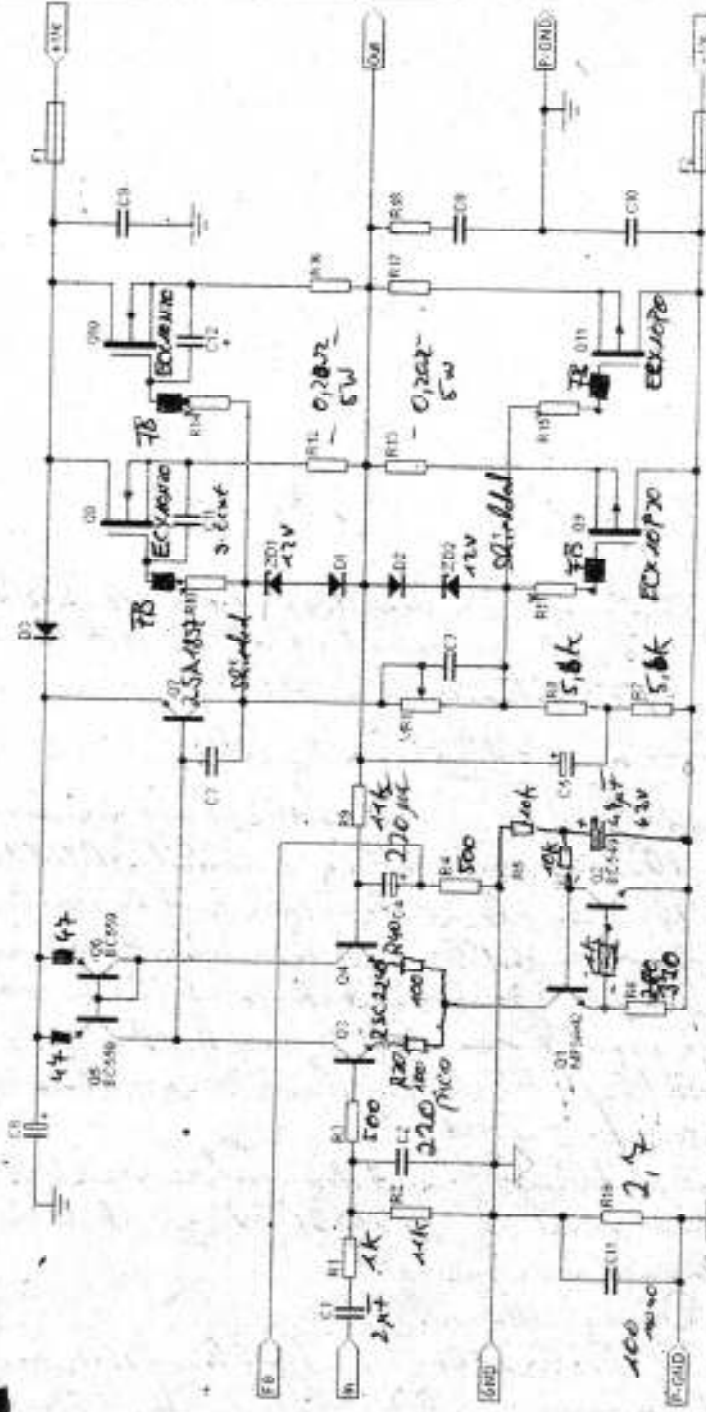


Distortion is reduced ten times to 0.0004% @ 1 kHz
 with source resistors being 0.2% the ideal quiescent current is 100 μ A
 $P_{SRD} \approx 20 \text{ dB}$



USE OF EXTENDED MOSFETS

Gate resistors are same value.
 Extended in use
 running analog

$R_{10} + R_{11}$ } 47k - 100k
 $R_{14} + R_{15}$ } depending on FB
 FB wideband when 47k 4922455-1, 4000mA, REX003522
 500k @ 100MHz