

Jack Ocle-Brown

### **Instantaneous power dissipation in class-B power transistor**

Using complex amplifier load impedance

$$\mathbf{Z} = Z_r + jZ_i = |\mathbf{Z}|e^{j\phi_z} \text{ where } j = \sqrt{-1} \quad 1.$$

And complex amplifier output voltage/current

$$I(t) = \Re(\mathbf{I}e^{j\omega t}) = \Re(|\mathbf{I}|e^{j\phi_i + j\omega t}) = |\mathbf{I}|\cos(\phi_i + \omega t) \quad 2.$$

$$V(t) = \Re(\mathbf{V}e^{j\omega t}) = \Re(|\mathbf{V}|e^{j\phi_v + j\omega t}) = |\mathbf{V}|\cos(\phi_v + \omega t) \quad 3.$$

Defining the complex output current to be

$$\mathbf{I} = -jI_p \quad 4.$$

This means that

$$I(t) = I_p \sin(\omega t) \quad 5.$$

Ohms law in complex units is simply

$$\mathbf{V} = \mathbf{I}\mathbf{Z} \quad 6.$$

Hence the complex output voltage is

$$\mathbf{V} = -jI_p\mathbf{Z} \quad 7.$$

Which means that

$$V(t) = I_p|\mathbf{Z}|\cos(\phi_z + \omega t - \pi/2) = I_p|\mathbf{Z}|\sin(\phi_z + \omega t) \quad 8.$$

Or

$$V(t) = V_p \sin(\phi_z + \omega t) \quad 9.$$

where  $V_p = I_p|\mathbf{Z}|$

The instantaneous power dissipated in the output transistor is

$$P(\omega t) = [V_r - V(t)]I(t) \quad 10.$$

Or

$$P(\omega t) = [V_r - V_p \sin(\phi_z + \omega t)]I_p \sin(\omega t) \quad 11.$$

Writing this in terms of voltages only

$$P(\omega t) = [V_r - V_p \sin(\phi_z + \omega t)]\frac{V_p}{|\mathbf{Z}|}\sin(\omega t) \quad 12.$$

Expanding

$$P(\omega t) = \frac{V_r V_p}{|\mathbf{Z}|}\sin(\omega t) - \frac{V_p^2}{|\mathbf{Z}|}\sin(\omega t)\sin(\phi_z + \omega t) \quad 13.$$

Differentiating

Jack Oclee-Brown

$$\frac{dP(\omega t)}{d\omega t} = \frac{V_r V_p}{|Z|} \cos(\omega t) - \frac{V_p^2}{|Z|} [\cos(\omega t) \sin(\phi_z + \omega t) + \sin(\omega t) \cos(\phi_z + \omega t)] \quad 14.$$

Maximum and minimum dissipation occurs when  $V_r = V_p$  and  $\frac{dP(\omega t)}{d\omega t} = 0$ . I.e.

$$\cos(\omega t) = \cos(\omega t) \sin(\phi_z + \omega t) + \sin(\omega t) \cos(\phi_z + \omega t) \quad 15.$$

$$\cos(\omega t) = \sin(2\omega t + \phi_z) \quad 16.$$

Due to the symmetry of the cosine function this has several solutions

$$\cos(\omega t) = \sin(2\omega t + \phi_z), \quad \cos(-\omega t) = \sin(2\omega t + \phi_z) \quad \text{and} \quad \cos(2\pi - \omega t) = \sin(2\omega t + \phi_z) \quad 17.$$

These can be written as


$$\sin(\omega t + \pi/2) = \sin(2\omega t + \phi_z), \quad \sin(-\omega t + \pi/2) = \sin(2\omega t + \phi_z) \quad \text{and} \quad \sin(-\omega t + \pi 5/2) = \sin(2\omega t + \phi_z) \quad 18.$$

$$\omega t = \frac{\pi}{2} - \phi_z, \quad \omega t = \frac{\pi}{6} - \frac{\phi_z}{3} \quad \text{and} \quad \omega t = \frac{5}{6}\pi - \frac{\phi_z}{3} \quad 19.$$

Or in degrees

$$\omega t = 90^\circ - \phi_z, \quad \omega t = 30^\circ - \frac{\phi_z}{3} \quad \text{and} \quad \omega t = 150^\circ - \frac{\phi_z}{3} \quad 20.$$

To check this we plot equation 13 for the case when  $V_p = V_r = |Z| = 1$

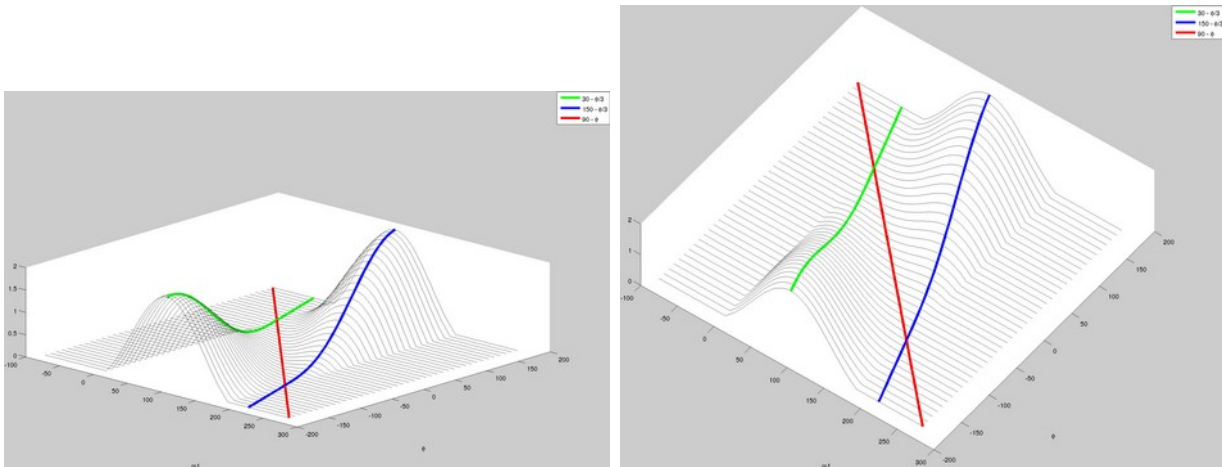

From this you can see that the expression  $\omega t = 90^\circ - \phi_z$  gives the minimum power dissipation phase,  $\omega t = 30^\circ - \frac{\phi_z}{3}$  gives the maximum dissipation phase when  $\phi_z < 0$ , and  $\omega t = 150^\circ - \frac{\phi_z}{3}$  gives the maximum when  $\phi_z > 0$ .

### **Average power dissipation in class B amplifier output transistor**

Integrate over instantaneous power for the on half cycle of the transistor:

$$P_{ave} = \int_{\omega t=0}^{\pi} \frac{1}{\pi} P(\omega t) d\omega t = \frac{2V_r V_p}{\pi |Z|} - \frac{V_p^2 \cos(\phi_z)}{2|Z|} \quad 21.$$

**EPDR**

Jack Ocle-Brown

EPDR gives the equivalent resistance that would dissipate the same peak power for the situation when  $V_p = V_r$ .

Inserting this into equation 13 results in

$$P(\omega t) = \frac{V_p^2}{|Z|} [1 - \sin(\phi_z + \omega t)] \sin(\omega t) \quad 22.$$

The instantaneous dissipation function has some nice symmetry so we can use just the maxima line for positive phase  $\phi_z > 0$  and write the peak dissipation as

$$P_{pk} = \frac{V_p^2}{|Z|} \left[ 1 - \sin\left(\frac{5}{6}\pi + \frac{2}{3}|\phi_z|\right) \right] \sin\left(\frac{5}{6}\pi - \frac{|\phi_z|}{3}\right) \quad 23.$$

For a resistor this expression simplifies to

$$P_{Rpk} = \frac{V_p^2}{R} \left[ 1 - \sin\left(\frac{5}{6}\pi\right) \right] \sin\left(\frac{5}{6}\pi\right) \quad 24.$$

Equating the resistor expression and the complex impedance expression we find the expression for EPDR:

$$R = |Z| \frac{\left[ 1 - \sin\left(\frac{5}{6}\pi\right) \right] \sin\left(\frac{5}{6}\pi\right)}{\left[ 1 - \sin\left(\frac{5}{6}\pi + \frac{2}{3}|\phi_z|\right) \right] \sin\left(\frac{5}{6}\pi - \frac{|\phi_z|}{3}\right)} \quad 25.$$