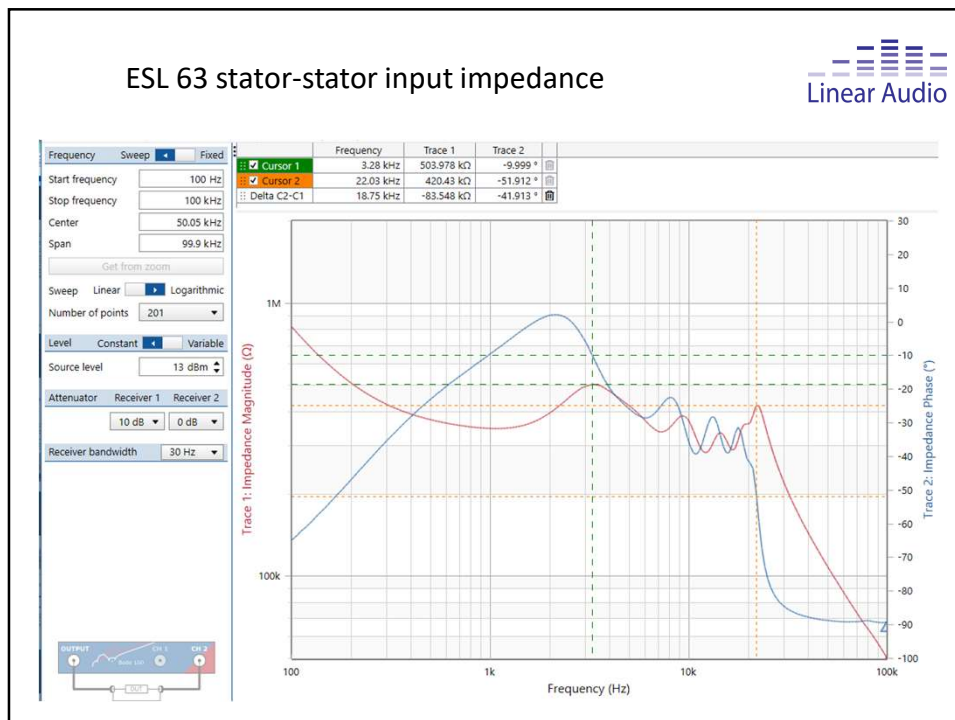


1



2




Amplifier requirements

- Two opposite phase drive voltages up to 5kV pk-pk
- Bridged load signal currents of up to 20mA pk-pk
- Initial all-solid-state design, based on IXYZ 4.5kV FETs and IGBTs
- Abandoned due to very high parasitic capacitances and small SOA

3

Issues with HV FETs/IGBTs in linear applications

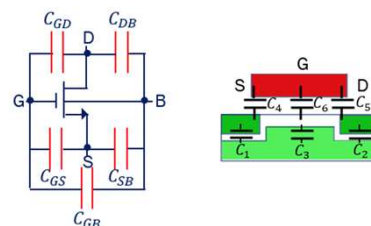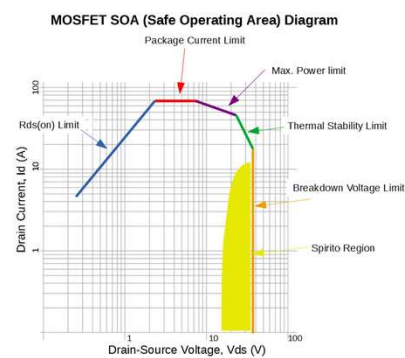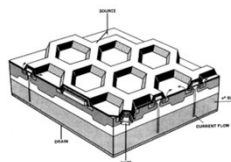- The Spirito Effect: each cell has the same gate-to-source voltage and the same capacitances but *not* the same gain. A higher gain cell conducts more current, causing a hotspot, leading to secondary breakdown.



- High gate charge/discharge currents cause distortion.


4

Way out

- Over to the dark side - compactron 6HS5 beam triode tubes!
- +/- 2.2kV design instead of +4.4kV to limit high voltage in box
- Current output into capacitive load for 1st order open loop roll off
- Rely on stable NFB for lowish Zout
- Monoblocs to limit cable length (capacitance)
- Software safety provisions


5

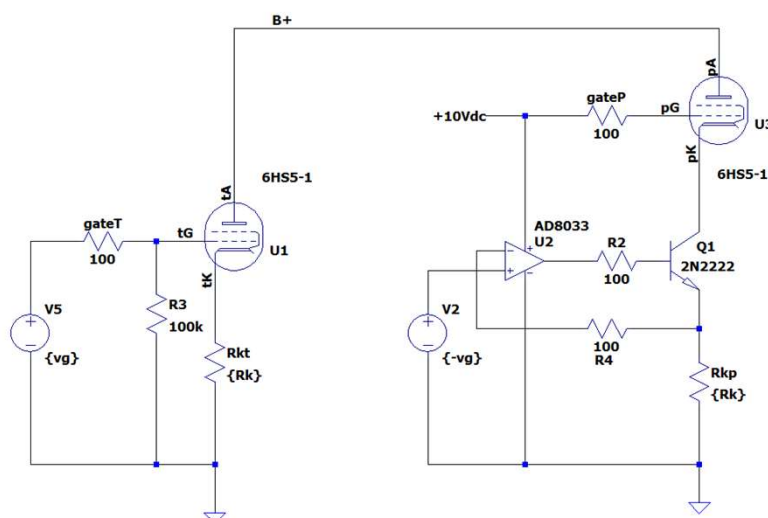Triode/Beam Triode Common Cathode versus Common Grid/transconductance drive



6

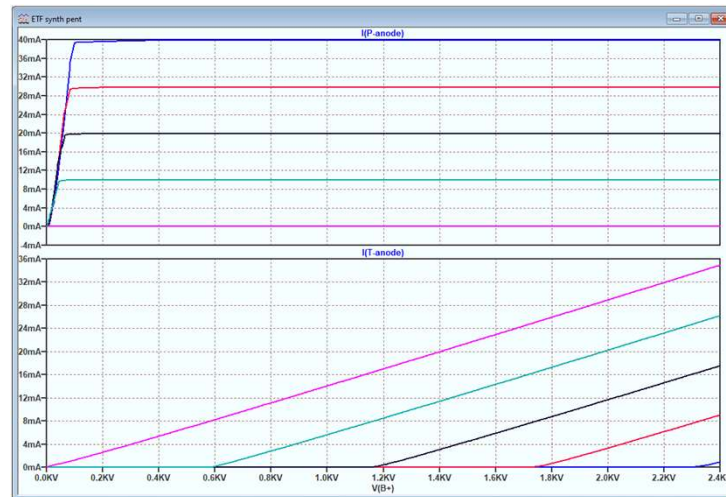
Common Grid drive turns a triode into a pentode



7

Basic output stage


- Modulated current source

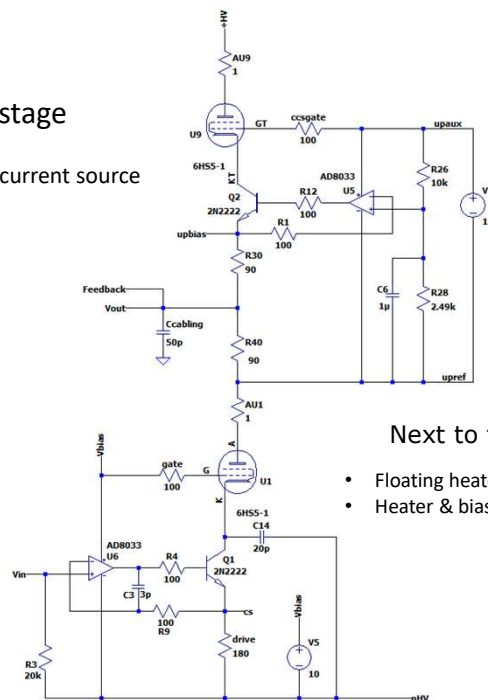


Next to tackle:

- Floating heater & bias for top tube;
- Heater & bias at -2.2kV for bottom tube

8

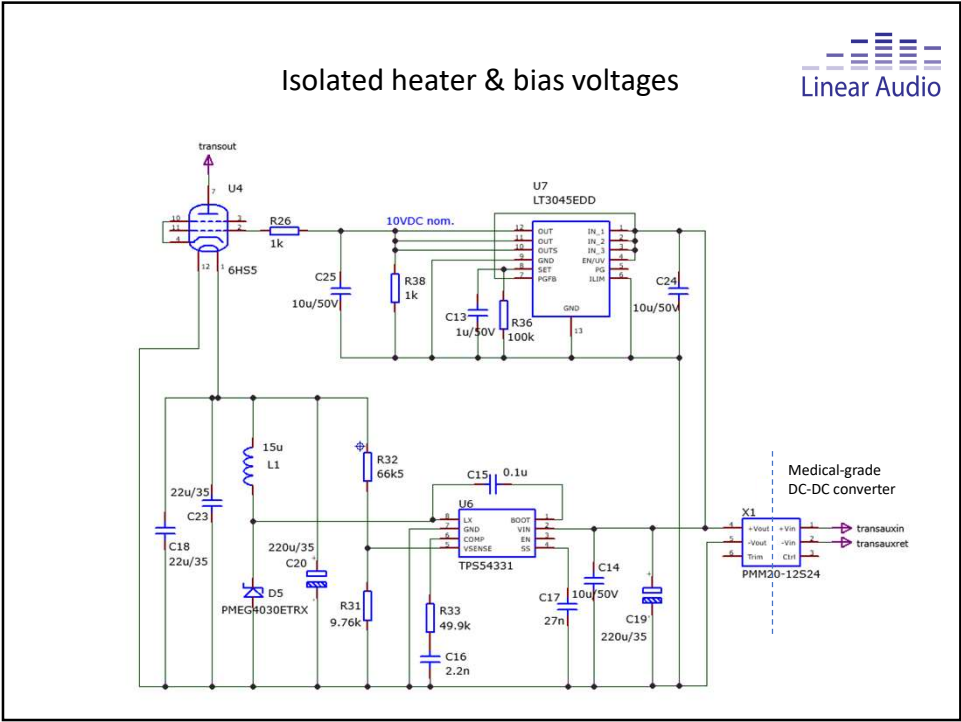

9

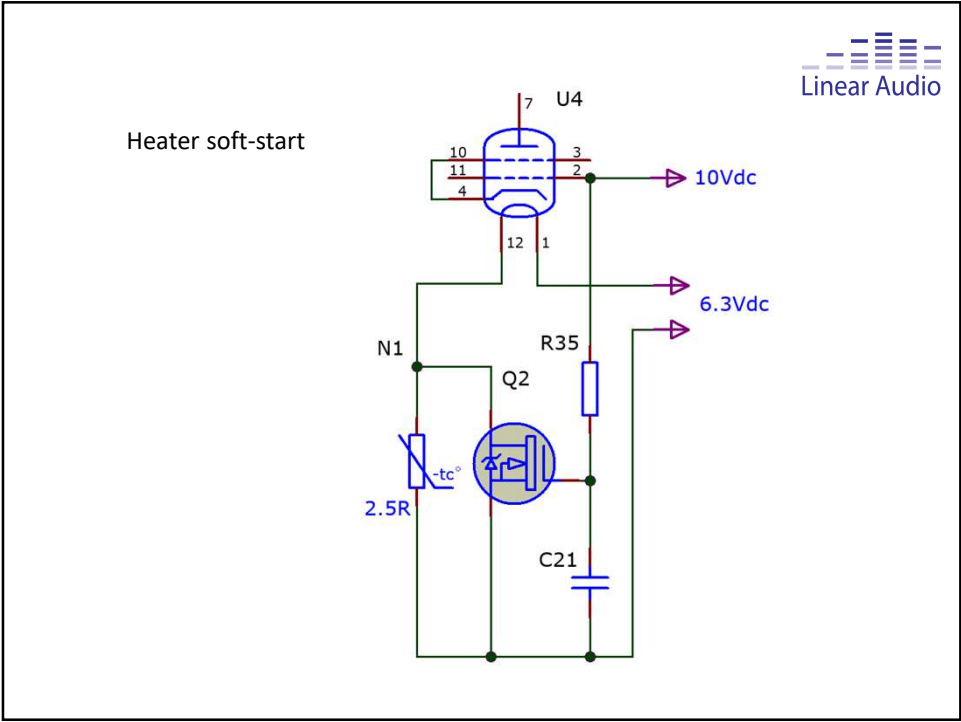


10

Next to tackle:


- Bringing the signal to -2.2kV reference

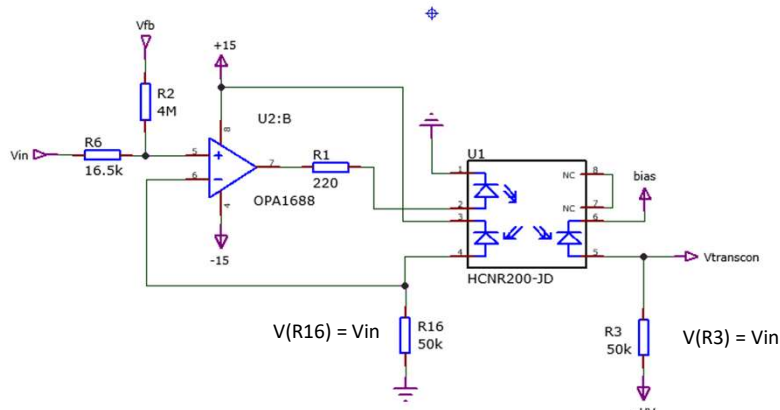Linear isolated optocoupler HCNR200/TIL300




11

Forward audio path

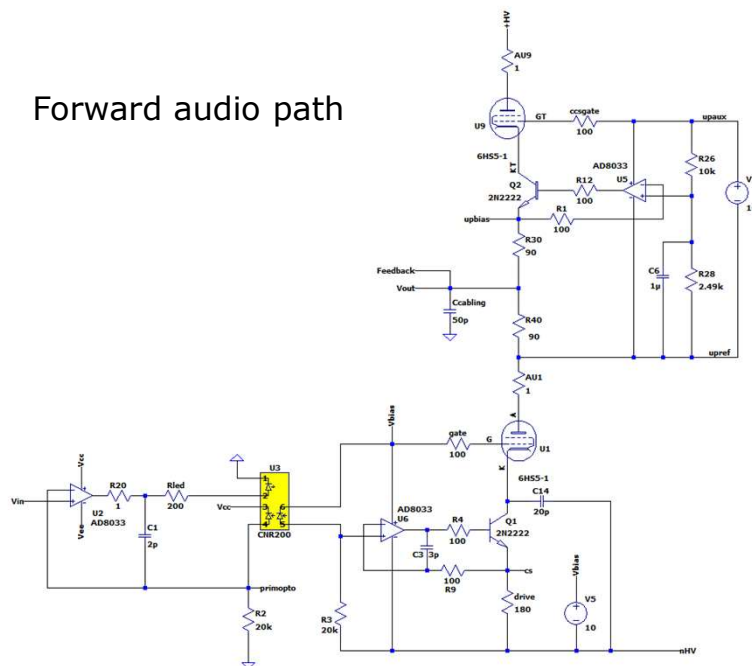


12

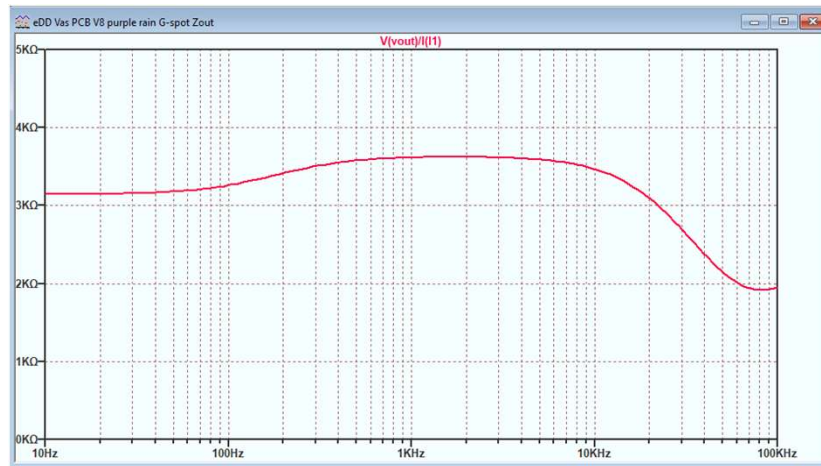Output impedance (simulated, matches measured)




13

Distortion at the stators – direct drive

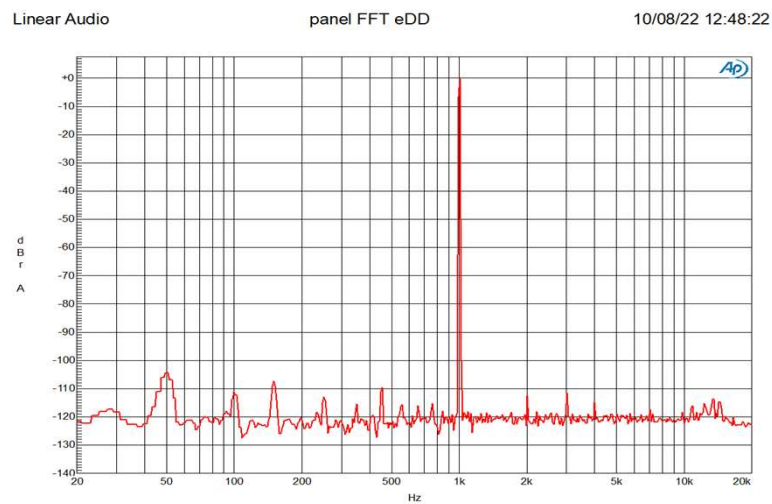

14

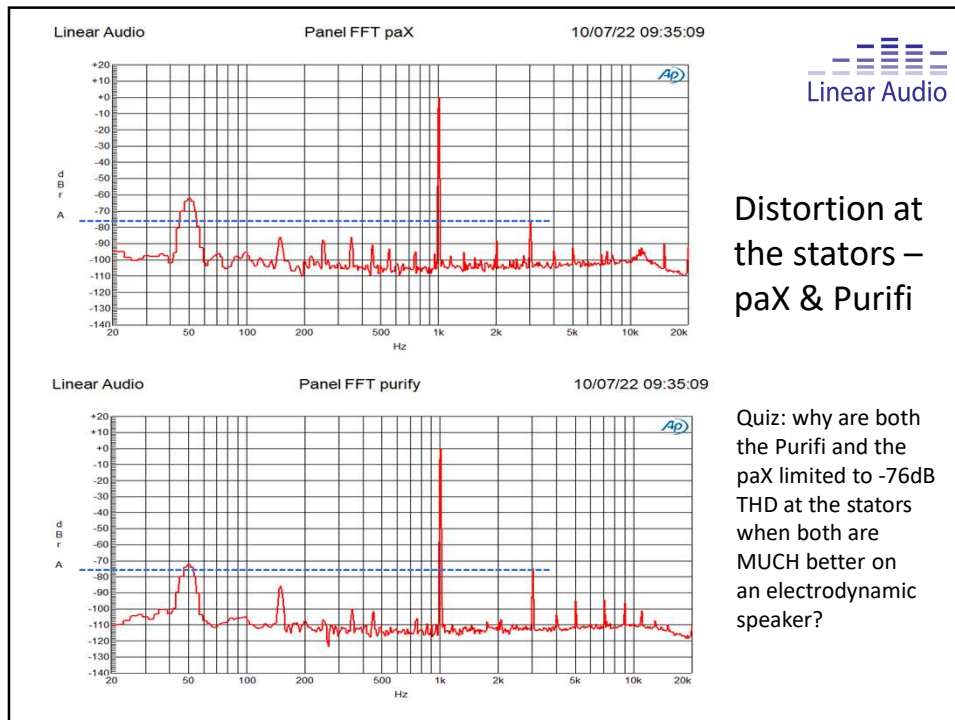

15

Speaker switching

Linear Audio


- Stator switching step-up output vs. direct drive output
- A/B direct and step-up drive comparison

16

Stator drive response matching



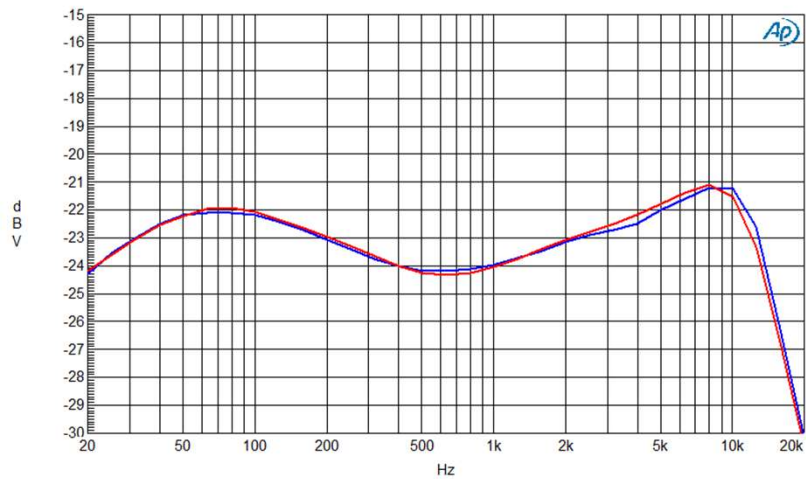Linear Audio Panel freq resp DD (red) and paX/Purify (blue) 09/27/22 10:59:37
[ADI-1]




17

System components



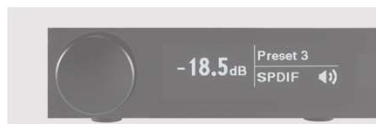Source:
Volumio Primo streamer
Wireless, USB, USBstick,
HD/SSD, TIDAL



Dirac Live! room correction:
miniDSP Flex Digital
2-input 4-output DSP



DAC & EQ:
RME ADI-2 Pro Fs R
'studio-in-a-box', used as
Dual Stereo DAC w/ EQ

18

DAC/EQ setup



- RME ADI-2 Pro FS R in AD/DA mode used as dual DAC
 - Level matching
 - Response EQ on direct drive

