



Delay switch to test turn on / off thump transient

Q2 is here an IRFP150 but R100 also works when built in practice. I don't have a working spice model for the R100 though. IRFP150 needs higher resistance on R14 though.