

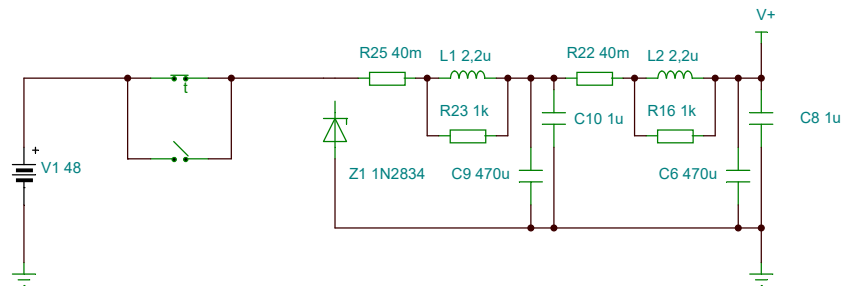
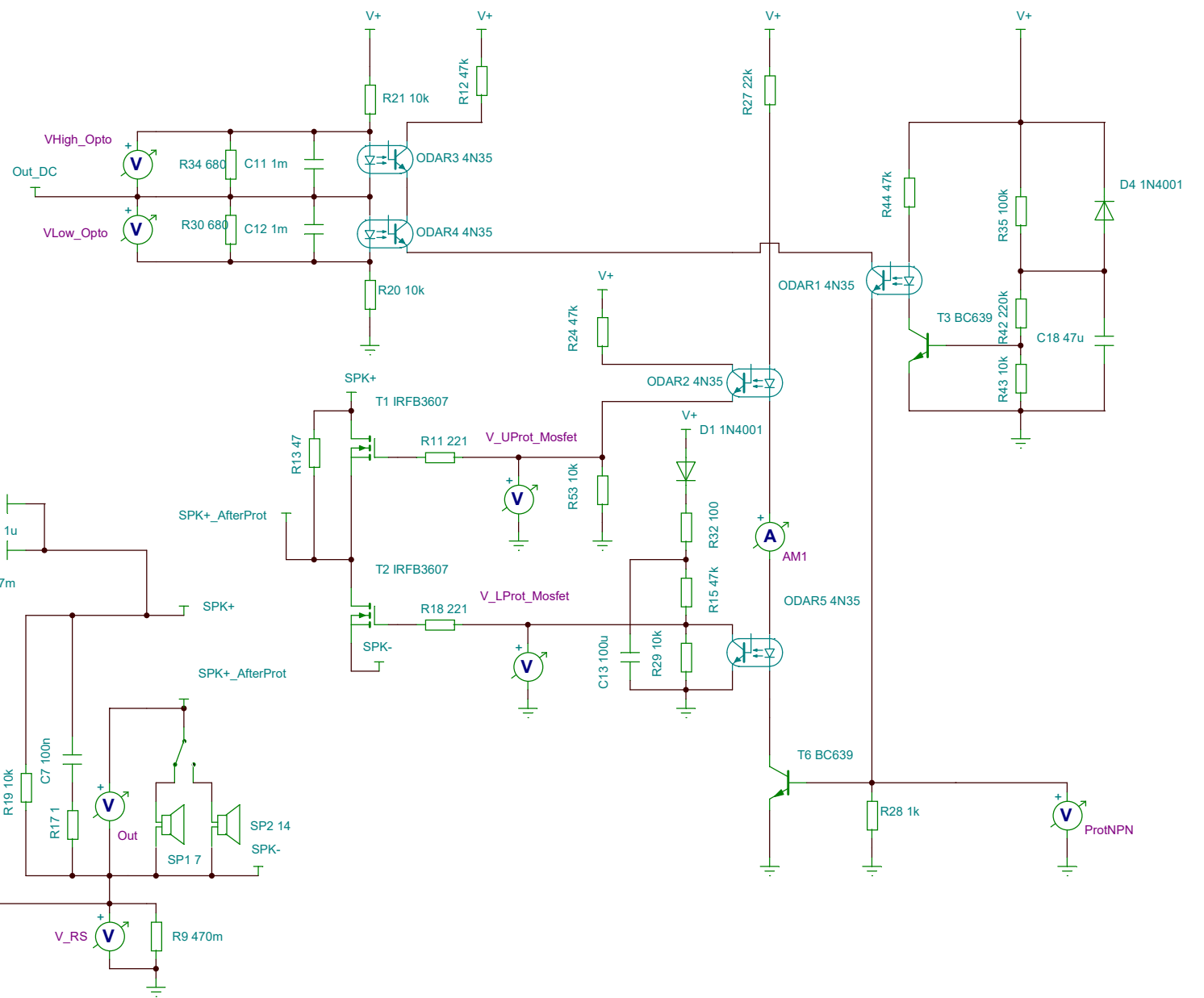
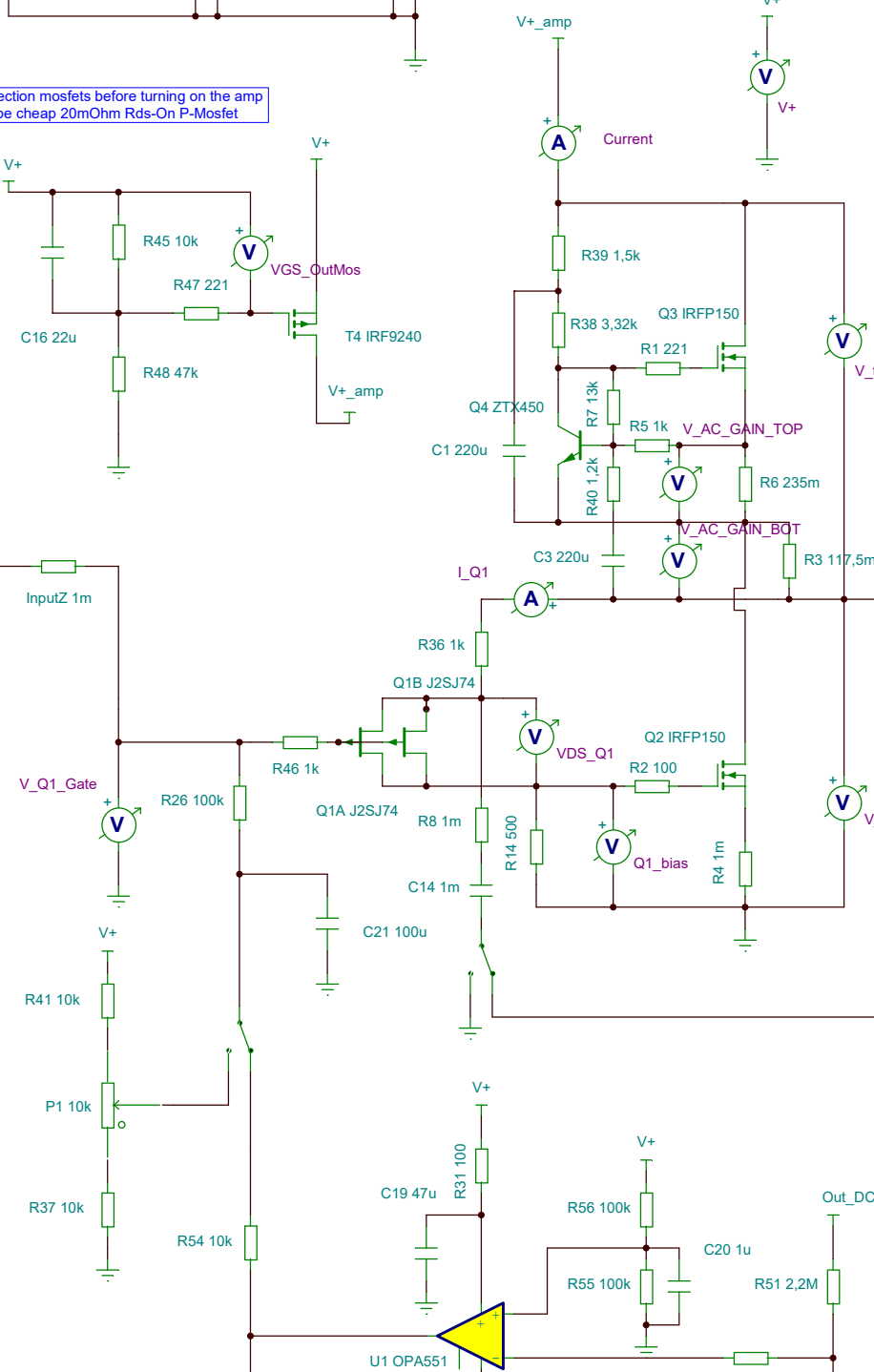


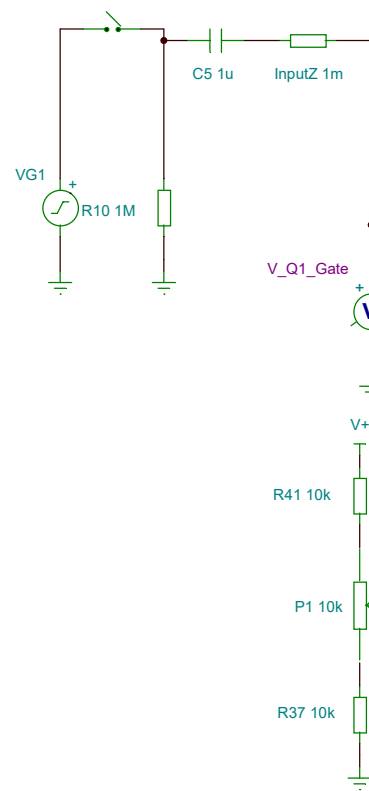Delay switch to test turn on / off thump transient



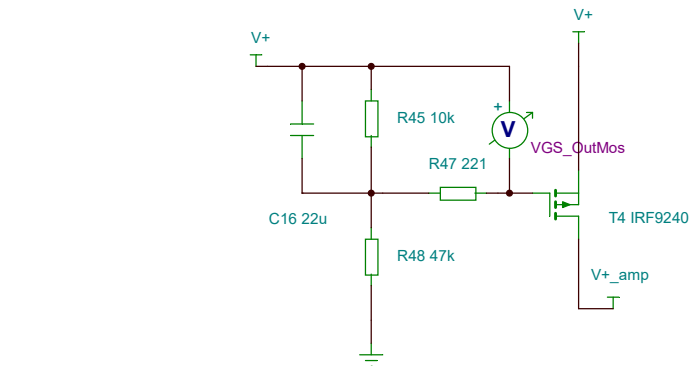Slow-start, bias the protection mosfets before turning on the amp  
IRF4905PBF seems to be cheap 20mOhm Rds-On P-Mosfet



Q2 is here an IRFP150 but R100 also works when built in practice.  
I don't have a working spice model for the R100 though.  
IRFP150 needs higher resistance on R14 though

