

# ***Feedback Amplifier Analysis Tools***

## *Application Report*

## IMPORTANT NOTICE

Texas Instruments and its subsidiaries (TI) reserve the right to make changes to their products or to discontinue any product or service without notice, and advise customers to obtain the latest version of relevant information to verify, before placing orders, that information being relied on is current and complete. All products are sold subject to the terms and conditions of sale supplied at the time of order acknowledgment, including those pertaining to warranty, patent infringement, and limitation of liability.

TI warrants performance of its products to the specifications applicable at the time of sale in accordance with TI's standard warranty. Testing and other quality control techniques are utilized to the extent TI deems necessary to support this warranty. Specific testing of all parameters of each device is not necessarily performed, except those mandated by government requirements.

Customers are responsible for their applications using TI components.

In order to minimize risks associated with the customer's applications, adequate design and operating safeguards must be provided by the customer to minimize inherent or procedural hazards.

TI assumes no liability for applications assistance or customer product design. TI does not warrant or represent that any license, either express or implied, is granted under any patent right, copyright, mask work right, or other intellectual property right of TI covering or relating to any combination, machine, or process in which such products or services might be or are used. TI's publication of information regarding any third party's products or services does not constitute TI's approval, license, warranty or endorsement thereof.

Reproduction of information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations and notices. Representation or reproduction of this information with alteration voids all warranties provided for an associated TI product or service, is an unfair and deceptive business practice, and TI is not responsible nor liable for any such use.

Resale of TI's products or services with statements different from or beyond the parameters stated by TI for that product or service voids all express and any implied warranties for the associated TI product or service, is an unfair and deceptive business practice, and TI is not responsible nor liable for any such use.

Also see: [Standard Terms and Conditions of Sale for Semiconductor Products](http://www.ti.com/sc/docs/stdterms.htm). [www.ti.com/sc/docs/stdterms.htm](http://www.ti.com/sc/docs/stdterms.htm)

### Mailing Address:

Texas Instruments  
Post Office Box 655303  
Dallas, Texas 75265

---

# Contents

<b>1</b>	<b>Introduction</b>	<b>1</b>
<b>2</b>	<b>Block Diagram Math and Manipulations</b>	<b>2</b>
<b>3</b>	<b>Feedback Equation and Stability</b>	<b>6</b>
<b>4</b>	<b>Bode Analysis of Feedback Circuits</b>	<b>8</b>
<b>5</b>	<b>Loop Plots Are the Key to Understanding Stability</b>	<b>12</b>
<b>6</b>	<b>The Second Order Equation and Ringing/Overshoot Predictions</b>	<b>15</b>
<b>7</b>	<b>Summary</b>	<b>16</b>
<b>8</b>	<b>References</b>	<b>16</b>

## List of Figures

1	Definition of Blocks	2
2	Summary Points	3
3	Definition of Control System Terms	3
4	Definition of an Electronic Feedback Circuit	3
5	Multiloop Feedback System	4
6	Block Diagram Transforms	5
7	Commercial Feedback System	6
8	Low-Pass Filter	8
9	Bode Plot of Low-Pass Filter Transfer Function	9
10	Band Reject Filter	9
11	Individual Pole Zero Plot of Band Reject Filter	10
12	Combined Pole Zero Plot of Band Reject Filter	10
13	When No Pole Exists in Equation 12	11
14	When Equation 12 Has a Single Pole	11
15	Magnitude and Phase Plot of Equation 14	12
16	Magnitude and Phase Plot of the Loop Gain Increased to $(K+C)$	13
17	Magnitude and Phase Plot of the Loop Gain With Pole Spacing Reduced	14
18	Phase Margin and Percent Overshoot vs Damping Ratio	16



---

# ***Feedback Amplifier Analysis Tools***

*Ronald Mancini*

---

## **ABSTRACT**

This paper gives the reader a command of the simplest set of tools required to analyze and design feedback amplifiers. These tools are fundamental, and they form the basis of feedback analysis and design.

---

## **1 Introduction**

Analysis tools have something in common with medicine because they both can be distasteful but necessary. Medicine often tastes bad or has undesirable side effects, and analysis tools involve lots of hard learning work before they can be applied to yield results. Medicine assists the body in fighting an illness; analysis tools assist the brain in learning/designing feedback circuits.

The analysis tools given here are a synopsis of salient points; thus, they are detailed enough to get you where you are going without any extras. The references, along with thousands of their counterparts, must be consulted when making an in-depth study of the field. Aspirin, home remedies, and good health practice handle the majority of health problems, and these analysis tools solve the majority of circuit problems.

I have little patience; therefore, I would not study these tools in detail prior to reading an application note. A little advanced study however, pays off for those who have patience.

## 2 Block Diagram Math and Manipulations

Electronic systems and circuits are often represented by block diagrams, and block diagrams have a unique algebra and set of transformations.[1] The block diagrams are used because they are a shorthand pictorial representation of the cause-and-effect relationship between the input and output in a real system. They are a convenient method for characterizing the functional relationships between components. It is not necessary to understand the functional details of a block to manipulate a block diagram.

The input impedance of each block is assumed to be infinite to preclude loading. Also, the output impedance of each block is assumed to be zero to enable high fan-out. The systems designer sets the actual impedance levels, but the fan-out assumption is valid because the block designers adhere to the system designer's specifications. All blocks multiply the input times the block quantity (see Figure 1) unless otherwise specified within the block. The quantity within the block can be a constant as shown in Figure 1(c), or it can be a complex math function involving Laplace transforms. The blocks can perform time-based operations such as differentiation and integration.

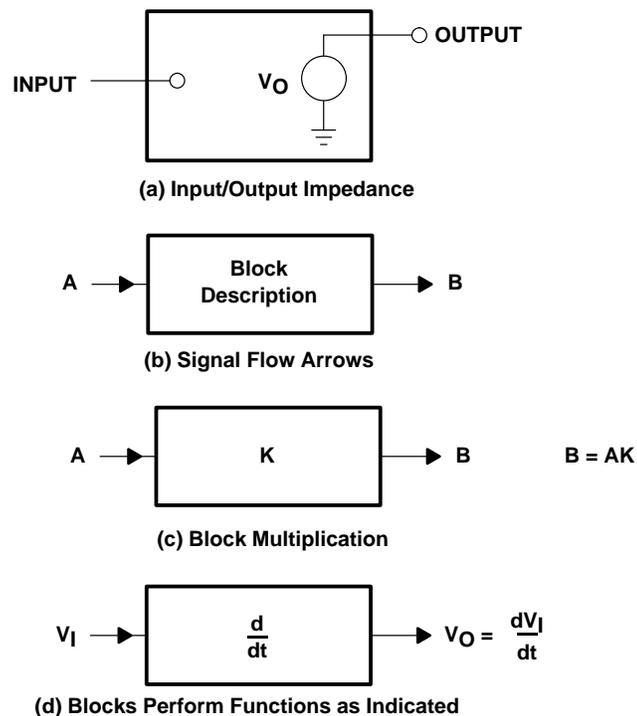


Figure 1. Definition of Blocks

Adding and subtracting are done in special blocks called summing points. Figure 2 gives several examples of summing points. Summing points can have unlimited inputs, can add or subtract, and can have mixed signs yielding addition and subtraction within a single summing point. Figure 3 defines the terms in a typical control system, and Figure 4 defines the terms in a typical electronic-feedback system. Multiloop feedback systems (Figure 5) are intimidating, but they can be reduced to a single-loop feedback system, as shown in Figure 5, by writing equations and solving for  $V_{OUT}/V_{IN}$ . An easier method for reducing multiloop feedback systems to single-loop feedback systems is to follow the rules and use the transforms given in Figure 6.

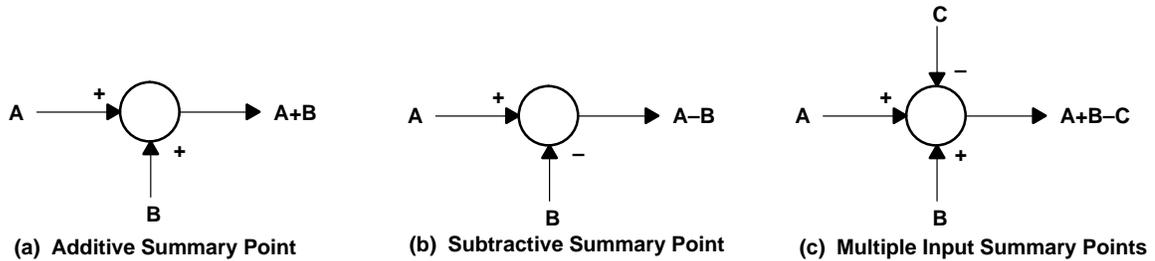


Figure 2. Summary Points

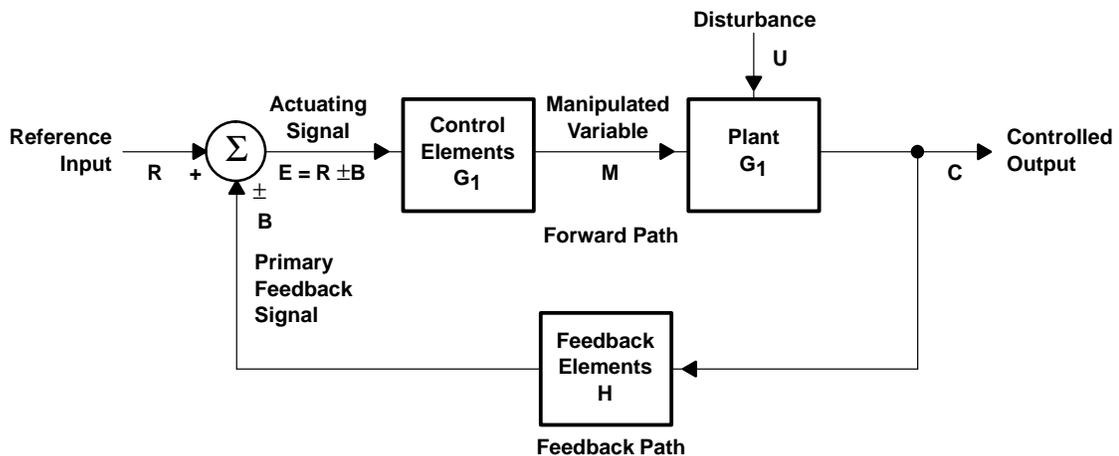


Figure 3. Definition of Control System Terms


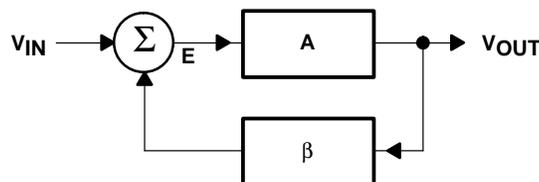


Figure 4. Definition of an Electronic Feedback Circuit

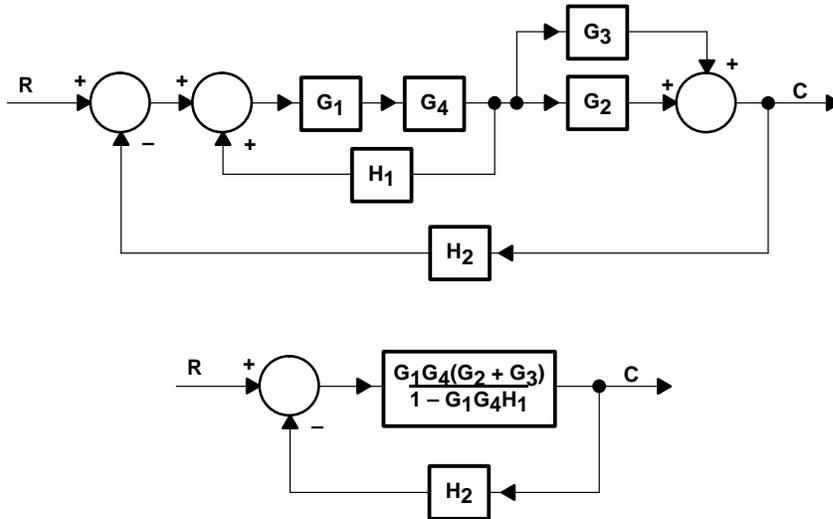

**Figure 5. Multiloop Feedback System**

Block diagram reduction rules:

- Combine cascade blocks
- Combine parallel blocks
- Eliminate interior feedback loops
- Shift summing points to the left
- Shift takeoff points to the right
- Repeat until canonical form is obtained

Figure 6 gives the block diagram transforms. The idea is to reduce the diagram to its canonical form because the canonical-feedback loop is the simplest form of a feedback loop, and its analysis is well documented. All feedback systems can be reduced to the canonical form, so all feedback systems can be analyzed with the same math. A canonical loop exists for each input to a feedback system; although the stability dynamics are independent of the input, the output results are input dependent. The response of each input of a multiple-input feedback system can be analyzed separately and added through superposition.

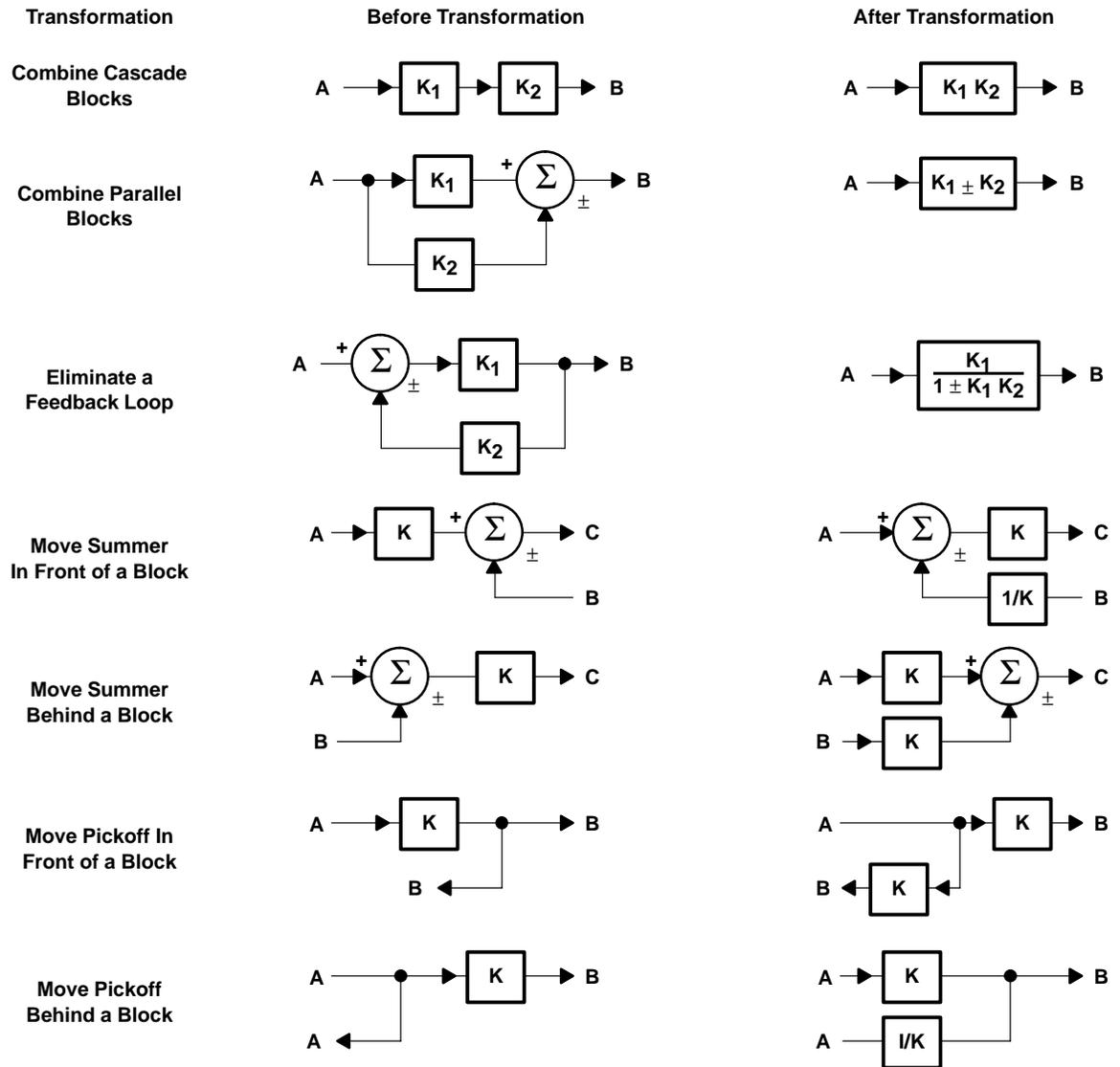


Figure 6. Block Diagram Transforms

### 3 Feedback Equation and Stability

Figure 7 shows the canonical form of a feedback loop with control system and electronic system terms. The terms make no difference except that they have meaning to the system engineers, but the math does have meaning, and it is identical for both types of terms. The electronic terms and negative feedback sign are used in this analysis, because subsequent application notes deal with electronic applications. The output equation is written in equation 1.

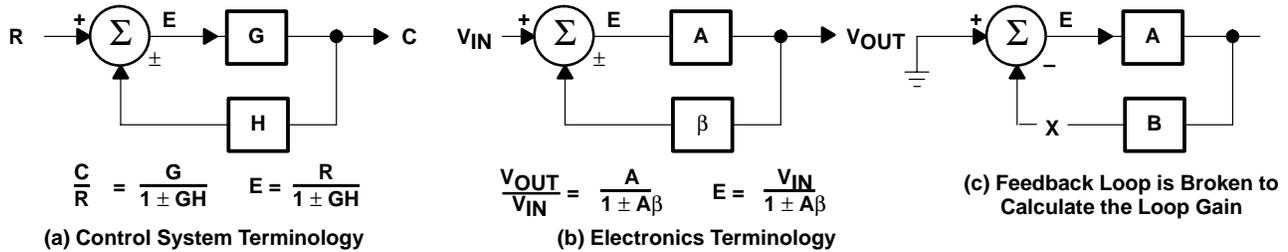


Figure 7. Commercial Feedback System

$$V_{OUT} = EA \tag{1}$$

The error equation is written in equation 2.

$$E = V_{IN} - \beta V_{OUT} \tag{2}$$

Combining equations 1 and 2 yields equation 3.

$$\frac{V_{OUT}}{A} = V_{IN} - \beta V_{OUT} \tag{3}$$

Collecting terms yields equation 4.

$$V_{OUT} \left( \frac{1}{A} + \beta \right) = V_{IN} \tag{4}$$

Rearranging terms yields the classic form of the feedback equation 5.

$$\frac{V_{OUT}}{V_{IN}} = \frac{A}{1 + A\beta} \tag{5}$$

Notice that when  $A\beta$  in equation 5 becomes very large with respect to one, the one can be neglected, and equation 5 reduces to equation 6 which is the ideal feedback equation. Under the conditions that  $A\beta \gg 1$ , the system gain is determined by the feedback factor ( $\beta$ ). Stable, passive-circuit components are used to implement the feedback factor, thus, in the ideal situation, the closed-loop gain is predictable and stable because  $\beta$  is stable and predictable.

$$\frac{V_{OUT}}{V_{IN}} = \frac{1}{\beta} \tag{6}$$

The quantity  $A\beta$  is so important that it has been given a special name, loop gain. In Figure 7, when the voltage inputs are grounded (current inputs are opened) and the loop is broken, the calculated gain is the loop gain ( $A\beta$ ). Now, keep in mind that we are using complex numbers which have magnitude and direction. When the loop gain approaches minus one, or to express it mathematically  $1\angle 180^\circ$ , equation 5 approaches  $1/0 = \infty$ . The circuit output heads for infinity as fast as it can using the equation of a straight line. If the output were not energy limited, the circuit would explode the world, but happily, it is energy limited, so somewhere it comes up against the limit.

Active devices in electronic circuits exhibit nonlinear phenomena when their output approaches a power supply rail, and the nonlinearity reduces the gain to the point where the loop gain no longer equals  $1\angle 180^\circ$ . Now the circuit can do two things; first it can become stable at the power supply limit, or second, it can reverse direction (because stored charge keeps the output voltage changing) and head for the negative power supply rail.

The first state where the circuit becomes stable at a power supply limit is named lockup; the circuit will remain in the locked up state until power is removed and reapplied. The second state where the circuit bounces between power supply limits is named oscillatory. Remember, the loop gain ( $A\beta$ ), is the sole factor determining stability of the circuit or system. Inputs are grounded or disconnected, so they have no bearing on stability. The loop-gain criteria is analyzed in depth in the Section 6.

Equations 1 and 2 are combined and rearranged to yield equation 7 which gives an indication of the system or circuit error.


$$E = \frac{V_{IN}}{1 + A\beta} \quad (7)$$

First, notice that the error is proportional to the input signal. This is the expected result because a bigger input signal results in a bigger output signal, and bigger output signals require more drive voltage. As the loop gain increases, the error decreases, thus, large loop gains are attractive for minimizing errors.

## 4 Bode Analysis of Feedback Circuits

H. W. Bode developed a quick, accurate, and easy method of analyzing feedback amplifiers, and he published a book about his techniques in 1945.[2] Operational amplifiers had not been developed when Bode published his book, but they fall under the general classification of feedback amplifiers, so they are easily analyzed with Bode techniques. The mathematical manipulations required to analyze a feedback circuit are complicated because they involve multiplication and division. Bode developed the Bode plot which simplifies the analysis through the use of graphical techniques.

The Bode equations are log equations which take the form  $20\text{LOG}(F(t)) = 20\text{LOG}(|F(t)|) + \text{phase angle}$ . The terms that are normally multiplied and divided can now be added and subtracted because they are log equations. The addition and subtraction is done graphically, thus easing the calculations and giving the designer a pictorial representation of circuit performance. Equation 8 is written for the low-pass filter shown in Figure 8.

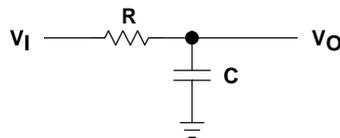

**Figure 8. Low-Pass Filter**

$$\frac{V_{\text{OUT}}}{V_{\text{IN}}} = \frac{1}{1 + RCs} = \frac{1}{1 + \tau s} \quad (8)$$

Where:


$$s = j\omega, \quad j = \sqrt{-1}, \quad \text{and } RC = \tau$$

The magnitude of this transfer function is  $|V_{\text{OUT}}/V_{\text{IN}}| = 1/\sqrt{(1^2 + (\tau\omega)^2)}$ . This magnitude,  $|V_{\text{OUT}}/V_{\text{IN}}| \cong 1$  when  $\omega = 0.1/\tau$ , it equals 0.707 when  $\omega = 1/\tau$ , and it is approximately = 0.1 when  $\omega = 10/\tau$ . These points are plotted in Figure 9 using straight line approximations. The negative slope is  $-20$  dB/decade or  $-6$  dB/octave. The magnitude curve is plotted as a horizontal line until it intersects the breakpoint where  $\omega = 1/\tau$ . The negative slope begins at the breakpoint because the magnitude decreases rapidly at that point. The gain is equal to 1 or 0 dB at very low frequencies, equal to 0.707 or  $-3$  dB at the break frequency, and it keeps falling with a  $-20$  dB/decade slope for higher frequencies.

The phase shift for the low-pass filter or any other transfer function is calculated with the aid of equation 9.

$$\phi = \text{tangent}^{-1}\left(\frac{1}{\omega\tau}\right) \quad (9)$$


The phase shift is much harder to approximate because the tangent function is nonlinear. Normally, the phase information is only required around the 0-dB intercept point for an active circuit, so the calculations are minimized. The phase is shown in Figure 9, and it is approximated by remembering that the tangent of  $90^\circ$  is 1, the tangent of  $60^\circ$  is  $\sqrt{3}$ , and the tangent of  $30^\circ$  is  $\sqrt{3}/3$ .

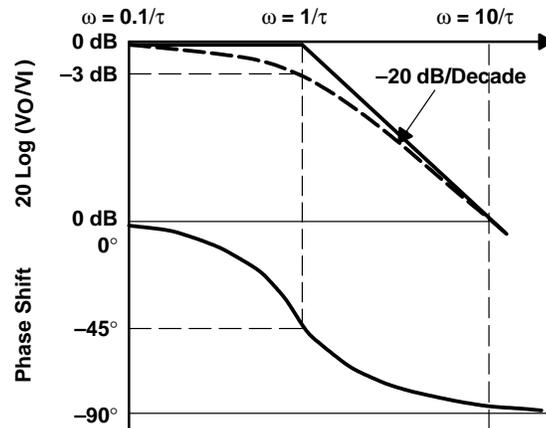

**Figure 9. Bode Plot of Low-Pass Filter Transfer Function**

A breakpoint occurring in the denominator is called a pole, and it slopes down. Conversely, a breakpoint occurring in the numerator is called a zero, and it slopes up. When the transfer function has multiple poles and zeros, each pole or zero is plotted independently, and the individual poles/zeros are added graphically. If multiple poles, zeros, or a pole/zero combination have the same breakpoint, they are plotted on top of each other. Multiple poles or zeros cause the slope to change by more than 20 dB/decade.

An example of a transfer function with multiple poles and zeros is a band reject filter (see Figure 10). The transfer function of the band reject filter is given in equation 10.

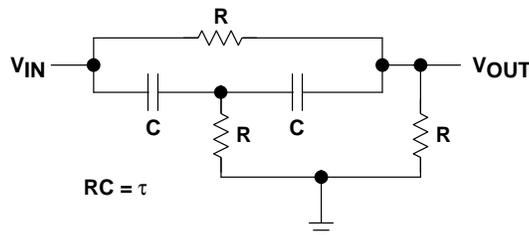

**Figure 10. Band Reject Filter**

$$G = \frac{V_{OUT}}{V_{IN}} = \frac{(1 + \tau s)(1 + \tau s)}{2 \left(1 + \frac{\tau s}{0.44}\right) \left(1 + \frac{\tau s}{4.56}\right)} \quad (10)$$

The pole zero plot for each individual pole and zero is shown in Figure 11, and the combined pole zero plot is shown in Figure 12.

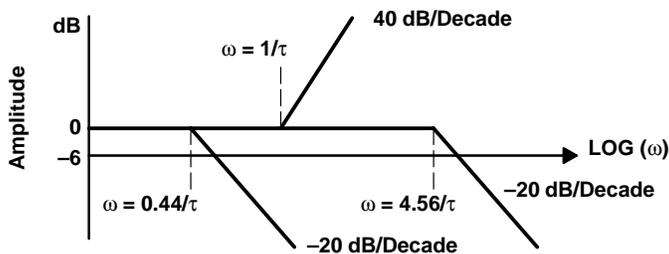


Figure 11. Individual Pole Zero Plot of Band Reject Filter

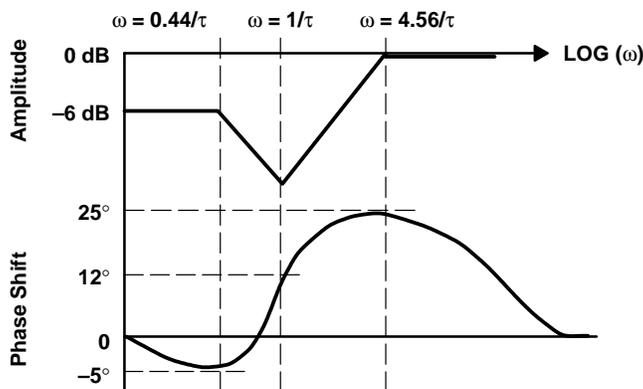


Figure 12. Combined Pole Zero Plot of Band Reject Filter

The individual pole zero plots show the dc gain of 1/2 plotting as a straight line from the -6-dB intercept. The two zeros occur at the same break frequency, thus they have a 40 dB/decade slope. The two poles are plotted at their breakpoints of  $\omega = 0.44/\tau$  and  $\omega = 4.56/\tau$ . The combined amplitude plot intercepts the axis at -6 dB because of the dc gain, and then breaks down at the first pole. When the amplitude function gets to the double zero, the first zero cancels out the pole, and the second zero breaks up. The upward slope continues until the second pole cancels out the second zero, and the amplitude is flat from that point out in frequency.

When the separation between all the poles and zeros is great, a decade or more in frequency, it is easy to draw the Bode plot. As the poles and zeros get closer the plot gets harder to make. The phase is especially hard to plot because of the tangent function, but picking a few salient points and sketching them in first gets a pretty good approximation.[3] The Bode plot enables the designer to get a good idea of pole zero placement, and it is valuable for fast evaluation of possible compensation techniques. When the situation gets critical, accurate calculations must be made and plotted to get an accurate result.


Consider equation 11.

$$\frac{V_{OUT}}{V_{IN}} = \frac{A}{1 + A\beta} \tag{11}$$

Taking the log of equation 11 yields equation 12

$$20\text{Log}\left(\frac{V_{OUT}}{V_{IN}}\right) = 20\text{Log}(A) - 20\text{Log}(1 + A\beta) \tag{12}$$

If  $A$  and  $\beta$  do not contain any poles or zeros there will be no break points. Then the Bode plot of equation 12 looks like that shown in Figure 13, and because there are no poles to contribute negative phase shift, the circuit cannot oscillate.

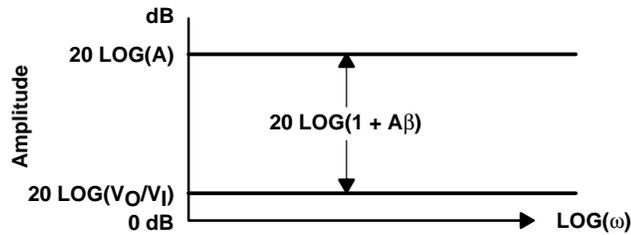


**Figure 13. When No Pole Exists in Equation 12**

All real amplifiers have many poles, but they are normally internally compensated so that they appear to have a single pole. Such an amplifier would have an equation similar to that given in equation 13.

$$A = \frac{a}{1 + j\frac{\omega}{\omega_a}} \quad (13)$$

The plot for the single pole amplifier is shown in Figure 14.

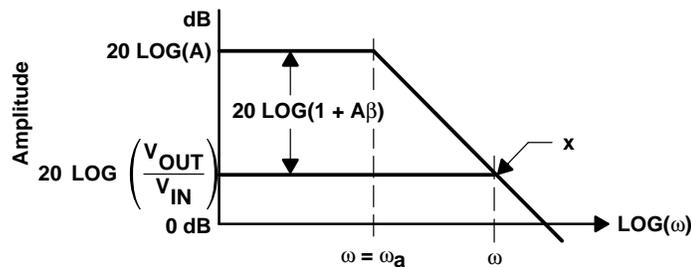

**Figure 14. When Equation 12 Has a Single Pole**

The amplifier gain,  $A$ , intercepts the amplitude axis at  $20\text{Log}(A)$ , and it breaks down at a slope of  $-20 \text{ dB/decade}$  at  $\omega = \omega_a$ . The negative slope continues for all frequencies greater than the breakpoint,  $\omega = \omega_a$ . The closed loop circuit gain intercepts the axis at  $20\text{Log}(V_{\text{OUT}}/V_{\text{IN}})$ , and because  $\beta$  does not have any poles or zeros, it is constant until its projection intersects the amplifier gain at point X. After intersection with the amplifier gain curve, the closed loop gain follows the amplifier gain because the amplifier becomes the controlling factor.

Actually, the closed loop gain starts to roll off earlier, and it is down 3 dB at point X. At point X the difference between the closed-loop gain and the amplifier gain is  $-3 \text{ dB}$ , thus, according to equation (12) the term  $-20\text{Log}(1+A\beta) = -3 \text{ dB}$ . The magnitude of 3 dB is  $\sqrt{2}$ , hence  $\sqrt{1 + (A\beta)^2} = \sqrt{2}$ , and elimination of the radicals shows that  $A\beta = 1$ . There is a method [4] of relating phase shift and stability to the slope of the closed-loop gain curves, but only the Bode method is covered here. An excellent discussion of poles, zeros, and their interaction is given by M. E Van Valkenberg,[5] and he also includes some excellent prose to liven the discussion.

## 5 Loop Gain Plots Are the Key to Understanding Stability

Stability is determined by the loop gain, and when  $A\beta = -1 = |1| \angle 180^\circ$  instability or oscillation occurs. If the magnitude of the gain exceeds one, it is usually reduced to one by circuit nonlinearities, so oscillation generally results for situations where the gain magnitude exceeds one.

Consider oscillator design which depends on nonlinearities to decrease the gain magnitude. If the engineer designed for a gain magnitude of one at nominal circuit conditions, the gain magnitude would fall below one under worst case circuit conditions causing oscillation to cease. Thus, the prudent engineer designs for a gain magnitude of one under worst case conditions knowing that the gain magnitude is much more than one under optimistic conditions. The prudent engineer depends on circuit nonlinearities to reduce the gain magnitude to the appropriate value, but this same engineer pays a price of poorer distortion performance. Sometimes a design compromise is reached by putting a nonlinear component, such as a lamp, in the feedback loop to control the gain without introducing distortion.

Some high-gain control systems always have a gain magnitude greater than one, but they avoid oscillation by manipulating the phase shift. The amplifier designer who pushes the amplifier for superior frequency performance has to be careful not to let the loop-gain phase shift accumulate to  $180^\circ$ . Problems with overshoot and ringing pop up before the loop gain reaches  $180^\circ$  phase shift. Thus, the amplifier designer must keep a close eye on loop dynamics. Ringing and overshoot are handled in the next section, so preventing oscillation is emphasized in this section. Equation 14 has the form of many loop-gain transfer functions or circuits, so it is analyzed in detail.

$$(A)\beta = \frac{(K)}{(1 + \tau_1(s))(1 + \tau_2(s))} \tag{14}$$

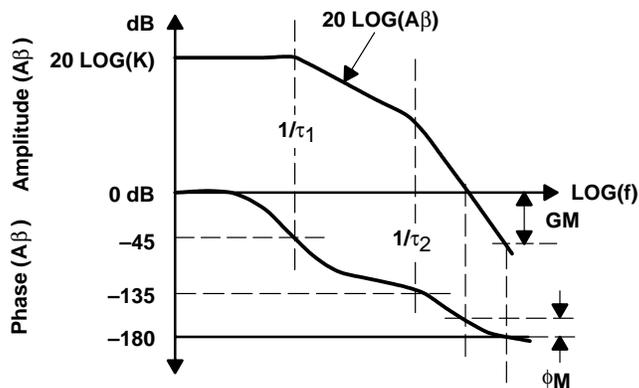



Figure 15. Magnitude and Phase Plot of Equation 14

The quantity,  $K$ , is the dc gain, and it plots as a straight line with an intercept of  $20\text{Log}(K)$ . The Bode plot of equation 14 is shown in Figure 15. The two break points,  $\omega = \omega_1 = 1/\tau_1$  and  $\omega = \omega_2 = 1/\tau_2$ , are plotted in the Bode plot. Each breakpoint adds  $-20\text{ dB/decade}$  slope to the plot, and  $45^\circ$  phase shift accumulates at each breakpoint. This transfer function is referred to as a two slope because of the two breakpoints. The slope of the curve when it crosses the  $0\text{ dB}$  intercept indicates phase shift and the ability to oscillate. Notice that a one slope can only accumulate  $90^\circ$  phase shift, so when a transfer function passes through  $0\text{ dB}$  with a one slope, it cannot oscillate. Furthermore, a two-slope system can accumulate  $180^\circ$  phase shift. Therefore, a transfer function with a two or greater slope is capable of oscillation.

A one slope crossing the  $0\text{ dB}$  intercept is stable, whereas a two or greater slope crossing the  $0\text{ dB}$  intercept may be stable or unstable depending upon the accumulated phase shift. Figure 15 defines two stability terms; the phase margin,  $\phi_M$ , and the gain margin,  $G_M$ . Of these two terms the phase margin is much more popular because phase shift is critical for stability. Phase margin is a measure of the difference in the actual phase shift and the theoretical  $180^\circ$  required for oscillation, and the phase margin measurement or calculation is made at the  $0\text{ dB}$  crossover point. The gain margin is measured or calculated at the  $180^\circ$  phase crossover point. Phase margin is expressed mathematically in equation 15.


$$\phi_M = 180 - \text{tangent}^{-1}(A\beta) \quad (15)$$

The phase margin in Figure 15 is very small ( $20^\circ$ ) so it is hard to measure or predict from the Bode plot. A designer probably doesn't want a  $20^\circ$  phase margin because the system overshoots and rings badly, but this case points out the need to calculate small phase margins carefully. The circuit is stable, and it does not oscillate because the phase margin is positive. Also, the circuit with the smallest phase margin has the highest frequency response and bandwidth.

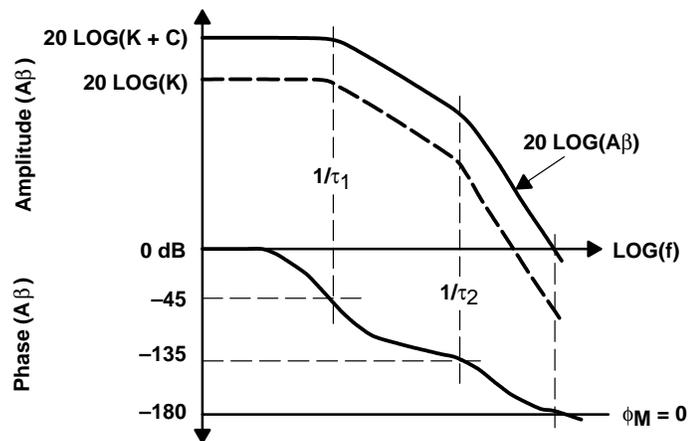

**Figure 16. Magnitude and Phase Plot of the Loop Gain Increased to (K+C)**

Increasing the loop gain to  $(K+C)$  as shown in Figure 16 shifts the magnitude plot up. If the pole locations are kept constant, the phase margin reduces to zero as shown, and the circuit will oscillate. The circuit is not good for much in this condition because production tolerances and worst case conditions insure that the circuit will oscillate when you want it to amplify, and vice versa.

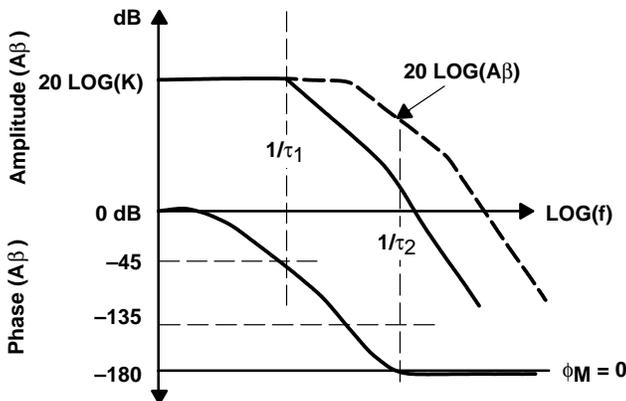

**Figure 17. Magnitude and Phase Plot of the Loop Gain With Pole Spacing Reduced**

The circuit poles are spaced closer in Figure 17, and this results in a faster accumulation of phase shift. The phase margin is zero because the loop-gain phase shift reaches 180° before the magnitude passes through 0 dB. This circuit oscillates, but it is not a very stable oscillator because the transition to 180° phase shift is very slow. Stable oscillators have a very sharp transition through 180°.

When the closed-loop gain is increased, the feedback factor ( $\beta$ ) is decreased, because  $V_{OUT}/V_{IN} = 1/\beta$  for the ideal case. This in turn decreases the loop gain, ( $A\beta$ ) thus, the stability increases. In other words, increasing the closed-loop gain makes the circuit more stable. Stability is not important except to oscillator designers because overshoot and ringing become intolerable to linear amplifiers long before oscillation occurs. The overshoot and ringing situation is investigated in the next section.

## 6 The Second Order Equation and Ringing/Overshoot Predictions

The second order equation is a common approximation used for feedback system analysis because it describes a two-pole circuit which is the most common approximation used. All real circuits are more complex than two poles, but except for a small fraction, they can be represented by a two-pole equivalent. The second order equation is extensively described in electronic and control literature[6].

$$(1 + A\beta) = 1 + \frac{K}{(1 + \tau_1 s)(1 + \tau_2 s)} \quad (16)$$

After algebraic manipulation, equation 16 is presented in the form of equation 17.

$$s^2 + s \frac{\tau_1 + \tau_2}{\tau_1 \tau_2} + \frac{1 + K}{\tau_1 \tau_2} = 0 \quad (17)$$

Equation 17 is compared to the second order control equation 18, and the damping ratio ( $\zeta$ ) and natural frequency ( $\omega_N$ ) are obtained through like term comparisons.

$$s^2 + 2\zeta\omega_N s + \omega_N^2 \quad (18)$$

Comparing these equations yields formulas for the phase margin and percent overshoot as a function of damping ratio.


$$\omega_N = \sqrt{\frac{1 + K}{\tau_1 \tau_2}} \quad (19)$$

$$\xi = \frac{\tau_1 + \tau_2}{2\omega_N \tau_1 \tau_2} \quad (20)$$

When the two poles are well separated, equation 21 is valid.

$$\phi_M = \text{tangent}^{-1}(2\xi) \quad (21)$$

The salient equations are plotted in Figure 18 which enables a designer to determine the phase margin and overshoot when the gain and pole locations are known.

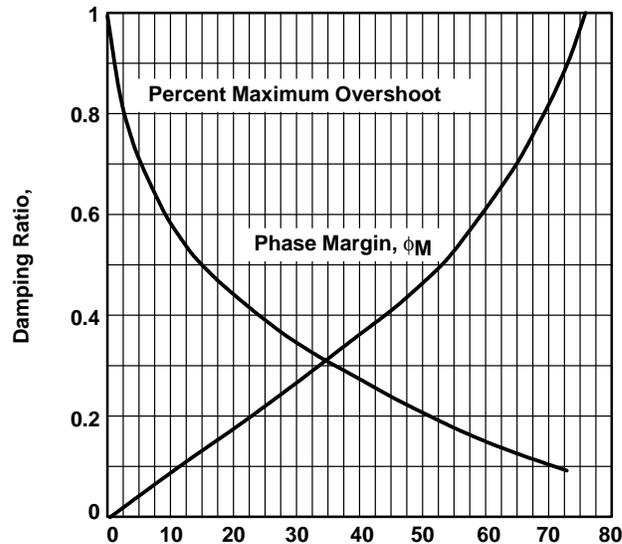

**Figure 18. Phase Margin and Overshoot vs Damping Ratio**

Enter Figure 18 at the calculated damping ratio, say 0.4, and read the overshoot at 25% and the phase margin at 42°. If a designer had a circuit specification of 5% maximum overshoot, then the damping ratio must be 0.78 with a phase margin of 62°.

## 7 Summary

These equations and examples are adequate to get designers started in the design and analysis of feedback circuits. When the engineers reach the point where the examples and equations given here are inadequate, they must go to the references for more information. If the engineers find themselves digging through the references on a regular basis, they should consider becoming analog design engineers.

## 8 References

1. DiStefano, Stubberud, and Williams, *Theory and Problems of Feedback and Control Systems, Schaum's Outline Series*, Mc Graw Hill Book Company, 1967
2. Bode, H. W., *Network Analysis And Feedback Amplifier Design*, D. Van Nostrand, Inc., 1945
3. Frederickson, Thomas, *Intuitive Operational Amplifiers*, McGraw Hill Book Company, 1988
4. Bower, J. L. and Schultheis, P. M., *Introduction To The Design Of Servomechanisms*, Wiley, 1961
5. Van Valkenberg, M. E., *Network Analysis*, Prentice-Hall, 1964
6. Del Toro, V., and Parker, S., *Principles of Control Systems Engineering*, McGraw-Hill, 1960.