 


DESIGN IDEA

The FET Constant Current Source

INTRODUCTION

The combination of low associated operating voltage and high output impedance make the FET attractive as a constant current source. An adjustable current source may be built with a FET, a variable resistor and a small battery, Figure 1. For good thermal stability, the FET should be biased near the zero T.C. point.¹



Field-Effect Transistor Current Source
Figure 1

Whenever the FET is operated in the saturated region, its output conductance is very low. This occurs whenever the drain-source voltage V_{DS} is significantly greater than the cut-off voltage $V_{GS(off)}$. The FET may be biased to operate as a constant current source at any current below its saturation current I_{DSS} .

For a given device where I_{DSS} and $V_{GS(off)}$ are known, the approximate V_{GS} required for a given I_D is

$$V_{GS} = V_{GS(off)} \left[1 - \left(\frac{I_D}{I_{DSS}} \right)^{1/k} \right] \quad (1)$$

where k can vary from 1.7 to 2.0, depending upon device geometry. The series resistor R_S required between source and gate is

$$R_S = \frac{V_{GS}}{I_D} \quad (2)$$

A change in supply voltage, or change in load impedance, will change I_D by only a small factor because of the low output conductance g_{OSS} .

$$\Delta I_D = \Delta V_{DS} g_{OSS} \quad (3)$$

The value of g_{OSS} is an important consideration in the accuracy of a constant current source. As g_{OSS} may range from less than $1 \mu\text{mho}$ to more than $50 \mu\text{mho}$ according to the FET type, the dynamic impedance can be greater than 1 megohm to less than 20K. This corresponds to a current stability range of $1 \mu\text{A}$ to $50 \mu\text{A}$ per volt. The value of g_{OSS} depends also on the operating point, being highest at I_{DSS} and at low V_{DS} . Output conductance g_{OSS} decreases approximately linearly with I_D , becoming less as the FET is biased toward cut-off. The relationship is

$$\frac{I_D}{I_{DSS}} = \frac{g_{OSS}}{g'_{OSS}} \quad (4)$$

where


$$g_{OSS} = g'_{OSS} \quad (5)$$

when

$$V_{GS} = 0 \quad (6)$$

So as $V_{GS} \gg V_{GS(off)}$, $g_{OSS} \gg \text{zero}$. For best regulation, I_D must be considerably less than I_{DSS} .

 It is possible to achieve much lower g_{OSS} per unit I_D by cascading two FETs as shown in Figure 2.



Cascade FET Current Source
Figure 2

Now, I_D is regulated by Q_1 and $V_{DS1} = -V_{GS2}$. The d-c value of I_D is controlled by R_S and Q_1 . However, Q_1 and Q_2 both affect current stability. The circuit output conductance is derived as follows:

Figure 2 is redrawn in Figure 3 for the condition $V_{GS1} = 0$.

 


Figure 3

$$i_o = i_2 + v_{gs2}g_{fs2} = v_{ds2}g_{oss2} - i_o \frac{g_{fs2}}{g_{oss1}} \quad (7)$$

$$i_o = \frac{v_{ds2}g_{oss2}g_{oss1}}{g_{oss1} + g_{fs2}} \quad (8)$$

$$v_o = v_{ds1} + v_{ds2} = v_{ds2} + \frac{i_o}{g_{oss1}} \quad (9)$$

$$v_o = v_{ds2} \frac{g_{oss1} + g_{oss2} + g_{fs2}}{g_{oss1} + g_{fs2}} \quad (10)$$

$$g_o = \frac{i_o}{v_o} = \frac{g_{oss1}g_{oss2}}{g_{oss1} + g_{oss2} + g_{fs2}} \quad (11)$$

If $g_{oss1} = g_{oss2}$ (12)

$$g_o = \frac{g_{oss}}{2 + g_{fs}/g_{oss}} \quad (13)$$

When

$R_S \neq 0$ as in Figure 2 (14)

$$g_o = \frac{g_{oss}^2}{2g_{oss} + g_{fs} + R_S(g_{fs}^2 + g_{oss}g_{fs} + g_{oss}^2)} \quad (15)$$

$$\approx \frac{g_{oss}^2}{g_{fs}(1 + R_Sg_{fs})} \quad (16)$$


In either case ($R_S = 0$ or $R_S \neq 0$), the circuit output conductance is considerably less than the g_{oss} of a single FET.

In designing any cascaded FET current source, both FETs must be operated with adequate drain-gate voltage V_{DG} . That is,

$$V_{DG} > V_{GS(off)}, \text{ preferably } V_{DG} > 2 V_{GS(off)} \quad (17)$$


If $V_{DG} < 2 V_{GS(off)}$, the g_{oss} will be significantly increased, and circuit g_o will deteriorate. For example: A 2N4340 has typical $g_{oss} = 4 \mu\text{mho}$ at $V_{DS} = -20 \text{ V}$ and $V_{GS} = 0$. At $V_{DS} \approx -V_{GS(off)} = 2 \text{ V}$, $g_{oss} \approx 100 \mu\text{mho}$.

 The best FETs for current sources are those having long gates and consequently very low g_{oss} . The Siliconix 2N4869 exhibits typical $g_{oss} = 1 \mu\text{mho}$ at $V_{DS} = 20 \text{ V}$. A single 2N4869 in the circuit of Figure 4 will yield a current source adjustable from $5 \mu\text{A}$ to 1 mA with internal impedance greater than 2 megohms .







Adjustable Current Source
Figure 4

 The cascade circuit of Figure 5 provides a current adjustable from $2 \mu\text{A}$ to 1 mA with internal resistance greater than 10 megohms .



Cascade FET Current Source
Figure 5

    For each circuit discussed, g_{oss} is represented by the following equations:



REFERENCES

(1) "Biasing FETs for Zero DC Drift," Evans, L., *Electrotechnology*, August 1964.