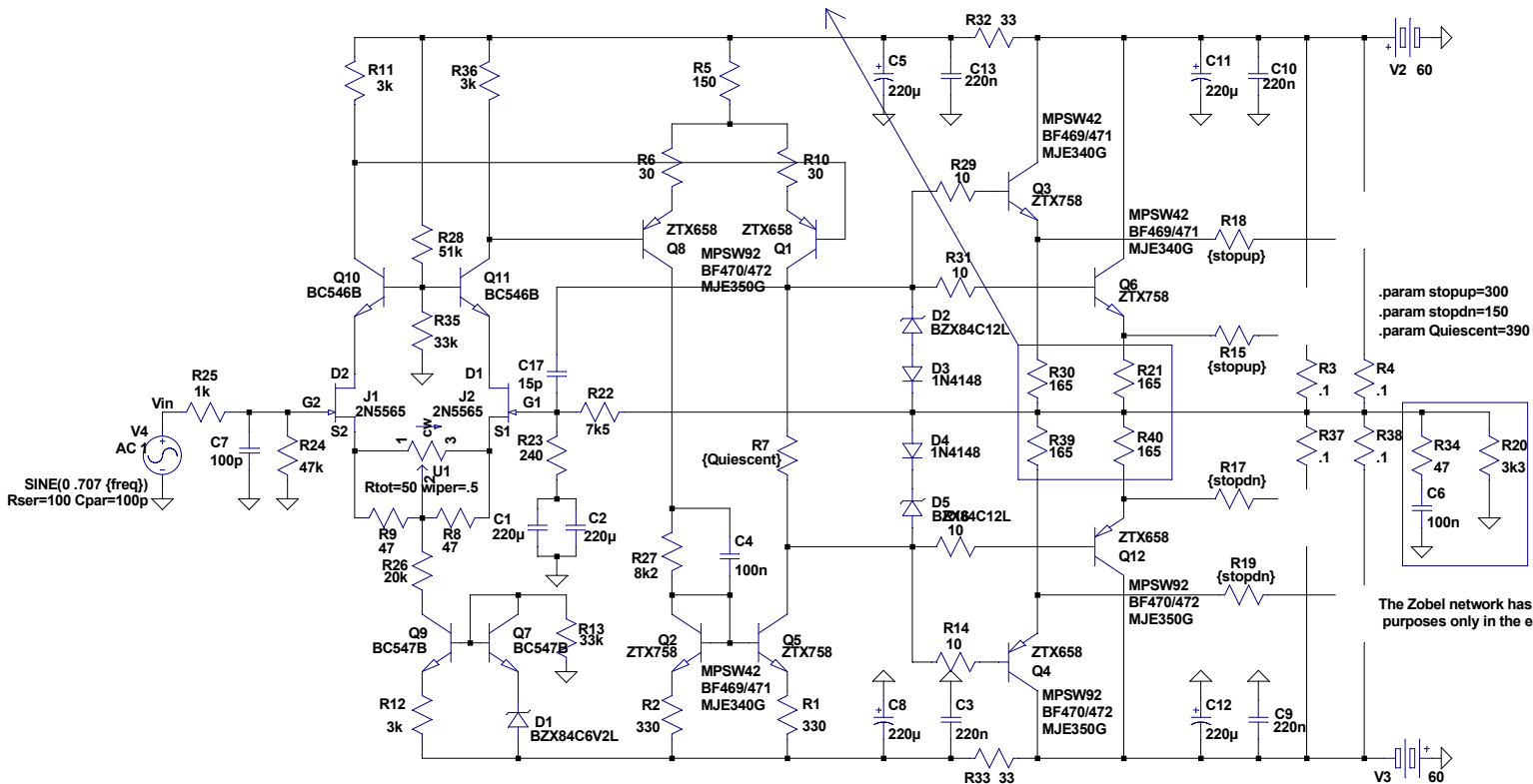


The way the resistors are connected and the values shown are at the limit of max. dissipations of originally used 2N5401/2N5551.



The Zobel network has been changed and the R20 temporarily added for prevention purposes only in the event that the amplifier is not happy with no load on its output.